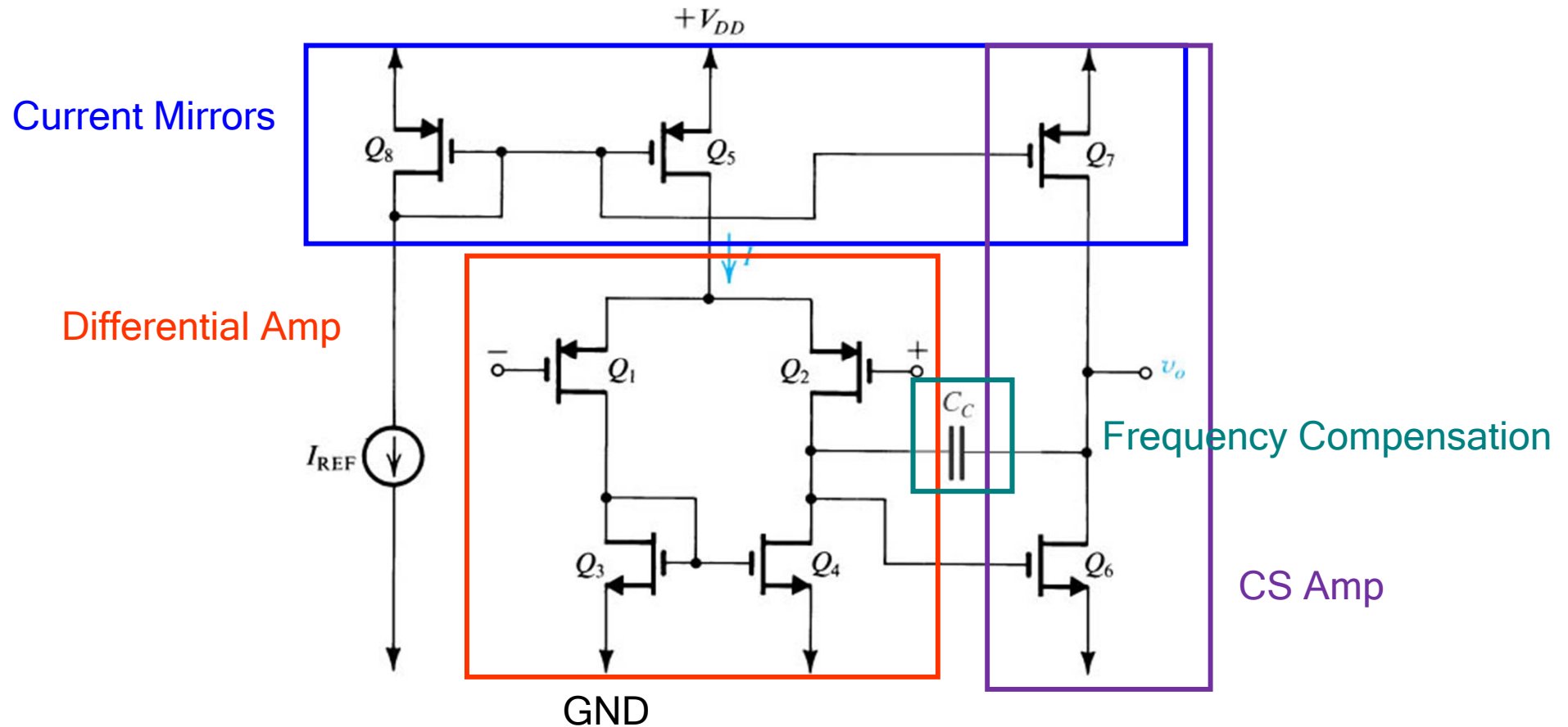



# Lect. 17: Two-Stage Amplifier

Qualitative analysis of two-stage transconductance amplifier



# Lect. 17: Two-Stage Amplifier

## Input Common-Mode Range

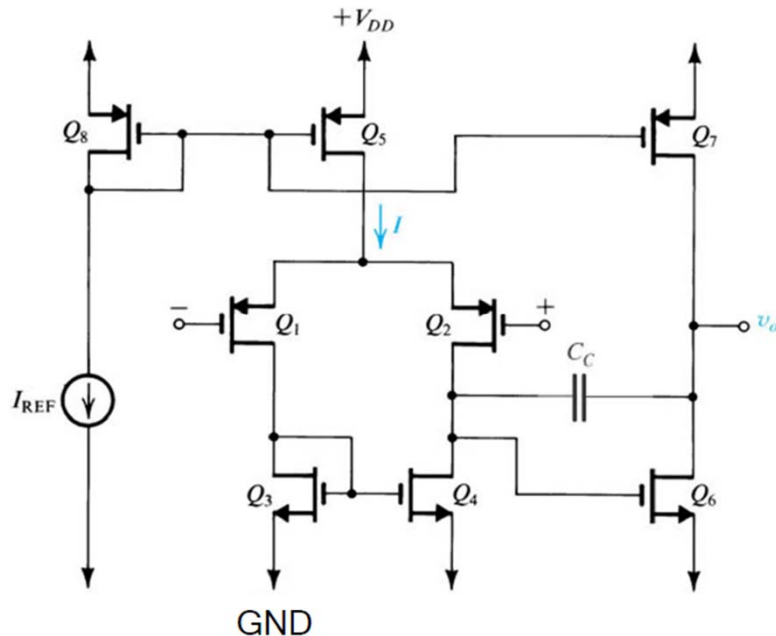

Large  $I \rightarrow$  Large  $V_{SG5}$ ,  $V_{SG1}$ ,  $V_{GS3}$   
 $\rightarrow$  Small input CM range

For  $V_{CM,min}$ ,  $Q_1$ ,  $Q_2$  should be in saturation

$$V_{SD1} > V_{SG1} - |V_{TH,p}|$$

$$V_{S1} - V_{D1} > V_{S1} - V_{CM} - |V_{TH,p}|$$

$$V_{CM} > V_{D1} - |V_{TH,p}|$$

$$V_{CM,min} = V_{GS3} - |V_{TH,p}|$$

For  $V_{CM,max}$ ,  $Q_5$  should be in saturation

$$V_{SD5} > V_{SG5} - |V_{TH,p}|$$


$$V_{S5} - V_{D5} > V_{S5} - V_{G5} - |V_{TH,p}|$$

$$V_{D5} < V_{G5} + |V_{TH,p}| = V_{DD} - V_{SG5} + |V_{TH,p}|$$


$$V_{CM} + V_{SG1} < V_{DD} - V_{SG5} + |V_{TH,p}|$$

$$V_{CM,max} = V_{DD} - V_{SG5} - V_{SG1} + |V_{TH,p}|$$

# Lect. 17: Two-Stage Amplifier

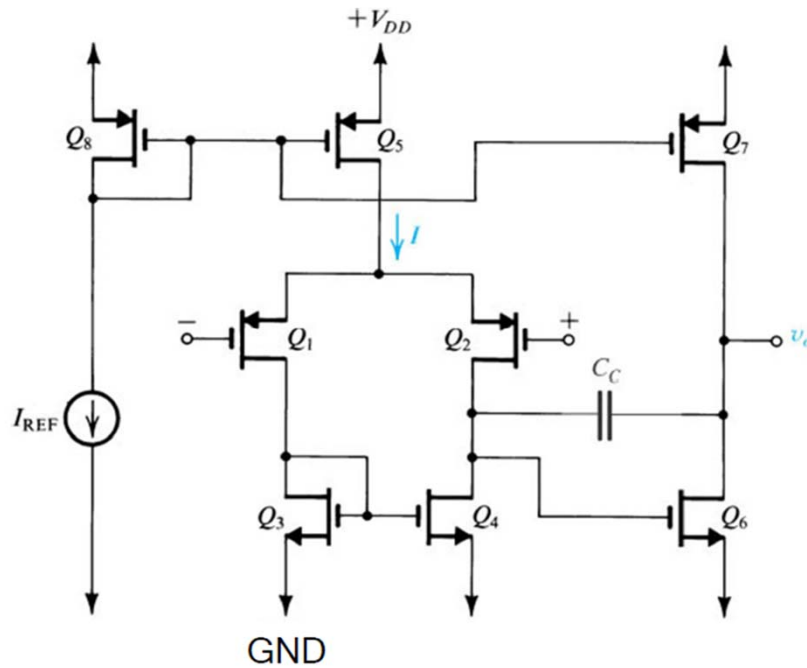

Equivalent Circuit

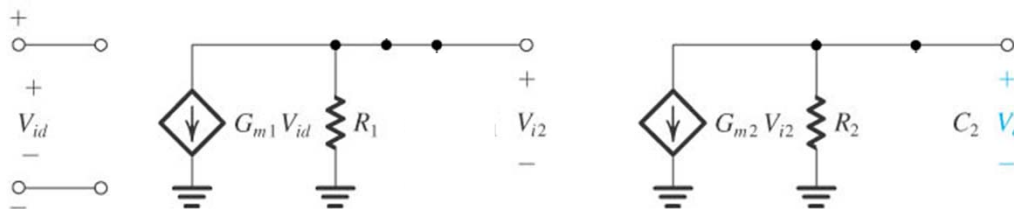

Voltage Gain (DC)

Two CS amps in cascade

$$G_{m1} =$$

$$R_1 =$$

$$A_{v1} =$$

$$G_{m2} =$$


$$R_2 =$$

$$A_{v2} =$$


$$A_v =$$

$$R_{in} =$$

$$R_{out} =$$

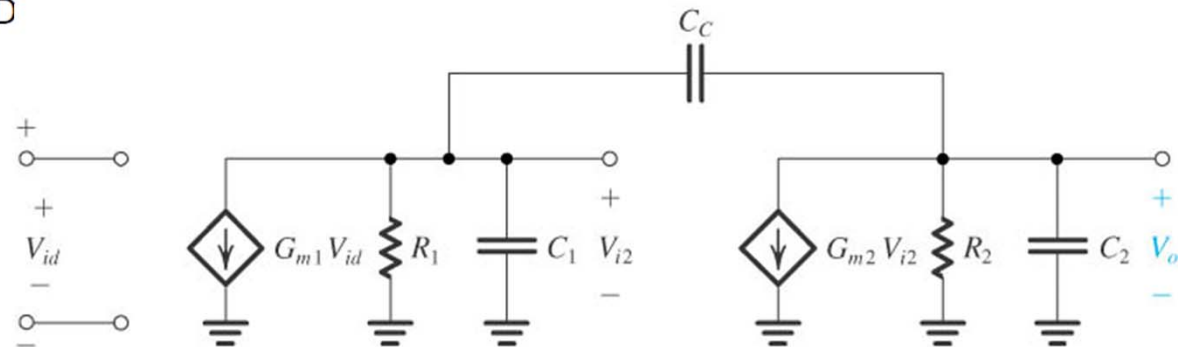

# Lect. 17: Two-Stage Amplifier

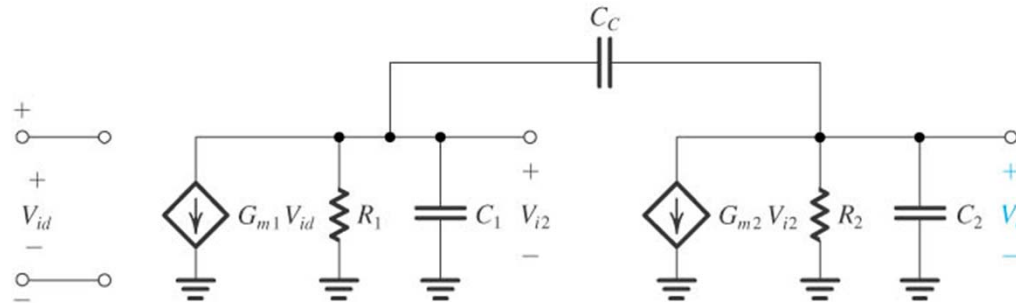


$$\frac{V_o(s)}{V_{id}(s)} = ?$$

$$\omega_{P,in} \sim \frac{1}{R_1 [C_1 + (1 + G_{m2}R_2)C_C]} \sim \frac{1}{R_1 G_{m2} R_2 C_C}$$

$$\omega_{P2} \sim \frac{1}{R_2 \left[ \left( 1 + \frac{1}{G_{m2}R_2} \right) C_C + C_2 \right]} \sim \frac{1}{R_2 (C_C + C_2)}$$

Reduce  $C_C$  for bandwidth enhancement


Why do we need  $C_C$ ?

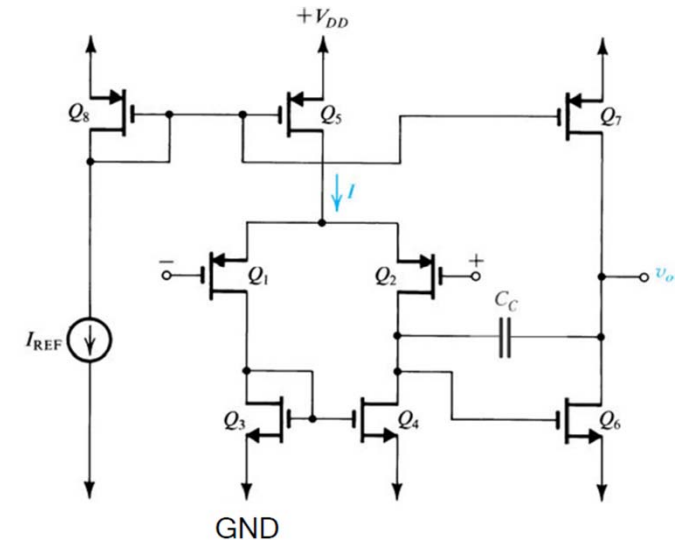

# Lect. 17: Two-Stage Amplifier

## Design Project #1 (Due May 4. Details available in [tera.yonsei.ac.kr](http://tera.yonsei.ac.kr))
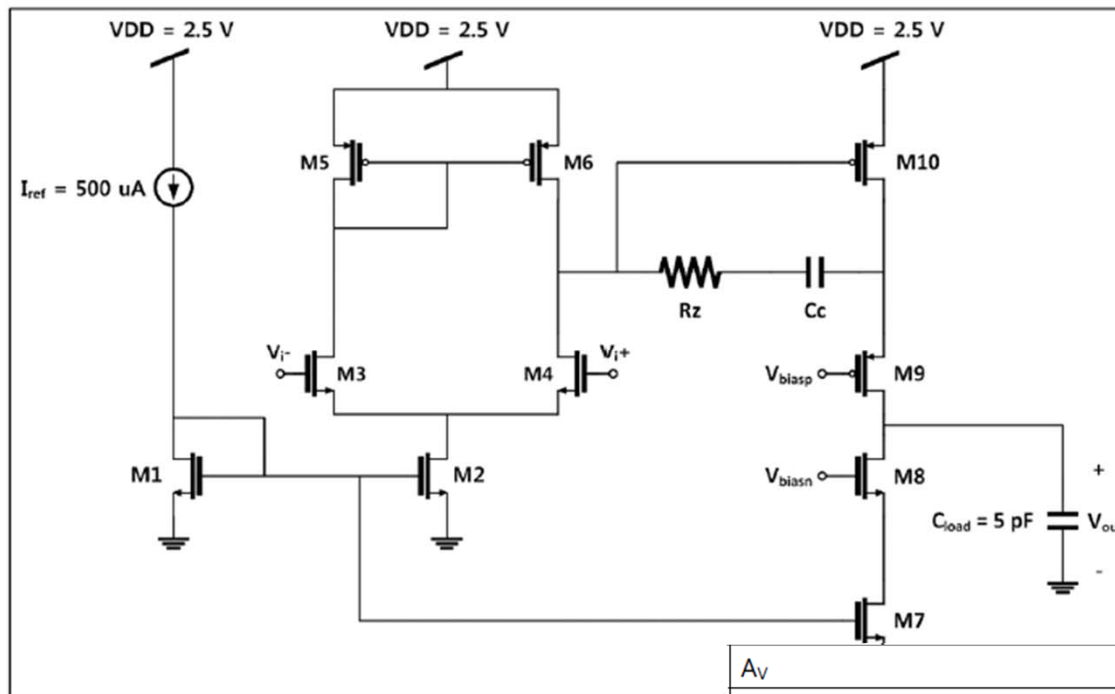
## Two-stage OTA (Operational Transconductance Amplifier)



$A_v$	> 76 dB
Bandwidth	> 25 kHz
Phase Margin	> 75 °
CMRR	> 75 dB
Input Common Mode Range	> 1.8 V
Power Consumption	< 2.5 mW