

ENSC327

Communications Systems

11: FM Modulation



Jie Liang
School of Engineering Science
Simon Fraser University

Outline

- Two methods of generating FM waves:
 - Direct method
 - Indirect Method: **Armstrong's** wideband frequency modulator

Review of frequency deviation:

Angle modulation: $s(t) = A_c \cos(2\pi f_c t + \phi(t))$

Instantaneous frequency $f_i(t) = \frac{1}{2\pi} \frac{d\theta_i(t)}{dt} = f_c + \frac{1}{2\pi} \frac{d\phi(t)}{dt}$


Frequency deviation $\Delta f = \max \left| \frac{1}{2\pi} \frac{d\phi(t)}{dt} \right|$.

Frequency deviation for FM signals: $\Delta f = k_f \max |m(t)|$.

For example, FM radio allows 75kHz deviation to each side of the carrier.

Direct FM Generation

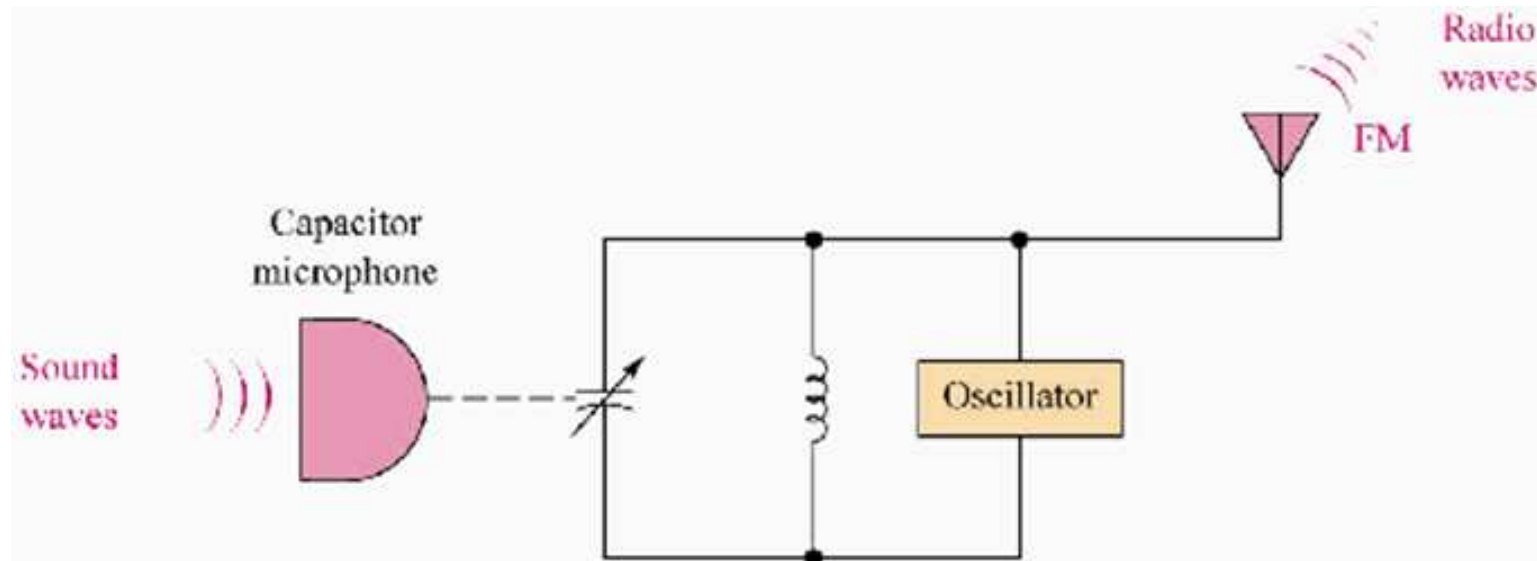- ❑ The carrier freq is directly varied by the input signal
- ❑ Can be accomplished by **Voltage-Controlled Oscillator (VCO)**, whose output frequency is proportional to the voltage of the input signal.
- ❑ A VCO example: implemented by variable capacitor




Problems of direct FM generator

- The carrier freq of VCO tends to **drift** away.
 - (Crystal oscillator cannot be used in direct FM: its freq is too stable, and is difficult to change.)
 - Feedback freq stabilization circuit is required:
 - The complexity is increased.
- The **frequency deviation** with direct FM is only about 5 KHz, too small for wideband FM:
 - Recall: the max frequency deviation in commercial FM radio is 75kHz.



Indirect Method: Armstrong Modulator

- ❑ First obtain **NBFM** via a NBPM circuit with crystal oscillator
- ❑ Then apply **frequency multiplier**
 - Increase both the **carrier frequency** and the **freq deviation**
- ❑ If necessary, use **mixer** to concatenate multiple multipliers
 - Mixer only changes the **carrier frequency**, but **not** the **frequency deviation**.
- ❑ Indirect FM is preferred when the stability of carrier frequency is of major concern (e.g., in commercial FM broadcasting)

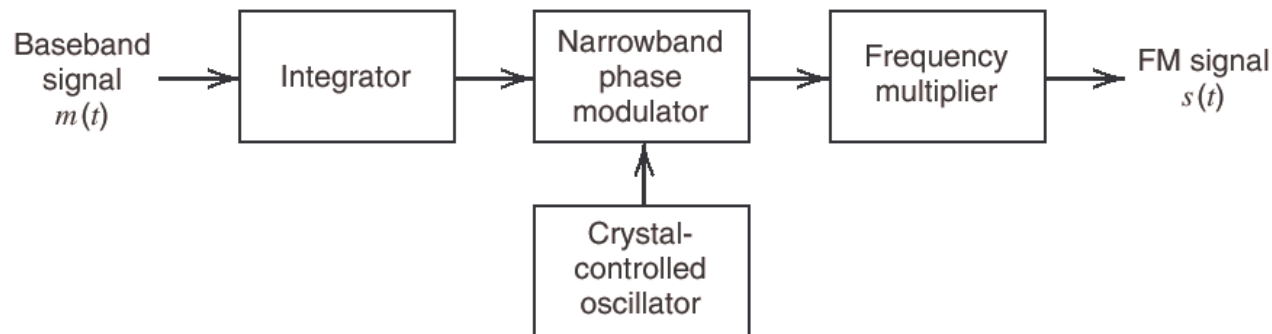

Recall: Narrow-band FM

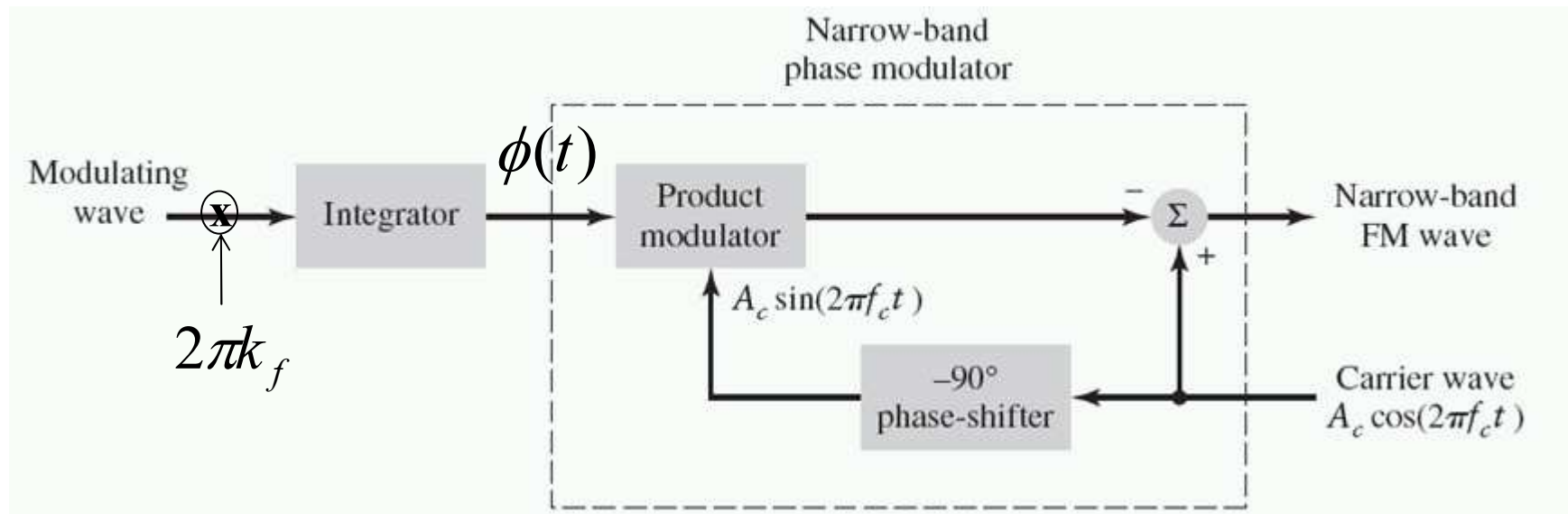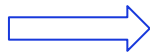- if Δf is small: $s(t) = A_c \cos(2\pi f_c t + \phi(t))$



Crystal oscillator can be used to get stable frequency (prevent drifting)

But **frequency deviation** of NBFM is small.

To get larger one, use **freq multiplier**...

Frequency Multipliers

- How to increase the frequency deviation ?
- Answer: **trigonometric identity!**


From $s(t) = A_c \cos(2\pi f_c t + 2\pi k_f \int_0^t m(\tau) d\tau)$

If we can get the **squared** signal:

Frequency Multipliers

If we can get $s^3(t)$:

Freq Multipliers via Nonlinear Circuit

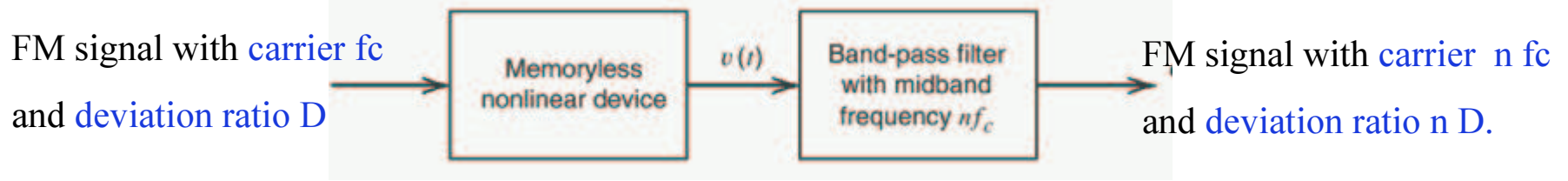


- A general **nonlinear circuit** produces

$$v(t) = a_1 s(t) + a_2 s^2(t) + \dots + a_n s^n(t)$$

- The highest carrier frequency:
- The highest freq sensitivity factor:
- The bandpass filter:
 - Center:
 - Passband width:
 - In practice: $n = 2$, or 3 . Larger n is not efficient.
 - But can concatenate multiple stages to obtain higher orders.

Mixer & Frequency Multiplier

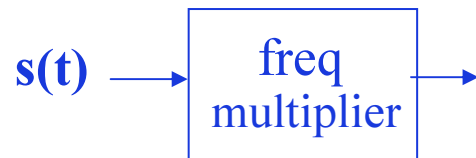
- Frequency multiplier increases the freq and deviation **together**.
- How to adjust them **separately** to get more flexibilities?



- Input: $s(t) = A_c \cos(2\pi f_c t + \phi(t))$, with freq deviation Δf .
- After freq multiplier:
- After multiplying with local freq f_1 :


- After BPF:

Armstrong's Indirect FM

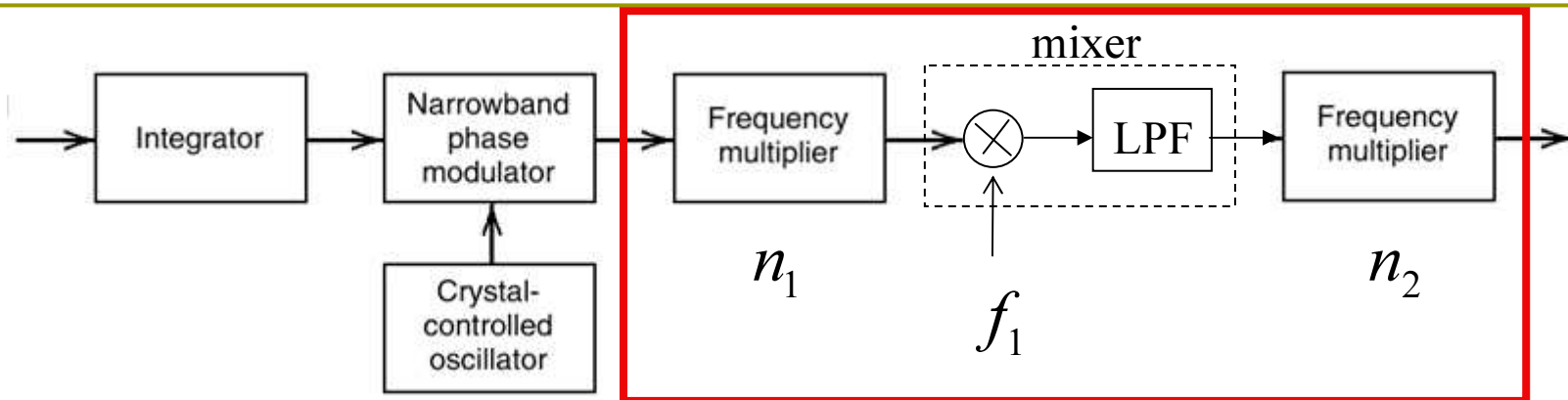

- Two stages of multiplier and one mixer are used.
 - Allow flexible choices of carrier freq and freq deviation.
 - The first stage multiplier amplifies both f_c and Δf .
 - The mixer brings down the central freq.
 - The second stage amplifies f_c and Δf again.


Example

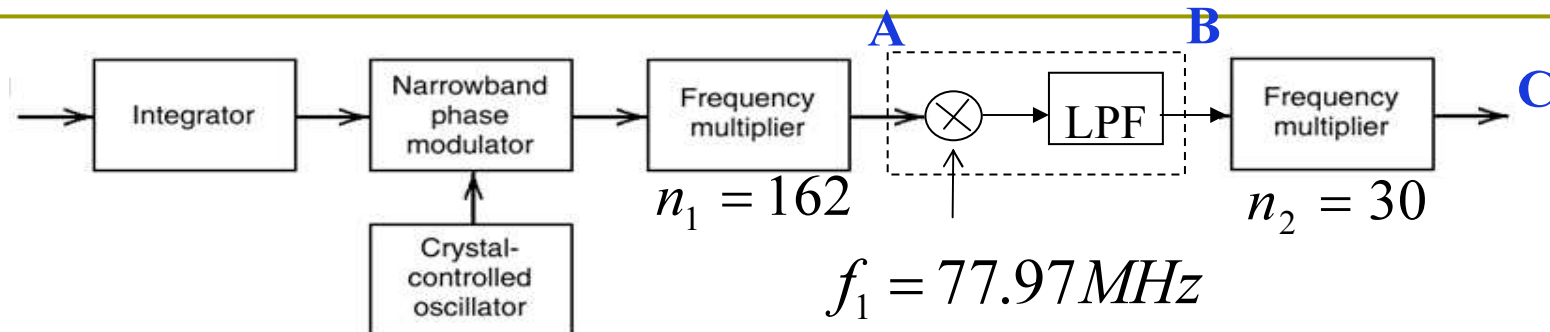

NBPM output : $f = 500 \text{ kHz}$, $\Delta f = 15.432 \text{ Hz}$

Find f and Δf at A, B, C.

Example

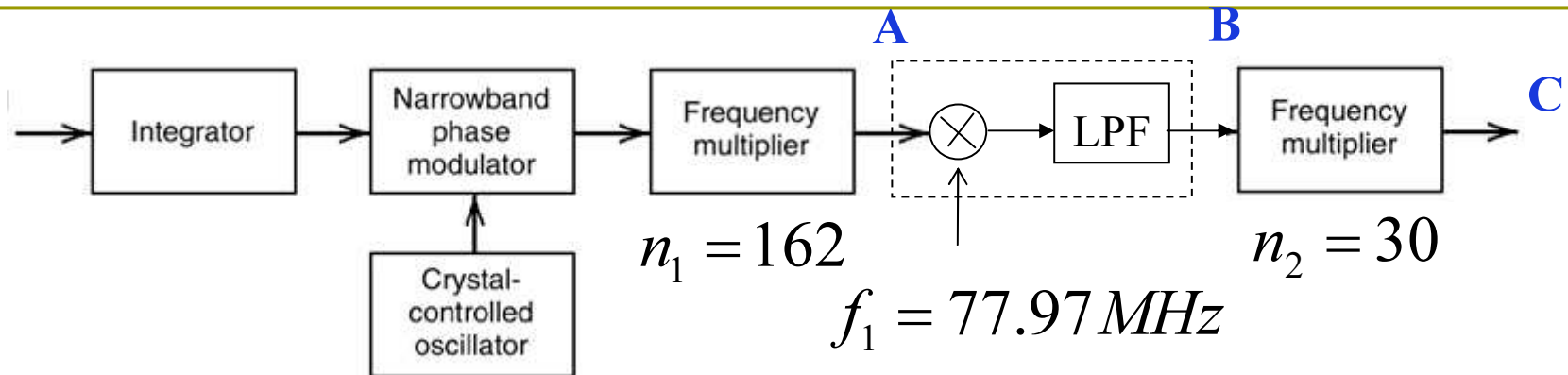

Total multiplier for Δf :

Summary

- Direct FM generation:

- The carrier freq is directly varied by the input signal
- Frequency drifting is a problem
- Freq deviation $< 5\text{KHz}$

- Indirect FM generation:

- NBFM followed by freq multiplier
 - Use nonlinear circuit to get multiplier
- Can use mixer to change the carrier freq
- Combination of mixer and multiplier provides flexibilities.

Reference

- **Direct FM generation:**

<http://www.ycars.org/EFRA/Module%20B/directfm.htm>

- **Indirect FM generation:**

<http://www.ycars.org/EFRA/Module%20B/indirectfm.htm>