
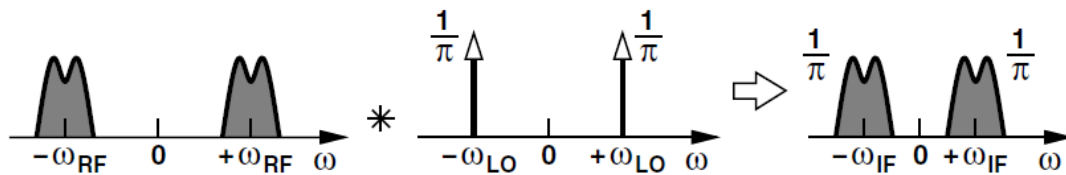


RF Mixers (II)

Passive Mixers

- “Return-to-Zero” Implementations:

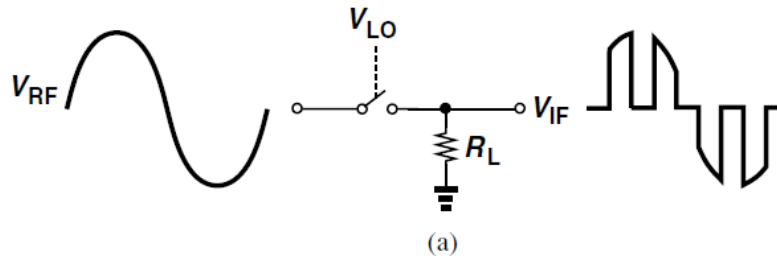


Conversion Gain:

How about single-balanced and double-balanced?

RX mixers are not very common in modern RF design.

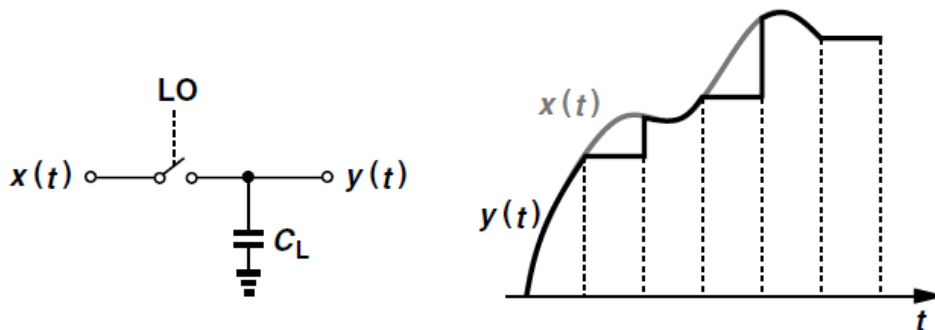- “Non-Return-to-Zero” (Sampling) Mixers: Case I: Voltage-Driven



Conversion Gain Calculation:


$$|Y_1(f) + Y_2(f)|_{IF} = \sqrt{\frac{1}{\pi^2} + \frac{1}{4}} [|X(f - f_{LO})| + |X(f + f_{LO})|]$$

How about single-balanced and double-balanced?

Noise Calculation:

$$\overline{V_{n,in,SB}^2} = \frac{kT}{2 \left(\frac{1}{\pi^2} + \frac{1}{4} \right)} \left(3.9R_1 + \frac{1}{2C_1 f_{LO}} \right)$$

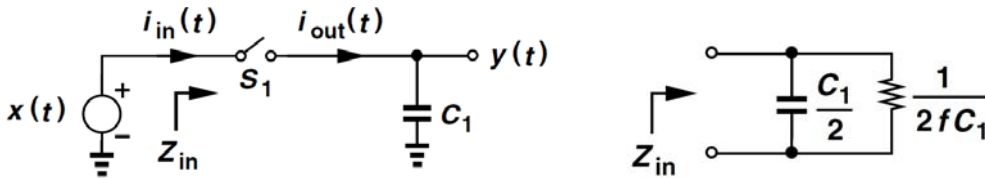
Input impedance for $\omega \sim \omega_{LO}$:



How about single-balanced and double-balanced?


- **Flicker Noise:** Passive mixers generate little flicker noise in the baseband output if the transistors do not enter saturation at any point during the cycle and carry no dc current.

Case II: Current-Driven

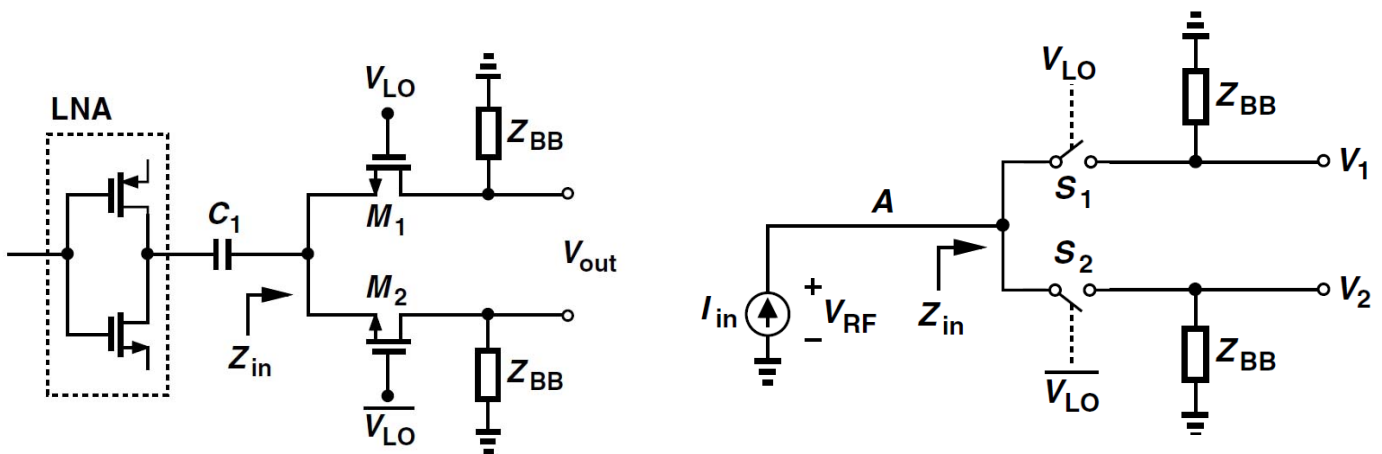


1. Assume a certain frequency response for Z_{BB} :

2. Apply a band-limited signal current:

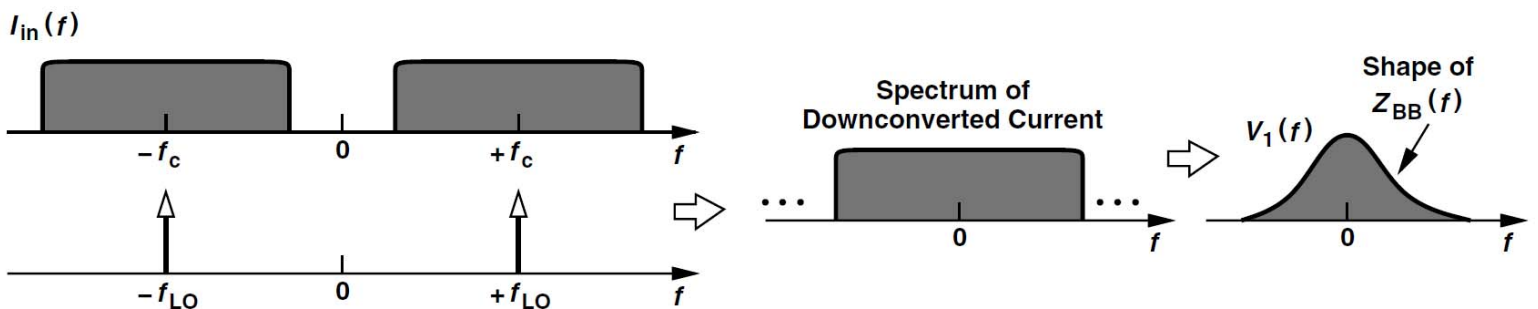

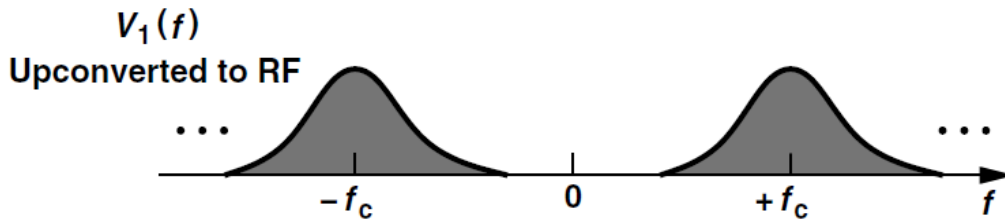3. Now the baseband signal is mixed with LO and returns to node A:



- The baseband impedance is “translated” to f_c .
- Can obtain very high Qs in RF!



Noise and Nonlinearity:

Since the switches are in series with a current source, they should contribute negligible noise and nonlinearity. In practice, though, some corruption occurs.

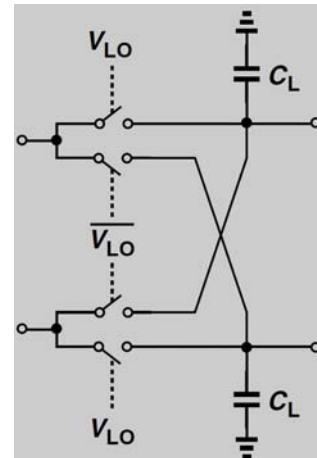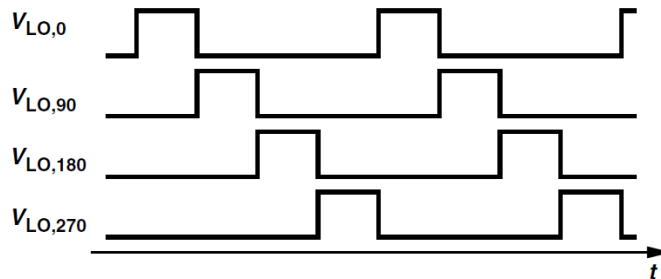
Problem of Current Division:

In a double-balanced mixer, the input current would split two ways, reducing the conversion gain:




- Need to use 25% duty cycle for the LOs:



Example:
[Mirzaei, VLSI Symp. '10]

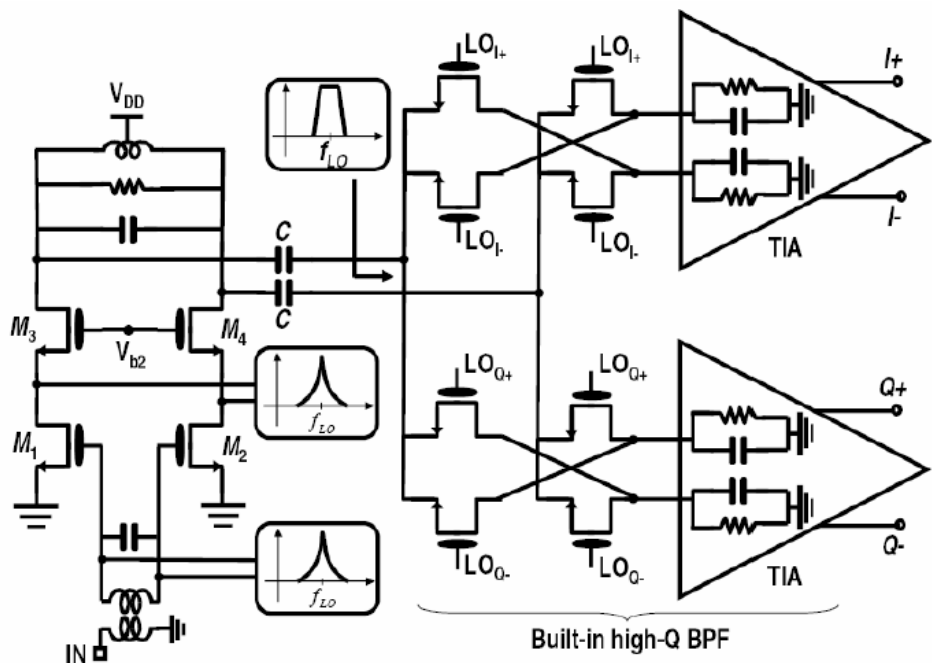


Active Mixers

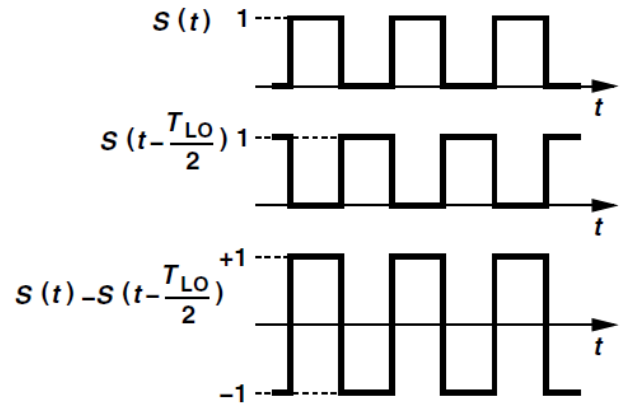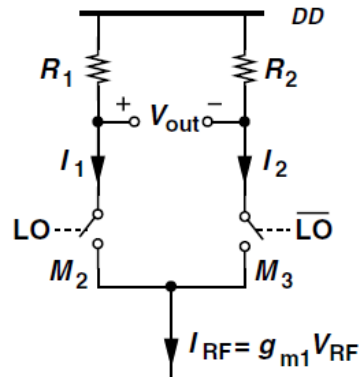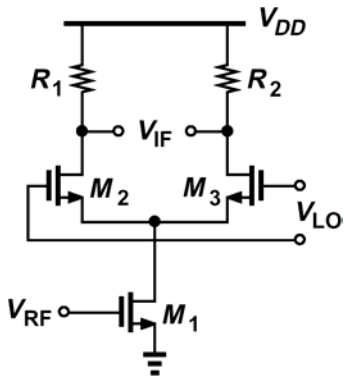

$$V_{out}(t) = I_{RF}(t)R_D \cdot \frac{4}{\pi} \cos \omega_{LO}t + \dots$$

- Conversion Gain :




- Voltage Headroom Issues :

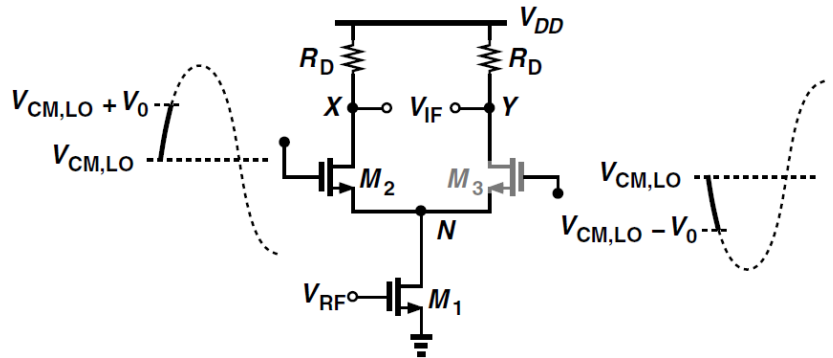

$$V_{R,max} = V_{DD} - \left[V_{GS1} - V_{TH1} + \left(1 + \frac{\sqrt{2}}{2} \right) (V_{GS2,3} - V_{TH2}) \right]$$


- Noise in Active Mixers

Periodically-Switched White Noise:

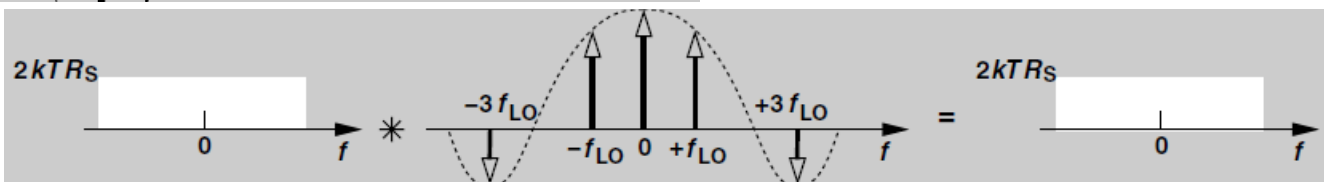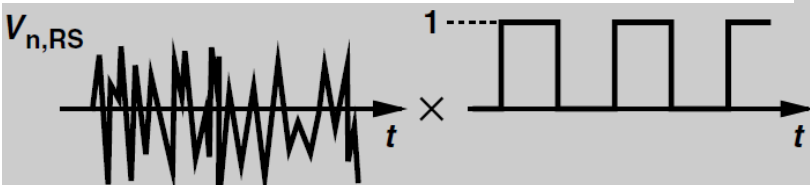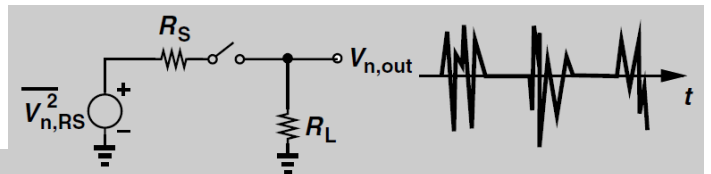

Observations:

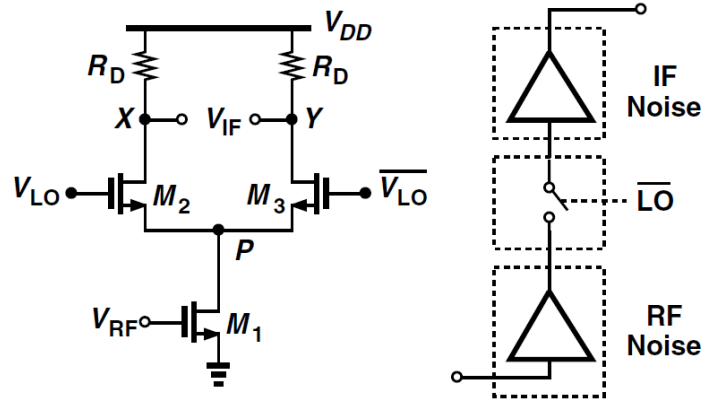1. Noise current of M1 is periodically-switched.
2. R_D 's directly add noise to IF.
3. M2 and M3 contribute noise for only a fraction of the period.





If only 1 and 2 are considered:

$$\overline{V_{n,X}^2} = \frac{1}{2} \left(\overline{I_{n,M1}^2} \right) R_D^2 + 4kTR_D$$

Referred to the input:

$$\overline{V_{n,in}^2} = \pi^2 kT \left(\frac{\gamma}{g_{m1}} + \frac{2}{g_{m1}^2 R_D} \right)$$

Flicker Noise in Active Mixers:

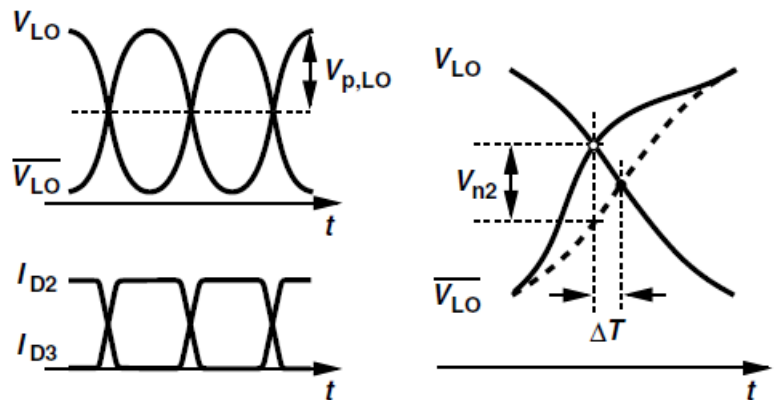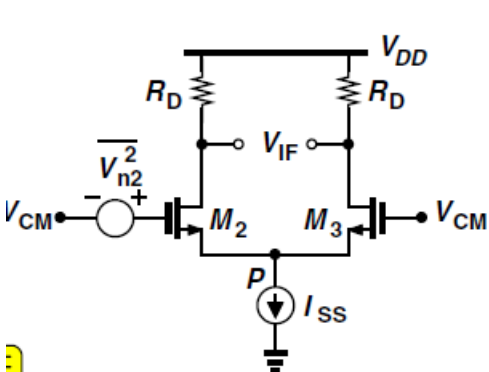

Step 1:

$$V_{CM} + V_{p,LO} \sin \omega_{LO} t + V_{n2}(t) = V_{CM} - V_{p,LO} \sin \omega_{LO} t$$

Step 2:

$$|\Delta T| = \frac{|V_{n2}(t)|}{2V_{p,LO}\omega_{LO}}$$

Step 3:

$$I_{n,out}(t) = \sum_{k=-\infty}^{+\infty} \frac{2I_{SS}V_{n2}(t)}{S_{LO}} \delta \left(t - k\frac{T_{LO}}{2} \right) \quad V_{n,out}(f)|_{k=0} = \frac{I_{SS}R_D}{\pi V_{p,LO}} V_{n2}(f)$$

