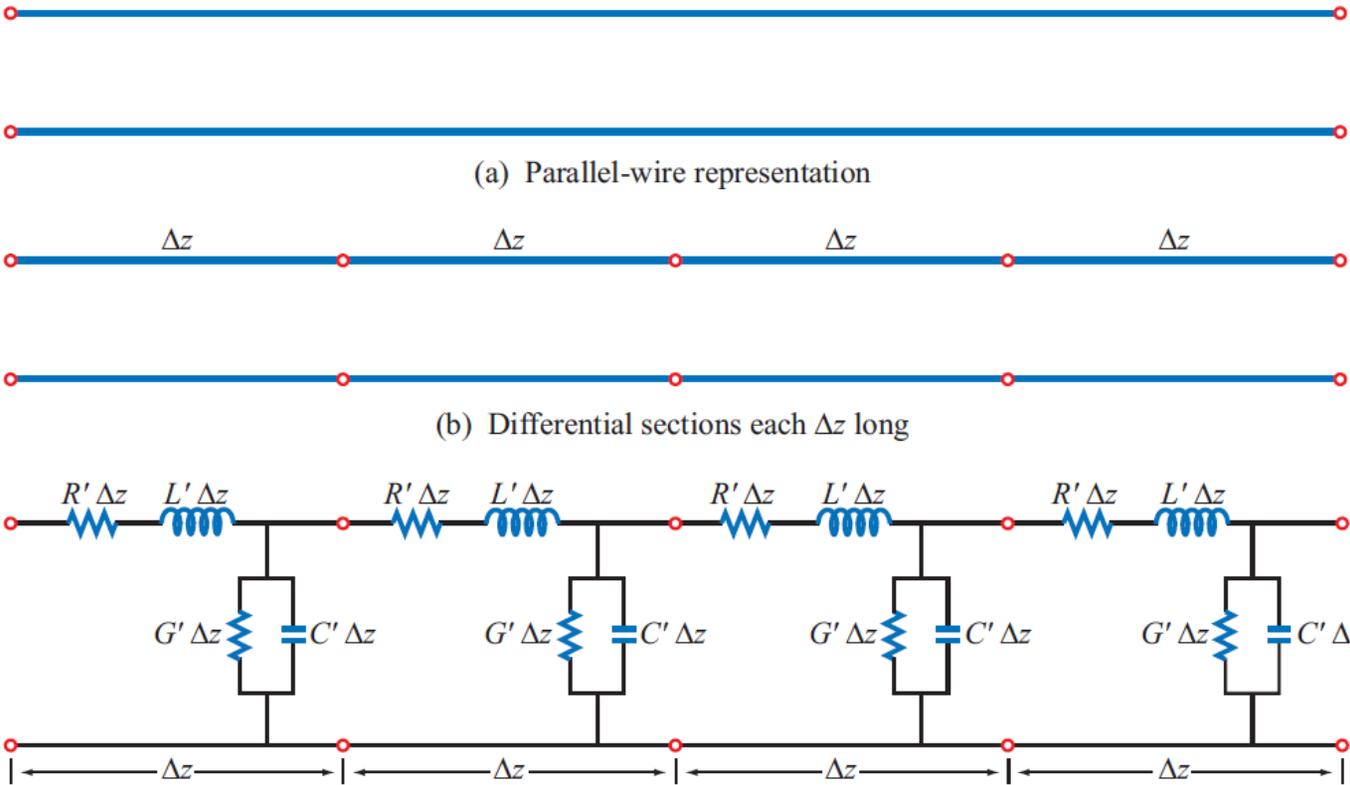


INTRODUCTION TO TRANSMISSION LINES

PART II

DR. FARID FARAHMAND
FALL 2012

Transmission Line Model




(c) Each section is represented by an equivalent circuit


Transmission-line parameters R' , L' , G' , and C' for three types of lines.

Parameter	Coaxial	Two-Wire	Parallel-Plate	Unit
R'	$\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{2R_s}{\pi d}$	$\frac{2R_s}{w}$	Ω/m
L'	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]$	$\frac{\mu h}{w}$	H/m
G'	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\sigma w}{h}$	S/m
C'	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right]}$	$\frac{\epsilon w}{h}$	F/m

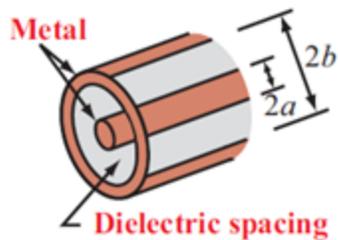
Notes: (1) $R_s = \sqrt{\pi f \mu_c / \sigma_c}$. (2) μ , ϵ , and σ pertain to the insulating material between the conductors. (3) $R_s = \sqrt{\pi f \mu_c / \sigma_c}$. (4) μ_c and σ_c pertain to the conductors. (5) If $(D/d)^2 \gg 1$, then $\ln \left[(D/d) + \sqrt{(D/d)^2 - 1} \right] \simeq \ln(2D/d)$.



(a) Coaxial line

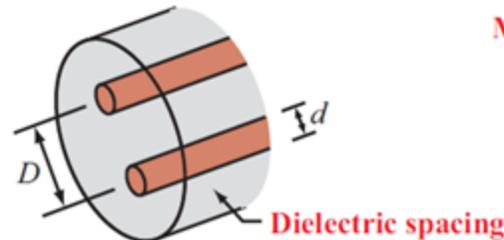

(b) Two-wire line

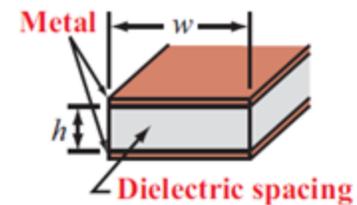


(c) Parallel-plate line

Simulation Example

Module 2.3 **Lossless Microstrip Line**

Select: Permittivity vs. Strip Width ▾

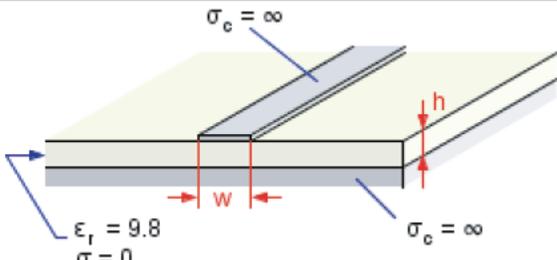


$\epsilon_r = 9.8$
 $\sigma = 0$

$\mu_c = \infty$
 $\sigma_c = \infty$

$f = 1.794$ [GHz]

Effective Relative Permittivity

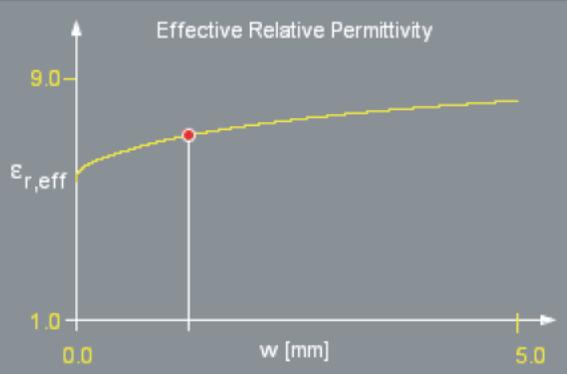

Input

Strip width $w = 1.276$ [mm]

Substrate thickness $h = 0.635$ [mm]

Frequency $f = 1.794E9$ [Hz]

ϵ_r

9.8

Update

Output


Structure Data

$w = 1.276$ [mm] $w/h = 2.009$
 $h = 0.635$ [mm]


$Z_0 = 33.324$ [Ω]
 $\epsilon_{eff} = 7.074$
 $u_p = 1.128$ [10^8 m/s]
 $\lambda_p = 0.063$ [m]

$C' = 266.037$ [pF/m]
 $L' = 295.433$ [nH/m]
 $R' = 0$ [Ω /m]
 $G' = 0$ [S/m]

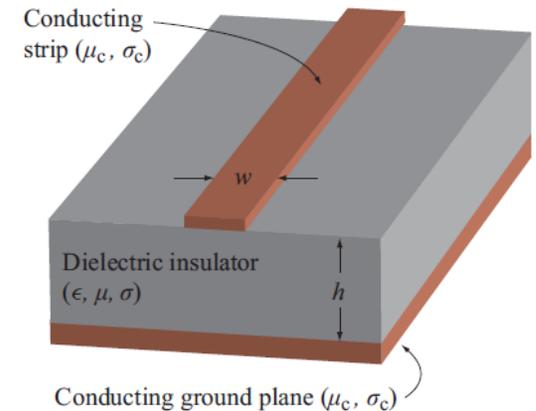
$\alpha = 0$ [Np/m]
 $\beta = 99.932$ [rad/m]



(a) Longitudinal view



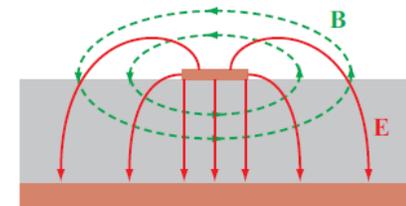


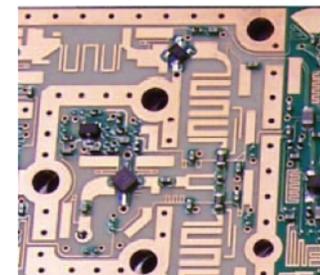(b) Cross-sectional view with E and B field lines




(c) Microwave circuit

Transmission Line Model

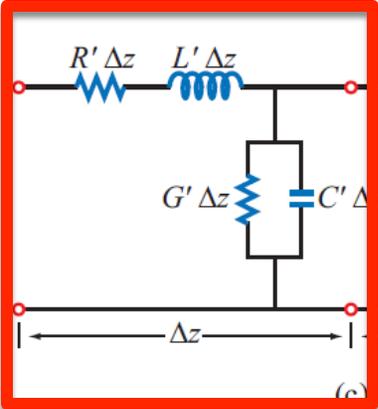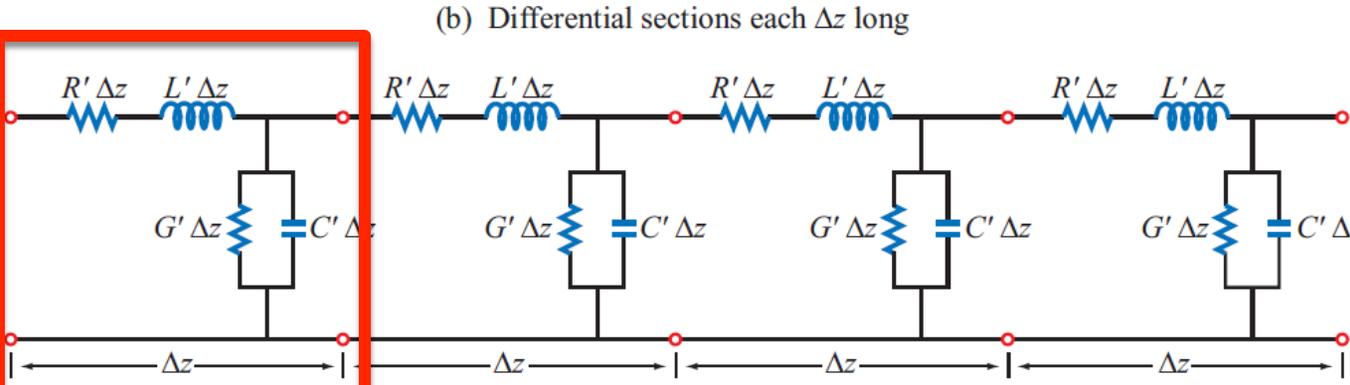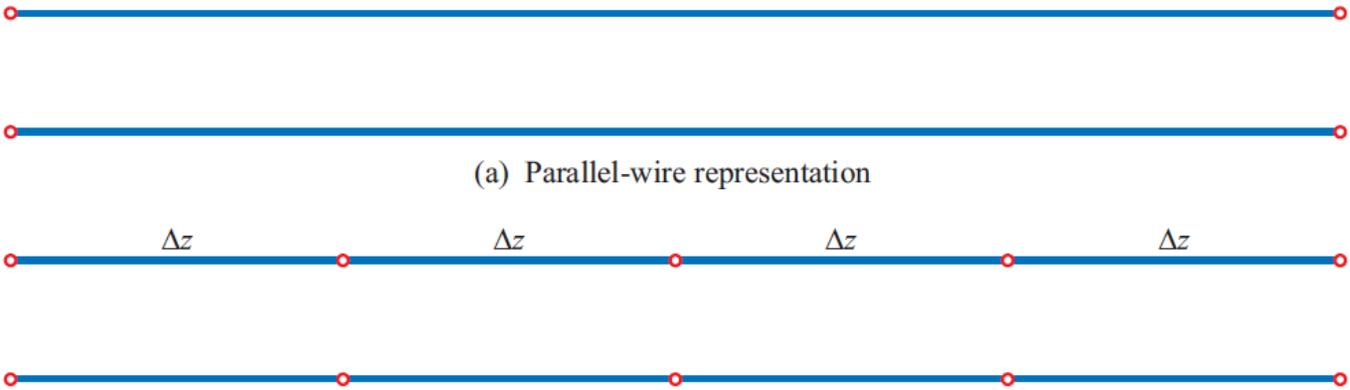

Transmission-Line Equations

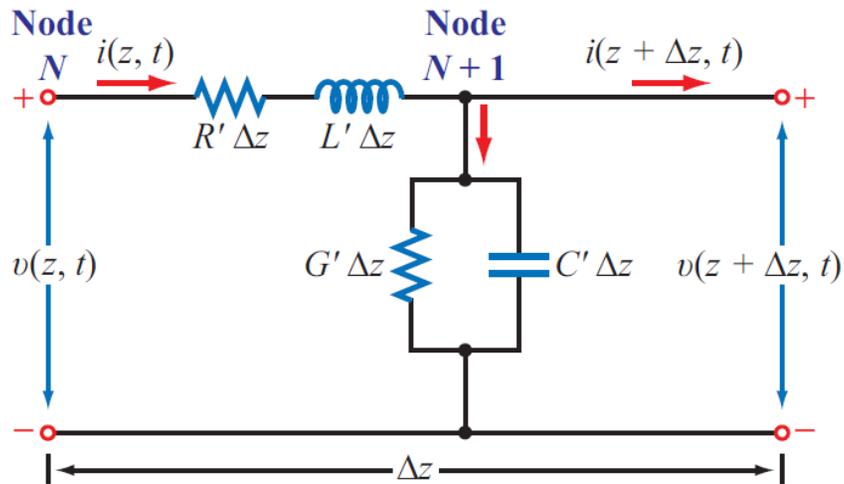

Remember:

Kirchhoff Voltage Law:

$$V_{in} - V_{out} - V_{R'} - V_{L'} = 0$$

Kirchhoff Current Law:

$$I_{in} - I_{out} - I_{C'} - I_{G'} = 0$$

Note:

$$V_L = L \cdot di/dt$$

$$I_C = C \cdot dv/dt$$

$$Ae^{j\theta} = A\cos(\theta) + Aj\sin(\theta)$$

$$\cos(\theta) = A \operatorname{Re}[Ae^{j\theta}]$$


$$\sin(\theta) = A \operatorname{Im}[Ae^{j\theta}]$$

$$E(z) = |E(z)| e^{j\theta_z}$$

$$|e^{j\theta}| = 1$$

$$C = A + jB \rightarrow \theta = \tan^{-1} \frac{B}{A}; |C| = \sqrt{A^2 + B^2}$$

Transmission-Line Equations

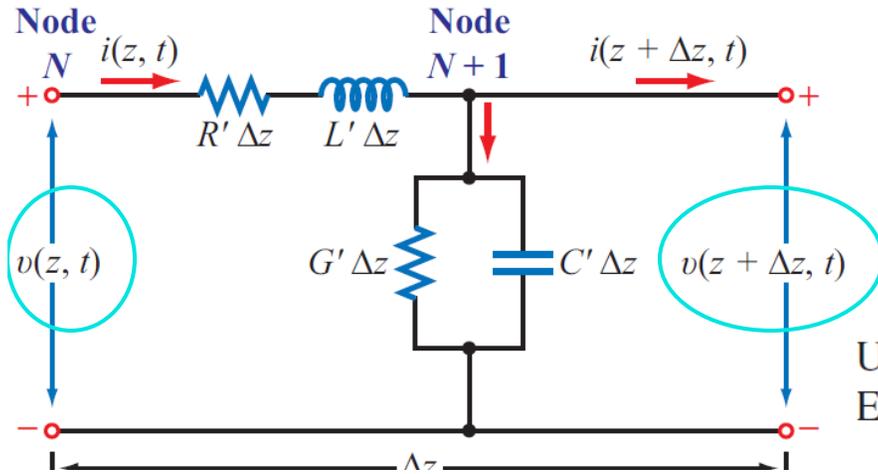

$$i(z, t) - G' \Delta z v(z + \Delta z, t) - C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0.$$

Upon dividing all terms by Δz and taking the limit $\Delta z \rightarrow 0$, Eq. (2.15) becomes a second-order differential equation:

$$v(z, t) - R' \Delta z i(z, t) - L' \Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0.$$

$$-\frac{\partial i(z, t)}{\partial z} = G' v(z, t) + C' \frac{\partial v(z, t)}{\partial t}$$

Upon dividing all terms by Δz and rearranging them, we obtain

$$-\left[\frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} \right] = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}.$$

In the limit as $\Delta z \rightarrow 0$, Eq. (2.13) becomes a differential equation:

$$-\frac{\partial v(z, t)}{\partial z} = R' i(z, t) + L' \frac{\partial i(z, t)}{\partial t}$$

ac signals: use phasors

$$v(z, t) = \Re[\tilde{V}(z) e^{j\omega t}],$$

$$i(z, t) = \Re[\tilde{I}(z) e^{j\omega t}],$$

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$


Transmission
Line Equation
in Phasor
Form

Derivation of Wave Equations

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

$$-\frac{d\tilde{I}(z)}{dz} = (G' + j\omega C') \tilde{V}(z).$$

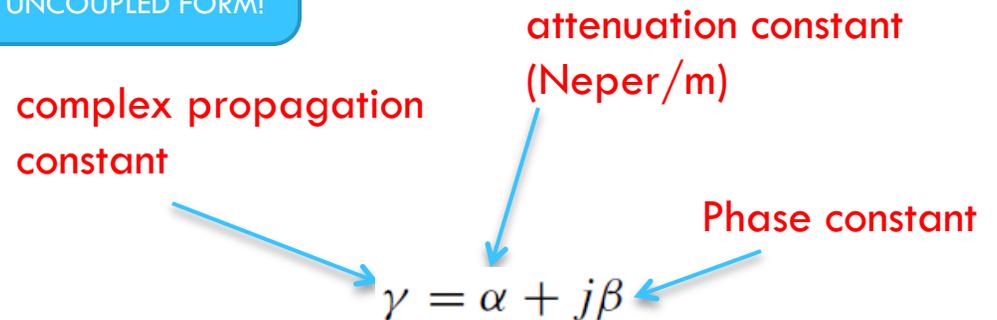Transmission Line Equation
First Order Coupled Equations!
WE WANT UNCOUPLED FORM!



Combining the two equations leads to:

$$\frac{d^2\tilde{V}(z)}{dz^2} - (R' + j\omega L')(G' + j\omega C') \tilde{V}(z) = 0,$$

$$\frac{d^2\tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0$$

Second-order differential equation

Wave Equations for Transmission Line

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}$$

Impedance and Shunt Admittance of the line

$$\alpha = \Re(\gamma)$$

$$= \Re\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{Np/m}),$$

$$\beta = \Im(\gamma)$$

$$= \Im\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{rad/m}).$$

Pay Attention to UNITS!

Solution of Wave Equations (cont.)

Characteristic Impedance of the Line (ohm)

$$\frac{d^2 \tilde{V}(z)}{dz^2} - \gamma^2 \tilde{V}(z) = 0,$$

$$\frac{d^2 \tilde{I}(z)}{dz^2} - \gamma^2 \tilde{I}(z) = 0.$$

Note that Z_0 is NOT $V(z)/I(z)$

$$\frac{V_0^+}{I_0^+} = Z_0 = \frac{-V_0^-}{I_0^-},$$

Using:

$$-\frac{d\tilde{V}(z)}{dz} = (R' + j\omega L') \tilde{I}(z),$$

It follows that: $\tilde{I}(z) = \frac{\gamma}{R' + j\omega L'} [V_0^+ e^{-\gamma z} - V_0^- e^{\gamma z}]$


Proposed form of solution:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$


$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega),$$

So What does V^+ and V^- Represent?

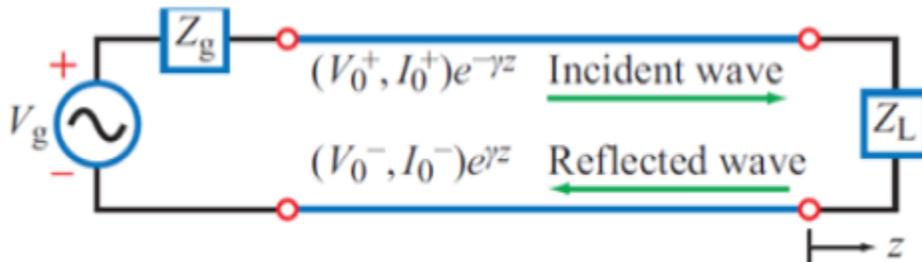

Pay att. To Direction

Solution of Wave Equations (cont.)

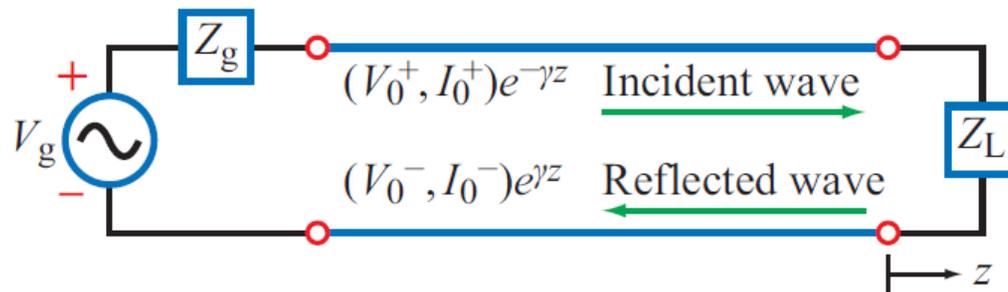

The presence of two waves on the line propagating in opposite directions produces a standing wave.

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

So, $V(z)$ and $I(z)$ have two parts:

Applet for standing wave:

<http://www.physics.smu.edu/~olness/www/05fall1320/applet/pipe-waves.html>

Example: Air-Line

Assume the following waves:

$$V(z,t) = 10 \cos(2\pi \cdot 700 \cdot 10^6 - 20z + 5)$$

$$I(z,t) = 0.2 \cos(2\pi \cdot 700 \cdot 10^6 - 20z + 5)$$

Assume having perfect dielectric insulator and the wire have perfect conductivity with no loss

Draw the transmission line model and Find C' and L' ; Assume perfect conductor and perfect dielectric materials are used!

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega),$$

$$\begin{aligned} \beta &= \Im m(\gamma) \\ &= \Im m\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{rad/m}). \end{aligned}$$

Note: If atten. Is zero \rightarrow real part MUST be zero!

With $R' = G' = 0$,

Perfect Conductor \rightarrow
 $R_s=0 \rightarrow R' = 0$
 Perfect Dielec
 $\rightarrow \text{COND}=0 \rightarrow$
 $G'=0$


$$\begin{aligned} \beta &= \Im m\left[\sqrt{(j\omega L')(j\omega C')}\right] \\ &= \Im m\left(j\omega\sqrt{L'C'}\right) = \omega\sqrt{L'C'}, \\ Z_0 &= \sqrt{\frac{j\omega L'}{j\omega C'}} = \sqrt{\frac{L'}{C'}}. \end{aligned}$$

The ratio of β to Z_0 is

$$\frac{\beta}{Z_0} = \omega C',$$

or

$$C' = \frac{\beta}{\omega Z_0}$$

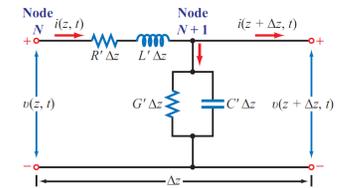

$$\begin{aligned} &= \frac{20}{2\pi \times 7 \times 10^8 \times 50} \\ &= 9.09 \times 10^{-11} \text{ (F/m)} = 90.9 \text{ (pF/m)}. \end{aligned}$$

From $Z_0 = \sqrt{L'/C'}$, it follows that

$$\begin{aligned} L' &= Z_0^2 C' \\ &= (50)^2 \times 90.9 \times 10^{-12} \\ &= 2.27 \times 10^{-7} \text{ (H/m)} = 227 \text{ (nH/m)}. \end{aligned}$$

Transmission Line Characteristics

- Line characterization
 - ▣ Propagation Constant (function of frequency)
 - ▣ Impedance (function of frequency)
 - Lossy or Lossless
- If lossless (low ohmic losses)
 - ▣ Very high conductivity for the insulator
 - ▣ Negligible conductivity for the dielectric

Lossless Transmission Line

$$\gamma = \sqrt{(R' + j\omega L')(G' + j\omega C')}.$$

If $R' \ll \omega L'$ and $G' \ll \omega C'$

Then:

$$\gamma = \alpha + j\beta = j\omega\sqrt{L'C'},$$

$$\begin{aligned} \alpha &= 0 && \text{(lossless line),} \\ \beta &= \omega\sqrt{L'C'} && \text{(lossless line).} \end{aligned}$$

What is Z_0 ?
$$Z_0 = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}}$$

$$\lambda = \frac{2\pi}{\beta} = \frac{2\pi}{\omega\sqrt{L'C'}},$$


$$u_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{L'C'}}.$$

$$\begin{aligned} \beta &= \omega\sqrt{\mu\varepsilon} && \text{(rad/m),} \\ u_p &= \frac{1}{\sqrt{\mu\varepsilon}} && \text{(m/s),} \end{aligned}$$

Non-dispersive line:
All frequency components have the same speed!

The Big Idea....

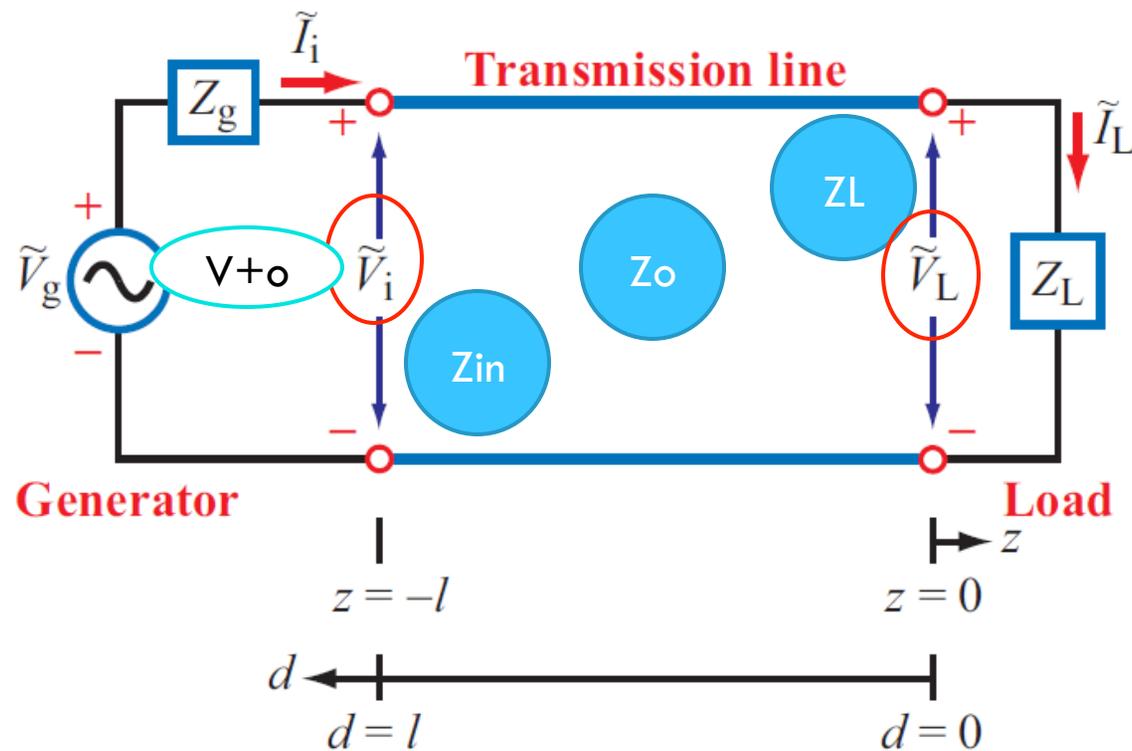Impedance is measured at different points in the circuit!



What is the voltage/current magnitude at different points on the line in the presence of load??

Voltage Reflection Coefficient

Consider looking from the Load point of view

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V})$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A})$$

$$\tilde{V}_L = \tilde{V}(z=0) = V_0^+ + V_0^-$$


$$\tilde{I}_L = \tilde{I}(z=0) = \frac{V_0^+}{Z_0} - \frac{V_0^-}{Z_0}$$

At the load ($z = 0$):

$$Z_L = \frac{\tilde{V}_L}{\tilde{I}_L}$$

$$Z_L = \left(\frac{V_0^+ + V_0^-}{V_0^+ - V_0^-} \right) Z_0$$

The smaller the better!

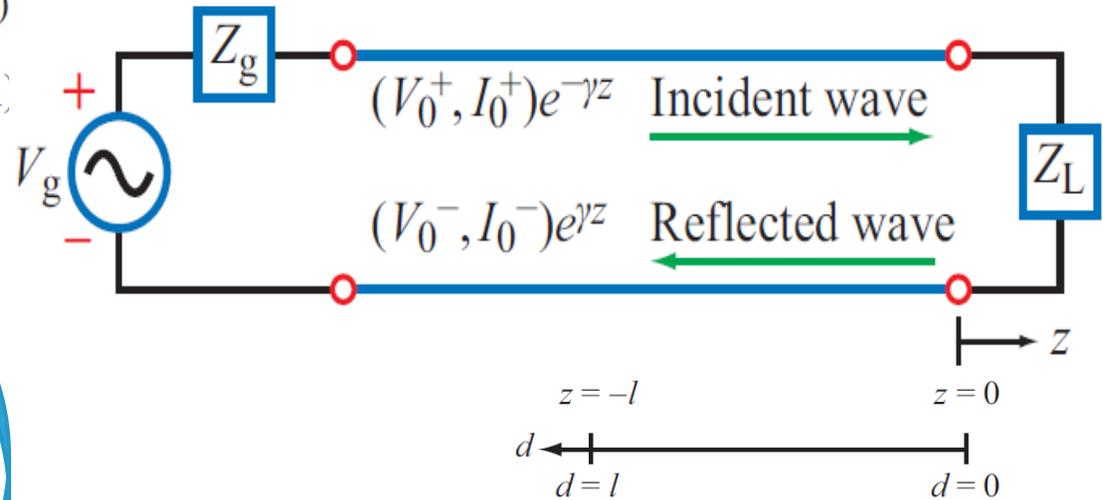

$$\Gamma = \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \quad \text{Reflection coefficient}$$

$$= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1}$$

$$= \frac{z_L - 1}{z_L + 1} \quad (\text{dimensionless}),$$

$$z_L = \frac{Z_L}{Z_0} \quad \text{Normalized load impedance}$$

Expressing wave in phasor form:

□ Remember:

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z} \quad (\text{V}),$$

$$\tilde{I}(z) = I_0^+ e^{-\gamma z} + I_0^- e^{\gamma z} \quad (\text{A}).$$

□ If lossless

□ no attenuation constant

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

$$V_0^- = \Gamma V_0^+$$

All of these wave representations
are **along** the
Transmission Line

Special Line Conditions (Lossless)

- Matching line
 - ▣ $Z_L = Z_0 \rightarrow \Gamma = 0; V_{\text{ref}} = 0$
- Open Circuit
 - ▣ $Z_L = \text{INF} \rightarrow \Gamma = 1; V_{\text{ref}} = V_{\text{inc}}$
- Short Circuit
 - ▣ $Z_L = 0 \rightarrow \Gamma = -1; V_{\text{ref}} = -V_{\text{inc}}$

$$\begin{aligned}\Gamma &= \frac{V_0^-}{V_0^+} = \frac{Z_L - Z_0}{Z_L + Z_0} \\ &= \frac{Z_L/Z_0 - 1}{Z_L/Z_0 + 1} \\ &= \frac{Z_L - 1}{Z_L + 1} \quad (\text{dimensionless}),\end{aligned}$$

Remember:
Everything is with respect
to the load so far!




$$\frac{I_0^-}{I_0^+} = -\frac{V_0^-}{V_0^+} = -\Gamma.$$

$V_{\text{ref}} = V_{\text{reflected}}; V_{\text{inc}} = V_{\text{incident}}$

Voltage Reflection Coefficient

$$\Gamma = |\Gamma| e^{j\theta_r}$$

Reflection Coefficient $\Gamma = |\Gamma| e^{j\theta_r}$

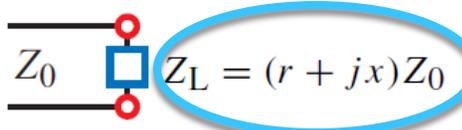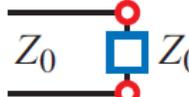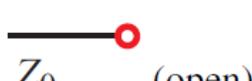Load	$ \Gamma $	θ_r
 $Z_L = (r + jx)Z_0$	$\left[\frac{(r-1)^2 + x^2}{(r+1)^2 + x^2} \right]^{1/2}$	$\tan^{-1} \left(\frac{x}{r-1} \right) - \tan^{-1} \left(\frac{x}{r+1} \right)$
 Z_0	0 (no reflection)	irrelevant
 (short)	1	$\pm 180^\circ$ (phase opposition)
 (open)	1	0 (in-phase)
 $jX = j\omega L$	1	$\pm 180^\circ - 2 \tan^{-1} x$
 $jX = \frac{-j}{\omega C}$	1	$\pm 180^\circ + 2 \tan^{-1} x$


Pay attention!

Normalized load impedance

$$z_L = Z_L / Z_0 = (R + jX) / Z_0 = r + jx$$

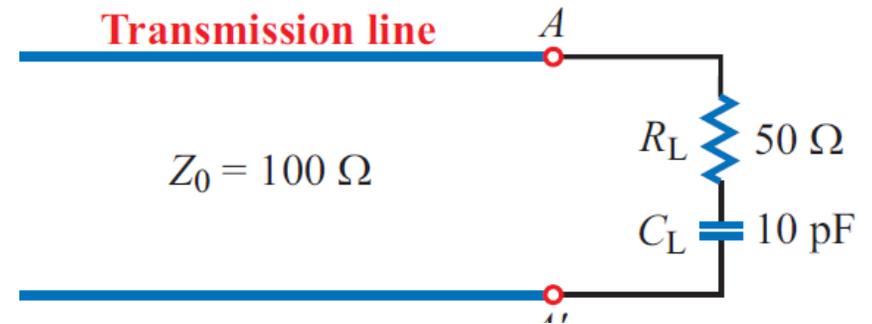Example

A $100\text{-}\Omega$ transmission line is connected to a load consisting of a $50\text{-}\Omega$ resistor in series with a 10-pF capacitor. Find the reflection coefficient at the load for a 100-MHz signal.



Standing Waves


Finding Voltage Magnitude

$$V_0^- = \Gamma V_0^+ \quad \text{When lossless!}$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$

$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

We are interested to know what happens to the magnitude of the $|V|$ as such **interference** is created!

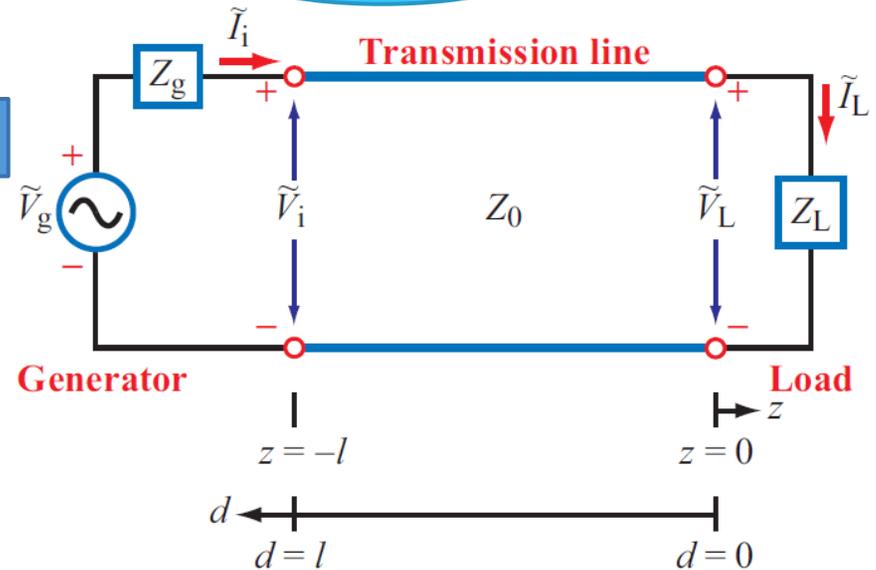


Remember: Standing wave is created due to **interference** between the traveling waves (incident & reflected)

Note: When there is no REFLECTION Coef. Of Ref. = 0 \rightarrow No standing wave!

Standing Wave
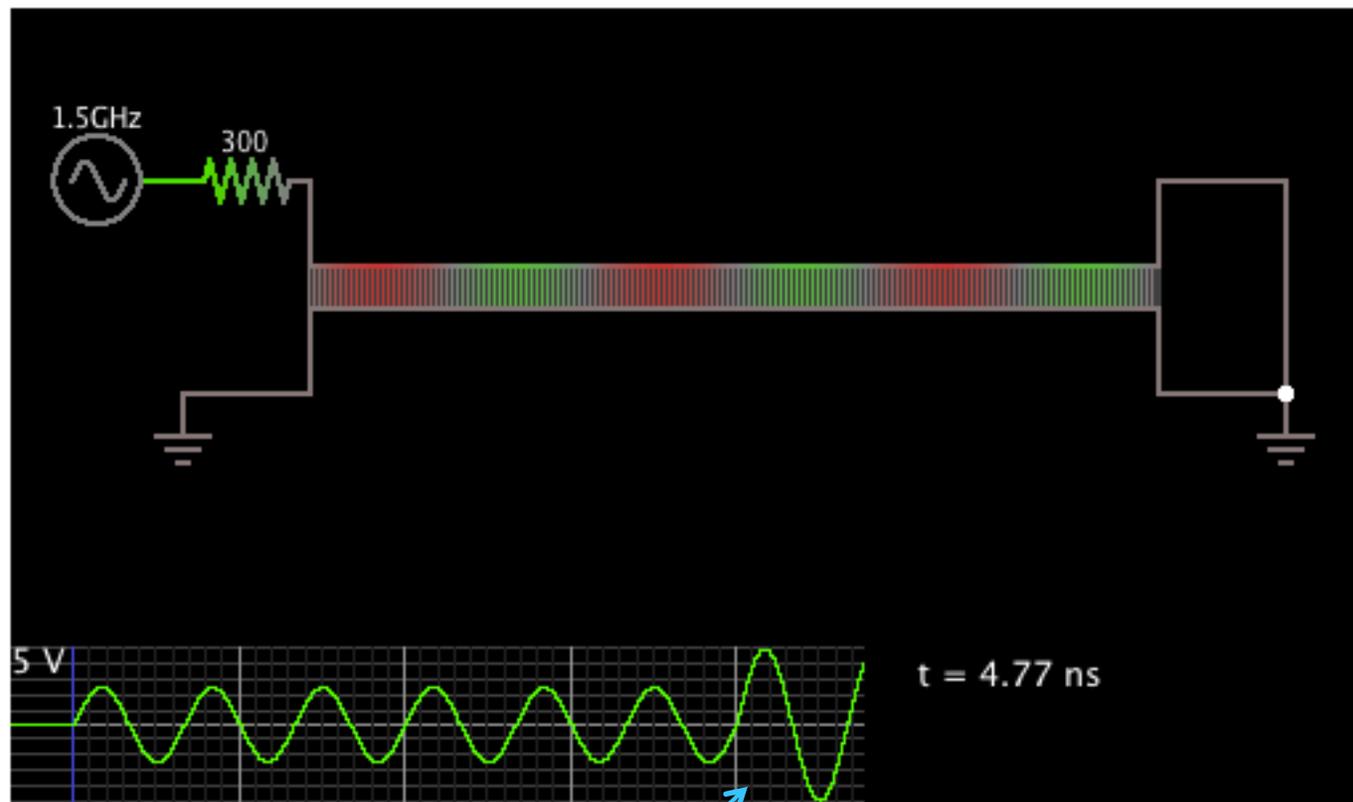
<http://www.falstad.com/circuit/e-tlstand.html>



Due to standing wave the received wave at the load is now different

Standing Waves

Finding Voltage Magnitude

$$V_0^- = \Gamma V_0^+$$

$$\tilde{V}(z) = V_0^+ (e^{-j\beta z} + \Gamma e^{j\beta z}),$$


$$\tilde{I}(z) = \frac{V_0^+}{Z_0} (e^{-j\beta z} - \Gamma e^{j\beta z}).$$

$$|\tilde{V}(d)| = |V_0^+| \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}$$

$$|\tilde{I}(d)| = \frac{|V_0^+|}{Z_0} \left[1 + |\Gamma|^2 - 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}$$

Remember max current occurs where minimum voltage occurs (indicating the two waves are interfering destructively)!

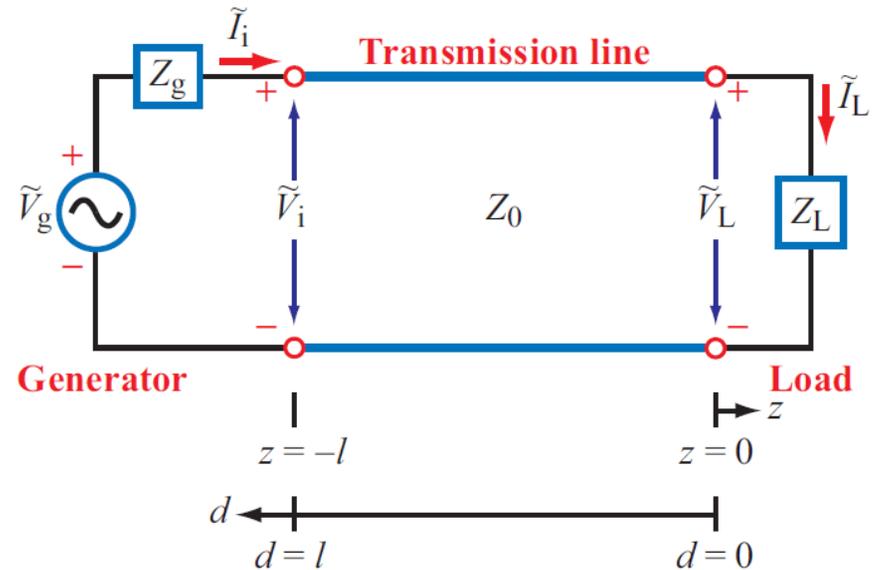Let's see how the magnitude looks like at different z values!




voltage magnitude at $z = -d$

current magnitude at the source

Standing Wave Patterns for 3 Types of Loads



(Matched, Open, Short)

No reflection, No standing wave

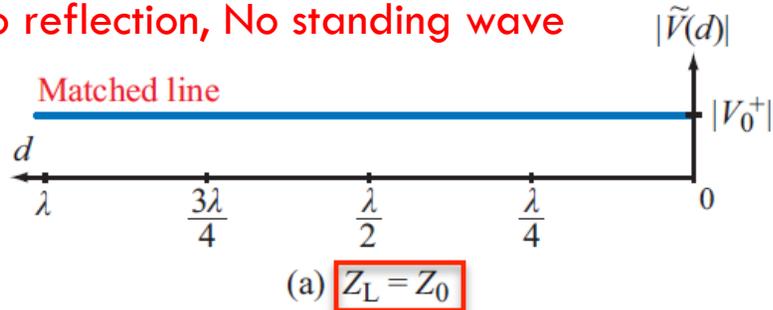

$$|\tilde{V}(d)| = |V_0^+| \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}.$$

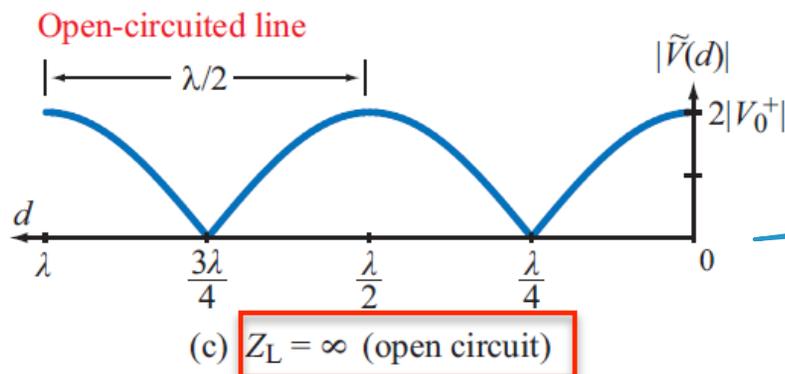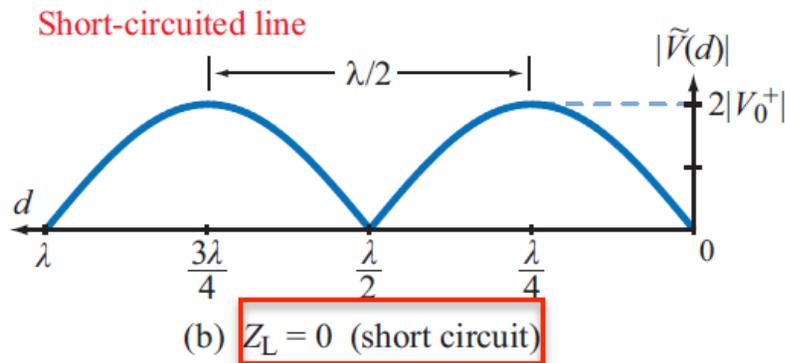- Matching line
 - $Z_L = Z_0 \rightarrow \Gamma = 0; V_{ref} = 0$
- Short Circuit
 - $Z_L = 0 \rightarrow \Gamma = -1; V_{ref} = -V_{inc}$ (angle $-/+ \pi$)
- Open Circuit
 - $Z_L = \infty \rightarrow \Gamma = 1; V_{ref} = V_{inc}$ (angle is 0)




Remember max current occurs where minimum voltage occurs!

Standing Wave Patterns for 3 Types of Loads


(Matched, Open, Short)

No reflection, No standing wave

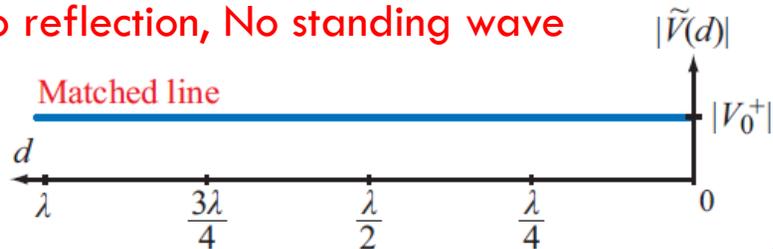


(a) $Z_L = Z_0$

Short-circuited line

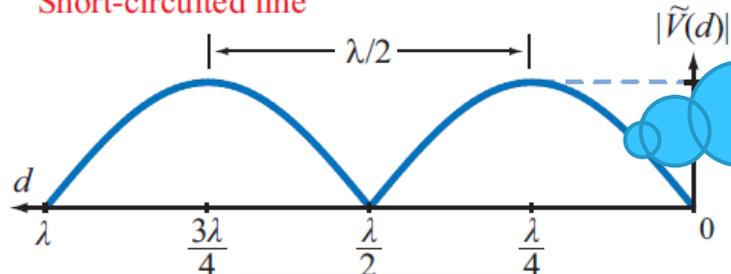

(b) $Z_L = 0$ (short circuit)

Open-circuited line

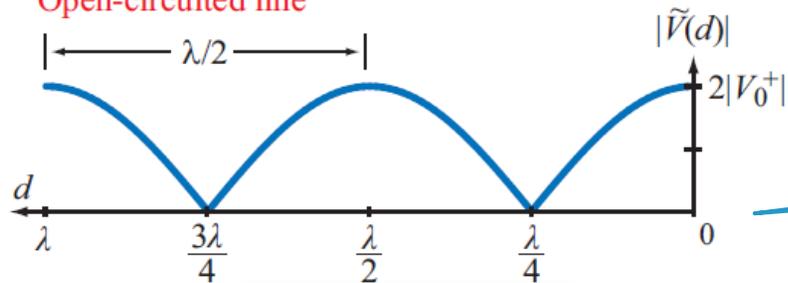

(c) $Z_L = \infty$ (open circuit)

BUT WHEN DO
MAX & MIN
Voltages Occur?

Remember max current occurs
where minimum voltage occurs!

Finding Maxima & Minima Of Voltage Magnitude

$$|\tilde{V}(d)| = |V_0^+| \left[1 + |\Gamma|^2 + 2|\Gamma| \cos(2\beta d - \theta_r) \right]^{1/2}.$$

$$|\tilde{V}|_{\min} = |V_0^+| [1 - |\Gamma|],$$

$$\text{when } (2\beta d_{\min} - \theta_r) = (2n + 1)\pi$$


$$|\tilde{V}(d)| = |\tilde{V}|_{\max} = |V_0^+| [1 + |\Gamma|],$$

$$S = \frac{|\tilde{V}|_{\max}}{|\tilde{V}|_{\min}} = \frac{1 + |\Gamma|}{1 - |\Gamma|} \quad (\text{dimensionless})$$


S = Voltage Standing Wave Ratio (VSWR)

For a matched load: **S = 1**

For a short, open, or purely reactive load:
S(open) = S(short) = INF where $|\Gamma| = 1$;

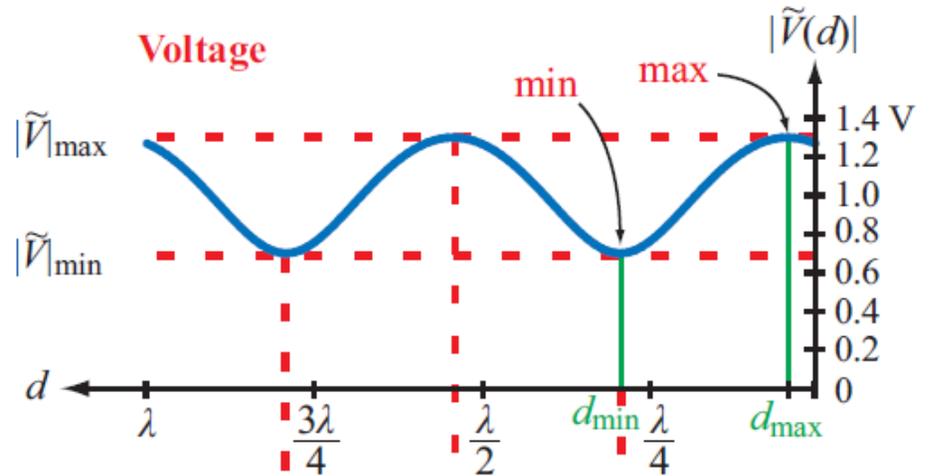


(a) $|\tilde{V}(d)|$ versus d

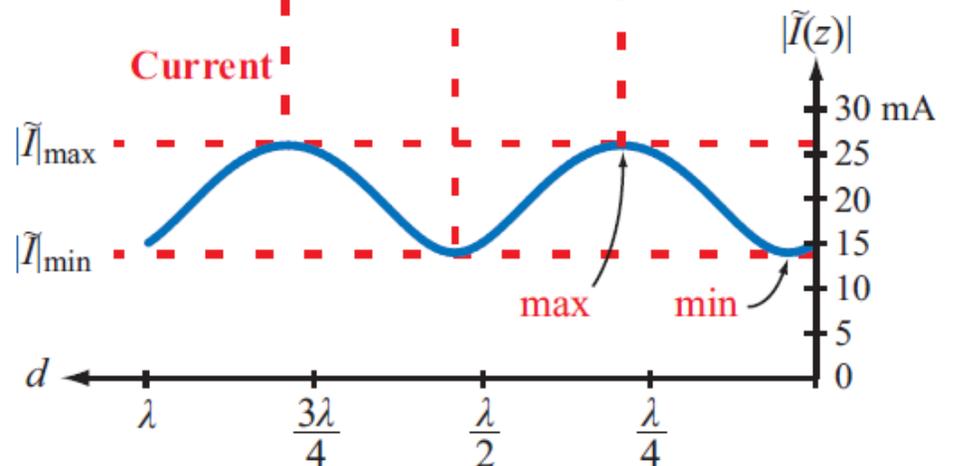

(b) $|\tilde{I}(d)|$ versus d

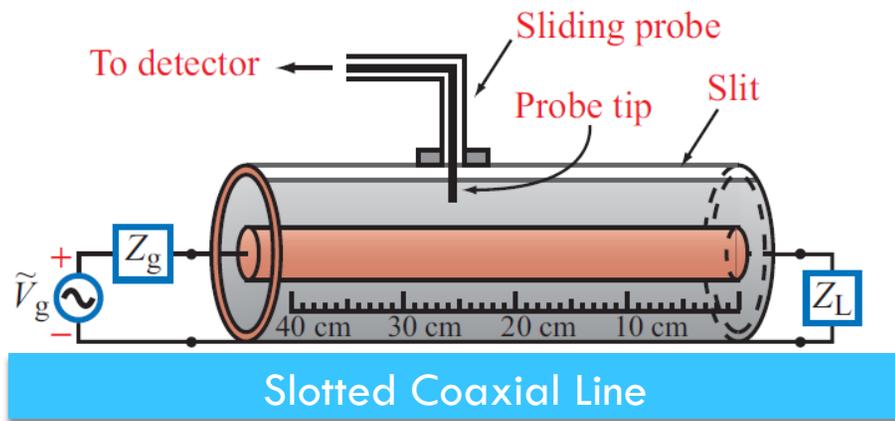Example Measuring Z_L with a Slotted Line



$$Z_0 = 50 \Omega,$$

$$S = 3,$$

$$d_{\min} = 12 \text{ cm}.$$

Since the distance between successive voltage minima is $\lambda/2$,

$$\lambda = 2 \times 0.3 = 0.6 \text{ m},$$

and

$$\beta = \frac{2\pi}{\lambda} = \frac{2\pi}{0.6} = \frac{10\pi}{3} \quad (\text{rad/m}).$$

$$|\Gamma| = \frac{S - 1}{S + 1}$$

$$= \frac{3 - 1}{3 + 1}$$

$$= 0.5.$$

$$2\beta d_{\min} - \theta_r = \pi, \quad \text{for } n = 0 \text{ (first minimum),}$$

which gives

$$\theta_r = 2\beta d_{\min} - \pi$$

$$= 2 \times \frac{10\pi}{3} \times 0.12 - \pi$$

$$= -0.2\pi \text{ (rad)}$$

$$= -36^\circ.$$

Hence,

$$\Gamma = |\Gamma|e^{j\theta_r}$$

$$= 0.5e^{-j36^\circ}$$

$$= 0.405 - j0.294.$$

$$Z_L = Z_0 \left[\frac{1 + \Gamma}{1 - \Gamma} \right]$$

$$= 50 \left[\frac{1 + 0.405 - j0.294}{1 - 0.405 + j0.294} \right]$$

$$= (85 - j67) \Omega.$$

What is the Reflection Coefficient (Γ_d) at any point away from the load? (assume lossless line)


At a distance d from the load:

$$\begin{aligned}
 Z(d) &= \frac{\tilde{V}(d)}{\tilde{I}(d)} \\
 &= \frac{V_0^+ [e^{j\beta d} + \Gamma e^{-j\beta d}]}{V_0^+ [e^{j\beta d} - \Gamma e^{-j\beta d}]} Z_0 \\
 &= Z_0 \left[\frac{1 + \Gamma e^{-j2\beta d}}{1 - \Gamma e^{-j2\beta d}} \right] \\
 &= Z_0 \left[\frac{1 + \Gamma_d}{1 - \Gamma_d} \right] \quad (\Omega),
 \end{aligned}$$

where we define

$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j\theta_r} e^{-j2\beta d} = |\Gamma| e^{j(\theta_r - 2\beta d)}$$

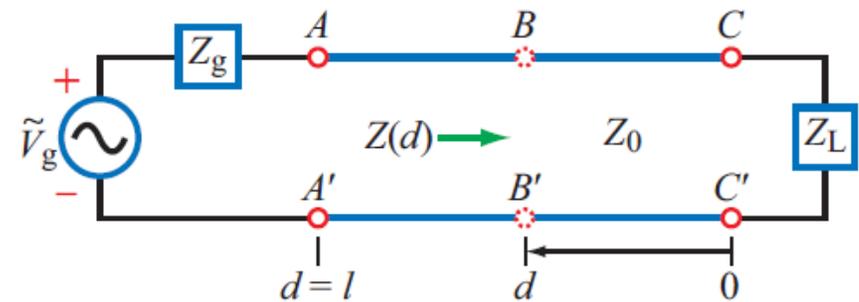as the *phase-shifted voltage reflection coefficient*,



(a) Actual circuit

Wave impedance

Example

<http://www.bessernet.com/Ereflecto/tutorialFrameset.htm>

Reflectometer Calculator

Type a value in one of the fields below and hit 'enter':

Reflection Coefficient

SWR

Return Loss



Mismatch Loss


eR

Z1

Show two interfaces

Resume

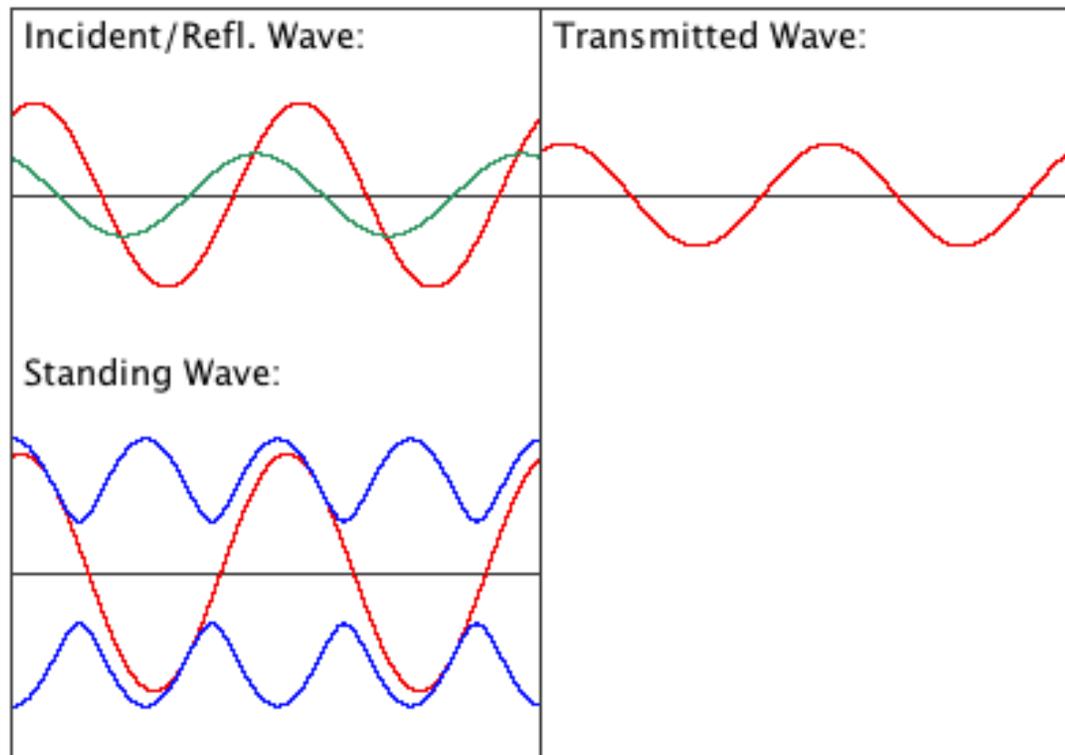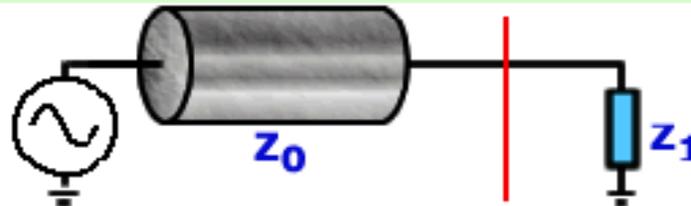

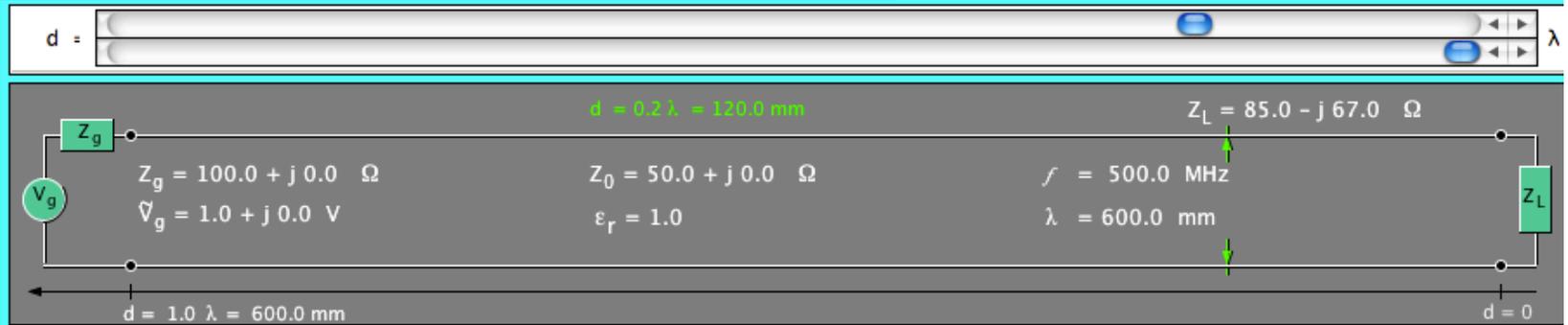

Example

Set Line
Length units: [λ] [m]

Low Loss Approximation

Characteristic Impedance $Z_0 = 50.0 \Omega$
Frequency $f = 5.0E8 \text{ Hz}$
Relative Permittivity $\epsilon_r = 1.0$
Line Length $l = 1.0 \lambda$

$Z_L = 85 + j -67 \Omega$
 Impedance Admittance
Update

Set Generator

$V_g = 1.0 + j 0.0 \text{ V}$
 $Z_g = 100.0 + j 0.0 \Omega$


Output Transmission Line Data 2

SWR = 3.0125 (load)



Amplitude of Incident Voltage Wave [V]
 $V_0^+ = 0.380534 - j 0.043266$
= 0.382986 $\angle -0.1132 \text{ rad}$

Location of First Voltage Maximum & Minimum
 $d(\text{max}) = 0.44997 \lambda = 269.9809 \text{ mm}$
 $d(\text{min}) = 0.19997 \lambda = 119.9809 \text{ mm}$

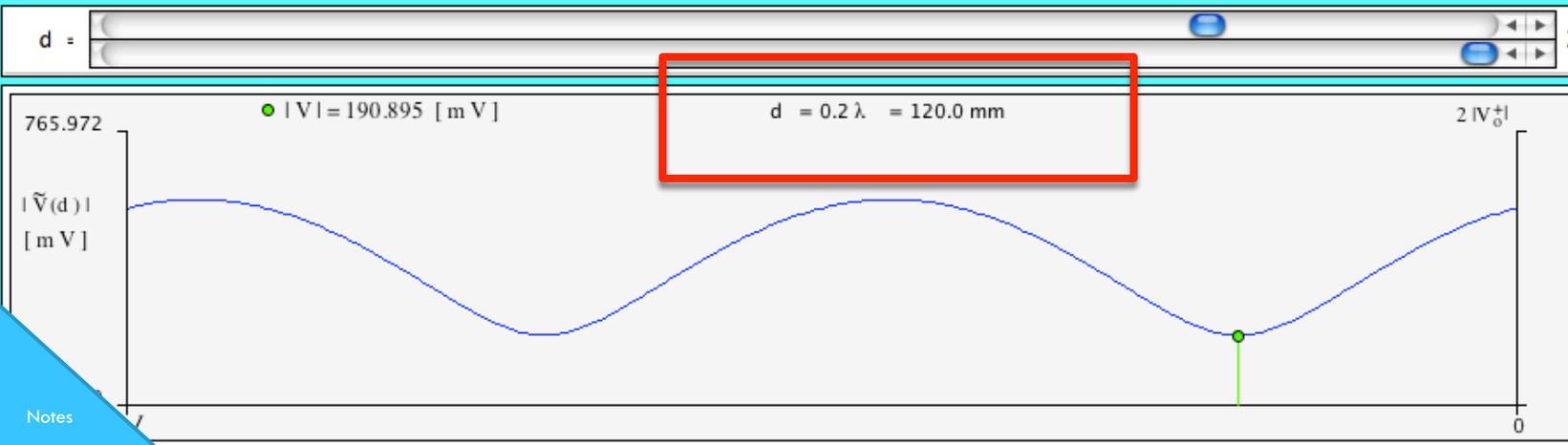TIME-AVERAGE POWER
 $P(\text{abs}) = 1.097794 \text{ [mW]}$ Absorbed by load
 $P(Z_g) = 1.291522 \text{ [mW]}$ Absorbed by Z_g



Input Impedance

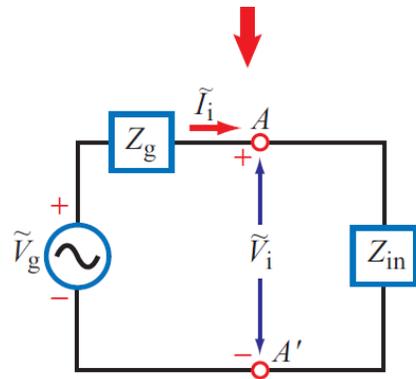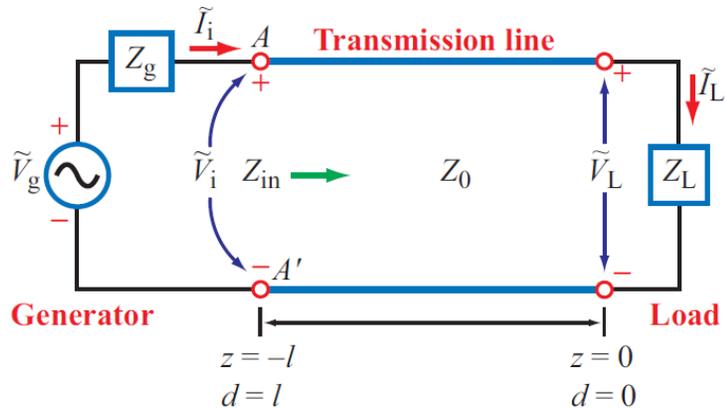

At input, $d = l$:
$$Z_{in} = Z(l) = Z_0 \left[\frac{1 + \Gamma_l}{1 - \Gamma_l} \right].$$

$$\Gamma_l = \Gamma e^{-j2\beta l} = |\Gamma| e^{j(\theta_r - 2\beta l)}.$$

Wave Impedance

$$Z_d = Z_0 \left[\frac{1 + \Gamma_d}{1 - \Gamma_d} \right]$$


$$\begin{aligned} Z_{in} &= Z_0 \left(\frac{z_L \cos \beta l + j \sin \beta l}{\cos \beta l + j z_L \sin \beta l} \right) \\ &= Z_0 \left(\frac{z_L + j \tan \beta l}{1 + j z_L \tan \beta l} \right). \end{aligned}$$

Short-Circuit/Open-Circuit Method

- For a line of known length l , measurements of its input impedance, one when terminated in a short and another when terminated in an open, can be used to find its characteristic impedance Z_0 and electrical length βl

$$Z_{\text{in}}^{\text{sc}} = \frac{\tilde{V}_{\text{sc}}(l)}{\tilde{I}_{\text{sc}}(l)} = jZ_0 \tan \beta l.$$
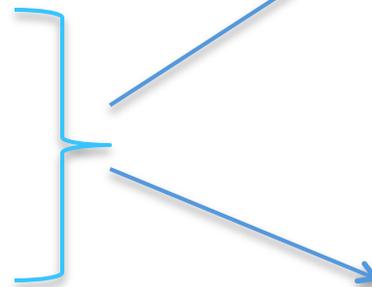
$$Z_{\text{in}}^{\text{oc}} = \frac{\tilde{V}_{\text{oc}}(l)}{\tilde{I}_{\text{oc}}(l)} = -jZ_0 \cot \beta l.$$



$$Z_0 = \sqrt{+Z_{\text{in}}^{\text{sc}} Z_{\text{in}}^{\text{oc}}},$$

$$\tan \beta l = \sqrt{\frac{-Z_{\text{in}}^{\text{sc}}}{Z_{\text{in}}^{\text{oc}}}}.$$

Standing Wave Properties

Voltage Maximum	$ \tilde{V} _{\max} = V_0^+ [1 + \Gamma]$
Voltage Minimum	$ \tilde{V} _{\min} = V_0^+ [1 - \Gamma]$
Positions of voltage maxima (also positions of current minima)	$d_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}, \quad n = 0, 1, 2, \dots$
Position of first maximum (also position of first current minimum)	$d_{\max} = \begin{cases} \frac{\theta_r \lambda}{4\pi}, & \text{if } 0 \leq \theta_r \leq \pi \\ \frac{\theta_r \lambda}{4\pi} + \frac{\lambda}{2}, & \text{if } -\pi \leq \theta_r \leq 0 \end{cases}$
Positions of voltage minima (also positions of current maxima)	$d_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}, \quad n = 0, 1, 2, \dots$
Position of first minimum (also position of first current maximum)	$d_{\min} = \frac{\lambda}{4} \left(1 + \frac{\theta_r}{\pi} \right)$
Input Impedance	$Z_{\text{in}} = Z_0 \left(\frac{z_L + j \tan \beta l}{1 + j z_L \tan \beta l} \right) = Z_0 \left(\frac{1 + \Gamma_l}{1 - \Gamma_l} \right)$
Positions at which Z_{in} is real	at voltage maxima and minima
Z_{in} at voltage maxima	$Z_{\text{in}} = Z_0 \left(\frac{1 + \Gamma }{1 - \Gamma } \right)$
Z_{in} at voltage minima	$Z_{\text{in}} = Z_0 \left(\frac{1 - \Gamma }{1 + \Gamma } \right)$
Z_{in} of short-circuited line	$Z_{\text{in}}^{\text{sc}} = j Z_0 \tan \beta l$
Z_{in} of open-circuited line	$Z_{\text{in}}^{\text{oc}} = -j Z_0 \cot \beta l$
Z_{in} of line of length $l = n\lambda/2$	$Z_{\text{in}} = Z_L, \quad n = 0, 1, 2, \dots$
Z_{in} of line of length $l = \lambda/4 + n\lambda/2$	$Z_{\text{in}} = Z_0^2 / Z_L, \quad n = 0, 1, 2, \dots$
Z_{in} of matched line	$Z_{\text{in}} = Z_0$
$ V_0^+ $ = amplitude of incident wave; $\Gamma = \Gamma e^{j\theta_r}$ with $-\pi < \theta_r < \pi$; θ_r in radians; $\Gamma_l = \Gamma e^{-j2\beta l}$.	

Power Flow

□ How much power is flowing and reflected?

□ Instantaneous $P(d,t) = v(d,t) \cdot i(d,t)$

■ Incident

■ Reflected

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)],$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$

□ Average power: $P_{av} = P_{av}^i + P_{av}^r$

■ Time-domain Approach

■ Phasor-domain Approach (z and t independent)

■ $\frac{1}{2} \operatorname{Re}\{I^*(z) \cdot V(z)\}$


Average Power

(Phasor Approach)

Avg Power: $\frac{1}{2} \text{Re}\{I(z) * V_{-}(z)\}$

$$P^i(d, t) = \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t + 2\beta d + 2\phi^+)]$$

$$P^r(d, t) = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} [1 + \cos(2\omega t - 2\beta d + 2\phi^+ + 2\theta_r)].$$

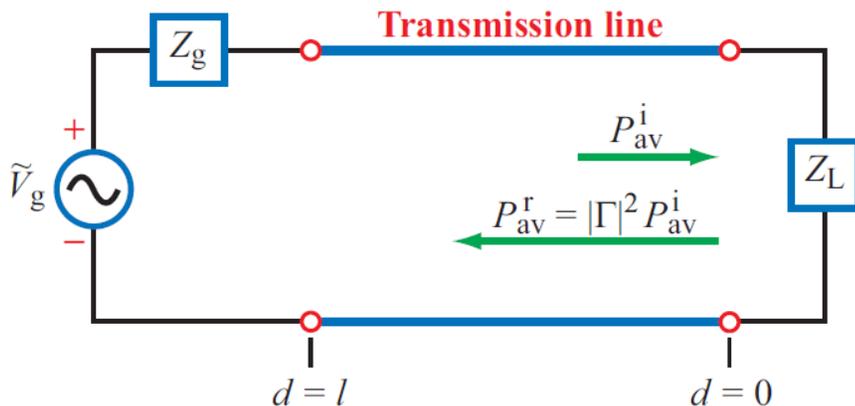

$$V_0^+ = \left(\frac{\tilde{V}_g Z_{in}}{Z_g + Z_{in}} \right) \left(\frac{1}{e^{j\beta l} + \Gamma e^{-j\beta l}} \right).$$

Fraction of power reflected!

$$P_{av}^i = \frac{|V_0^+|^2}{2Z_0} \quad (\text{W}),$$

which is identical with the dc term of $P^i(d, t)$ given by Eq. (2.102a). A similar treatment for the reflected wave gives

$$P_{av}^r = -|\Gamma|^2 \frac{|V_0^+|^2}{2Z_0} = -|\Gamma|^2 P_{av}^i.$$

The average reflected power is equal to the average incident power, diminished by a multiplicative factor of $|\Gamma|^2$.

Summary

TEM Transmission Lines

$$L'C' = \mu\varepsilon$$

$$\frac{G'}{C'} = \frac{\sigma}{\varepsilon}$$

$$\alpha = \Re(\gamma) = \Re\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{Np/m})$$

$$\beta = \Im(\gamma) = \Im\left(\sqrt{(R' + j\omega L')(G' + j\omega C')}\right) \quad (\text{rad/m})$$

$$Z_0 = \frac{R' + j\omega L'}{\gamma} = \sqrt{\frac{R' + j\omega L'}{G' + j\omega C'}} \quad (\Omega)$$

$$\Gamma = \frac{z_L - 1}{z_L + 1}$$

Step Function Transient Response

$$V_1^+ = \frac{V_g Z_0}{R_g + Z_0}$$

$$V_\infty = \frac{V_g R_L}{R_g + R_L}$$

$$\Gamma_g = \frac{R_g - Z_0}{R_g + Z_0}$$

$$\Gamma_L = \frac{R_L - Z_0}{R_L + Z_0}$$

Lossless Line

$$\alpha = 0$$

$$\beta = \omega\sqrt{L'C'}$$

$$Z_0 = \sqrt{\frac{L'}{C'}}$$

$$u_p = \frac{1}{\sqrt{\mu\varepsilon}} \quad (\text{m/s})$$

$$\lambda = \frac{u_p}{f} = \frac{c}{f} \frac{1}{\sqrt{\varepsilon_r}} = \frac{\lambda_0}{\sqrt{\varepsilon_r}}$$

$$d_{\max} = \frac{\theta_r \lambda}{4\pi} + \frac{n\lambda}{2}$$

$$d_{\min} = \frac{\theta_r \lambda}{4\pi} + \frac{(2n+1)\lambda}{4}$$

$$S = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

$$P_{\text{av}} = \frac{|V_0^+|^2}{2Z_0} [1 - |\Gamma|^2]$$

Practice

- 1- Assume the load is $100 + j50$ connected to a 50 ohm line. Find coefficient of reflection (mag, & angle) and SWR. Is it matched well?
- 2- For a 50 ohm lossless transmission line terminated in a load impedance $Z_L = 100 + j50$ ohm, determine the fraction of the average incident power reflected by the load. Also, what is the magnitude of the average reflected power if $|V_o| = 1$?
- 3- Make sure you understand the slotted line problem.
- 4- Complete the Simulation Lab answer the following questions:
 - Remove the MLOC so the TEE will be open. How does the result change? Take a snapshot. Briefly explain.
 - In the original circuit, what happen if we use paper as the dielectric (paper has ϵ_r of 3.85). Take a snapshot. Briefly explain.
 - For the obtained Z_o in your Smith Chart calculate the admittance. You must show all your work.
 - What exactly is $\text{mag}(S_{11})$? How is it different from coefficient of reflection? Is the reflection of coefficient measured at the source or load?
 - What happens if the impedance of the source (TERM1) is changed to 25 ohm? How does the impedance on the smith chart change?
 - How do you calculate the effective length?