

Register Files - HDL


Last updated 2/22/21

Register Files - HDL


- These slides introduce VHDL based Register Files
- Upon completion: You should be able design and use Register Files

Register Files - HDL

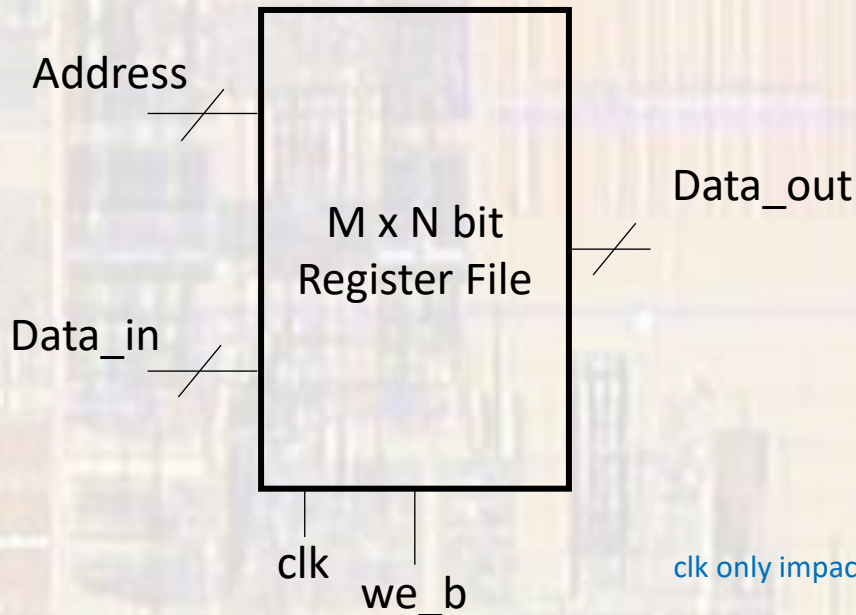- Register File – simple
 - Group of n-bit registers
 - Accessed via a multiplexor (address)




clk only impacts writes

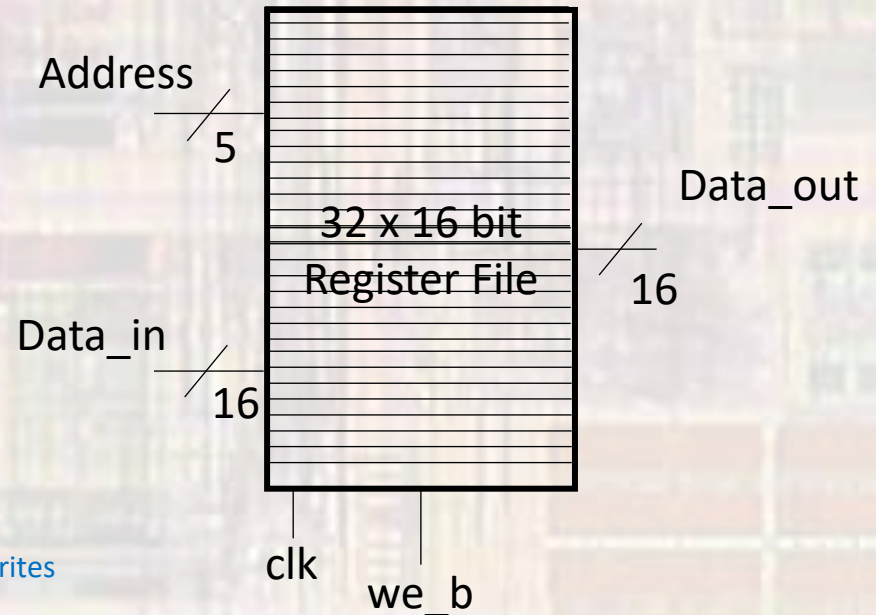

Register Files - HDL

- Register File – simple
 - Output data (from reg at Address) – always available
 - Write requires we_b low and clk ↑

	we_b	addr	data_in	data_out
	1	7	472	?
clk ↑ →	0	7	472	?
	1	7	472	472
	1	7	93	472
	1	12	93	?
clk ↑ →	0	12	93	93
	1	12	93	?
	1	23	0	?
clk ↑ →	0	23	0	0
	1	23	0	472
	1	7	55	93
	1	12	55	

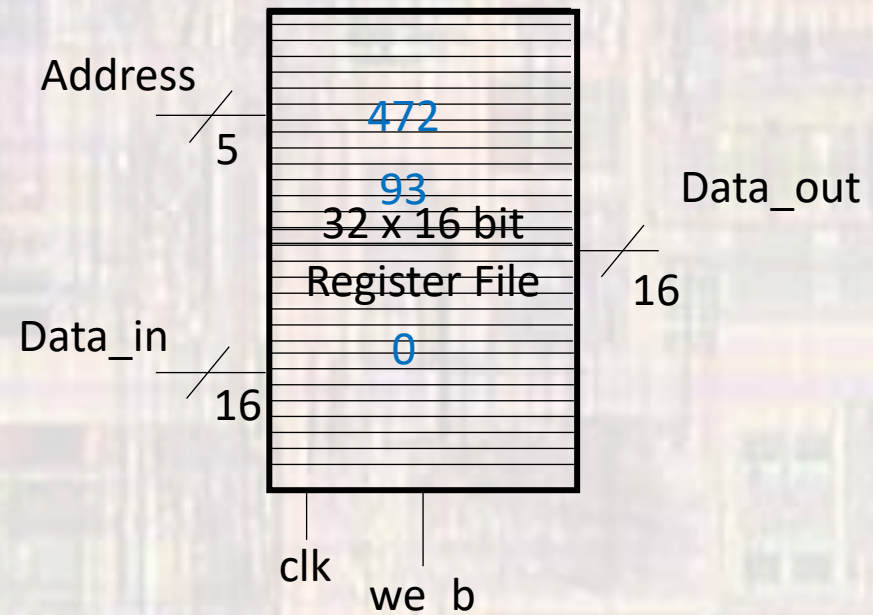


clk only required for writes, reads are asynchronous

In normal application, clock would always be running


Register Files - HDL

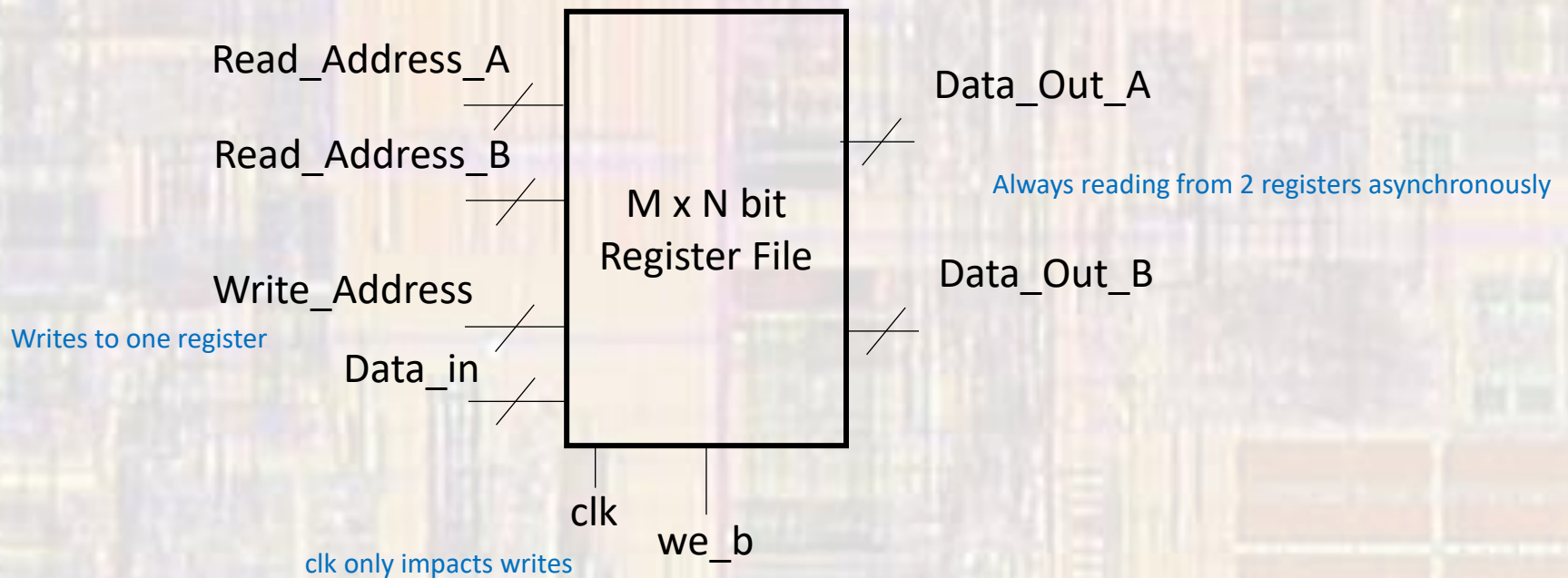- Register File – multi-port
 - Group of n-bit registers
 - Accessed via a multiplexor
 - Can have multiple inputs and outputs



Register Files - HDL

- 32 x 8 bit register file

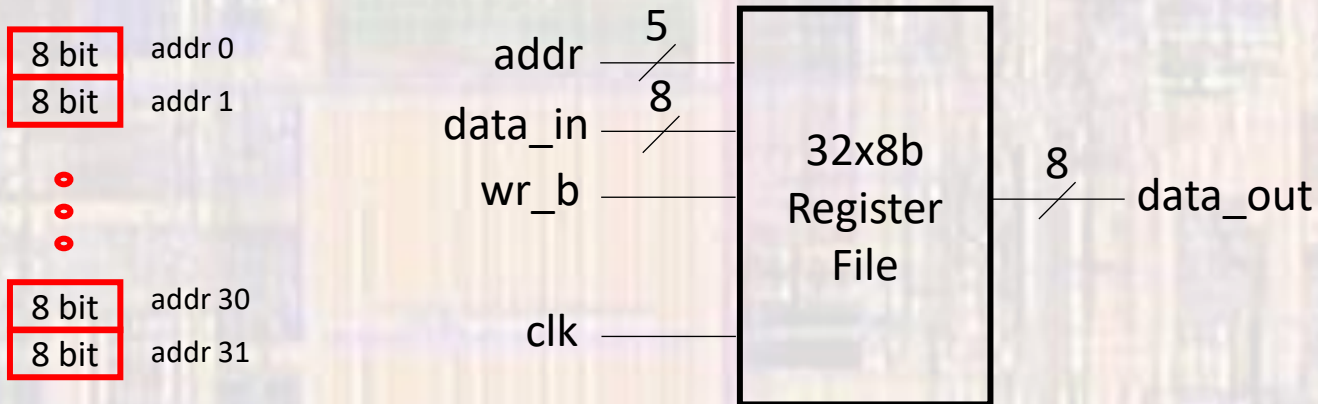

Register Files - HDL

- 32 x 8 bit register file

```
-- reg_file_32x8b
-- created by johnsontimoj
-- 5/7/18
-- rev 0
--
-- Support for 32, 8 bit registers
-- Support for 1 data outputs
-- Support for 1 data input
--
-----
-- Inputs: clk, reg address, data in, we_bar
-- Outputs: data out
-----

library ieee;
use ieee.std_logic_1164.all;
use ieee.numeric_std.all;

entity reg_file_32x8b is
  port (
    i_clk:          in std_logic;
    i_addr:         in std_logic_vector(4 downto 0); --32 registers
    i_data_in:      in std_logic_vector(7 downto 0); -- 8 bit data
    i_we_b:         in std_logic;
    o_data_out:     out std_logic_vector(7 downto 0) -- 8 bit data
  );
end entity;
```

Register Files - HDL


- 32 x 8 bit register file

Create a new 'type'
The new 'type' is an array of std_logic_vector

```
architecture behavioral of reg_file_32x8b is
  -- Create an "TYPE" for an array of 8 bit registers
  type REG_FILE is array(0 to 31) of std_logic_vector(7 downto 0);
  -- Create a signal of the array type
  signal reg_32x8b: REG_FILE;
  --
  -- Special command to stop Quartus from inferring a RAM
  -- Must also turn off assignments / settings / compiler settings/
  -- advanced settings (synthesis) / auto RAM replacement --> off
  attribute ramstyle : string;
  attribute ramstyle of reg_32x8b : signal is "logic";

begin
  -- register logic
  process(i_clk)
  begin
    if(rising_edge(i_clk)) then
      if(i_we_b = '0') then
        reg_32x8b(to_integer(unsigned(i_addr))) <= i_data_in;
      end if;
    end if;
  end process;


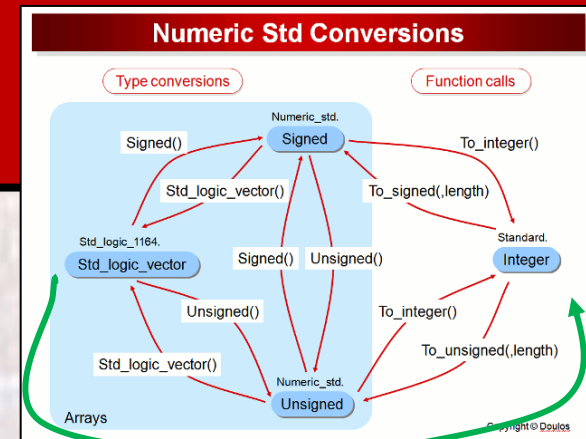
  -- output logic
  process(all)
  begin
    o_data_out <= reg_32x8b(to_integer(unsigned(i_addr)));
  end process;
end behavioral;
```



Need the address as an integer to index the array.
Address is SLV coming in – need to pass through unsigned along the way

Register Files - HDL

- 32 x 8 bit register file

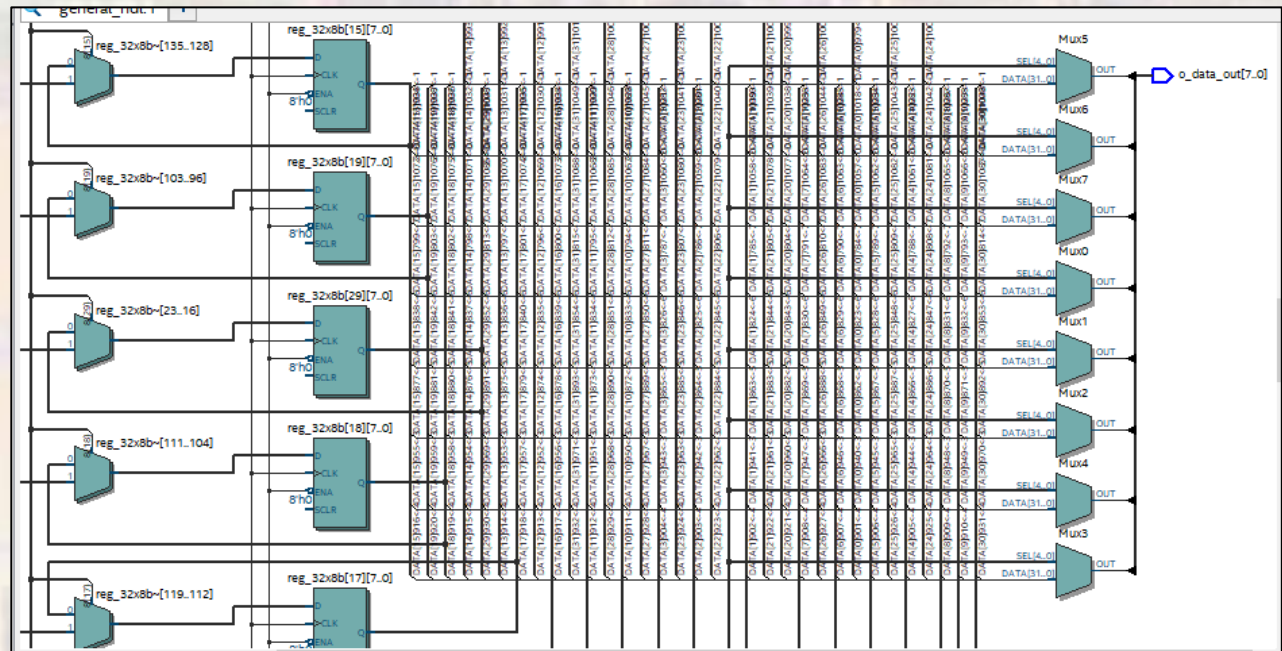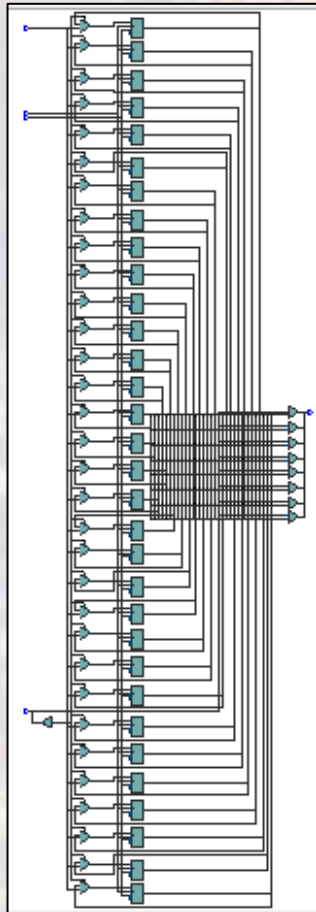

Register Files - HDL

- 32 x 8 bit register file - testbench

```
-----  
-- reg_file_32x8b_tb.vhd1  
--  
-- created: 3/18/18  
-- by: johnsontimj  
-- rev: 0  
--  
-- testbench for 32 by 8 bit register file  
-- of reg_file_32x8b.vhd1  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity reg_file_32x8b_tb is  
  -- no port entry - testbench  
end entity;  
  
architecture testbench of reg_file_32x8b_tb is  
  signal CLK: std_logic;  
  signal DATA_IN: std_logic_vector(7 downto 0);  
  signal ADDR: std_logic_vector(4 downto 0);  
  signal WE_B: std_logic;  
  
  signal DATA_OUT: std_logic_vector(7 downto 0);  
  
  constant PER: time := 20 ns;
```

```
-----  
-- Component prototype  
-----  
component reg_file_32x8b is  
  port (  
    i_clk: in std_logic;  
    i_addr: in std_logic_vector(4 downto 0); --32 registers  
    i_data_in: in std_logic_vector(7 downto 0); -- 8 bit data  
    i_we_b: in std_logic;  
  
    o_data_out: out std_logic_vector(7 downto 0) -- 8 bit data  
  );  
end component;  
  
begin  
  
-----  
-- Device under test (DUT)  
-----  
DUT: reg_file_32x8b  
  port map(  
    i_clk => CLK,  
    i_addr => ADDR,  
    i_we_b => WE_B,  
    i_data_in => DATA_IN,  
    o_data_out => DATA_OUT  
  );
```

Register Files - HDL




- 32 x 8 bit register file - testbench

```
-----  
-- Test processes  
-----  
  
-- Clock process  
clock: process -- note - no sensitivity list allowed  
begin  
  CLK <= '0';  
  wait for PER/2;  
  infinite: loop  
    CLK <= not CLK; wait for PER/2;  
  end loop;  
end process;  
  
-- Reset process  
-- no reset  
  
-- Run Process  
run: process -- note - no sensitivity list allowed  
begin  
  -- initialize inputs  
  DATA_IN <= "00000000";  
  WE_B <= '1';  
  ADDR <= (others => '0');  
  
  -- read with no write prior - should be unknowns  
  wait for 2*PER;  
  WE_B <= '1';  
  wait for PER;  
  for i in 0 to 31 loop  
    ADDR <= std_logic_vector(to_unsigned(i, 5));  
    DATA_IN <= x"A5";  
    wait for 2*PER;  
  end loop;  
  
  -- write  
  WE_B <= '0';  
  wait for PER;  
  for i in 0 to 31 loop  
    ADDR <= std_logic_vector(to_unsigned(i, 5));  
    DATA_IN <= not DATA_IN; -- toggles A5 and 5A  
    wait for 2*PER;  
  end loop;  
  
end process;
```

```
-- read  
wait for 2*PER;  
WE_B <= '1';  
wait for PER;  
for i in 0 to 31 loop  
  ADDR <= std_logic_vector(to_unsigned(i, 5));  
  DATA_IN <= x"00";  
  wait for 2*PER;  
end loop;  
  
-- read again to make sure write did not occur  
-- overwrite with 1s  
wait for 2*PER;  
WE_B <= '0';  
wait for PER;  
for i in 0 to 31 loop  
  ADDR <= std_logic_vector(to_unsigned(i, 5));  
  DATA_IN <= x"FF";  
  wait for 2*PER;  
end loop;  
  
-- read again to make sure write did occur  
wait for 2*PER;  
WE_B <= '1';  
wait for PER;  
for i in 0 to 31 loop  
  ADDR <= std_logic_vector(to_unsigned(i, 5));  
  DATA_IN <= x"A5";  
  wait for 2*PER;  
end loop;  
end process run;  
  
-----  
-- End test processes  
-----  
  
end architecture;
```


Register Files - HDL

 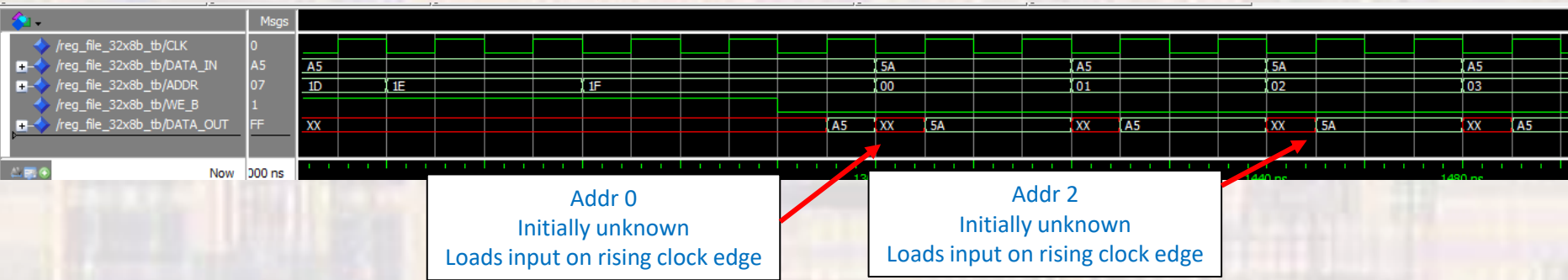 - 32 x 8 bit register file - verification



Register Files - HDL

- 32 x 16 bit register file , 2 outputs

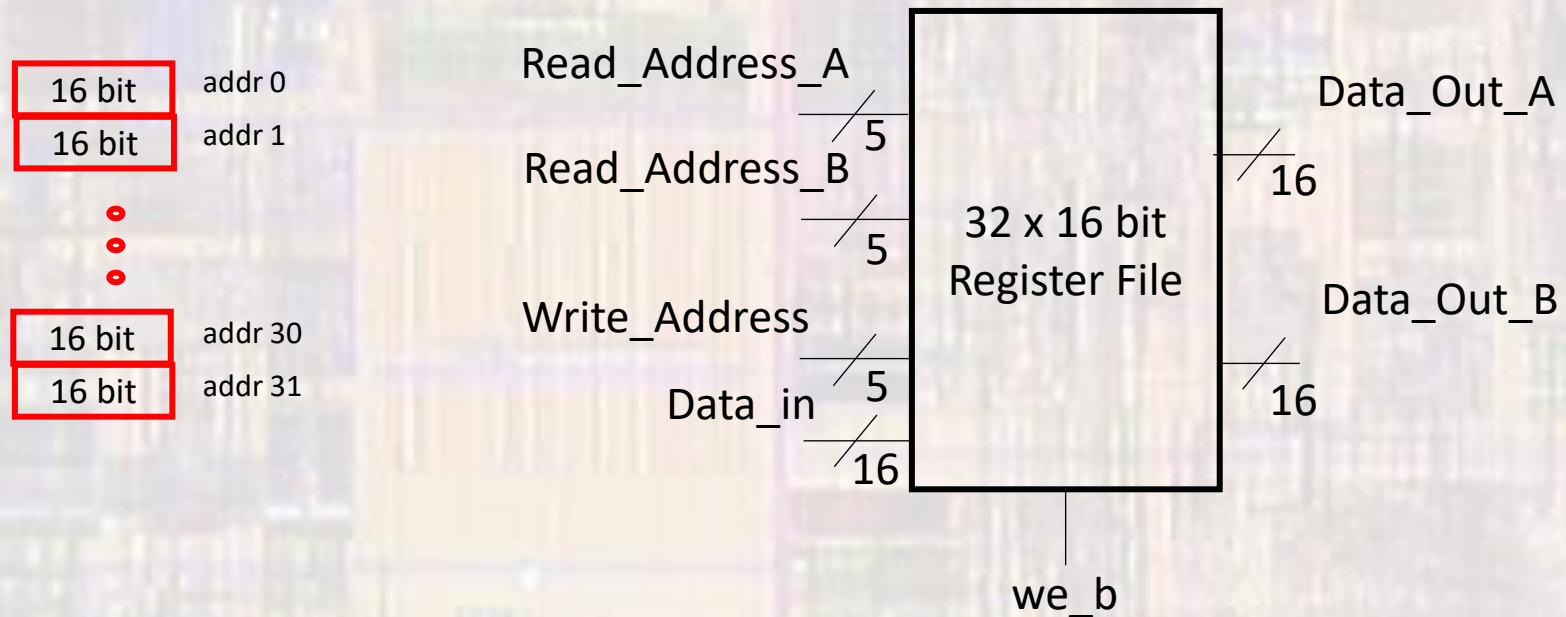

Register Files - HDL

- 32 x 16 bit register file, 2 outputs

```
--  
-- reg_file_32x16bx2.vhd1  
--  
-- created 3/18/18  
-- tj  
--  
-- rev 0  
-----  
--  
-- 32 word by 16 bit register file with 2 outputs  
-----  
--  
-- Inputs: rstb, clk, addr_a, addr_b, data in, wr bar  
-- Outputs: data out a, data out b  
-----  
--  
-----  
--  
-----  
library ieee;  
use ieee.std_logic_1164.all;  
use ieee.numeric_std.all;  
  
entity reg_file_32x16bx2 is  
  generic (  
    constant ADDR_WIDTH  : positive := 5;  
    constant MEM_DEPTH   : positive := 32;  
    constant WORD_WIDTH  : positive := 16  
  );  
  port (  
    i_clk:          in  std_logic;  
    i_addr_a:       in  std_logic_vector((ADDR_WIDTH - 1) downto 0);  
    i_addr_b:       in  std_logic_vector((ADDR_WIDTH - 1) downto 0);  
  
    i_wr_addr:      in  std_logic_vector((ADDR_WIDTH - 1) downto 0);  
    i_wr_b:         in  std_logic;  
    i_data_in:      in  std_logic_vector((WORD_WIDTH - 1) downto 0);  
  
    o_data_out_a:   out std_logic_vector((WORD_WIDTH - 1) downto 0);  
    o_data_out_b:   out std_logic_vector((WORD_WIDTH - 1) downto 0)  
  );  
end entity;
```

Register Files - HDL

- 32 x 16 bit register file, 2 outputs


Create a new 'type'
The new 'type' is an array of std_logic_vector

```
architecture behavioral of reg_file_32x16x2 is
-- Create an "TYPE" for an array of 1 bit registers
--
type REG_FILE is array(0 to (MEM_DEPTH - 1)) of std_logic_vector((WORD_WIDTH - 1) downto 0);
-- Create a signal of the array type
--
signal reg_32x16x2: REG_FILE;
--
-- Special command to stop Quartus from inferring a RAM
-- Must also turn off assignments / settings / compiler settings/
-- advanced settings (synthesis) / auto RAM replacement --> off
attribute ramstyle : string;
attribute ramstyle of reg_32x16x2 : signal is "logic";

begin
process(i_clk)
begin
if(rising_edge(i_clk)) then
if(i_wr_b = '0') then
reg_32x16x2(to_integer(unsigned(i_wr_addr))) <= i_data_in;
end if;
end if;
end process;

-- output_logic
o_data_out_a <= reg_32x16x2(to_integer(unsigned(i_addr_a)));
o_data_out_b <= reg_32x16x2(to_integer(unsigned(i_addr_b)));
end architecture;
```

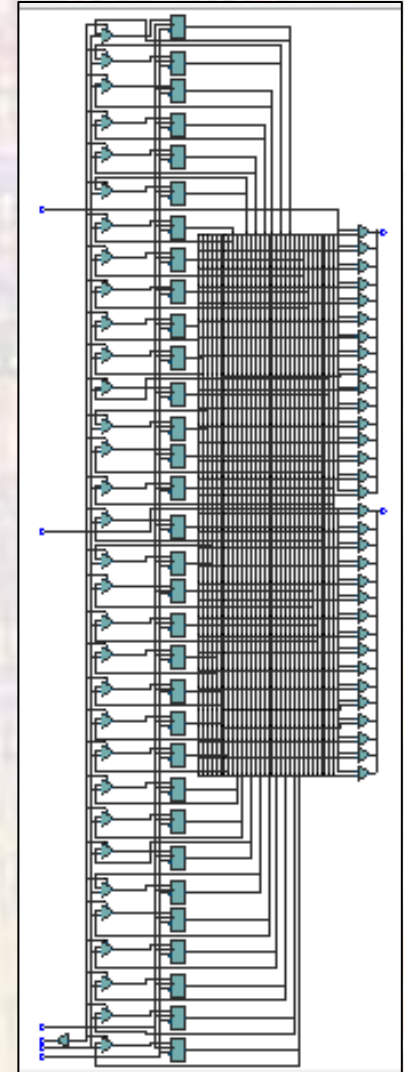Need the address as an integer to index the array.
Address is SLV coming in – need to pass through
unsigned along the way



Register Files - HDL

- 32 x 16 bit register file, 2 outputs – testbench
 - Normal clock process
 - No reset process
 - Read A and B outputs opposite directions(unknown)
 - Write to all locations (1-0 pattern)
 - Read A and B outputs opposite directions(1-0 pattern)
 - Write to all locations (0-1 pattern)
 - Read A and B outputs opposite directions(0-1 pattern)
 - Exercise Write address and data but with no wr_b
 - Read A and B outputs opposite directions(no change)