



UiO : Department of Informatics  
University of Oslo

IN5230  
Electronic noise –  
Estimates and countermeasures

Lecture X (Razavi 7)  
Noise – Razavi – Chapter 7



1


UiO : Department of Informatics  
University of Oslo

## MOSFET Thermal Noise<sup>(29)</sup>

- MOS transistors exhibit thermal noise with the most significant source being the noise generated in the channel
- For long-channel MOS devices operating in saturation, the channel noise can be modeled by a current source connected between the drain and source terminals with a spectral density

$$\overline{I_n^2} = 4kT\gamma g_m \quad \text{Red: Equation}$$

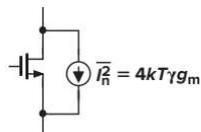- The coefficient 'γ' (not body effect coefficient) is derived to be 2/3 for long-channel transistors and is higher for submicron MOSFETs
- As a rule of thumb, Razavi assume  $\gamma=1$




Red:  
Figure

2

2

## MOSFET Thermal: Example

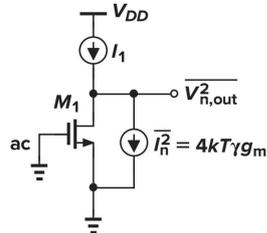

- The maximum output noise occurs if the transistor sees only its own output impedance as the load, i.e., if the external load is an ideal current source
- Output noise voltage spectrum is given by (7.29,7.30)


$$S_{out}(f) = S_{in}(f)|H(f)|^2$$

$$\overline{V_n^2} = \overline{I_n^2} r_O^2 = (4kT\gamma g_m) r_O^2$$

3

3

## MOSFET Thermal: Example

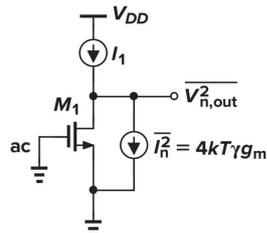


- Noise current of a MOS transistor decreases if the transconductance drops
- Noise measured at the output of the circuit does not depend on where the input terminal is because input is set to zero for noise calculation. ( $V_{gs}$  is not a part of the expression for  $I_n$ ).
- The output resistance  $r_o$  does not produce noise because it is not a physical resistor

4

4

### MOSFET Thermal Noise

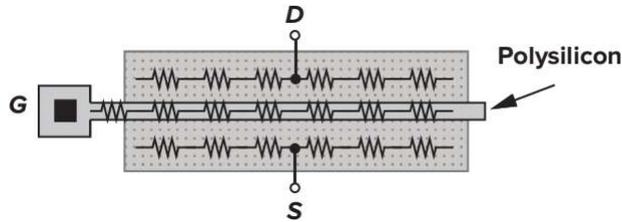


- Ohmic sections of a MOSFET have a finite resistivity and exhibit thermal noise
- For a wide transistor, source and drain resistance is negligible whereas the gate distributed resistance may become noticeable

5

5

### MOSFET Thermal Noise

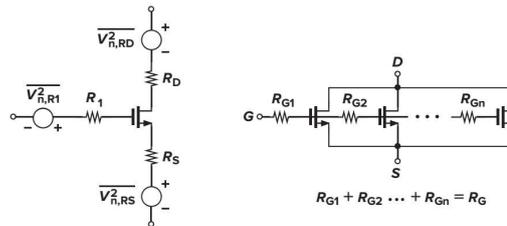


- In the noise model (left fig), the lumped resistance  $R_1$  represents the distributed gate resistance
- In the distributed structure of the right figure, unit transistors near the left end see the noise of only a fraction of  $R_G$  whereas those near the right end see the noise of most of  $R_G$
- It can be proven that  $R_1 = R_G/3$  and hence the noise generated by gate resistance is  $\overline{V_{nRG}^2} = 4kT R_G/3$

**Red:  
Equation**

6

6

### MOSFET Thermal Noise

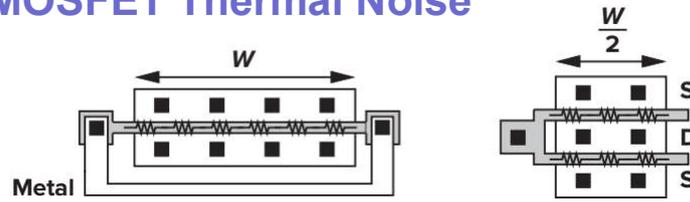


- Effect of  $R_G$  can be reduced by proper layout
- In left fig, the two ends of the gate are shorted by a metal line, reducing the distributed resistance from  $R_G$  to  $R_G/4$
- Alternatively, the transistor can be folded as in the right figure so that each gate “finger” exhibits a resistance of  $R_G/4$  for composite transistor

7

7

### MOSFET Thermal Noise: Example

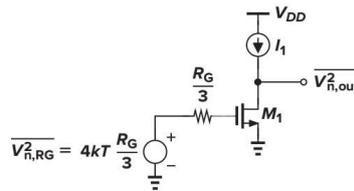

- If the total distributed gate resistance is  $R_G$ , the output noise voltage due to  $R_G$  is given by (7.32)

$$\overline{V_{n,out}^2} = 4kT \frac{R_G}{3} (g_m r_O)^2$$


- For the gate resistance noise to be negligible, we must ensure (7.33)

$$\frac{R_G}{3} \ll \frac{\gamma}{g_m} \quad \text{Yellow Equation}$$

8

8

## Flicker Noise <sup>(36)</sup>

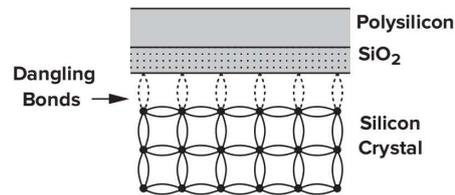

- At the interface between the gate oxide and silicon substrate, many “dangling” bonds appear, giving rise to extra energy states
- Charge carriers moving at the interface are randomly trapped and later released by such energy states, introducing “flicker” noise in the drain current
- Other mechanisms in addition are believed to generate flicker noise

9

9

## Flicker Noise

- Average power of flicker noise cannot be predicted easily
- It varies depending on cleanness of oxide-silicon interface and from one CMOS technology to another
- Flicker noise is more easily modelled as a voltage source in series with the gate and in saturation region, is roughly given by


$$\overline{V_n^2} = \frac{K}{C_{ox} WL} \cdot \frac{1}{f} \quad \text{Red: Equation}$$

- K is a process-dependent constant on the order of 10E-25V<sup>2</sup>F

10

10

## Flicker Noise

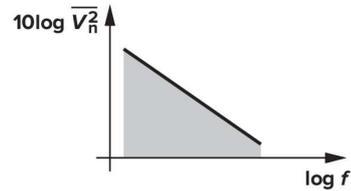


- The noise spectral density is inversely proportional to frequency
  - Trap and release phenomenon occurs at low frequencies more often
- Flicker noise is also called “1/f” noise
- To reduce 1/f noise, device area must be increased
- Generally, PMOS devices exhibit less 1/f noise than NMOS transistors
  - Holes are carried in a “buried” channel, at some distance from the oxide-silicon interface

11

11
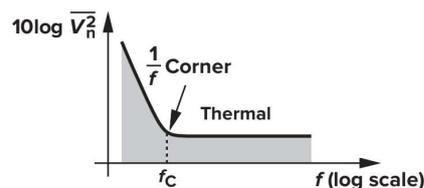
## Flicker Noise Corner Frequency

- At low frequencies, the flicker noise power approaches infinity
- At very slow rates, flicker noise becomes indistinguishable from thermal drift or aging of devices
  - Noise component below the lowest frequency in the signal of interest does not corrupt it significantly
- Intersection point of thermal noise and flicker noise spectral densities is called “corner frequency”  $f_c$




Yellow:  
Figure

12

12
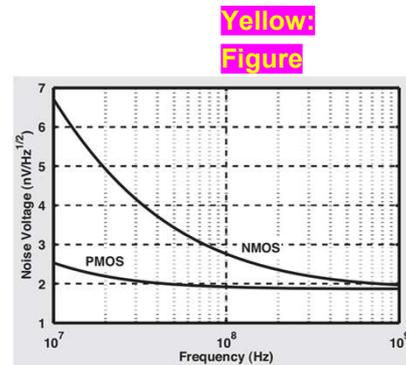
## Nanometer Design Notes


- $W/L = 5\mu\text{m}/40\text{nm}$ ,
- $I_D = 250\mu\text{A}$
- Low frequencies: Flicker noise
- High frequencies: Thermal noise
- $\Rightarrow$  PMOS exhibit less noise than NMOS (and PNP less than NPN)
- $\Rightarrow$  NMOS noise corner at several hundred MHz



13

13

## Representation of Noise in Circuits

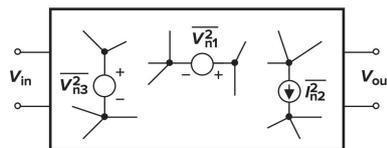


- To find the output noise, the input is set to zero and total noise is calculated at the output due to all the noise sources in the circuit
- This is how noise is measured in laboratories and in simulations

14

14
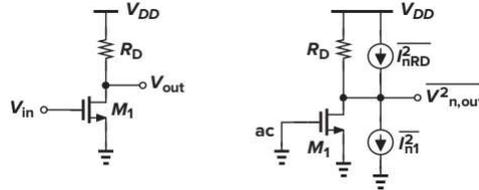
## Representation of Noise in Circuits: Example



- To find: Total output noise voltage of the common-source stage (left fig)
- Follow noise analysis procedure described earlier
- Thermal and flicker noise of  $M_1$  and thermal noise of  $R_D$  are modelled as current sources (right fig)

$$\overline{I_{n,th}^2} = 4kT\gamma g_m \quad \overline{I_{n,1/f}^2} = Kg_m^2 / (C_{ox}WLf) \quad \overline{I_{n,RD}^2} = 4kT/R_D$$


- Output noise voltage per unit bandwidth, added as power quantities is

$$\overline{V_{n,out}^2} = \left( 4kT\gamma g_m + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2$$

Equation 15

15
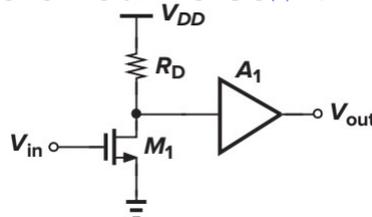
## Input-Referred Noise <sup>(42)</sup> 1/9




- Output-referred noise does not allow a fair comparison of noise in different circuits since it depends on the gain
- In above figure, a CS (Common-Source) stage is succeeded by a noiseless amplifier with voltage gain  $A_1$ , then the net output noise is now multiplied by  $A_1^2$
- This may indicate that circuit becomes noisier as  $A_1$  increases, which is incorrect since the signal level also increases proportionally, and net SNR at the output does not depend on  $A_1$

16

16

### Input-Referred Noise 2/9

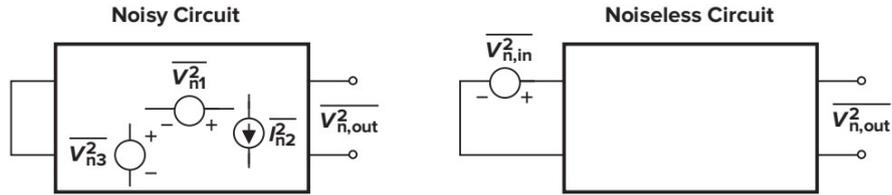


- Input-referred noise represents the effect of all noise sources in the circuit by a single source  $V_{n,in}^2$ , at the input such that the output noise in right fig is equal to that in left fig.
- If the voltage gain is  $A_v$ , then we must have
 
$$\overline{V_{n,out}^2} = A_v^2 \overline{V_{n,in}^2}$$
- The input-referred noise voltage in this simple case is simply the output noise divided by the gain squared.

17

17

### Input-Referred Noise: Example 3/9

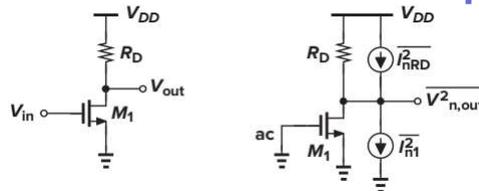

- For the simple CS stage, the input-referred noise voltage is given by (7.45,7.46,7.47)
 
$$\overline{V_{n,in}^2} = \frac{\overline{V_{n,out}^2}}{A_v^2}$$

$$= \left( 4kT\gamma g_m + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} \cdot g_m^2 + \frac{4kT}{R_D} \right) R_D^2 \frac{1}{g_m^2 R_D^2}$$


$$= 4kT \frac{\gamma}{g_m} + \frac{K}{C_{ox}WL} \cdot \frac{1}{f} + \frac{4kT}{g_m^2 R_D}$$
- First and third terms combined can be viewed as thermal noise of an equivalent resistance  $R_T$ , so that the equivalent input-referred thermal noise is  $4kTR_T$

18

18
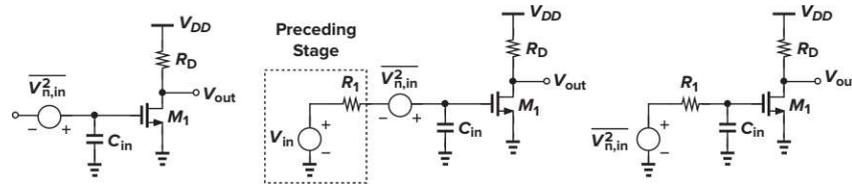
### Input-Referred Noise 4/9

- Single voltage source in series with the input is an incomplete representation of the input-referred noise for a circuit with a finite input impedance and driven by a finite source impedance
- For the CS stage, the input-referred noise voltage is independent of the preceding stage




- If the preceding stage is modelled by a Thevenin equivalent with an output impedance of  $R_1$ , the output noise due to voltage division is  $(7.48, 7.49) \quad \overline{V_{n,out}^2} = \overline{V_{n,in}^2} \left| \frac{1}{R_1 C_{in} j\omega + 1} \right|^2 (g_m R_D)^2 = \frac{4kT \gamma g_m R_D^2}{R_1^2 C_{in}^2 \omega^2 + 1}$  <sup>19</sup>

19
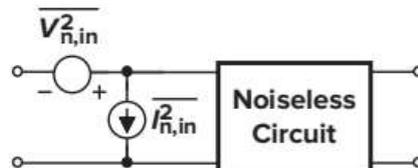
### Input-Referred Noise 5/9

- The previous result is incorrect since the output noise due to  $M_1$  does not diminish as  $R_1$  increases
- To solve this issue, we model the input-referred noise by both a series voltage source and a parallel current source, so that if the output impedance of the previous stage assumes large values, thereby reducing the effect of  $\overline{V_{n,in}^2}$  the noise current still flows through the finite impedance, producing noise at the input
- It can be proved that  $\overline{V_{n,in}^2}$  and  $\overline{I_{n,in}^2}$  are necessary and sufficient to represent the noise of any linear two-port circuit





20

20
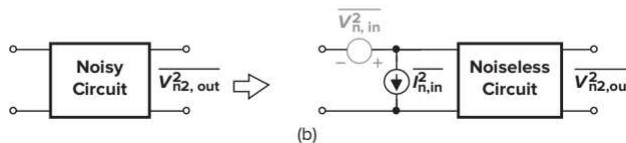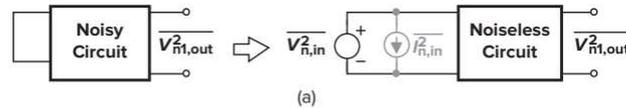
### Input-Referred Noise 6/9

- To calculate  $\overline{V_{n,in}^2}$  and  $\overline{I_{n,in}^2}$ , two extreme cases are considered: zero and infinite source impedances




Yellow:  
Figure

- If the source impedance is zero (fig a),  $\overline{I_{n,in}^2}$  flows through  $\overline{V_{n,in}^2}$  and has no effect at the output. i.e. the output noise measured arises solely from  $\overline{V_{n,in}^2}$
- If the input is left open (fig b), then  $\overline{V_{n,in}^2}$  has no effect and the output noise is only due to  $\overline{I_{n,in}^2}$

21

21

### Input-Referred Noise: Example 7/9

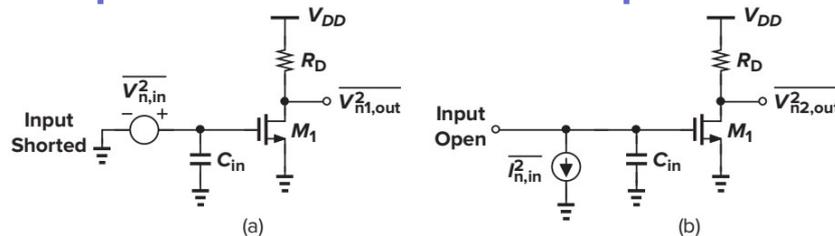

- For the circuit in fig a), the input-referred noise voltage is simply (7.50) 
$$\overline{V_{n,in}^2} = 4kT \frac{\gamma}{g_m} + \frac{4kT}{g_m^2 R_D}$$
- To obtain the input-referred noise current, the input is left open and we find the output noise in terms of  $\overline{I_{n,in}^2}$
- The noise current flows through  $C_{in}$ , generating at the output (fig b) (7.51)

$$\overline{V_{n2,out}^2} = \overline{I_{n,in}^2} \left( \frac{1}{C_{in}\omega} \right)^2 g_m^2 R_D^2$$

22

22

UiO : Department of Informatics  
University of Oslo

### Input-Referred Noise: Example 8/9

(a) (b)

- This value must be equal to the output of the noisy circuit when the input is open. (7.52)

$$\overline{V_{n2,out}^2} = \left(4kT\gamma g_m + \frac{4kT}{R_D}\right) R_D^2 \quad \overline{V_{n2,out}^2} = \overline{I_{n,in}^2} \left(\frac{1}{C_{in}\omega}\right)^2 g_m^2 R_D^2$$

- Thus (7.53) 
$$\overline{I_{n,in}^2} = (C_{in}\omega)^2 \frac{4kT}{g_m^2} \left(\gamma g_m + \frac{1}{R_D}\right)$$

23

23

UiO : Department of Informatics  
University of Oslo

### Input-Referred Noise 9/9

- The input noise current  $\overline{I_{n,in}^2}$ , becomes significant for low enough values of the input impedance  $Z_{in}$

- In above figure,  $Z_s$  denotes the output impedance of the preceding circuit; total noise voltage sensed by the second stage at node X is (7.54) 
$$V_{n,X} = \frac{Z_{in}}{Z_{in} + Z_s} V_{n,in} + \frac{Z_{in} Z_s}{Z_{in} + Z_s} I_{n,in}$$
- If  $\overline{I_{n,in}^2} |Z_s|^2 \ll \overline{V_{n,in}^2}$ , the effect of  $I_{n,in}$  is negligible
- Thus, the input-referred noise current can be neglected if (7.55)


$$|Z_s|^2 \ll \frac{\overline{V_{n,in}^2}}{\overline{I_{n,in}^2}}$$

24

24
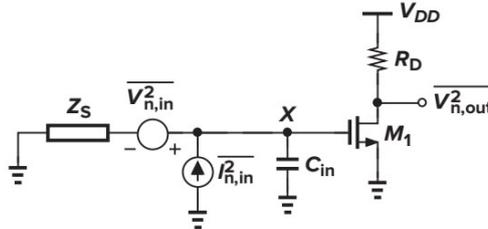
## Input-Referred Noise: Correlation 1/8

- Input-referred noise voltages and currents may be correlated
- Noise calculations must include correlations between the two
- Use of both a voltage source and a current source to represent the input-referred noise does not “count the noise twice”




- It can be proved that the output noise is correct for any source impedance  $Z_s$ , with both  $\overline{V_{n,in}^2}$  and  $\overline{I_{n,in}^2}$  included

25

25

## Input-Referred Noise: Correlation 2/8

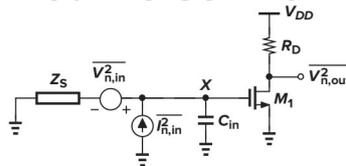

- Assuming  $Z_s$  is noiseless for simplicity, we first calculate the total noise voltage at the gate of  $M_1$  due to  $\overline{V_{n,in}^2}$  and  $\overline{I_{n,in}^2}$ .
- Cannot apply superposition of powers since they are correlated, but can be applied to voltages and currents since the circuit is linear and time-invariant
- Therefore, if  $V_{n,M1}$  denotes the gate-referred noise voltage of  $M_1$  and  $V_{n,RD}$  the noise voltage of  $R_D$  then (7.56,7.57)


$$V_{n,in} = V_{n,M1} + \frac{1}{g_m R_D} V_{n,RD}$$

$$I_{n,in} = C_{in} s V_{n,M1} + \frac{C_{in} s}{g_m R_D} V_{n,RD}$$

26

26

## Input-Referred Noise: Correlation 3/8

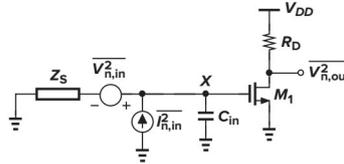


- $V_{n,M1}$  and  $V_{n,RD}$  appear in both  $V_{n,in}$  and  $I_{n,in}$ , creating a strong correlation between the two
- Adding the contributions of  $V_{n,in}$  and  $I_{n,in}$  at node X, as if they were deterministic quantities, we have (7.58, 7.59)

$$V_{n,X} = V_{n,in} \frac{1}{\frac{1}{C_{in}s} + Z_S} + I_{n,in} \frac{\frac{Z_S}{C_{in}s}}{\frac{1}{C_{in}s} + Z_S} = \frac{V_{n,in} + I_{n,in} Z_S}{Z_S C_{in}s + 1}$$

27

27

## Input-Referred Noise: Correlation 4/8

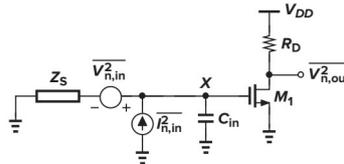

- Substituting for  $V_{n,in}$  and  $I_{n,in}$

$$V_{n,X} = \frac{1}{Z_S C_{in}s + 1} \left[ V_{n,M1} + \frac{1}{g_m R_D} V_{n,RD} + C_{in}s Z_S (V_{n,M1} + \frac{1}{g_m R_D} V_{n,RD}) \right]$$

$$= V_{n,M1} + \frac{1}{g_m R_D} V_{n,RD}$$

- $V_{n,X}$  is independent  $\overline{V_{n,out}^2} = g_m^2 R_D^2 \overline{V_{n,X}^2}$
- It follows that  $= 4kT \left( \gamma g_m + \frac{1}{R_D} \right) R_D^2$

$\Rightarrow V_{n,in}$  and  $I_{n,in}$  do not double count the noise!

28

28


## Input-Referred Noise: Correlation 5/8

- In some cases, it is simpler to consider the output short-circuit noise current—rather than the output noise voltage
- This current is then multiplied by the circuit's output resistance to yield the output noise voltage or simply divided by a proper gain to give input-referred quantities

29

29

## (Example) (6/8)

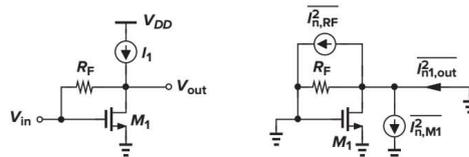

- To find: Input-referred noise voltage and current. Assume  $I_1$  is noiseless and  $\lambda=0$
- To compute the input-referred noise **voltage**, we short the input port (right fig). Here, it is also possible to short the output port and hence (7.63)

$$\overline{I_{n1,out}^2} = \frac{4kT}{R_F} + 4kT\gamma g_m$$


- The output impedance of the circuit with the input shorted is simply  $R_F$ , therefore (7.64)

$$\overline{V_{n1,out}^2} = \left( \frac{4kT}{R_F} + 4kT\gamma g_m \right) R_F^2$$

30

30
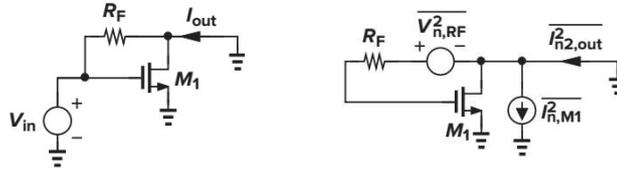
### Input-Referred Noise: Correlation (Example) 7/8



- Input-referred noise **voltage** can be found by dividing previous equation by voltage gain or  $\overline{I_{n1,out}^2}$  by  $G_m^2$
- As shown in left fig, (7.65, 7.66)

$$G_m = \frac{I_{out}}{V_{in}} = g_m - \frac{1}{R_F}$$


- Therefore, (7.67)

$$\overline{V_{n,in}^2} = \frac{\frac{4kT}{R_F} + 4kT\gamma g_m}{\left(g_m - \frac{1}{R_F}\right)^2}$$

31

31
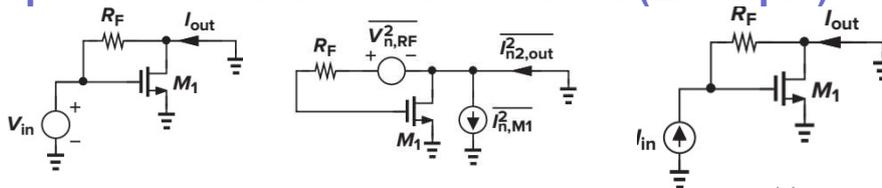
### Input-Referred Noise: Correlation (Example) 8/8



- To find the input-referred noise **current** (middle), we find the output noise current with the input left open (7.68)

$$\overline{I_{n2,out}^2} = 4kT R_F g_m^2 + 4kT \gamma g_m$$

- Next, we need to find the current gain of the circuit according to the arrangement in left figure
- Since,  $V_{GS} = I_{in} R_F$  and  $I_D = g_m I_{in} R_F$  (7.69, 7.70)

$$I_{out} = g_m R_F I_{in} - I_{in} = (g_m R_F - 1) I_{in}$$


- Thus, (7.71)

$$\overline{I_{n,in}^2} = \frac{4kT R_F g_m^2 + 4kT \gamma g_m}{(g_m R_F - 1)^2}$$

32

32
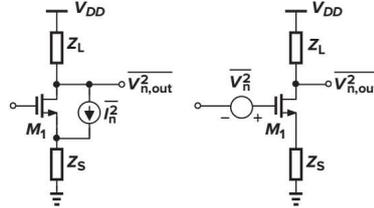
## Noise in Single-Stage Amplifiers: Lemma



- Lemma: The circuits in the figure are equivalent at low frequencies if  $\overline{V_n^2} = \overline{I_n^2}/g_m^2$  and the circuits are driven by a finite impedance
- $\Rightarrow$  The noise source can be transformed from a drain-source current to a gate series voltage for arbitrary  $Z_s$

33


33

## Common-Source (CS) Stage 1/4

- From a previous example, the input-referred noise voltage of a simple CS stage was found to be <sup>(7.75)</sup>

$$\overline{V_{n,in}^2} = 4kT \left( \frac{\gamma}{g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{K}{C_{ox} W L} \frac{1}{f}$$

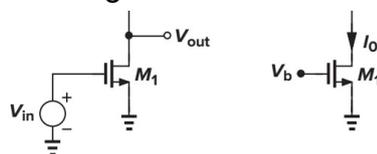- From above expression,  $4kT\gamma/g_m$  is the thermal noise current expressed as a voltage in series with the gate




- To reduce input-referred noise voltage, transconductance must be maximized if the transistor is to amplify a voltage signal applied to its gate (left fig) whereas it must be minimized if operating as a current source (fig b).

34

34

## Common-Source Stage: Example 2/4

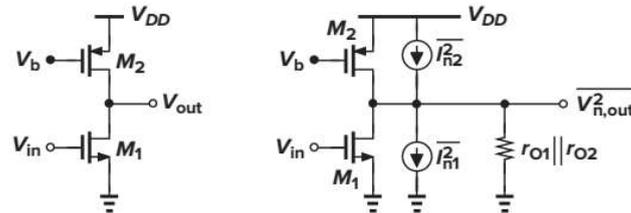


- We want to find: a) Input-referred thermal noise, b) total output thermal noise with a load capacitance  $C_L$
- Representing the thermal noise of  $M_1$  and  $M_2$  by current sources and noting that they are uncorrelated <sup>(7.76)</sup>

$$\overline{V_{n,out}^2} = 4kT(\gamma g_{m1} + \gamma g_{m2})(r_{O1} \parallel r_{O2})^2$$

35

35

## Common-Source Stage: Example 3/4

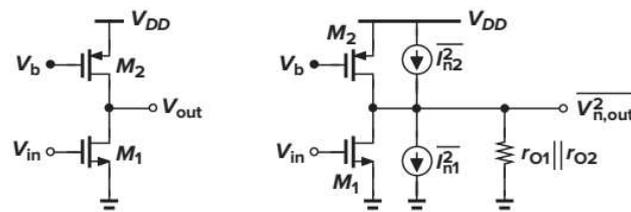

- Since the voltage gain is equal to  $g_{m1}(r_{O1} \parallel r_{O2})$ , total noise voltage referred to the gate of  $M_1$  is <sup>(7.77,7.78)</sup>


$$\overline{V_{n,in}^2} = 4kT(\gamma g_{m1} + \gamma g_{m2}) \frac{1}{g_{m1}^2} = 4kT\gamma \left( \frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$

- Thus,  $g_{m2}$  must be minimized because  $M_2$  serves as a current source rather than a transconductor

36

36

### Common-Source Stage: Example 4/4

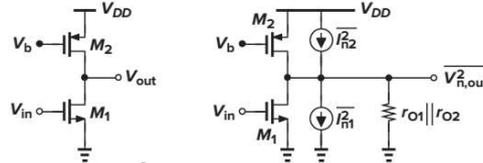

- Total output noise with  $C_L$  is <sup>(7.79,7.80)</sup>

$$\overline{V_{n,out,tot}^2} = \int_0^\infty 4kT\gamma(g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})^2 \frac{df}{1 + (r_{O1} \parallel r_{O2})^2 C_L^2 (2\pi f)^2}$$

$$\overline{V_{n,out,tot}^2} = \gamma(g_{m1} + g_{m2})(r_{O1} \parallel r_{O2}) \frac{kT}{C_L}$$

- A low-frequency input sinusoid of amplitude  $V_m$  yields an output amplitude equal to  $g_{m1}(r_{O1} \parallel r_{O2})V_m$  with an output SNR of <sup>(7.81,7.82)</sup>

Yellow:

Equation

$$SNR_{out} = \left[ \frac{g_{m1}(r_{O1} \parallel r_{O2})V_m}{\sqrt{2}} \right]^2 \cdot \frac{1}{\gamma(g_{m1} + g_{m2})(r_{O1} \parallel r_{O2})(kT/C_L)}$$

$$= \frac{C_L}{2\gamma kT} \cdot \frac{g_{m1}^2(r_{O1} \parallel r_{O2})}{g_{m1} + g_{m2}} V_m^2$$

37

37

### Common-Gate Stage: Thermal noise <sup>(64)</sup> 1/5

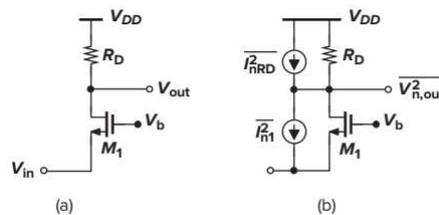



Figure 7.46 (a) CG stage; (b) circuit including noise sources.

- Neglecting channel-length modulation, we represent the thermal noise of  $M_1$  and  $R_D$  by two current sources
- Due to low input impedance of the circuit, the input-referred noise current is not negligible even at low frequencies

38

38

### Common-Gate Stage: Thermal noise 2/5

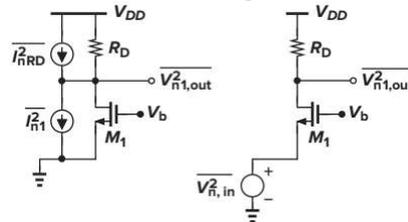

- To calculate the input-referred noise **voltage**, we **short the input to ground** and equate the output noises of the circuits. (7.93,7.94)

$$\left(4kT \gamma g_m + \frac{4kT}{R_D}\right) R_D^2 = \overline{V_{n,in}^2} (g_m + g_{mb})^2 R_D^2$$


**Yellow:**  
**Equation**

$$\overline{V_{n,in}^2} = \frac{4kT (\gamma g_m + 1/R_D)}{(g_m + g_{mb})^2}$$

39

39

### Common-Gate Stage: Thermal noise 3/5

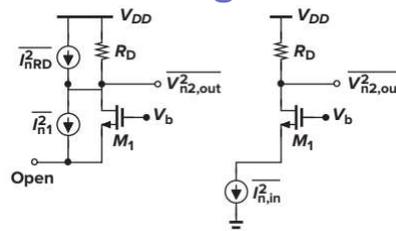


- To calculate the input-referred noise **current**, we **leave the input open** and equate the output noises of the circuits.
- $I_{n1}$  produces no noise at the output since the sum of the currents at the source of  $M_1$  is zero.
- The output noise voltage is therefore  $4kTR_D$  and hence:

$$\overline{I_{n,in}^2} R_D^2 = 4kTR_D \quad \overline{I_{n,in}^2} = \frac{4kT}{R_D} \quad \text{Yellow: Equation}$$

40

40

### Common-Gate Stage: Thermal noise 4/5

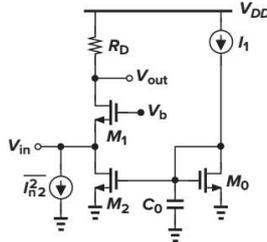

- Bias current source in the common-gate stage also contributes thermal noise
- Current mirror arrangement establishes bias current of M2 as a multiple of I1



First we look at M2:

- If input is shorted to ground, drain noise current of M2 does not contribute to input-referred noise voltage
- If input is open, all of  $\overline{I_{n2}^2}$  flows from M1 and RD, producing an output noise of  $\overline{I_{n2}^2 R_D^2}$  and hence an input-referred noise current of  $\overline{I_{n2}^2}$
- It is desirable to minimize transconductance of M2, at the cost of reduced output swing.

41

41

### Common-Gate Stage: Flicker noise 5/5

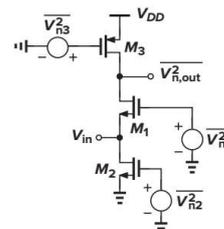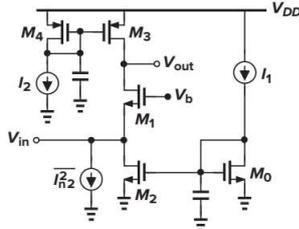

- Approximating the voltage gain as  $(g_{m1} + g_{mb1})(r_{O1} || r_{O3})$  (7.105)

$$\overline{V_{n,in}^2} = \frac{1}{C_{ox} f} \left[ \frac{g_{m1}^2 K_N}{(WL)_1} + \frac{g_{m3}^2 K_P}{(WL)_3} \right] \frac{1}{(g_{m1} + g_{mb1})^2}$$

- With the input open, the output noise is approximately (7.106)

$$\overline{V_{n2,out}^2} = \frac{1}{C_{ox} f} \left[ \frac{g_{m2}^2 K_N}{(WL)_2} + \frac{g_{m3}^2 K_P}{(WL)_3} \right] R_{out}^2$$


- It follows that (7.107)

$$\overline{I_{n,in}^2} = \frac{1}{C_{ox} f} \left[ \frac{g_{m2}^2 K_N}{(WL)_2} + \frac{g_{m3}^2 K_P}{(WL)_3} \right]$$

42

42

### Source Followers: Thermal Noise 1/2

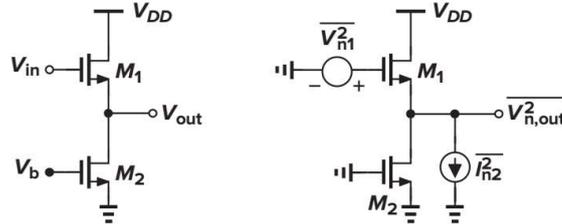


- Since the input impedance of the source follower is quite high, the input-referred noise current can be neglected for moderate driving source impedances
- To compute the input-referred noise voltage, the output noise of M2 can be expressed as (7.108)

$$\overline{V_{n,out}^2}|_{M2} = \overline{I_{n2}^2} \left( \frac{1}{g_{m1}} \parallel \frac{1}{g_{mb1}} \parallel r_{O1} \parallel r_{O2} \right)^2$$

43

43

### Source Followers: Thermal Noise 2/2

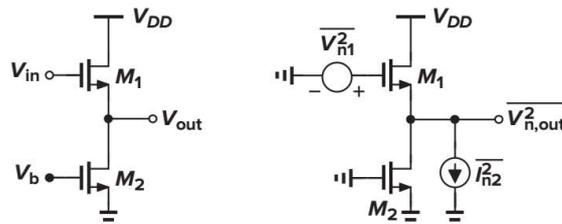

- The voltage gain is
- $$A_v = \frac{\frac{1}{g_{mb1}} \parallel r_{O1} \parallel r_{O2}}{\frac{1}{g_{mb1}} \parallel r_{O1} \parallel r_{O2} + \frac{1}{g_{m1}}}$$
- Total input-referred noise voltage is (7.110,7.111)

$$\overline{V_{n,in}^2} = \overline{V_{n1}^2} + \frac{\overline{V_{n,out}^2}|_{M2}}{A_v^2} = 4kT\gamma \left( \frac{1}{g_{m1}} + \frac{g_{m2}}{g_{m1}^2} \right)$$


Yellow:  
Equation

- Source followers add noise to the input signal and provide a voltage gain less than unity

44

44

### Cascode Stage 1/3

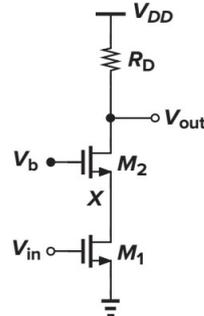


- In the cascode stage, the noise currents of M1 and RD flow mostly through RD at low frequencies
- Noise contributed by M1 and RD is quantified in a common-source stage (7.112)

$$\overline{V_{n,in}^2}|_{M1,RD} = 4kT \left( \frac{\gamma}{g_{m1}} + \frac{1}{g_{m1}^2 R_D} \right)$$

45

45

### Cascode Stage 2/3

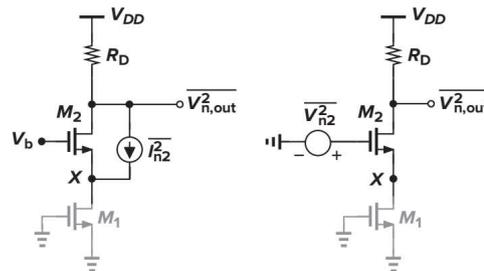


- As shown in left figure, M2 contributes negligibly to noise at the output, especially at low frequencies
- If channel-length modulation of M1 is neglected, then  $I_{n2} + I_{D2} = 0$  and hence M2 does not affect  $V_{n,out}$
- From another perspective, in the equivalent circuit of the right figure, voltage gain from  $V_{n2}$  to the output is small if impedance at node X is large (7.112)

46

46

## Cascode Stage 3/3

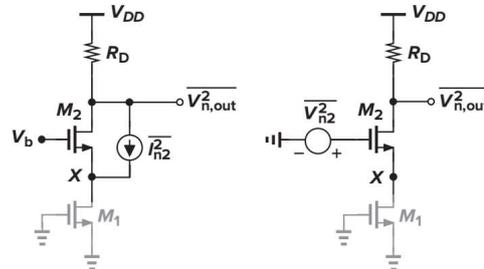

- At high frequencies, the total capacitance at node X,  $C_x$  gives rise to a gain, increasing the output noise (7.113)


$$\frac{V_{n,out}}{V_{n2}} \approx \frac{-R_D}{1/g_{m2} + 1/(C_x s)}$$

- This capacitance also reduces the gain from the main input to the output by shunting the signal current produced by M1 to ground

47

47

## Noise in Current Mirrors 1/4

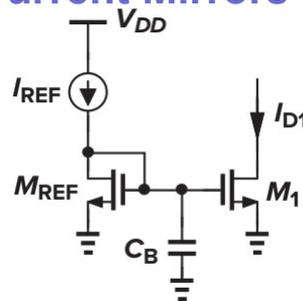

- In the above current-mirror topology :  $(W/L)_1 = N(W/L)_{REF}$
- The factor  $N$  is in the range of 5 to 10 to minimize power consumed by the reference branch
- To determine the flicker noise in  $I_{D1}$ , we assume  $\lambda = 0$  and  $I_{REF}$  is noiseless

48

48

UiO : Department of Informatics  
University of Oslo

### Noise in Current Mirrors 2/4

- In the Thevenin equivalent for  $M_{REF}$  and its flicker noise, the open-circuit voltage  $V_{n,REF}$  (middle fig) and the Thevenin resistance is  $1/g_{m,REF}$  (right fig)
- The noise voltage at node X and  $V_{n1}$  add and drive the gate of  $M_1$  producing (7.114)

$$\overline{I_{n,out}^2} = \left( \frac{g_{m,REF}^2}{C_B^2 \omega^2 + g_{m,REF}^2} \overline{V_{n,REF}^2} + \overline{V_{n1}^2} \right) g_{m1}^2$$

- Since  $(W/L)_1 = N(W/L)_{REF}$  and typically  $L_1 = L_{REF}$ , we observe that  $\overline{V_{n,REF}^2} = N \overline{V_{n1}^2}$

49

49

UiO : Department of Informatics  
University of Oslo

### Noise in Current Mirrors 3/4

- It follows that (7.115)

$$\overline{I_{n,out}^2} = \left( \frac{N g_{m,REF}^2}{C_B^2 \omega^2 + g_{m,REF}^2} + 1 \right) g_{m1}^2 \overline{V_{n1}^2}$$

- For the noise of the diode-connected device to be small, we need  $(N - 1)g_{m,REF}^2 \ll C_B^2 \omega^2$  and hence (7.117)


$$C_B^2 \gg \frac{(N - 1)g_{m,REF}^2}{\omega^2}$$

- This can be lead to  $C_B$  being very high

50

50

### Noise in Current Mirrors 4/4

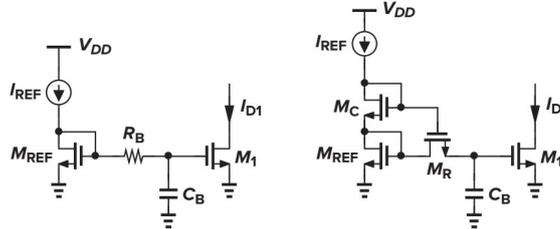


- In order to reduce noise contributed by  $M_{REF}$  and avoid a large capacitor, we can **insert a resistance** between its gate and  $C_B$ , so that it follows that (7.118)

$$\overline{I_{n,out}^2} = \left[ \frac{g_{m,REF}^2}{(1 + g_{m,REF} R_B)^2 C_B^2 \omega^2 + g_{m,REF}^2} (\overline{V_{n,REF}^2} + \overline{V_{n,RB}^2}) + \overline{V_{n1}^2} \right] g_{m1}^2$$

- $R_B$  lowers the filter cutoff frequency but also contributes its own noise
- The MOS device  $M_R$  with a small overdrive provides a high resistance and occupies a moderate area

51

### Noise in Differential Pairs

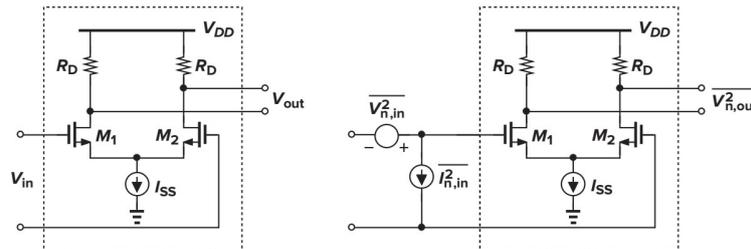


- As shown in left figure, a differential pair can be viewed as a two-port circuit
- It is possible to model the overall noise as depicted in right figure
- For low-frequency operation,  $\overline{I_{n,in}^2}$  is negligible

52

52

### Noise in Differential Pairs

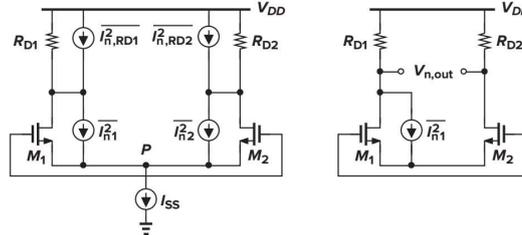


- To calculate the thermal component  $\overline{V_{n,in}^2}$ , we first obtain the total output noise with inputs shorted together (left).
- Since In1 and In2 are uncorrelated, node P cannot be considered a virtual ground, so cannot use half-circuit concept
- Derive contribution of each source individually (right fig).

53

53

### Noise in Differential Pairs

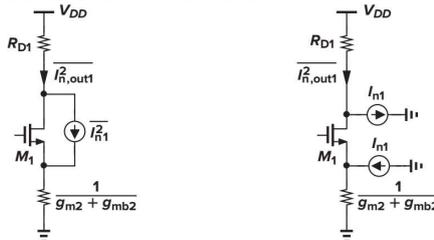


- In left fig, to calculate the contribution of In1, neglecting channel-length modulation, it can be proven that half of In1 flows through RD1 and the other half through M2 and RD2 (right fig).
- The differential output noise due to M1 is equal to (7.119)

$$V_{n,out}|_{M1} = \frac{I_{n1}}{2} R_{D1} + \frac{I_{n1}}{2} R_{D2}$$

54

54

### Noise in Differential Pairs

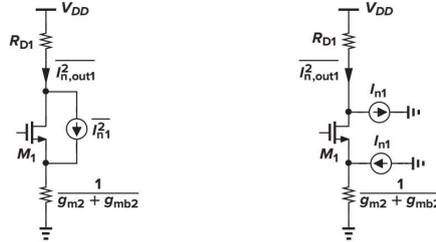


- If  $R_{D1}=R_{D2}=R_D$ ,  $\overline{V_{n,out}^2}|_{M1} = \overline{I_{n1}^2} R_D^2$      $\overline{V_{n,out}^2}|_{M2} = \overline{I_{n2}^2} R_D^2$
- Thus (7.122)  $\overline{V_{n,out}^2}|_{M1,M2} = (\overline{I_{n1}^2} + \overline{I_{n2}^2}) R_D^2$
- Taking into account the noise of  $R_{D1}$  and  $R_{D2} \dots$  (7.123, 7.124)
 
$$\overline{V_{n,out}^2} = (\overline{I_{n1}^2} + \overline{I_{n2}^2}) R_D^2 + 2(4kTR_D)$$

$$= 8kT (\gamma g_m R_D^2 + R_D)$$
- Dividing by the square of the diff gain (7.125)
 
$$\overline{V_{n,in}^2} = 8kT \left( \frac{\gamma}{g_m} + \frac{1}{g_m^2 R_D} \right)$$

55

55

### Noise in Differential Pairs

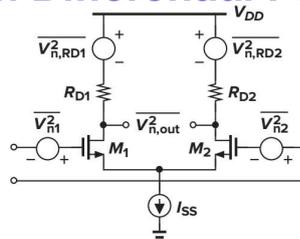


- Input-referred noise voltage can also be calculated using the previous lemma
- The noise of  $M_1$  and  $M_2$  can be modelled as a voltage source in series with their gates
- The noise of  $R_{D1}$  and  $R_{D2}$  is divided by  $g_m^2 R_D^2$  resulting in previously obtained equation
- Including 1/f noise (7.126)
 
$$\overline{V_{n,in,tot}^2} = 8kT \left( \frac{\gamma}{g_m} + \frac{1}{g_m^2 R_D} \right) + \frac{2K}{C_{ox} WL} \frac{1}{f}$$

**Yellow:**  
**Equation**

56

56

### Noise in Differential Pairs

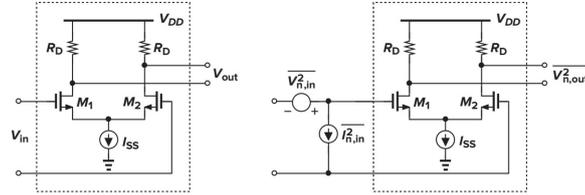

- If the differential input is zero and the circuit is symmetric, the noise in  $I_{SS}$  divides equally between  $M_1$  and  $M_2$ , and produces only a common-mode noise voltage at the output
- For a small differential input  $\Delta V_{in}$ , we have <sup>(7.129, 7.130)</sup>


$$\Delta I_{D1} - \Delta I_{D2} = g_m \Delta V_{in} = \sqrt{2\mu_n C_{ox} \frac{W}{L} \left( \frac{I_{SS} + I_n}{2} \right)} \Delta V_{in}$$

- $I_n$  denotes the noise in  $I_{SS}$  and we have  $I_n \ll I_{SS}$
- As circuit departs from equilibrium,  $I_n$  is more unevenly divided, generating differential output noise

57

57

### Noise in five-transistor OTA

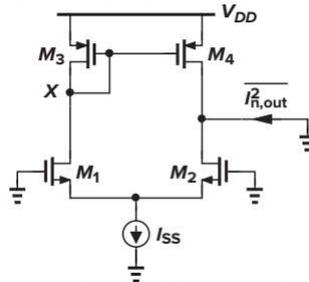

- The Norton noise equivalent is sought by first computing the output short-circuit noise current. This is then multiplied by the output resistance and divided by the gain to get input-referred noise voltage
- Transconductance is approximately  $g_{m1,2}$
- Output noise current due to  $M_1$  and  $M_2$  is this transconductance multiplied by gate-referred noises of  $M_1$  and  $M_2$ , i.e.  $g_{m1,2}^2 (4kT\gamma/g_{m1} + 4kT\gamma/g_{m2})$

58

58

UiO : Department of Informatics  
University of Oslo

### Noise in five-transistor OTA

- The noise current of  $M_3$  primarily circulates through the diode-connected impedance  $1/g_{m3}$ , producing a voltage at the gate of  $M_4$  with spectral density  $4kT\gamma/g_{m3}$
- This noise is multiplied by  $g_{m4}^2$  as it emerges from the drain of  $M_4$ ; the noise current of  $M_4$  also flows directly through the output short-circuit thus  $\overline{I_{n,out}^2} = 4kT\gamma(2g_{m1,2} + 2g_{m3,4})$
- Multiplying this noise by  $R_{out}^2 \approx (r_{O1,2} || r_{O3,4})^2$  and dividing the result by  $A_v^2 = G_m^2 R_{out}^2$  the total input-referred noise is

$$\overline{V_{n,in}^2} = 8kT\gamma \left( \frac{1}{g_{m1,2}} + \frac{g_{m3,4}}{g_{m1,2}^2} \right)$$

Yellow: Equation

59

59

UiO : Department of Informatics  
University of Oslo

### Noise in five-transistor OTA


- The output voltage in the OTA  $V_{out}$  is equal to  $V_x$
- If  $I_{ss}$  fluctuates, so do  $V_x$  and  $V_{out}$
- Since the tail noise current  $I_n$  splits equally between  $M_1$  and  $M_2$ , the noise voltage at  $X$  is given by  $\overline{I_n^2}/(4g_{m3}^2)$  and so is the noise voltage at the output

60

60
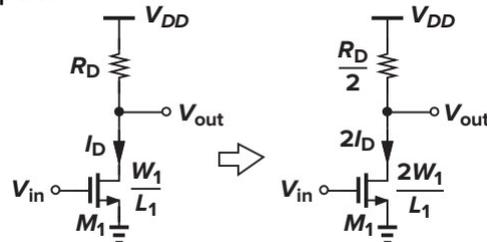
## Noise-Power Trade-off

- Noise contributed by transistors “in the signal path” is inversely proportional to their transconductance
  - Suggests a trade-off between noise and power consumption




- In the simple CS stage, we double  $W/L$  and  $I_{D1}$  and halve  $R_D$ , maintaining voltage gain and output swing
- Input-referred thermal and flicker noise power is halved, at the cost of power consumption

61

61

## Noise-Power Trade-off

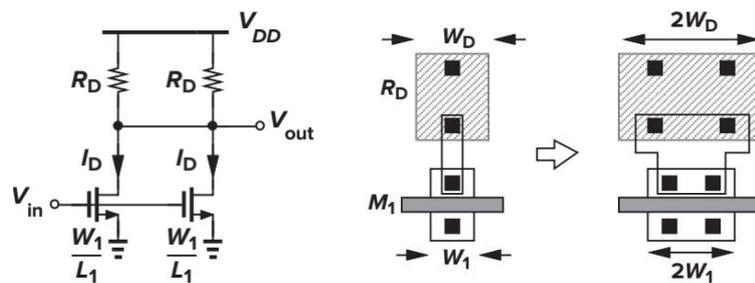


- Called “linear scaling”, the earlier transformation can be viewed as placing two instances of the original circuit in parallel
- Alternatively, it can be said that the widths of the transistor and the resistor are doubled

62

62

### Noise-Power Trade-off

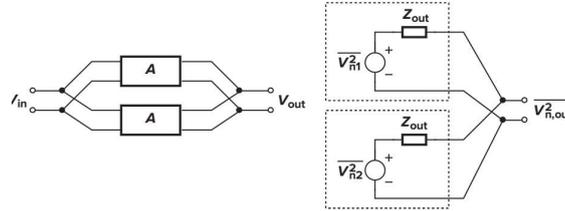


- In general, if two instances of a circuit are placed in parallel, the output noise is halved
- Proven by setting the input to zero and constructing a Thevenin equivalent for each
- Since  $V_{n1,out}$  and  $V_{n2,out}$  are uncorrelated, we can use superposition of powers to write (7.143, 7.144)

$$\overline{V_{n,out}^2} = \frac{\overline{V_{n1,out}^2}}{4} + \frac{\overline{V_{n2,out}^2}}{4} = \frac{\overline{V_{n1,out}^2}}{2}$$

63

63

### Noise Bandwidth

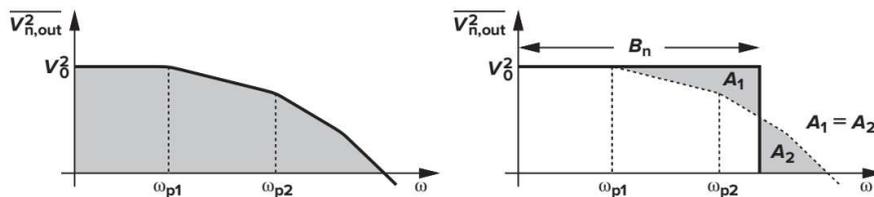

- Total noise corrupting a signal in a circuit results from all frequency components in the bandwidth of the circuit
- For a multipole system with noise spectrum as in left figure, total output noise is (7.145)

$$\overline{V_{n,out,tot}^2} = \int_0^\infty \overline{V_{n,out}^2} df$$

- As shown in right figure, the total noise can also be expressed as


$$V_0^2 \cdot B_n = \int_0^\infty \overline{V_{n,out}^2} df$$

- , where the bandwidth  $B_n$ , called the “noise bandwidth” is chosen such that (7.146)

64

64

## Problem of Input Noise Integration

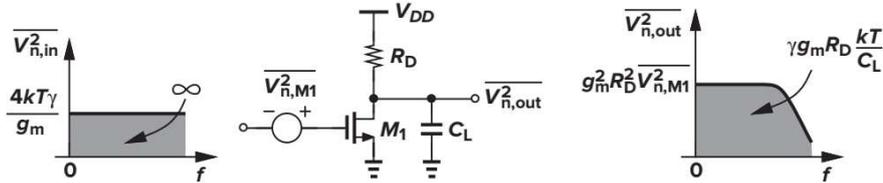

- In the CS stage above, it is assumed that  $\lambda=0$  and noise of  $R_D$  is neglected with only thermal noise of  $M_1$  considered.
- Output noise spectrum is the amplified and low-pass filtered noise of  $M_1$ , easily lending to integration
- Input-referred noise voltage, however, is simply  $\overline{V_{n,M1}^2}$ , carrying an infinite power and prohibiting integration
- For fair comparison of different designs, we can divide the integrated output noise by the low-frequency gain, for example (7.147,7.148)

$$\overline{V_{n,in,tot}^2} = \gamma g_m R_D \frac{kT}{C_L} \cdot \frac{1}{g_m^2 R_D^2} = \frac{\gamma}{g_m R_D} \frac{kT}{C_L} \quad 65$$