

# wireless world


APRIL 1977 35p

**Metal detector**  
**Stereo coder**

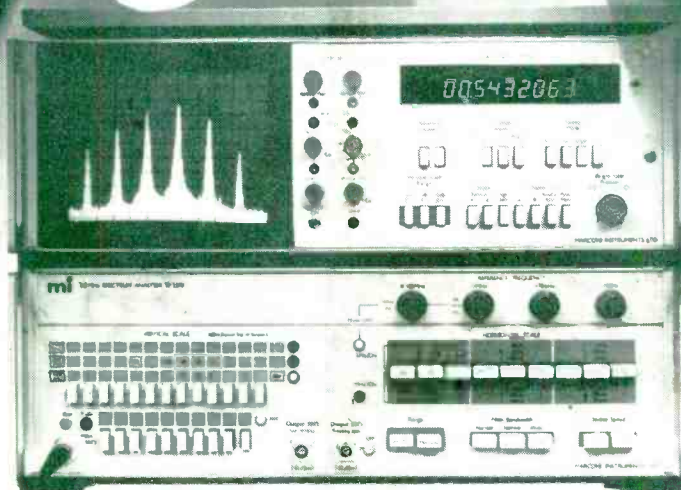**Radio schools in Honduras**

Australia \$A1.20  
Canada \$1.50  
Denmark Kr. 11.00  
Finland Fmk. 6.50  
Germany Dm. 4.50  
Greece Dr. 45.00  
Holland Dfl. 4.50  
Italy L. 900  
Malaysia M\$3.25  
New Zealand \$NS1.40  
Norway Kr. 10.00 incl. moms  
Portugal Esc. 40.00  
South Africa R. 1.10  
Spain Ptas. 80.00  
Sweden Kr. 6.90 incl. moms  
U.S.A. \$1.50





# The Production Test Bottleneck Smasher!

You've never seen a faster, more accurate way of measuring frequency response from 30Hz to 110MHz

Slash your production-test times and divert your skilled engineers to more important work with our TF 2370 Spectrum Analyser. It will reduce to simple operations, complicated measurements such as response, level, gain, signal purity, modulation and many more, with a speed and degree of accuracy that has to be seen to be believed. Forget everything you have heard about spectrum analysers. The TF 2370 is unique. It employs advanced technology to make it reliable and as easy to operate as a multimeter. The facts speak for themselves.

- \* Flicker-free display of frequency response from 30 Hz to 110 MHz on a high-brightness c.r.t.
- \* Electronic graticule, with a  $\pm 15\%$  variation of horizontal divisions for pin-point positioning against waveform display.
- \* Press-button selection of three amplitude scales: one linear and two logarithmic with expansion to 1 dB/div. with an accuracy of  $\pm 0.1$  dB/dB.
- \* 9-digit electronic counter automatically gives centre frequency, reads any other frequency corresponding to manually-adjusted 'bright line' position on display, or the

difference frequency between the two, at the press of a button. All to an accuracy of  $\pm 2$  Hz  $\pm$  reference frequency accuracy on high resolution and manual. Internal reference frequency provided with setting accuracy of 1 in  $10^7$ .

- \* Internal generator supplies synchronous signal source for measuring such items as networks and filters.
- \* For comparative measurements, unique memory storage system will retain one display indefinitely as required, for simultaneous display with waveform produced by items under test.
- \* Automatic adjustment of amplifier gain to give optimum lowest-noise performance with full protection against input overloading.
- \* Automatic selection of optimum sweep speed.
- \* With the 5 Hz filter, signals 100 Hz from a response at 0dB can be measured to  $-70$  dB.


Now ask for a demonstration. It could prove that the TF 2370 is a better cure for your headaches than aspirin. We are standing by for your call.

**mi MARCONI INSTRUMENTS**

Marconi Instruments Limited · Longacres · St. Albans · Hertfordshire · England · AL4 0JN.  
Telephone: St. Albans 59292 · Telex: 23350.

www.marconi-instruments.com

WW-001 FOR FURTHER DETAILS

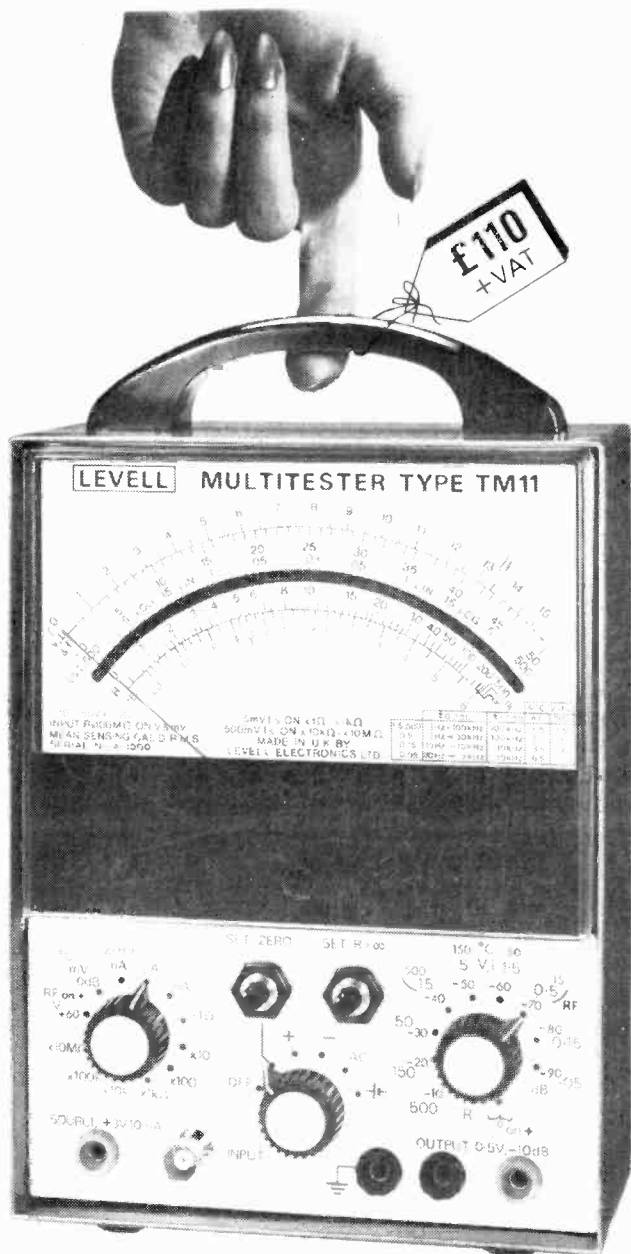

**VERSATILE**

**RELIABLE**

**PORTABLE**

**120 BASIC RANGES**

- AC V, I & dB : 50 $\mu$ V/500V fsd, 50pA/500mA fsd, -90dB/+50dB mid scale. Acc.  $\pm 1.5\%$  fsd above 500 $\mu$ V & 500pA. Response 3Hz/200kHz above 500 $\mu$ V and 500nA. Input R = 100M $\Omega$  on volts.
- DC V, I & NULL : 150 $\mu$ V/500V fsd, 150pA/500mA fsd, polarity reversible. Acc.  $\pm 1.5\%$  fsd above 500 $\mu$ V & 500pA. Input R = 100M $\Omega$  on volts. 5 Null ranges have centre zero lin/log scale covering  $\pm 4$  decades.
- RESISTANCE : 0.2 $\Omega$ /10G $\Omega$  in 7 ranges, polarity reversible. Low test voltage for solid state circuits.
- LEAKAGE at 3V : Uses 3V source with current ranges to test capacitors, diodes and resistance up to 100G $\Omega$ .
- VOLT DROP at 10mA : Uses 10mA source with voltage ranges to test diodes, LED's and resistance down to 10m $\Omega$ .

**30 OPTIONAL RANGES**

- RF VOLTS : 0.5V/500V fsd, 10kHz/1GHz, using RF Probe. Price £22 + VAT.
- HIGH VOLTS : 1.5kV/50kV fsd, AC/DC, using HV Probe. Price £16 + VAT.
- HIGH CURRENT : 1.5A/50A fsd, AC/DC, using Current Shunt. Price £15 + VAT.
- TEMPERATURE : -150 $^{\circ}$ C/+500 $^{\circ}$ C fsd in 7 ranges using Temperature Probe. Price £38 + VAT.


The instrument operates from a 9 volt battery, life 1000 hrs., or, AC mains when optional Power Supply Unit is fitted. Size is 240mm x 150mm x 80mm. Weight is 1.75 kg. Meter scale length is 140mm. Leather case is available at £13 + VAT.

**LEVELL ELECTRONICS LTD.**

MOXON STREET, BARNET, HERTS., ENGLAND, EN5 5SD.  
TEL: 01-449 5028/440 8686

WW — 054 FOR FURTHER DETAILS
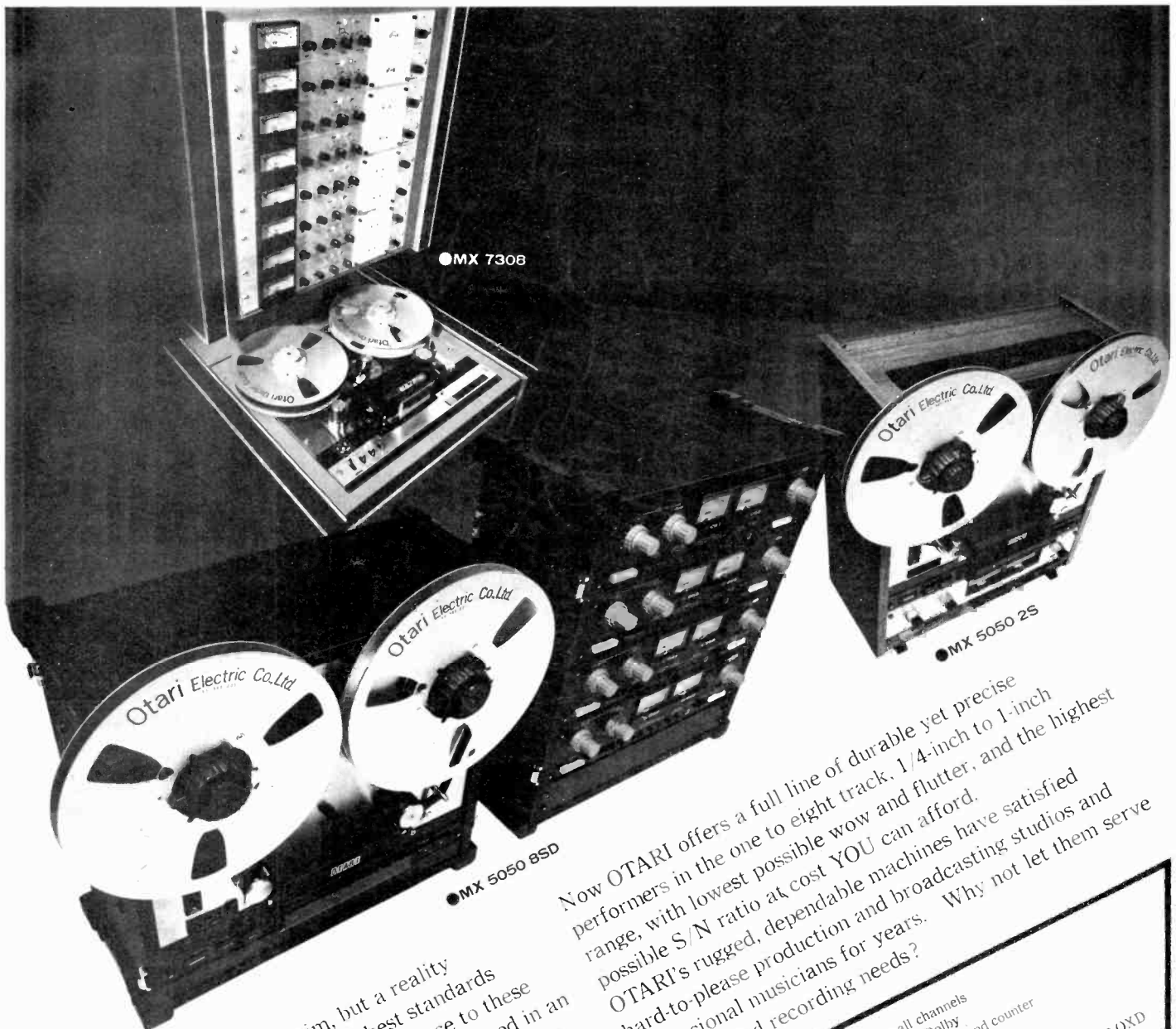
# Professional Performance at Popular Prices!



At OTARI, this is not just a claim, but a reality brought by the application of the highest standards of technology and precision. And adherence to these standards by OTARI sound specialists has resulted in even greater lineup of full capability, professional tape recorders in compact packages with all the performance, features, and reliability you expect from more expensive machines.

#### ●MX 5050 2S

- \* Exceptional S/N ratio and crosstalk
- \* Motion sensing control logic prevents tape damage
- \* Selective reproduce for overdubbing (standard)
- \* Front accessible bias, EQ, and operating level
- \* Built-in test and cue oscillator
- \* Professional 600 ohm  $\pm$  4 dB outputs and XLR connectors.
- \* Front panel edit and cue controls
- \* DC servo capstan option

#### Four heads Bias adjustable for new high energy master tapes

#### ●MX 5050 8SD

- \* 1/2-inch eight channel recorder
- \* XLR line input and output connectors
- \* Test and calibration oscillator
- \* Variable speed DC servo capstan
- \* Plug-in card electronics and head assembly
- \* Motion sensing control logic prevents tape damage

- \* Selective reproduce on all channels
- \* Interface jack for dbx and Dolby
- \* Accessible heads, minute and second counter
- \* Front adjustable cue and edit control
- \* Easily accessible electronics adjustments
- \* Also available in four channel 1/4" and 1/2" MX 5050 QXD

\* Exclusive OTARI features.

Now OTARI offers a full line of durable yet precise performers in the one to eight track, 1/4-inch to 1-inch range, with lowest possible wow and flutter, and the highest possible S/N ratio at cost YOU can afford. OTARI's rugged, dependable machines have satisfied hard-to-please production and broadcasting studios and professional musicians for years. Why not let them serve YOUR sound recording needs?

## OTARI®

Contact OTARI today for full information

Otari Electric Co., Ltd., Otari Bldg., 4-29-18, Minami Ogikubo, Suginami-ku, Tokyo 167, Japan. Phone: (03)333-9631

U. S. A.: Otari Corporation, 981 Industrial Road, San Carlos, California 94070, Phone: 415 593-1648

●Canada: Noresco Manufacturing Co., Ltd., 100 Floral Parkway, Toronto, Ontario M6L2C5 Phone (416) 249-7316

●U. K.: C. E. Hammond & Co., Ltd. 105 109 Oyster Lane, Byfleet, Surrey KT14 7LA, Phone: Byfleet 41131

●France: Reditec 62-66, Rue Louis Ampère (Zone Industrielle des Chanoux), 93360 Neuilly-Plaisance, Phone: 935-9786

●Belgium: Trans European Music S. A. Koevijverstraat 105, 1710 Dilbeek, Phone: (02) 569 1823

●Netherlands: Selectronic B. V. Sluisplein 3-4, Ouderkerk aan de Amstel, Postbus 28, Phone: 02963 4838 4966

●Australia: Klarion Enterprises (Pty.) Ltd. Regent House, 63 Kingsway, South Melbourne, 3205, Phone: 61 3801

●Singapore: Otari Electric Co., Ltd., Singapore Representative Office, 2701-A 27th Floor, International Plaza, Anson Road, Singapore (2)

WW-081 FOR FURTHER DETAILS

www.americanradiohistory.com




Automatic test equipment on your assembly lines will dramatically reduce production costs. But it must be the right type of equipment; low priced, easy to use, and readily adaptable to your various test needs. Like the Wayne Kerr Testmatics.

After installing a Testmatic, one company reported a 70% saving in year one; the Testmatic took just 20 seconds to do what used to take 20 minutes.

Another company - manufacturers of plug-in PCBs - bought a Testmatic after a thorough search of the test equipment market. Because the Testmatic was capable of making 60 separate checks in just six seconds, production bottle-necks became a thing of the past. Again, big cost savings were achieved.

No matter what testing costs you now - in salaries, overheads, rejects, errors, hold-ups, test equipment... anything - Wayne Kerr Testmatics will make immediate and significant savings. In many cases, Testmatics have a pay-back period of less than twelve months. Find out more by completing the coupon.

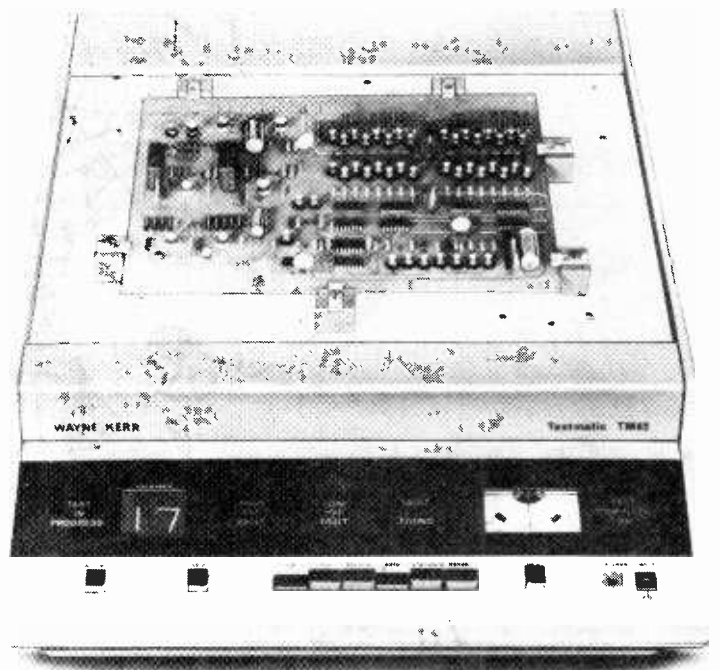**If assembly-line testing costs you £20,000 per year, that could be £14,000 too much.**



**Wayne Kerr Testmatics.**



**Wilmot Breeden Electronics**  
Ferrograph      Rendar      Wayne Kerr

Wilmot Breeden Electronics Limited,  
442 Bath Road, Slough, SL1 6BB,  
England. Telephone: Burnham (06286)  
62511 Telex: 847297

**The more they work, the more you save.**

Please send me information on the Wayne Kerr Testmatics.

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_


Address \_\_\_\_\_

\_\_\_\_\_ Telephone \_\_\_\_\_

Wilmot Breeden Electronics Limited,  
442 Bath Road, Slough, SL1 6BB, England.  
Telephone: Burnham (06286) 62511 Telex: 847297

WWA/77

# Eddystone VHF Monitoring System 1538

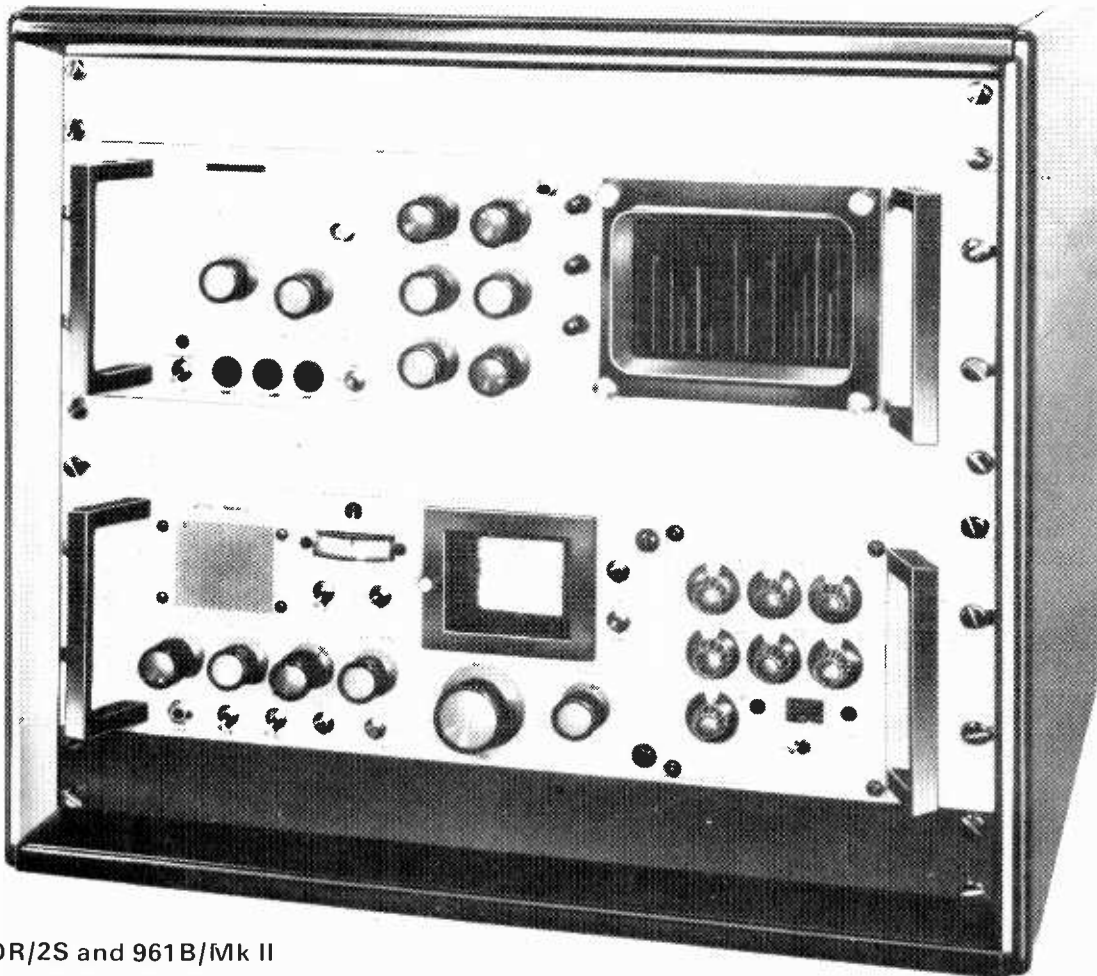


1990R/2S and 961B/Mk II

Modes AM, FM, CW, Pulse, covering the spectrum 25MHz to 500MHz.

Receiver available with synchroniser or crystal facility.

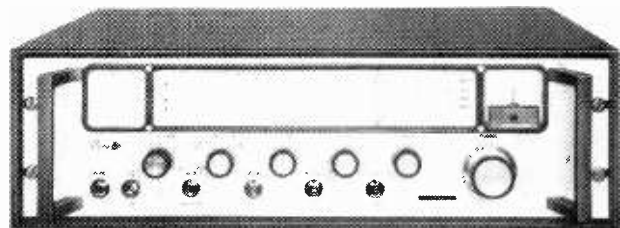990R (*illustrated right*) is alternative VHF receiver covering 27MHz to 240MHz.



*Please write for an illustrated brochure*

DCA No : 10D/CA/5967

## Eddystone Radio Limited

Member of Marconi Communication Systems Limited

Alvechurch Road, Birmingham B31 3PP, England

Telephone : 021-475 2231 Telex : 337081

A GEC-Marconi Electronics Company




WW-074 FOR FURTHER DETAIL

[www.americanradiohistory.com](http://www.americanradiohistory.com)



We've  
 extended Arrow  
 subminiature choice  
 with **snap-in rocker and  
 paddle action**

You can tell a popular switch range by the way it grows. Especially with up-to-the-minute Arrow-Hart thinking behind it. C series for example . . . performance-proven 3A, 250V AC rated subminiature lever switches. *You like them . . . everyone approves them.* So now, new C series models offer extra features. Fast snap-in assembly to beat ever-rising labour costs . . . rocker action and confident paddle-lever action to match today's control panel ideas. Positive, long-life switching, in a rugged, lightweight moulded body with solder lug terminals. Wide circuit choice too . . . single or double pole, two or three way. Good thinking from Arrow-Hart . . . right in line with your needs in business machinery and test gear, aerospace and telecom applications.

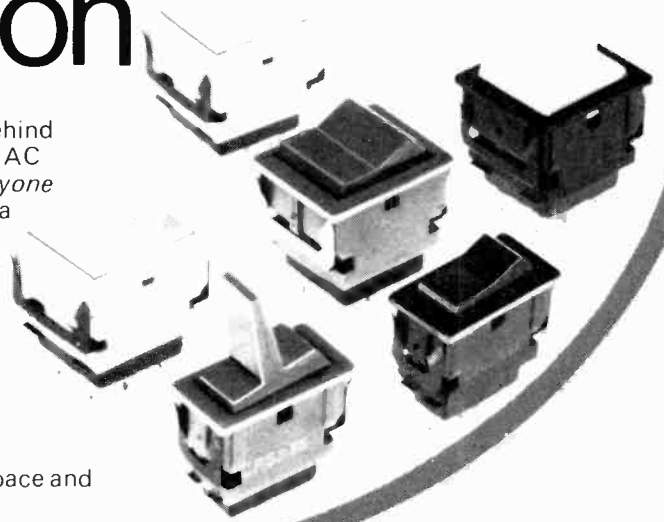

We've got interesting literature on the extended Arrow C series ranges

**Arrow  
 Hart**  
 always  
 thinking  
 ahead

See us on **STAND 37C**  
 at the Institution of Electronics 8th Scottish  
 Exhibition & Convention — March 22-24



**Arrow-Hart (Europe) Ltd.**  
 Plymbridge Road, Estover, Plymouth PL6 7PN, England.  
 Tel: Plymouth (STD 0752) 701155 Telex: 45340

**Midlands Office:**  
 1626/8 Coventry Road, Yardley, Birmingham B26 1AN.  
 Telephone: 021-707 0696.

**Scottish Office:**  
 13 Murray Place, Stirling.  
 Telephone: 0786 3823.

WW-035 FOR FURTHER DETAILS

## F. M. TUNER MODULES BY

These modules are fully assembled, tested and guaranteed units, as featured in our tuner. Designed by experts in integrated circuit technology and applications, they represent the finest available modules, ideal for incorporation into top quality home built systems.

# Icon Design

The Electronic Design Specialists

M1, M2, M3, M4, M5, AND NOW:—

## M6 DIGITAL FREQUENCY METER (WATCH FOR FURTHER ADDITIONS)

- ★ CMOS CIRCUITRY
- ★ FULL POWER SUPPLY
- ★ MOUNTS INSIDE TUNER
- ★ 4 DIGIT L.E.D. DISPLAY
- ★ NO TAMPERING WITH FRONT END REQUIRED
- ★ MONEY BACK GUARANTEE

We are very pleased to be able to announce this new module which has been in development for over 12 months. It has been designed to suit the specific requirements of F.M. tuners, to provide accurate station identification at a glance, at a sensible price and a sensible size. The complete outfit, which is NOT a kit, consists of the transformer, logic and display module and local oscillator take-off board. This latter fits directly to our main receiver board, and requires NO direct connections or modifications to the LP1186 front end module.

If you are interested drop us a line for full details and prices of all our modules.



Correction and Diagnostic Sheets for the original article design (W.W. April / May 1974) still available.



A **booklet** is available for 50p (post free U.K.) Fully describing the completely **updated** tuner. Prices subject to 12.5% VAT

To:

*Icon Design*

33 Restrop View  
Purton, WILTS  
SN5 9DG

## HIGH POWER DC-COUPLED AMPLIFIER



- ★ UP TO 500 WATTS RMS FROM ONE CHANNEL
- ★ DC-COUPLED THROUGHOUT
- ★ OPERATES INTO LOADS AS LOW AS 1 OHM
- ★ FULLY PROTECTED AGAINST SHORT CCT, MISMATCH, ETC.
- ★ 3 YEAR WARRANTY ON PARTS AND LABOUR

The DC300A Power Amplifier is the successor to the world famous DC300 which is so widely used in Industrial, and Research applications in this country. It is DC-coupled throughout so providing a power bandwidth from DC to over 20,000Hz. The ability of the DC300A to operate without fuss into totally reactive loads while delivering its full power, and maintaining its faithful reproduction of Pulse or complex waveforms has established the DC300A as the world's leading power amplifier. Each of the two channels will operate into loads as low as 1 ohm, and the amplifier can be rapidly connected as a single ended amplifier providing over 650 watts RMS into a 4 ohms load, and still providing a bandwidth down to DC. Below is a brief specification of the DC300A, but if you require a data sheet, or a demonstration of this fine equipment please let us know.

Power Bandwidth	DC 20kHz @ 150 watts + 1db. 0db	Slewing Rate	8 volts per microsecond
Power at clip point (1 chan)	500 watts rms into 2.5 ohms	Load impedance	1 ohm to infinity
Phase Response	+0. -15 DC to 20kHz. 1 watt 8Ω	Input sensitivity	1.75 V for 150 watts into 8Ω
Harmonic Distortion	Below 0.05% DC to 20kHz	Input Impedance	10K ohms to 100K ohms
Intermod. Distortion	Below 0.05% 0.01 watt to 150 watts	Protection	Short mismatch & open cct. protection
Damping Factor	Greater than 200 DC to 1kHz at 8Ω	Power supply	120-256V 50-400Hz
Hum & Noise (20-20kHz)	At least 110db below 150 watts	Dimensions	19" Rackmount, 7" High, 9 3/4" Deep
Other models in the range: D60 — 60 watts per channel		D150A — 150 watts per channel	

Other models available from 100 watts to 3000 watts



### MACINNES LABORATORIES LTD.

Macinnes House, Carlton Park Industrial Estate  
Saxmundham, Suffolk IP17 2NL. Tel: (0728) 2262 2615

### MACINNES FRANCE

18 Rue Botzaris  
Paris 75019, France  
Tel: 206-60-80 or 206-83-61

WW-021 FOR FURTHER DETAILS





# CONNECT UP WITH THE WORLD AT THE LONDON ELECTRONIC COMPONENT SHOW

LECS 77 brings you a host of the world's major component manufacturers.

LECS 77 is the twenty fifth London Electronic Component Show – the British based show which consistently attracts the close attention of the World's component buyers. The show coincides with the expected upturn in manufacturing industry and improvement of national economies. LECS 77 gives you a unique opportunity to assess the best of the world market at the right moment.

Visit LECS 77 and connect up with the world.

**THE LONDON ELECTRONIC COMPONENT SHOW  
17–20 MAY 1977, OLYMPIA, LONDON**



Organised by Industrial and Trade Fairs Ltd.,  
Radcliffe House, Blenheim Court, Solihull,  
West Midlands B91 2BG, England. Telephone: 021-705 6706.  
Telex: 337073. Cables: Indatfa Solihull

Sponsored by Radio and Electronic Component Manufacturers Federation.



I am interested in LECS 77. Please send me further details and ..... complimentary tickets.  
Details of the special hotel and travel arrangements  tick box if applicable

Name \_\_\_\_\_

Position \_\_\_\_\_

Company \_\_\_\_\_

Address \_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_  
\_\_\_\_\_



Complete and return to  
Industrial & Trade Fairs Ltd.,  
Radcliffe House, Blenheim Court, Solihull,  
West Midlands B91 2BG, England.

# The International Microphone



For over 40 years Beyer Dynamic microphones and headphones have served the needs of professional 'Sound Men' throughout the world. The M500 (Illustrated) is only one of a range of microphones now serving thousands of users who still demand high quality performance and reliability. Brochure showing the full range of microphones, headphones and accessories available on request.

**BEYER DYNAMIC**

BEYER DYNAMIC (GB) LTD  
1 Clair Road, Haywards Heath, Sussex. Tel: 51003


WW - 076 FOR FURTHER DETAILS

## Z & I AERO SERVICES LTD.

Head Office: 44A WESTBOURNE GROVE, LONDON W2 5SF  
Tel.: 727 5641 Telex: 261306

Retail Branch:  
85 Tottenham Court Road  
London W1. Tel: 580 8403

### MULTIMETER F4313 (Made in USSR)

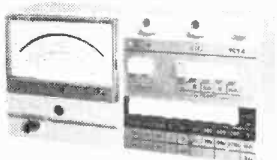

**SENSITIVITY:**  
1200V DC range: 10,000 Ω/V  
Other DC ranges: 20,000 Ω/V  
1200 AC range: 6,000 Ω/V  
600V AC range: 15,000 Ω/V  
300V AC range: 15,000 Ω/V  
Other AC ranges: 20,000 Ω/V.


AC/DC current ranges: 60-120-600 μA-3-12-300mA-1-2-6A  
AC/DC voltage ranges: 60-300mV-1-2-6-30-120-300-600-1200V  
Resistance ranges: 300Ω-10-100-1000K  
Accuracy: 1.5% DC, 2.5% AC (of full scale deflection)

Mirror scale and knife edge pointer. Taut suspension of movement. Transistor amplifier is used for all AC ranges thus achieving a common linear scale for both AC and DC ranges.

Meter is protected by a transistorised cut-out relay circuit. Range selection is achieved by clearly marked piano keys. Power source: 5V 5V dry cells. Dimensions: 95 x 225 x 120mm.

PRICE £39.50 plus VAT  
Packaging and postage £1.10

### OSCILLOSCOPE CI-5 Made in USSR

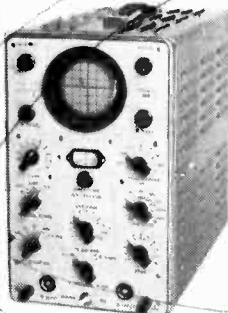

Extremely simple and easy to use single beam oscilloscope. Well proved design based on standard octal valves makes servicing and maintenance straightforward and inexpensive. Because of its bandwidth of 10 MHz the instrument is suitable for general electronic applications and educational purposes where a sophisticated instrument would be both too expensive and delicate. 3in. tube giving a 50 x 50mm clear display. Amplitude and time base calibrations. Sensitivity 30mm/v max. Triggered and free-running time base suitable for displaying pulses from 0.1 μsec. to 3m sec. A.C. mains operation.

Price £55.00 ex. works, plus VAT  
Packaging and carriage (U.K. only) £3.00

### A SELECTION FROM OUR LARGE STOCKS

TRANSISTORS									
2N696	0.15	*2N3705	0.10	AF239	0.36	BF177	0.18	*1N4004	0.05
2N697	0.15	*2N3706	0.10	ASY26	0.25	BF178	0.32	*1N4005	0.05
2N706	0.10	*2N3707	0.10	ASY27	0.30	BF179	0.35	*1N4006	0.06
2N706A	0.10	*2N3708	0.10	ASY28	0.30	BF180	0.31	*1N4007	0.06
2N753	0.23	*2N3709	0.10	BC107	0.10	BF181	0.35	*1N4148	0.04
2N929	0.14	*2N3710	0.10	BC107A	0.12	BF184	0.29	*1N5408	0.20
2N930	0.14	*2N3711	0.10	BC107B	0.12	BF185	0.30	*BY101	0.15
2N1131	0.25	*2N3819	0.35	BC108	0.10	*BF194	0.08	*BY105	0.15
2N1132	0.25	*2N3904	0.20	BC108A	0.12	*BF195	0.08	*BY126	0.10
2N1302	0.17	*2N3905	0.25	BC108B	0.12	*BF196	0.10	*BY127	0.13
2N1303	0.15	*2N3906	0.25	BC109	0.12	*BF197	0.11	*BY140	0.10
2N1304	0.20	AC125	0.20	BC109A	0.12	BF200	0.28	*BY164	0.50
2N1305	0.20	AC126	0.20	BC109B	0.12	BFX88	0.20	BZK61	0.20
2N1306	0.27	AC127	0.17	BC109C	0.12	BFY50	0.19	series	0.20
2N1307	0.25	AC132	0.25	*BC147	0.12	*BFY51	0.19	BZY88	0.10
2N1308	0.25	AC176	0.22	*BC149	0.08	BFY52	0.20	series	0.10
2N1309	0.25	AC187	0.20	*BC158	0.10	*BU208	2.00	*OA70	0.07
2N1613	0.17	AC188	0.18	*BC171	0.10	OC36	0.65	*OA79	0.07
2N1711	0.18	AC199	0.20	BC178	0.18	OC41	0.25	*OA81	0.07
2N2221	0.20	ACV22	0.14	*BC182	0.11	OC45	0.20	*OA85	0.07
2N2222A	0.20	AD161	0.38	*BC182A	0.10	OC70	0.15	*OA90	0.07
2N2369A	0.25	AD162	0.38	BC186	0.25	OC71	0.15	*OA91	0.07
2N2646	0.40	AD211	1.25	BC187	0.25	OC72	0.18	*OA95	0.07
2N2905	0.25	AD212	1.25	*BC212	0.11	OC75	0.15	*OA200	0.07
2N2906	0.20	AF106	0.25	*BC238	0.11	OC76	0.18	*OA202	0.08
2N2907	0.20	AF114	0.17	BCY32	1.20	OC81	0.20	RAS310AF	0.35
*2N2926	0.10	AF115	0.17	BCY37	0.15	OC83	0.30	RAS508AF	0.40
2N3053	0.20	AF116	0.17	BCY70	0.15	OC84	0.30	TTL SERIES	
2N3054	0.65	AF117	0.17	BCY72	0.15	OC206	0.70	Russian made	
2N3055	0.55	AF118	0.25	*BG237	0.39	OCP71	0.90	Special offer	
2N3391	0.17	AF124	0.25	BD115	0.39	ORP12	0.60	7400	0.09
2N3392	0.17	AF125	0.25	BD132	0.39	*IP30A	0.50	7401	0.09
2N3393	0.15	AF126	0.25	BD133	0.45			7410	0.09
2N3414	0.20	AF127	0.25	*BD137	0.30			7420	0.11
2N3415	0.15	AF139	0.30	BF135	0.28	*IN914	0.05	7422	0.20
*2N3702	0.10	AF178	0.50	*BF152	0.20	*IN1001	0.04	7430	0.11
*2N3703	0.10	AF180	0.50	BF167	0.25	*1N4002	0.05	7440	0.11
*2N3705	0.10	AF181	0.50	BF173	0.25	*1N4003	0.05	7450	0.11

P&P 25p min. (U.K. only). Please add 8% VAT + 12.5%

MINIMUM EXPORT ORDER £100  
FULLY GUARANTEED



1976/1977  
CATALOGUE  
AVAILABLE 30p

WW - 060 FOR FURTHER DETAILS

£62.40 total




# Join the Digital Revolution

Understand the latest developments in calculators, computers, watches, telephones, television, automotive instrumentation . . .

Each of the 6 volumes of this self-instruction course measures 11 3/4" x 8 1/4" and contains 60 pages packed with information, diagrams and questions designed to lead you step-by-step through number systems and Boolean algebra, to memories, counters and simple arithmetic circuits, and on to a complete understanding of the design and operation of calculators and computers.

Design of Digital Systems

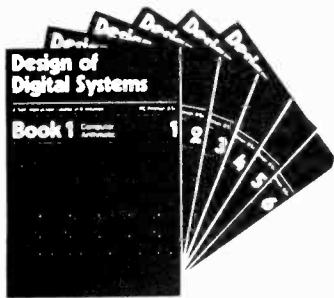

## £6.20

plus 80p packing and surface post anywhere in the world

Payments may be made in foreign currencies

Quantity discounts available on request

VAT zero rated

Also available — a more elementary course assuming no prior knowledge except simple arithmetic  
Digital Computer Logic and Electronics

In 4 volumes

1. Basic Computer Logic
2. Logical Circuit Elements
3. Designing Circuits to Carry Out Logical Functions
4. Flipflops and Registers

## £4.20

plus 80p P. & P

Offer Order both courses for the bargain price £9.70, plus 80p P. & P.

**Designer  
Manager  
Enthusiast  
Scientist  
Engineer  
Student**

These courses were written so that you could teach yourself the theory and application of digital logic. Learning by self instruction has the advantages of being quicker and more thorough than classroom learning. You work at your own speed and must respond by answering questions on each new piece of information before proceeding to the next.

### Guarantee—no risk to you

If you are not entirely satisfied with Design of Digital Systems or Digital Computer Logic and Electronics, you may return them to us and your money will be refunded in full, no questions asked.

To Cambridge Learning Enterprises, Dept. COM, FREEPOST  
Rivermill House, St. Ives, Huntingdon, Cambs PE17 4RR

\*Please send me set(s) of Design of Digital Systems at £7.00 each p & p included

\*or set(s) of Digital Computer Logic and Electronics at £5.00 each, p & p included

or combined set(s) at £10.50 each, p & p included

Name


Address

delete as applicable

No need to use a stamp — just print FREEPOST on the envelope

ww4
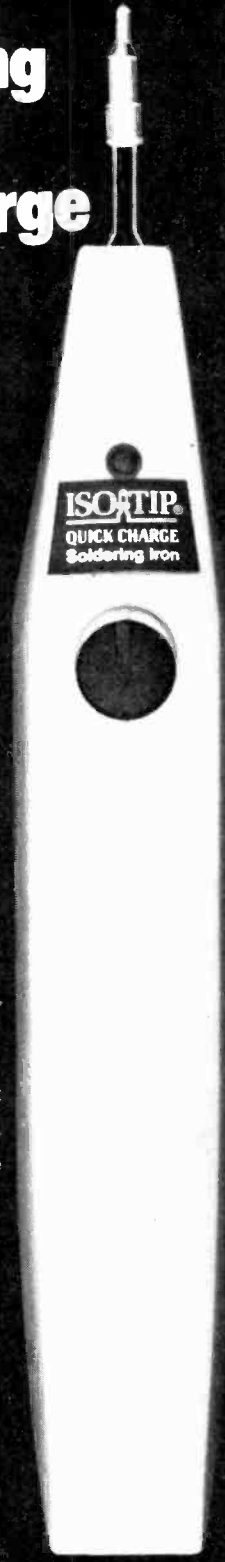
# Introducing the new Quick Charge Cordless Soldering Iron



- Solder heat in five seconds
- No wires to restrict use
- Completely recharges in only 4 hours!
- No need for earthing
- Capacity to solder up to 125 joints

This new rechargeable soldering iron from Greenwood brings added freedom to professional soldering. The Quick Charge recharges so fast that completely dead battery cells can be brought to full charge in about 4 hours — three times faster than before. In its stand the Quick Charge is, of course, being continually charged. A wide range of tips and now also a P.C. Drill attachment make this the most 'versatile' professional soldering iron available.



Illustration actual size.

## Greenwood Electronics

Greenwood Electronics, Portman Road, Reading, RG3 1NE  
Telephone: 0734-595844, Telex 848659

WW—025 FOR FURTHER DETAILS


# transformers

mains, audio, microphone, ferrite core and other wound components

A wide range of transformers manufactured in production quantities to customers individual requirements

Prompt Prototype Service available

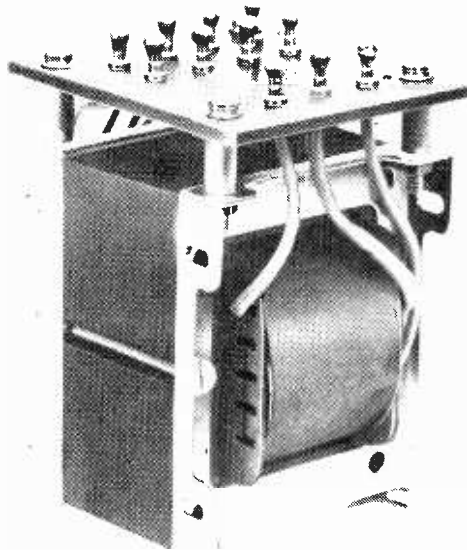TRANSFORMER WITH UNIVERSAL END FRAMES AND TURRET LUG CONNECTIONS



MICROPHONE TRANSFORMER IN MUMETAL CAN



TRANSFORMER WITH TWO HOLE CLAMP AND SOLDER TAG CONNECTIONS

## Drake Transformers Limited

Telephone: Billericay 51155

Kennel Lane, Billericay, Essex.

WW — 065 FOR FURTHER DETAILS


# A. D. BAYLISS & SON LTD.

## Behind this name there's a lot of real POWER!

Illustrated right is a **TITAN DRILL**

Mounted in a multi-purpose stand. This drill is a powerful tool running on 12v DC at approx 9000 rpm with a torque of 350 gm. cm. Chuck capacity 3.00 m/m. The multi-purpose stand is robustly constructed of steel and aluminium. The base and bracket are finished in hammer blue. Also available for use in the stand is the **RELIANT DRILL** which is a smaller version of the Titan. Approx. speed 9000 rpm. 12v DC, torque 35 gm. cm. Capacity 2.4 m/m.

- |                                  |                             |
|----------------------------------|-----------------------------|
| <b>TITAN DRILL &amp; STAND</b>   | <b>£19.50</b>               |
|                                  | + 8% VAT = £21.06 + £1 P&P  |
| TITAN DRILL ONLY                 | <b>£8.90</b>                |
|                                  | + 8% VAT = £9.61 + 35p P&P  |
| <b>RELIANT DRILL &amp; STAND</b> | <b>£16.27</b>               |
|                                  | + 8% VAT = £17.52 + £1 P&P  |
| RELIANT DRILL ONLY               | <b>£5.22</b>                |
|                                  | + 8% VAT = £5.64 + 35p P&P  |
| <b>TITAN MINI KIT DRILL</b>      | <b>£14.75</b>               |
| Plus 20 Tools                    | + 8% VAT = £15.93 + 50p P&P |
| <b>RELIANT MINI KIT DRILL</b>    | <b>£12.00</b>               |
| Plus 20 Tools                    | + 8% VAT = £13.08 + 50p P&P |
| <b>TRANSFORMER UNIT</b>          | <b>£8.55</b>                |
|                                  | + 8% VAT = £9.23 + 75p P&P  |

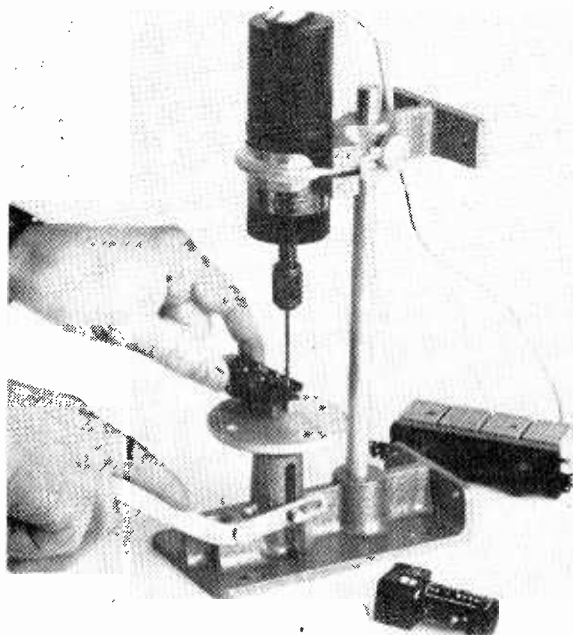


These are examples of the extensive range of power tools designed to meet the needs of development engineers, laboratory workers, model makers and others requiring small precision production aids. To back up the power tools, Expo offer a comprehensive selection of Drills, Grinding Points and other tools. SEND STAMP for full details to main distributors.

**A. D. BAYLISS & SON LTD.,** Pfera Works, Redmarley, Glos. GL19 3JU  
Stockists Richards Electric, Worcester and Gloucester; Hoopers of Ledbury; Hobbs of Ledbury; D&D Models, Hereford; Bertella, Gloucester

WW—084 FOR FURTHER DETAILS




### ESP Mini-C-Dekade

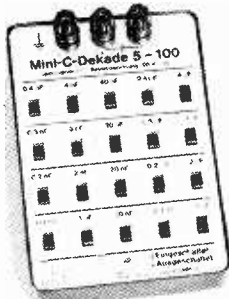

Mini-C-Dekade Type 5-100  
Range 100pF to 11  $\mu$ F  
Accuracy 2%  
Rating 100V DC  
Size 10 x 15 x 4 cm  
Fits neatly in to the palm of the hand

**Price £69**  
EX VAT

### ESP Mini-T-Dekade

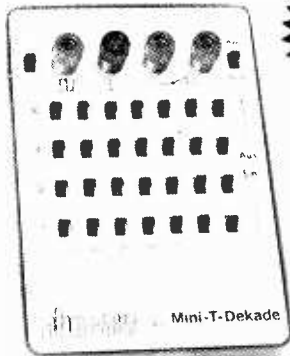


UP TO  
ONE  
MILLION  
SECONDS  
DELAY

#### UNIVERSAL TIMER

1  $\mu$ sec to 1 000 000 secs  
The Mini-T-Dekade has unique features offering engineers a new fast, accurate means of designing and building electronic circuits  
Time range—1. 1 $\mu$ s to 9.999999 secs II. 0.1  $\mu$ s to 999999.9 secs Ranges are switched in 7 decades using BCD code.  
Output — 25mA, 30V and 10W, 0.5A, 200V DC  
Quartz crystal—2 MHz. Stability, 50 ppm  
Power supply—N Cd cell 12V 225m Ah

**Price £195** EX VAT

### ESP Mini-R-Dekade

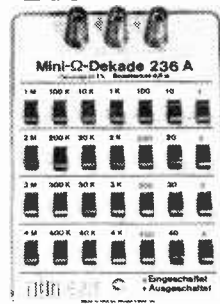

Mini-R-Dekade Type 236A  
Range 1 ohm to 11 Mohm  
Accuracy 1%  
Max Dissipation 0.5W  
Size 10 x 15 x 3 cm  
Fits neatly into the palm of the hand

**Price £49** EX VAT


### ESP Mini DVM



**LIQUID CRYSTAL  
AUTO RANGING**  
Mini DVM Type 3201  
Functions  
DC V 200, 2000 mV  
20 200 V  
1000 V  
200 mV  
AC V 2000 mV  
20 200 V  
500 V  
DC A 200 2000  $\mu$ A  
20 200 mA  
200  $\mu$ A  
AC A 2000  $\mu$ A  
20 200 mA  
OHM 2 20 K $\Omega$   
200 2000 K $\Omega$

**Price £84** EX VAT

### ESP Mini C-Meter

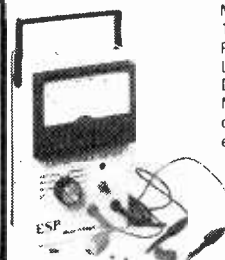

Mini C-Meter 100A  
1pF to 10  $\mu$ F  
Portable  
Linear Scale  
Direct reading  
Measures any type of capacitor including electrolytics

**Price £49** EX VAT

## Auto ranging Automatic Capacitance Bridge Model ESP 300A 1pF to 2000 $\mu$ F

A complete range of British-made instruments designed to simplify capacitance measuring

- Accurate and sensitive
- Requires no manual balancing
- Takes less than a second to measure a capacitor
- Updates changes in capacitance automatically
- Wide range of applications



STAND 554C  
LECS OLYMPIA  
17-20 MAY 1977



Electronic Services and Products Limited  
MIDDLE MARCH  
LONG MARCH INDUSTRIAL ESTATE  
DAVENTRY  
NORTHANTS. NN11 4PQ  
Telephone: (03272) 76720




Autoranging  
capacitance bridge  
**£225.00 + V.A.T.**

Send for technical literature and free booklet: "Modern methods of capacitance measuring"  
Suppliers to: Ministry of Defence, Post Office, B.B.C., Government departments and Electronic Laboratories world-wide.

WW—088 FOR FURTHER DETAILS

## JES AUDIO INSTRUMENTATION

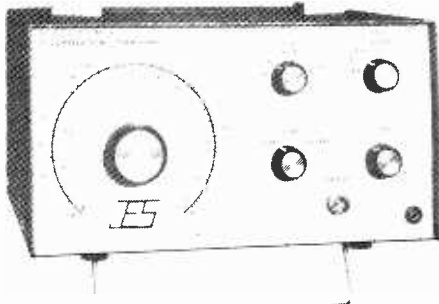

#### Si451 Millivoltmeter

- ★ 20 ranges also with variable control permitting easy reading of relative frequency response

**£60.00**

also available

#### Si452 Distortion Measuring Unit

- ★ low cost distortion measurement down to 0.01% with comprehensive facilities including L.F. cut switch, etc.

**£48.00**

ALL PRICES PLUS VAT

J. E. SUGDEN & CO. LTD., CARR STREET, CLECKHEATON, W. YORKS. BD19 5LA.

Tel. 0274-872501

WW—042 FOR FURTHER DETAILS



UP  
UP  
AND  
AWAY!



Look up to a Versatower installation and your radio communications will achieve new heights! Acclaimed as the World's leading telescopic tilt-over tower in the international field of radio communication.

A complete range of models: from 20 to 120 feet, static and mobile. Full details and specifications are in our brochure. Send for it today!

Strumech Engineering Limited,  
Portland House, Coppice Side,  
Brownhills, Walsall,  
West Midlands WS8 7EX.  
Telephone. Brownhills 4321


Due to the enormously increased demand for Versatower systems we have now opened our new West Works. Phone us - we'll be glad to show you around.

**STRUMECH**  
VERSATOWER  
SYSTEM



WW-079 FOR FURTHER DETAILS

## ELECTRONIC INDUSTRIAL THERMOMETER

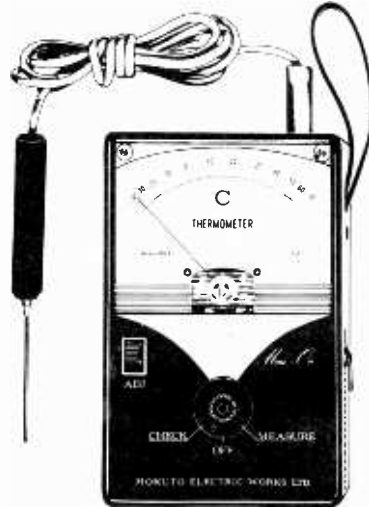

### THE MODERN WAY TO MEASURE TEMPERATURE

A Thermometer designed to operate as an Electronic Test Meter. Will measure temperature of Air, Metals, Liquids, Machinery, etc., etc. Just plug-in the Probe, and read the temperature on the large open scale meter. Supplied with carrying case, Probe and internal 1 1/2 volt standard size battery.


**Model "Mini-Z 1" measures from -40° C to + 70° C Price £25.00**  
**Model "Mini-Z 2" measures from -5° C to + 105° C Price £25.00**  
**Model "Mini-on Hi" measures from + 100° C to + 500° C £20.00**  
 (VAT 8% EXTRA)

Write for further details to

**HARRIS ELECTRONICS (LONDON)**  
 138 GRAY'S INN ROAD, LONDON. WC1X 8AX  
 ('Phone 01-837 7937)

WW-022 FOR FURTHER DETAILS

## BULK ERASURE PROBLEMS?

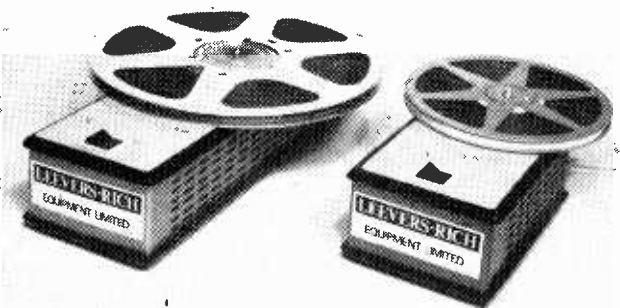

**LR71**  
**MAX REEL SIZE 11 1/2"**

**LR70**  
**MAX REEL SIZE 8 1/4"**

If it's personal we can only advise a diet or joining weightwatchers. If it's to do with tape, then why not consider the LR70/71 bulk tape erasers. They are simple to operate and will erase cassettes, cartridges and reels of tape up to a maximum reel size of 11 1/2" and tape width of 1", quickly and efficiently within the time it takes to read this advertisement.

The LR70/71 bulk erasers are currently used in Broadcast Companies, Recording Studios, Government Departments, Educational Establishments and the Computer Industry.

*Moderately priced and available from:*

**LEEVERS-RICH EQUIPMENT LIMITED**  
**INCORP. BIAS ELECTRONICS**  
 319 Trinity Road, Wandsworth, London SW18 3SL  
 Telephone 01-874 9054  
 Cables: Leemag London SW18. Telex 923455 Wembley

WW-044 FOR FURTHER DETAILS





# MXT-1000 AUDIO MIXING SYSTEM

8 channel, 2 group MXT-1000 - each channel fitted with compressor

The new MXT-1000  
A unique system enabling your own requirements to be built from standard equipment


Manufacturers of sound systems and electronics

Station Road, Wenden  
Saffron Walden  
Essex CB11 4LG  
Saffron Walden  
(0799) 40888

**audix**
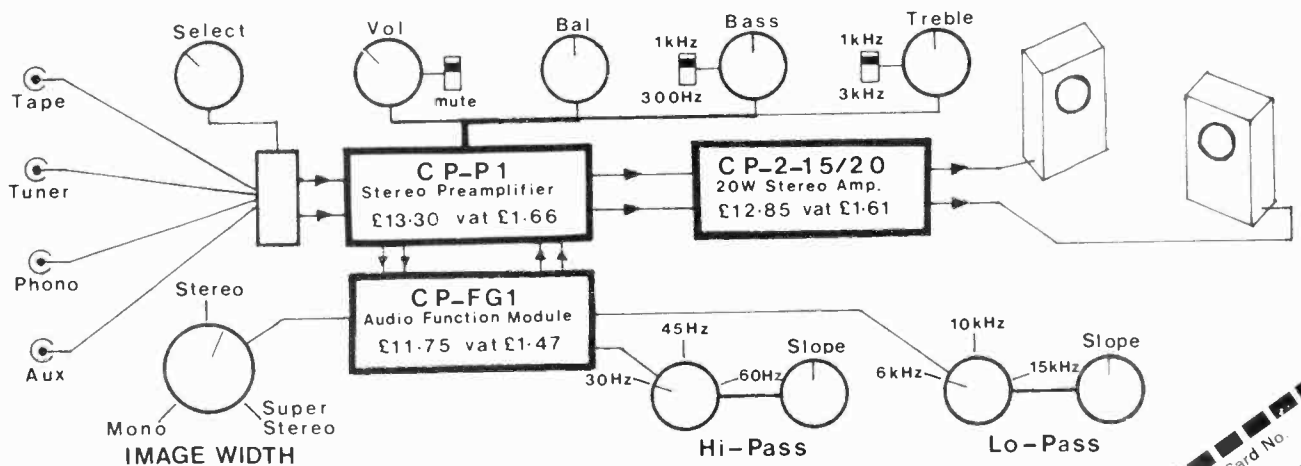
## Hi-Fi Systems that GROW with you

**MAGNUM III** System as well as the features illustrated, has 20W r.m.s. per channel (you could have 40), with typical distortion of only 0.07%. The magnetic input has >70dB. S/N ratio (Ref. 3mV) and an overload margin of 43dB.



For details of **CLIFFPALM AUDIO MODULES** send large s a e. or see ad. in Feb. W.W. **NOW EX STOCK.** All other parts required - knobs, pots (rotary and linear) switches, sockets, etc **NEW THIS MONTH.** P.C.B.s on which to build your MAGNUM I, II or III system **POWER MODULE CP-PS-18/2D. £6.50 + 81p V.A.T.**

Prices include full application data, post and packing U.K. only. These products carry a 2 year guarantee

**Cliffpalm Ltd.** DEPT. HW, 13 HAZELBURY CRESCENT LUTON, BEDS LU1 1DF. Tel. 0582-415832

Phone your order quoting Credit Card No.  
Please rush me  
I enclose a cheque/postal order crossed and  
made payable to Cliffpalm Ltd for: £

NAME \_\_\_\_\_ ADDRESS \_\_\_\_\_

WW-031 FOR FURTHER DETAILS

# Plug into world-wide coverage with the new T1000

## solid-state 2-30MHz Linear Amplifier

This compact desk-top package incorporates the following features

- New generation high power transistors giving 1000W PEP, 600WCW output.
- Broadband requires no operator tuning
- Full VSWR protection
- Drive requirements 70-120W

Full technical information is available on request from the sole distributors in the UK



Aero Electronics (AEL) Ltd.  
 Gatwick House, Horley  
 Surrey, England RH6 9SU. Telephone Horley 5353  
 Cables Aerocon. Telex Horley; Telex 871116 (Aerocon Horley)



WW—008 FOR FURTHER DETAILS

### BIMBOARD

Stop Ruining Your I.C.'s And Wasting Time Soldering  
 Plug Into The Revolutionary New

### BIMBOARD


The Only Professional Quality Breadboard That  
 Accepts All DIL Packages With 6 To 40 Pins

Incorporates Bus Strips For Vcc And Ground

Includes A Component Support Bracket

Has Over 500 Individual Sockets

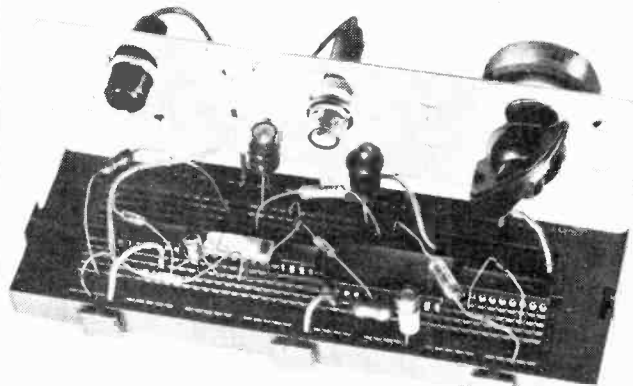And Allows You To Use And Re-Use  
 IC's, Transistors, LED's, 7 Segment Displays,  
 Diodes, Resistors, Capacitors




Only £9.72 (cheque with order) Including VAT and P.P.  
 Special Quantity Discounts Available For  
 Radio Clubs, Retail Outlets, Distributors

**BOSS INDUSTRIAL MOULDINGS LTD**

Higgs Industrial Estate, 2 Herpe Hill Road, London, SE24 0AU, England  
 Telephone 01-737 2383 Telex 919693

# nombrex

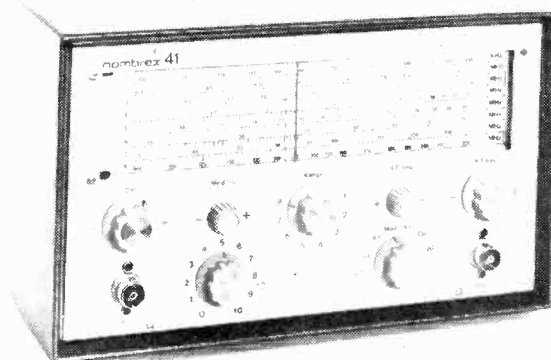

## MODEL 41 R.F. SIGNAL GENERATOR Price £54.85

PLUS V.A.T.

- ★ 150 KHz — 220 MHz on fundamentals.
- ★ 8 clear scales — Total length 130mm.
- ★ Spin-Wheel Slow Motion Drive 11 — 1 ratio.
- ★ Overall Accuracy — 2½%.
- ★ Modulation, Variable depth and frequency.
- ★ Internal Crystal Oscillator providing calibration checks throughout all ranges.
- ★ Mechanical scale adjustment for accurate alignment against internal 1MHz crystal oscillator.
- ★ Powered by 9V Battery.

Trade and Export enquiries welcome  
 Send for full technical leaflets  
 Post and Packing £1.00 extra

**NOMBREX LTD., POUND PLACE, WOLBOROUGH STREET,  
 NEWTON ABBOT, DEVON, TQ12 1NE  
 Tel. Newton Abbot 68297**


WW—019 FOR FURTHER DETAILS

# Edicron


## For Quality and Reliability

Edicron Limited  
 Redan House 1 Redan Place  
 London W2 4SA  
 Tel: 01-727 0101  
 Telex: 265531  
 Cables: Edicron London W2


Electronic Valves/Tubes

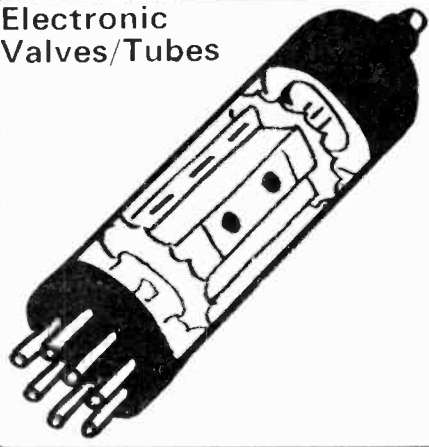


Resistors and Capacitors

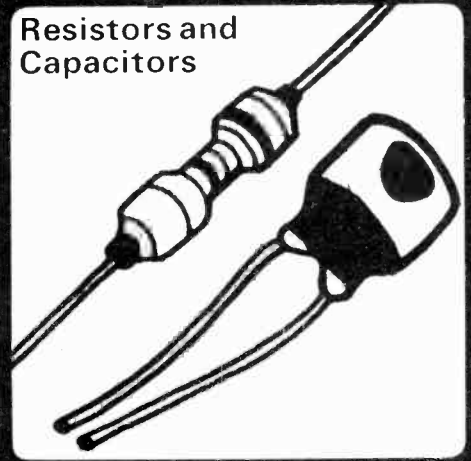


TV Picture Tubes

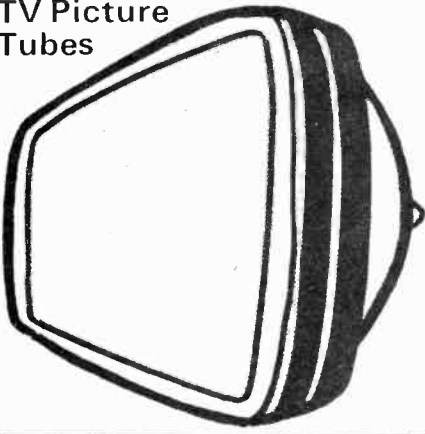

Transistors

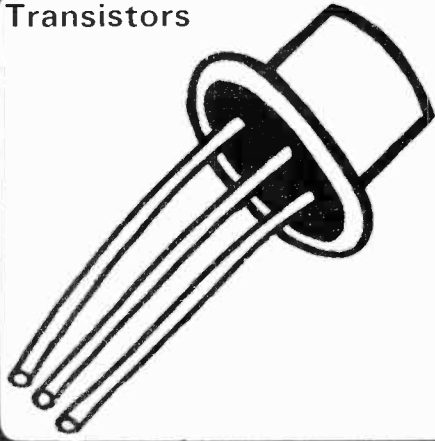

CR Gun Assemblies

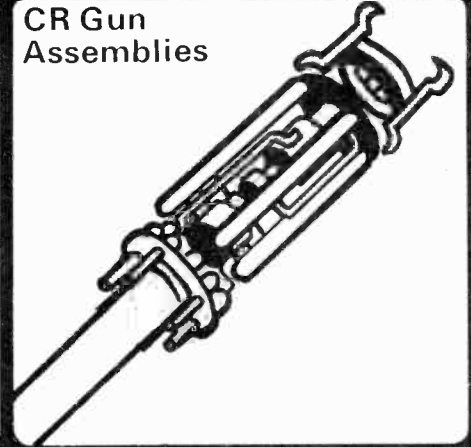


**EXPORT — INDUSTRY — WHOLESALE**

### The Quickest, Simplest Way of Punching Holes in Sheet Metal


Q-Max punches make clean, accurate holes every time. In no time. With no filing, no jagged edges, virtually no burrs—with no hard work. And no holes are barred. Round or square. Q-Max punches are available in sizes down to 10mm up to 75mm for use on sheet metal up to 16 gauge. No wonder they're used by all government services (Atomic, Military, Naval, Air, GPO, Ministry of Works) and all over the world by radio, motor and industrial manufacturers, plumbing and sheet metal trades and garages.

**57**  
metric  
and linear  
sizes

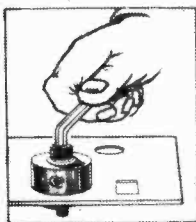

Wholesale and Export enquiries welcomed. Further details from, Q-Max (Electronics) Ltd, 44 Penton Street, London N19QA 01-278 2500

WW—039 FOR FURTHER DETAILS

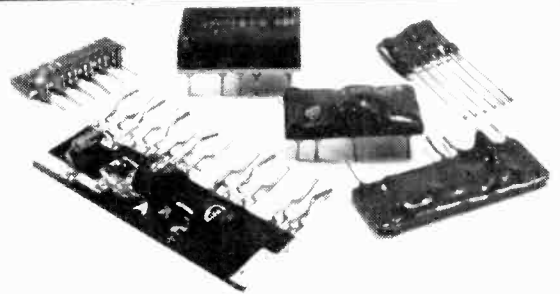

### FOR THICK FILM PRODUCTS, SAY ERIE

As the leading Thick Film manufacturer in the U.K., Erie are the obvious choice for these cost saving, highly reliable products, with over twelve years experience in the design and production of Passive and Hybrid Thick Film circuits. Erie offer a comprehensive range of units including:-

- Dual In Line Custom designed and Standard Resistor Networks in Ceramic Sandwich and Plastic Transfer Moulded formats.
- Single In Line Custom designed and Standard Resistor Networks.
- Power Resistors with Pluggable terminations, and High Value High Voltage wire ended Resistors.

Our experience, engineering and production facilities enable us to offer hybrid circuits in a variety of formats including Dual and Single In Line conformally coated and transfer moulded packages for a wide range of applications.

For more information about Thick Film contact:-


**ERIE ELECTRONICS LIMITED**  
 South Denes, Great Yarmouth, Norfolk.  
 Tel: 0493 56122 Telex: 97421

Components

WW—045 FOR FURTHER DETAILS



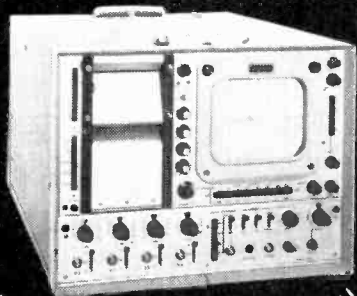**A NEW  
INSTRUMENT FOR  
WIDENING INDUSTRIAL  
APPLICATIONS**



**The FOR-4 Mark 2**

The new Medelec FOR-4-2 fibre optic recording oscilloscope is the result of a constant research and development policy. It incorporates many refinements which have been made to customers' special requirements.


The FOR-4-2 provides industrial and research users with high quality recording facilities at really low cost. X-Y Plot, Transient and Raster mode are all available in a single instrument.

**Special features of the Medelec FOR-4-2 include:**

- 10 times gain X and Y (1mV/cm on 4 Y channels)
- Fully automatic triggering (with higher sensitivity)
- Improved recording facilities (for greater flexibility)
- Light control filter (for excellent contrast)
- Wide speed range (from 0.1 to 1000 mm/sec—in 3 models)
- Internal loudspeaker (for audio monitoring)

For further information on the new FOR-4-2 or instruments in the range, contact:

**MEDELEC LIMITED**  
Manor Way, Woking  
Tel: Woking (048 62) 70331  
Telegrams: Medelec, Woking

**medelec** 

Leaders in  
Fibre Optic Recording

WW — 057 FOR FURTHER DETAILS

**Keep your tools handy  
in case...**



**With JENSEN**  
special quality industrial  
tool kits and cases

Send now for details of the superb Jensen range of tools, meters and accessory equipment, all in the most handy and robust cases — also available separately. Jensen products are specifically designed for industrial use, perfect for all engineers, technicians, electricians, instrument repairmen etc. Choice of more than twenty kits and cases.

Write for free Jensen catalogue to:



**SPECIAL PRODUCTS DISTRIBUTORS LTD,**  
81 Piccadilly, London W1V 0HL. Tel: 01-629 9556. Cables: Specipro London W1.

WW—070 FOR FURTHER DETAILS

**INSTANT CIRCUIT DESIGN  
WITH THE BUG SYSTEM**

**THE PROFESSIONAL BREADBOARDS FOR STUDENTS & HOBBYISTS!  
NO SOLDERING! USE ICs AGAIN & AGAIN!**

**SK10.** Takes up to eight 14 pin DILs. All components insert directly. Insertion life of 10,000 cycles. Contact resistance 5 milliohm average. Housing is acetal copolymer. **£13.38**

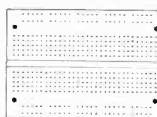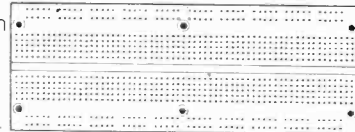

**SK50.** Half size version of SK10 for tight places and student use. Takes 4 DILs. **£7.80.**



**LABEL THOSE ICs.**


Self adhesive 'Bug Backs' for many 7400 series TTL ICs. Identify pins and device. Saves time and temper! Pack of 500 **£6.40.**



**LEARN DIGITAL ELECTRONICS**

**Bug Books Part I & II** 750 page learning system including 90 experiments on 50 different 7400 series TTL ICs. **£13.50 each.**

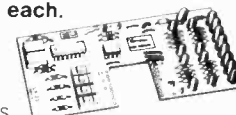**LR25.** A useful control package for digital circuits on SK10/SK50 sockets. Generates pulses. Monitors outputs. 8 LED indicators. 4 logic switches. 2 pulsers. Variable frequency clock. **£41.75.**



All prices include VAT and P. & P.


Send for the Bug System leaflet and order form or cheque with order.

**HEPWORTH ELECTRONICS**

Hepworth House, Worcester Road, Kidderminster DY10 1BG  
Telephone: Kidderminster 2212/3

WW—009 FOR FURTHER DETAILS

# NEW 3000 TWEETER

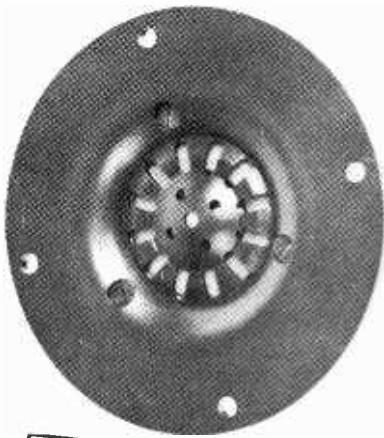

### Technical Data

**Frequency response:**  
2 Kc s to 15 Kc s withn 3db

**Impedance:**  
15 ohms or 8 ohms


**Flux Density:**  
10 000 gauss

**Dimensions Front Mounting:**

Body 2 1/4" (70.2 mm) dia x 1 1/4" (31 mm) deep  
Flange 3 1/2" (95 mm) x (3 mm) thick  
o all 1 1/8" (35 mm)

**Power Handling:**  
For use on 30 - 50 watt Amplifiers

**Suggested Crossover:**

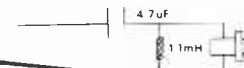

**COMBINE THE WELL-ESTABLISHED B200 WITH OUR BRAND NEW 3000 TWEETER TO PRODUCE A SOUND BOTH SMOOTH AND IMMEDIATE, WITH AN OPENNESS AND CLARITY THAT WILL ASTOUND YOU**




**Coles Electroacoustics Ltd.**

PINDAR ROAD HODDESDON EN11 0BZ  
Telephone Hoddesdon 66885 60060

Send a e for suggested cabinet arrangement  
**WW - 055 FOR FURTHER DETAILS**

## METER PROBLEMS?

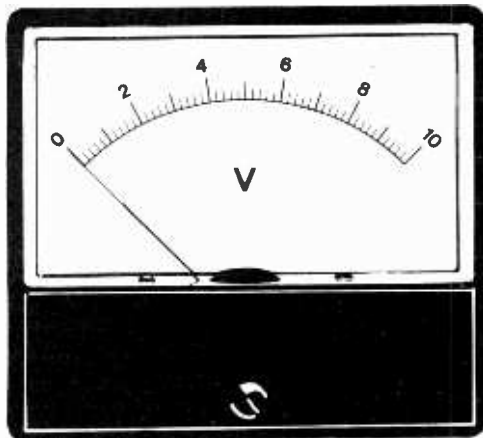

137 Standard Ranges in a variety of sizes and stylings available for 10-14 days delivery. Other Ranges and special scales can be made to order.

Full Information from:

**HARRIS ELECTRONICS (London)**

138 GRAYS INN ROAD, W.C.1 Phone: 01/837/7937

WW-053 FOR FURTHER INFORMATION

The world's most famous company in communication, the Nippon Electric Company Ltd., Tokyo, has developed the famous NED CQ radio amateur gears, being with regard to design, quality, reliability and price real pace-setters for today's communicators. First in history of amateur radio, such a big and famous company with more than 80 years of experience in construction of communication facilities, made its experience available to radio amateurs around the world.

The NEC, which has declared microwave space communication to its speciality, knows perfectly which attributes equipments must have for becoming bestsellers.

Today we present:

## NEC CQ 110 E DIGITAL,



allband, HF, 300 watt transceiver, 160 / 80 / 40 / 20 / 15 / 11 / 10A / 10B / 10C / 10D / WWV, modes FSK, USB, LSB, CW, AM, with separate 8 pole X-tal lattice filters for each mode fitted. Further features: Side tone at CW, VOX (automatic transmit-receive by talking into microphone), 11 meter CB band, all channels easily selectable through digital counter, excellent receiver sensitivity at extreme crossmodulation security by application for the 7360 low noise beam, deflection mixer tube.

This feature alone makes of the NEC CQ 110 E a top rider. Fixed channel communication on 22 channels is possible. A 60 page manual and a high quality dynamic microphone are supplied with the transceiver. Speaker, AC 100-235 volts and DC 13.5 volts power supplies are built in of course.

## NEC CQ 301



allband HF, 3KW, linear amplifier, 160/80/40/20/15/11/10 meter, for modern amateur communication. Two EIMAC 3-500 Z triodes, in zero bias grounded grid application guarantee long trouble free communication. The NEC CQ 301 can be driven by our CQ 110E or other excitors capable of about 50-100 watts of drive. AC power supply 100-235 volts is built in of course.


RETAILERS: Do not hesitate to accept our offer. Join us in selling these bestsellers!

Sole distributor in Europe:

**CEC** Corp., Via Valdani 1 - CH 6830 CHIASSO - SWITZERLAND  
Phone: (091) 44 26 51. Telex: 79959 CH

WW030 - FOR FURTHER DETAILS

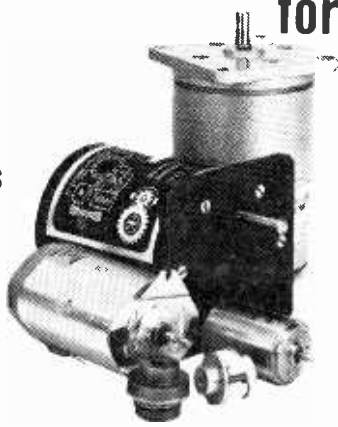servos  
synchronous  
steppers  
d.c. motors  
control systems  
gearboxes  
friction  
clutches  
instrument  
couplings



for a technical advisory service and  
off the shelf delivery, contact

**McLennan**

telephone 03446 5757/8

MOTOR STOCKISTS FOR:  
IMPEX, PORTESCAP  
PRINTED MOTORS



**McLENNAN SERVO SUPPLIES LTD.**  
KINGS ROAD, CROWTHORNE, BERKS.


WW-020 FOR FURTHER DETAILS

# VEROWIRE® GET THE CONNECTION

- A new and ideal wiring system for prototypes, Breadboards, and limited production.
- Achieves a permanent interconnection of components, at high speed, on a very high density.
- Based on the use of Verowire(R) wiring pen with unique spring wire clamp for wire retention, advancement and retraction.
- Moulded wiring combs fitted to board route the wire from point to point neatly holding and stabilising the wiring layout.
- By using a specially designed tool, I.C. legs are deformed and positively held in the board enabling the wire to be easily wrapped around them.
- Using a self-fluxing polyurethane coated wire, no pre-stripping is required. Connections are completed by soldering, melting the insulation and at the same time making a permanent soldered joint.
- A complete introductory Verowire kit is available consisting of a wiring pen, spools of wire, terminal pins and all tools necessary. A sample board from the Vero high density D.I.P. board range is also included in the introductory kit.
- Soldering iron now available from stock

Available world wide through  
3 subsidiary companies and  
25 agents.

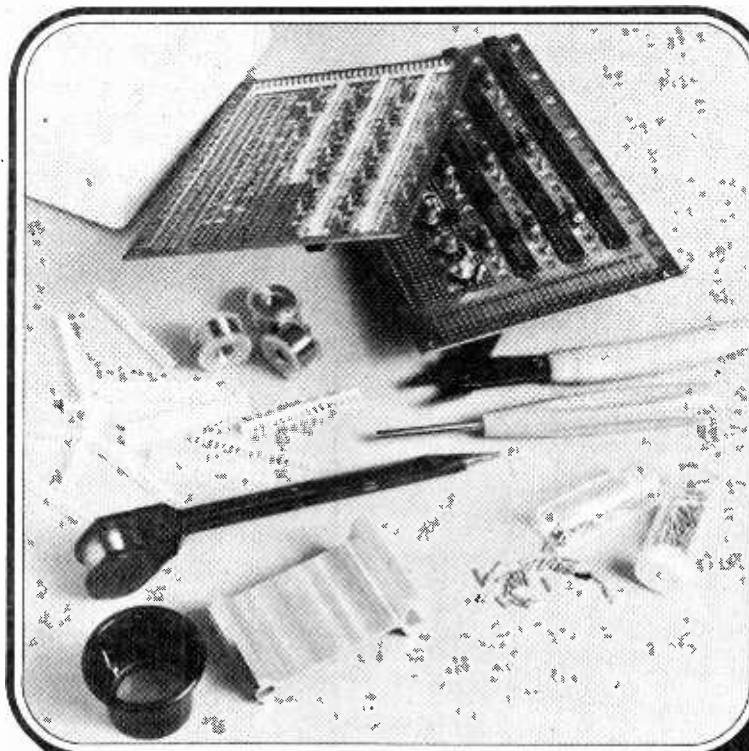Vero Electronics Ltd.  
Industrial Estate, Chandler's Ford,  
Eastleigh, Hampshire SO5 3ZR.  
Telephone: Chandler's Ford 2956  
Telex: 47551




**WORLD LEADERS IN PACKAGING TECHNOLOGY**

WW-077 FOR FURTHER DETAILS

**VERO**

**ANY MAKE-UP OR  
COPY QUERIES  
CONTACT  
JOHN GIBBON  
01-261 8353**

## ANTENNA DESIGN & PRODUCTION

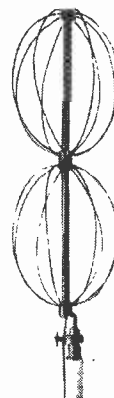

We are specialists in the  
design, development and  
production of all types of  
antennas and controls,  
including those to military  
specifications.


We invite your enquiries

**STRINGER CLARK ANTENNAS LTD.**  
CHILD OKEFORD • DORSET • DT11 8EH  
Telephone: 025886-8293

WW-040 FOR FURTHER DETAILS



the indispensable  
**BIRD43**

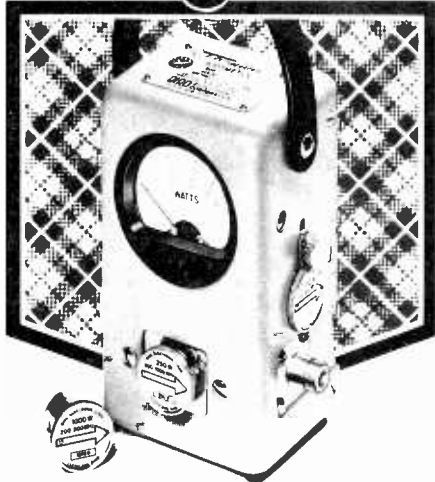

**THRULINE® WATTMETER**

0.45-2300 MHz / 0.1-10,000 watts

The Standard of the Industry  
What more need we say...

Exclusive UK representative

**aspen electronics limited**

2 KILDARE CLOSE, EASTCOTE, MIDDX. HA4 9UW  
TELEPHONE: 01-868 1188 — TELEX 8812727

WW—033 FOR FURTHER DETAILS

ELECTRONORGTECHNICA

**carbon film RESISTORS**

1/8 and 1/4w 70°C 5% tol. E.12

EX-STOCK

**£4.90 PER 1,000** PLUS V.A.T. & POSTAGE  
OF ONE VALUE

Minimum export order £100

Contact John Gingell



**AERO SERVICES LTD.**

44A Westbourne Grove  
London W2 5SF  
TEL 01-727 5641 TELEX 261306

WW — 059 FOR FURTHER DETAILS

*Crimson Elektrik*

**MINIMUM T.D. POWER AMPLIFIER MODULES**  
WE BELIEVE OUR MODULES ARE UNEQUALLED IN SOUND  
QUALITY, OVERALL PERFORMANCE & VALUE FOR MONEY

★ S/N > 110dB ★ 1.20 x 80 x 25mm ★ Fully prototyped ★ 250 mV/50kΩ ★ 1.2Hz - 35kHz - 3dB ★ 14 Trs 4D  
It has recently been shown that an amplifier with some traditionally desirable features (eg heavy feedback wide bandwidth) can actually sound worse than one with a poorer spec. This has been attributed to distortion caused by transients T.D. Carefully positioned compensation a rise time of 10µs settling time of 10µs ± 2µs and slewing rate of 6V/µs ensure minimum T.D. while T.H.D. is reduced to typically 0.1 - 0.4 max. at 1kHz by ultra-linear output triples, not by excessive feedback. This approach has yielded one of the cleanest sounding amplifiers available, regardless of cost.

- CE 608 180W rms/8v ± 15v £14.55
- CE 1004 100W rms/4v ± 15v £17.55
- CE 1008 100W rms/8v ± 15v £21.55

H/S kits 50p + 85p H/A kit 100p + 150p

Cheque / P.O. to: CRIMSON ELEKTRIK  
S.A.E. for full details: STATION ROAD  
Tel. (0) 533 386211 RATBY LEICESTER



CE 1008 - Domestic heatsink 150mm

WW—028 FOR FURTHER DETAILS

**ambit INTERNATIONAL** Trade Mark

The Wireless Specialists for components & modules.

EF5800, 7030 & 91196 - .9µV/30dB S/N., 0.2% THD  
Our top three FM tunermodules. (EF5800 shown with can off).



From left to right, the EF5800 6 circuit varicap FM tunerhead with the 7030 linear phase IF and the 91196 PLL stereo decoder with integral 55kHz 'birdy' filter. The system provides afc muting, meter drives, agc, auto stereo switch, & a specification that exceeds broadcast requirements. Now available with a new EF5801 tunerhead, with FET buffered oscillator output for synthesiser/frequency readout facilities.

EF5801...£17.45; EF5800...£14.00; 7030...£10.95; 91196...£12.99

Complete FM tuner kits/systems (Carriage £3 extra.)

*The Mark 8 Signalmaster - by Larsholt Electronics*

This tuner is based on the popular 7252 tuner set, and provides an incomparable combination of style and performance that can be built by even the relatively inexperienced constructor. Complete kit...£85.00; matching 25+25W amplifier...£79.00.

*International Mark 2 Tuner kits:*

Complete tuner kit, based around the 7253 tuner set, £65.00. Or just the chassis, cabinet, heavy aluminium front panel — for your own choice of modules - see our new info. leaflet on the International Tuner. (SAE please)

**NEW NEW NEW NEW NEW NEW NEW NEW**  
**BIONIC FERRET METAL LOCATOR**

Ambit has designed a new approach to cost effective sensitive metal locators, and now we proudly present the first of the family of 'Bionic Ferrets'. Details OA, but we can say it will detect a 10p piece at 8-10 inches. Coupled with low power consumption and many innovations, this is the first radically advanced detector that can be made from a kit. £37.99

Radio module selection: (Prices for kits in our catalogue & PL)

EF5800	Ambit 6 stage varicap 88-108MHz tunerhead	£14.00
EF5600	TOKO 5 stage varicap	£12.95
EC3302	TOKO 3 stage varicap	£7.50
7020	Dual ceramic filter FM IF system module	£6.95
92310	MPX decoder, with stereo filter and preamp	£6.95
93090	MPX decoder with CA3090AQ + filter stage	£7.35
91197	MW/LW varicap AM tuner module	£11.35
771	New 'Off-Air' UHF varicap TV sound tunermodule with mute, AFC, dual conversion, PSU	£27.00
9014	MW/LW/Stereo FM tuner chassis. Mech. tuned	£26.00

Components: ICs, coils, filters, trimmers, diode law pots etc.

HA1137W/3089E	FM IF	1.94	TOKO AM IFTs:	
TBA120	FM IF and demod	0.75	455/470kHz types	0.30
MC1350	FM IF preamp	0.97	10.7MHz types	0.33
SN76660N	FM IF and det.	0.75	(10mm square, with int. cap.)	
MC1310/4400	PLL MPX	2.20	455kHz Mechanical filters	
CA3090AQ	PLL MPX	3.75	4 or 7 kHz bandwidths	1.95
HA1196	PLL MPX	4.20	455kHz ceramic IF filters	
UA720	AM radio system	1.40	6 or 8 kHz bandwidth CFT 0.55	
TBA651	AM radio system	1.81	SFD455 (Murata)	0.75
HA1197	AM radio system	1.40	455kHz dual ceramic CFX	1.80
LM1496	balanced mixer	1.25	10.7MHz filters for WBFM:	
11C90	600MHz decade ctr	14.00	3132A 6 pole lin phase	2.25
LM380N	2 W Audio	1.00	3125N 4 pole lin phase	1.30
LM381N	audio preamp st.	1.81	CFS ceramic filters	0.50
TDA2020	20W audio amp	2.99	Pilot tone (MPX) filters:	
TCA940	10W audio amp	1.80	BLR3107N stereo	1.90
NE723	voltage reg IC	0.80*	BLR2007N	1.95
TDA1412	12v 600mA reg	0.95*	BLR3152/mono	0.97
78M20	20v 500mA	1.20*	BLR3172N tape bias trap, with TAA550B varicap regulator	0.50*
TAA550B	varicap regulator	0.50*	85 or 100kHz pole	0.97
NE560/1/2B	PLL ICs	3.50*	various chokes etc. see price list	
ICL8038CC	function gen	4.50*		

22turn 100k diode law trimpots, with integral knob 40p  
270° rotary 100k diode law tuning pot 32p  
Also...meters for tuners, AM tuning varicaps, MOSFETs etc....

post/packing 22p per order - except where indicated


General: All prices shown here exclude VAT, which is generally 12½%. (Except where marked\*). The latest price leaflet is available FOC with an SAE. Please send a (large) SAE with any enquiries. Full catalogue still 40p.

37 High Street, Brentwood, Essex. CM14 4RH.  
TELEPHONE (0277) 216029 - after 3pm if possible please.

WW—032 FOR FURTHER DETAILS
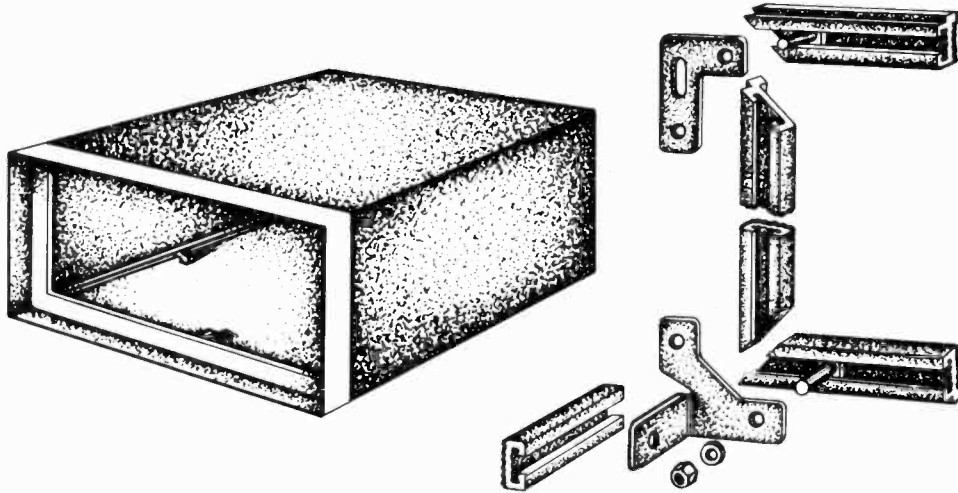
# when is a box not a box?

Instrument boxes are often sold in standard sizes — not always the most practical sizes for your needs. When bought they take up a lot of storage space.



WIDNEY DORLEC Series 3 is a new, simple constructional system for building cases, boxes, chassis, frames, drawers etc. etc. Just 3 basic extrusions and 3 simple brackets — available as components for DIY, kits,

or fully finished products to your design.


Custom made cases at prices you pay for standards. Ideal for Laboratories, Universities, small workshops. Call Cyril Vaughan on 021-359 3044 for more details.

Northern Stockist  
Widney Dorlec (Northern) Ltd.  
181a Bramhall Lane,  
Stockport.  
Telephone: 061-4801333.

## widney dorlec

P.O. Box 133,  
Birmingham B4 7BD.  
Telephone: 021-359 3044  
Telex: 338054.

WW—098 FOR FURTHER DETAILS

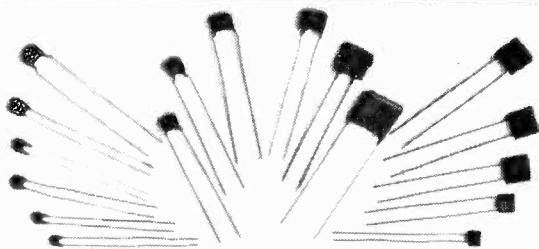

## WIDE RANGE OF MULTILAYER CERAMIC CAPACITORS

Erie Multilayer Ceramic Capacitors bring you

- ★ Longest experience among UK Manufacturers.
- ★ Total UK production from base ceramics to finished capacitor.
- ★ 12 chip sizes with choice of termination material. (incl. 4 discoidal)
- ★ 8 dipped sizes with choice of lead centres.
- ★ 5 moulded sizes, 3 radial lead, 2 axial leads.
- ★ Full BS9075 'N' specification approval on moulded radial types.

For full details of our extended range, write to


UK DISTRIBUTORS:  
ITT Electronic Services: 0279 26777  
Intel Electronics Ltd: 0462 812 505  
Compstock: 0268 27722

**ERIE ELECTRONICS LIMITED**  
Multilayer Ceramics Division  
South Denes, Great Yarmouth, Norfolk.  
Tel: 0493 56122 Telex: 97421

Components **ITT**

WW—046 FOR FURTHER DETAILS

# Take the strain off your cable

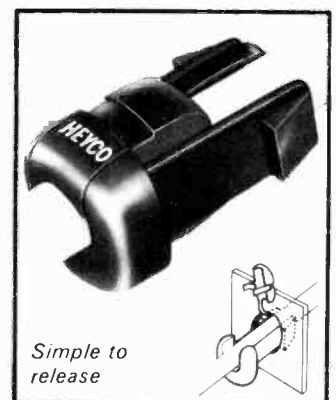

HEYCO NYLON STRAIN RELIEF BUSHINGS anchor and insulate cables passing through chassis. Lock to withstand 35lb push-back. Effects of 'push', 'pull' and 'twist' are absorbed.

HEYCO NYLON EXTENDED STRAIN RELIEF BUSHINGS do the same job as the standard strain reliefs but remain securely attached to the chassis during cable change.

### FREE SAMPLES

and catalogue showing our full range of bushings on request.



**Heyco Manufacturing Co. Ltd.**

Uddens Trading Estate,  
Nr. Wimborne, Dorset BH21 7NL  
Tel. Ferndown (STD: 0202) 871411/2/3  
Telegrams HEYCOMAN Wimborne Telex 41408

WW—072 FOR FURTHER DETAILS

# The greatest public show of home entertainment -at Olympia in September

That's the Audio Fair this year. It's moved with the market – as the emphasis changes, so does the Fair.

More people buy systems. More people look to home electronics for entertainment, as outside attractions become priced out of the market. More people want the package deal. So . . . not only audio and hi-fi, but also the whole spectrum of

**RADIO...TELEVISION...MUSIC...TV GAMES  
...RECORDS...TAPES...HOME RECORDING  
and MUSIC-MAKING**

More young people are among the buyers. More older people are getting into the new scene of sound. That's why the Audio Fair is a big family occasion, with the big family attractions.

Already the exhibitors include Agfa-Gevaert, Amstrad, Hitachi, National Panasonic, Natural Sound Systems, Rank, Sanyo – to name a few that indicate the width of appeal.

***There's a whole world of Home Entertainment  
at the Audio Festival and Fair this year.  
You ought to be there! It's Sound Sense!***

● **LONDON'S OLYMPIA** – the industry's favoured location, where the people and the money are . . . and the only venue with the size, scope and facilities for this great trade and public festival.

● **SEPTEMBER 12 to 18, 1977** – the preferred pre-Christmas selling-time period . . . and opening with a day and a half for the trade only.

● **BACKED** by major IPC specialist, trade and consumer publications, commanding a combined readership of 1,750,000.

● **ORGANISED** by the IPC Business Press specialist exhibition company, with a remarkable record and reputation for handling specialist fairs.

## THE COMPLETE HOME ENTERTAINMENT SHOW



To: Audio Fair,  
Iliffe Promotions Limited,  
Dorset House,  
Stamford Street,  
London SE1 9LU

*YES, I MUST find out more about the 1977  
International Audio Festival and Fair.  
Please send me an exhibitor's brochure  
right away.*

Name

Position in firm

Address

Products we want to exhibit





GEORG SIMON OHM

...The leaders through  
creativity

## GR 1657 Digibridge


Automatically measures R, L, C, D and Q. Ranging from  $0.001\Omega$  to  $99.999\text{ M}\Omega$ ,  $0.0001\text{ mH}$  to  $9999.9\text{ H}$ ,  $0.0001\text{ nF}$  to  $99999\mu\text{ F}$ . D from  $0001$  to  $9.999$  and Q from  $00.01$  to  $999.9$ . Basic accuracy  $0.2\%$ . Five digit display for R, L and C, four digit display for D and Q.

Microprocessor — directed ranging. Selectable test frequencies of  $1\text{ KHz}$  and  $100\text{ Hz}$  ( $120\text{Hz}$ ).

Series or parallel measurement selection. Built-in Kelvin test fixture tests radial and axial lead components. Other bridges from our range include:

<b>GR1650</b>	<b>GR1656</b>	<b>GR1608</b>	<b>GR1683</b>	<b>GR1685</b>
RLC Bridge	RLC Bridge	RLC Bridge	Digital RLC Bridge	Digital RLC Meter
Precision $1\%$	$0.1\%$	$0.05\%$	Automatic, $0.1\%$	Automatic, $0.1\%$

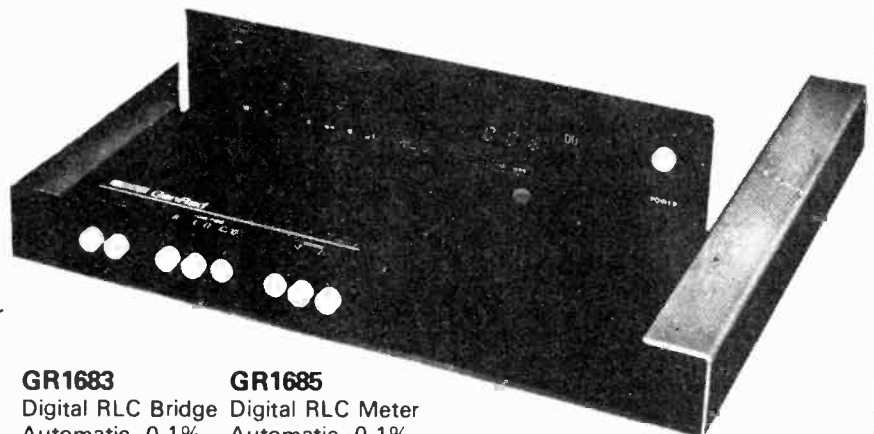It is easy to test components with GenRad. Write or call for descriptive literature to GenRad Ltd. Bourne End, Bucks SL8 5AT. (06285) 26611



# GenRad

# 15 — 240 Watts!

## HY5 Pre-amplifier

The HY5 is a mono hybrid amplifier ideally suited for all applications. All common input functions (mag Cartridge, tuner, etc.) are catered for internally, the desired function is achieved either by a multi-way switch or direct connection to the appropriate pins. The internal volume and tone circuits merely require connecting to external potentiometers (not included). The HY5 is compatible with all I.L.P. power amplifiers and power supplies. To ease construction and mounting a P.C. connector is supplied with each pre-amplifier.

**FEATURES:** Complete pre-amplifier in single pack — Multi-function equalization — Low noise — Low distortion — High overload — two simply combined for stereo

**APPLICATIONS:** Hi-Fi — Mixers — Disco — Guitar and Organ — Public address

**SPECIFICATIONS:**

**INPUTS:** Magnetic Pick-up 3mV Ceramic Pick-up 30mV Tuner 100mV Microphone 10mV Auxiliary 3-100mV, input impedance 47kΩ at 1kHz

**OUTPUTS:** Tape 100mV Main output 500mV R.M.S.


**ACTIVE TONE CONTROLS:** Treble ± 12dB at 10kHz Bass ± at 100Hz

**DISTORTION:** 0.1% at 1kHz Signal/Noise Ratio 68dB

**OVERLOAD:** 38dB on Magnetic Pick-up **SUPPLY VOLTAGE:** ± 16.5V

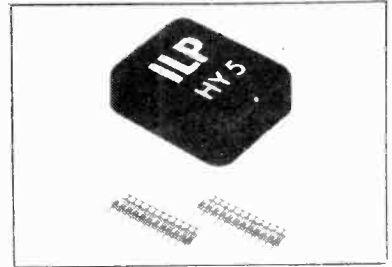**Price £5.22 + 65p VAT P&P free**

HY5 mounting board B1 48p + 6p VAT P&P free



## HY30 15 Watts into 8Ω

The HY30 is an exciting New kit from I.L.P. it features a virtually indestructible I.C. with short circuit and thermal protection. The kit consists of 1 I.C., heatsink, P.C. board, 4 resistors, 6 capacitors, mounting kit, together with easy to follow construction and operating instructions. This amplifier is ideally suited to the beginner in audio who wishes to use the most up-to-date technology available.

**FEATURES:** Complete kit — Low Distortion — Short Open and Thermal Protection — Easy to Build **APPLICATIONS:** Updating audio equipment — Guitar practice amplifier — Test amplifier — Audio oscillator


**SPECIFICATIONS:**

**OUTPUT POWER:** 15W R.M.S. into 8Ω **DISTORTION:** 0.1% at 15W

**INPUT SENSITIVITY:** 500mV **FREQUENCY RESPONSE:** 10Hz-16kHz — 3dB

**SUPPLY VOLTAGE:** ± 18V

**Price £5.22 + 65p VAT P&P free.**

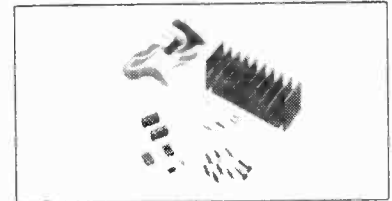

## HY50 25 Watts into 8Ω

The HY50 leads I.L.P.'s total integration approach to power amplifier design. The amplifier features an integral heatsink together with the simplicity of no external components. During the past three years the amplifier has been refined to the extent that it must be one of the most reliable and robust High Fidelity modules in the World.

**FEATURES:** Low Distortion — Integral Heatsink — Only five connections — 7 Amp output transistors — No external components

**APPLICATIONS:** Medium Power Hi-Fi systems — Low power disco — Guitar amplifier

**SPECIFICATIONS:** **INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 25W RMS into 8Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.04% at 25W at 1kHz

**SIGNAL/NOISE RATIO:** 75dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB

**SUPPLY VOLTAGE:** ± 25V **SIZE:** 105.50 x 25mm

**Price £6.82 + 85p VAT P&P free**



## HY120 60 Watts into 8Ω

The HY120 is the baby of I.L.P.'s new high power range designed to meet the most exacting requirements including load line and thermal protection, this amplifier sets a new standard in modular design.

**FEATURES:** Very low distortion — Integral Heatsink — Load line protection — Thermal protection — Five connections — No external components

**APPLICATIONS:** Hi-Fi — High quality disco — Public address — Monitor amplifier — Guitar and organ

**SPECIFICATIONS:**


**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 60W RMS into 8Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.04% at 60W at 1 kHz

**SIGNAL/NOISE RATIO:** 90dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** ± 35V

**Size:** 114 x 50 x 85mm

**Price £15.84 + £1.27 VAT P&P free.**

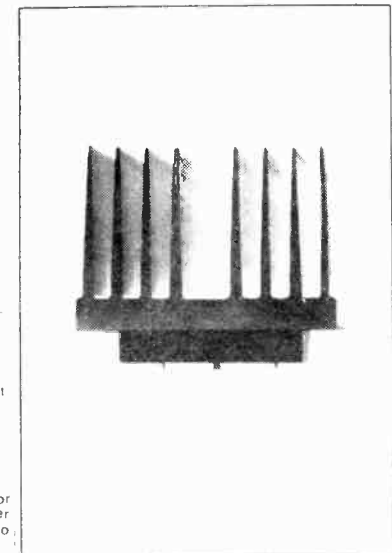

## HY200 120 Watts into 8Ω

The HY200 now improved to give an output of 120 Watts, has been designed to stand the most rugged conditions, such as disco or group while still retaining true Hi-Fi performance.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — Integral Heatsink — No external components

**APPLICATIONS:** Hi-Fi — Disco — Monitor — Power Slave — Industrial — Public address

**SPECIFICATIONS:**


**INPUT SENSITIVITY:** 500mV

**OUTPUT POWER:** 120W RMS into 8Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.05% at 100W at 1 kHz

**SIGNAL/NOISE RATIO:** 96dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** ± 45V

**Size:** 114 x 100 x 85mm

**Price £23.32 + £1.87 VAT P&P free.**

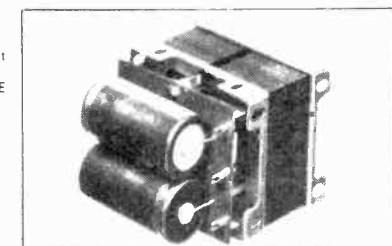

## HY400 240 Watts into 4Ω

The HY400 is I.L.P.'s 'Big Daddy' of the range producing 240W into 4Ω! It has been designed for high power disco or public address applications. If the amplifier is to be used at continuous high power levels a cooling fan is recommended. The amplifier includes all the qualities of the rest of the family to lead the market as a true high power hi-fidelity power module.

**FEATURES:** Thermal shutdown — Very low distortion — Load line protection — No external components

**APPLICATIONS:** Public address — Disco — Power slave — Industrial

**SPECIFICATIONS:**

**OUTPUT POWER:** 240W RMS into 4Ω **LOAD IMPEDANCE:** 4-16Ω **DISTORTION:** 0.1% at 240W at 1 kHz

**SIGNAL/NOISE RATIO:** 94dB **FREQUENCY RESPONSE:** 10Hz-45kHz — 3dB **SUPPLY VOLTAGE:** ± 45V

**INPUT SENSITIVITY:** 500mV **SIZE:** 114 x 100 x 85mm

**Price £32.17 + £2.57 VAT P&P free.**

### POWER SUPPLIES

PSU36 suitable for two HY30's **£5.22** plus 65p VAT P.P. free  
 PSU50 suitable for two HY50's **£6.82** plus 85p VAT P.P. free  
 PSU 70 suitable for 2 HY 120's **£13.75** plus £1.10 VAT P.P. free  
 PSU90 suitable for one HY200 **£12.65** plus £1.01 VAT P.P. free  
 PSU180 suitable for two HY200's or one HY400 **£23.10** plus £1.85 VAT P.P. free  
 18p plus tip VAT


TWO YEARS' GUARANTEE ON ALL OF OUR PRODUCTS

I.L.P. Electronics Ltd  
 Crossland House  
 Nackington, Canterbury  
 Kent CT4 7AD  
 Tel (0227) 63218

Please Supply \_\_\_\_\_  
 Total Purchase Price \_\_\_\_\_  
 I Enclose Cheque  Postal Orders  Money Order   
 Please debit my Access account  Barclaycard account   
 Account number \_\_\_\_\_  
 Name & Address \_\_\_\_\_  
 Signature \_\_\_\_\_



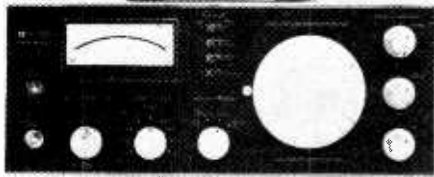**AUDIO LABORATORY INSTRUMENTS**  
for the professional



**LD03 Low Distortion oscillator**  
A continuously variable-frequency laboratory oscillator with a range 10Hz - 100kHz having virtually zero distortion over the audio frequency band with a fast setting time

**LDO3.B Low Distortion Oscillator, balanced output**  
A LDO3 but fitted with an output amplifier and screened balanced transformer providing a 600 ohm floating/balanced output, and 150 ohms unbalanced output

**DMS3 Distortion Measuring Set (illustrated)**  
Measures total harmonic distortion down to 0.001% speedily and accurately Direct reading from calibrated meter

**HSV1 High Sensitivity Voltmeter**  
As HSV1 but true r.m.s. reading.


**ANMI Audio Noisemeter**  
An accurate voltmeter and noisemeter with 16 ranges 10µV-300V f.s.d. Fitted weighting characteristics Wide band, DIN Audio Bank, IEC/DIN Curve 'A' and CCIR Average responding

**ANM2 Audio Noisemeter**  
As ANMI but true r.m.s. reading

**ANFI Audio Noisefilter**  
An active filter to CCIR weighting characteristic for use with external voltmeter (Ref Dolby Laboratories Inc., Bulletin No. 43, Mar 76)

Also in stock: All Radford Speaker drive units and crossovers and B & N/Radford monitor loud speaker systems

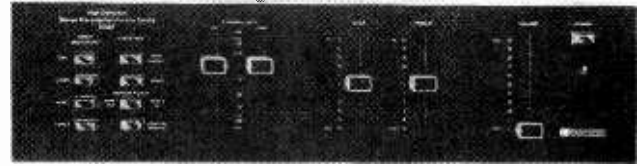**HIGH PERFORMANCE AMPLIFIERS**  
for the enthusiast and professional



**ZD22 Stereo Pre-amplifier Control Unit**  
A stereo pre-amplifier of virtually zero distortion Inputs for disc tuner and two tape machines providing comprehensive recording and reproducing facilities Sensitivities Disc 1mV, and Auxiliaries 50mV, for IV output Exceptional signal/noise ratio Output at clip level 18V r.m.s.

**ZD100 Power Amplifier**  
A stereo power amplifier of all aluminium construction with high thermal mass and designed for continuous operation at high output level Provides 150 watts per channel into 4 ohms and 90 watts per channel into 8 ohms at virtually zero distortion

**HD250 Stereo Integrated Amplifier**  
Uses ZD22 pre-amplifier with a power amplifier having a power output in excess of 50W per channel into 4-8 ohms Distortion less than 0.02% at rated power, typically less than 0.01% True complementary symmetry output Headphone output Inputs Disc tuner, and two tape machines

ZD22, ZD100, HD250 are available from stock  
Available soon ZD50 (110 w.p.c / 4 ohms, 70 w.p.c / 8 ohms) and ZD200 (250 w.p.c / 4 ohms, 150 w.p.c / 8 ohms)

Your Radford Dealer

**SWIFT OF WILMSLOW 5 SWAN STREET, WILMSLOW, CHESHIRE (TEL: 26213)**

Mail order and Personal Export enquiries —Wilmslow Audio Swan Works, Bank Square, Wilmslow (Tel 29599)

WW — 063 FOR FURTHER DETAILS

**FREQUENCY COUNTERS**

1/10 Hz to 1.2GHz

High performance instruments measuring frequency, period, time, freq./ratio and calibrated output facility. Fast delivery. Specials by arrangement.



TYPE 801B

CRYSTAL OVEN  
OPERATING MANUAL  
TWO TONE BLUE CASE

£274 250 MHz

Sensitivity 10mV. Stability 5 parts 10<sup>-10</sup>  
Resolution ± 1 Count

301M	32MHz 5 Digit £95	401A	32MHz 6 Digit £132
501	32MHz 8 Digit £188	701A	80MHz 8 Digit £205
801B/M	250MHz 8 Digit £274	901M	520MHz 8 Digit £375
		1001M	1.2GHz 8 Digit £670

Start/Stop versions plus £12 Memory versions available if not suffixed M £25 extra

Type 101 1MHz 100KHz 10 KHz Crystal Standard £95  
Type 103 Off/Air Standard £95

SUPPLIERS TO: Ministry of Defence, G.P.O., B.B.C., Government Depts., Crystal Manufacturers and Electronic Laboratories world-wide

**RCS** **R.C.S. ELECTRONICS**  
6 WOLSEY ROAD, ASHFORD  
MIDDX. TW15 2RB  
Telephone: Ashford (Code 69)  
53661/2

WW—049 FOR FURTHER DETAILS


**DATA AND COMMUNICATIONS TERMINALS**

Teletype 28, 32, 33, 35; 40  
TermiNet 30, 300 & 1200 (30 and 120 cps)  
Teleterm: 1132 and 1200 series (portable/fixed 30 cps)  
with integral coupler and RS 232C)  
Other page printers (by Siemens, ITT Creed, etc.)

- ★ Spares, repairs, overhauls and maintenance
- ★ Other types and models available
- ★ Refurbished units also available
- ★ Short and long period rentals
- ★ Minicomputer interfaces
- ★ Quantity discounts
- ★ Immediate delivery

**TELEPRINTER EQUIPMENT LTD.**  
70-80 AKEMAN STREET  
TRING, HERTS., U.K.

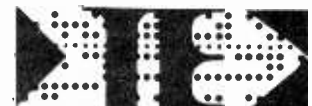Telephone 0442-82-4011  
Cables RAHNO Tring  
Telex 82362  
A/B Batelcom Tring



WW—014 FOR FURTHER DETAILS

# Blob Board Offer 30% off


Circuit diagram to circuit board in minutes. Layout circuit plan .1" graph paper. Select Blob Board, lay components out with leads on copper strip. Blob of solder onto lead and your circuit is complete. Blob Boards normally half price of competitive boards. Roller tinned to solder components directly. No drilling or mounting. Modifications in seconds. Blob Board is re-usable.

**I.C. PACK**

Comprises one of each:  
 ZB1C (for one 16-pin I.C. pad, approx. area 4.5 x 3in.)  
 ZB2C (for two 16-pin I.C. pads, approx. area 4.75 x 3.25in.)  
 ZB81C (for eight 16-pin I.C. pads, approx. area 9.5 x 7.5in.)  
 Regular Price: £2.66  
**OFFER PRICE: £1.79 inc**

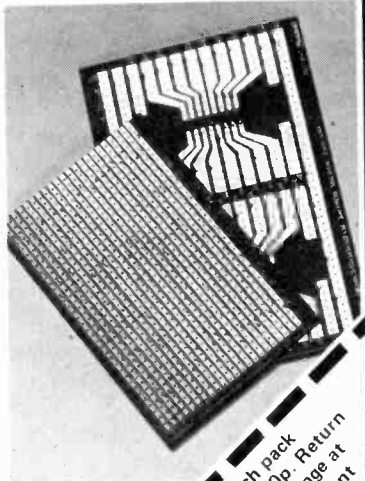**DISCRETE PACK**

Comprises one of each:  
 ZV1V (approx. area 2.5 x 5in.)  
 ZB5D (approx. area 3.6 x 2.4in.)  
 SB8D (approx. area 9 x 7.5in.)  
 Regular Price: £2.29  
**OFFER PRICE: £1.64 inc**



Free with each pack one ZB1V worth 30p. Return with order or exchange at your local component stockist. **30p.**



PB Electronics (Scotland) Ltd.  
 57, High Street, Saffron Walden,  
 Essex. CB10 1AA

WW-069 FOR FURTHER DETAILS

**QUARTZ  
 CRYSTALS  
 - FAST!**




AEL CRYSTALS LIMITED  
 Gatwick House, Horley, Surrey, England RH6 9SU  
 Telephone: Horley (02934) 5353 Telex: 87116 (Aerocon Horley)  
 Cables: Aerocon Telex Horley

WW-034 FOR FURTHER DETAILS
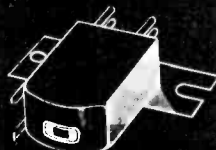
## TAPE HEADS

FIT A BRAND NEW HEAD AND TRANSFORM THE QUALITY OF YOUR TAPE PLAYER AN EXTENSIVE RANGE ALWAYS IN STOCK ASK FOR OUR SHORT FORM CATALOGUE



SPECIAL!

STANDARD HEADS TO FIT MOST TAPE PLAYERS AT BULK DISCOUNT PRICES. ENCLOSE 15p P & P WITH ORDER

MONO CASSETTE 90p  
 STEREO CASSETTE £2.00  
 STEREO 8 CARTRIDGES £1.00  
 M/S CASSETTE ERASE 60p

**MONOLITH**  
 THE MONOLITH ELECTRONICS CO. LTD.

Tel. Crewkerne 4321


5/7 Church Street, Crewkerne, Somerset, England.

WW-041 FOR FURTHER DETAILS
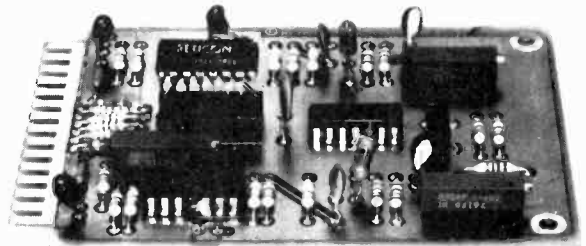
# This is an echo chamber?



Yes, and much more! It is the first N-channel Bucket Brigade Device designed with the audio engineer in mind. The SAD-1024 Serial Analog Delay will provide reverberation, echo, tremolo, vibrato and chorus effects in electronic organs and musical instruments. It will equalise speaker systems in an auditorium, or can be used in speech compression or voice scrambling systems. The SAD-1024, which contains two independent sections of 512 analog storage elements will accomplish all of these with a signal-to-noise ratio in excess of 75dB. The two sections may be used independently or they may be connected in sequence to provide 1024 clock periods of delay. The delay provided by the device can be continuously varied by the clock rate from less than one millisecond to more than one second. Other performance characteristics include: signal bandwidth from 0 to 200 KHz, less than 1% total harmonic distortion, 0dB insertion loss, and less than 5mW power requirements from a single 15V power supply. You get all these features for less than 1p per storage element in OEM quantities. We also offer an optional complete circuit card to help you evaluate this exciting new device. Other devices for applications such as time base correction in the video bandwidth are also available.



# RETICON®

The SAD-1024 and circuit card is available immediately from Reticon's sole UK distributors, Herbert Controls and Instruments Limited, Spring Road, Letchworth, Herts SG6 4AJ. Telephone: 04626-3841. Telex: 825535.

WW - 095 FOR FURTHER DETAILS



# MORE POWER— MORE TORQUE

with the

## •NEW MK. II DRILL•

**SPEED**  
10,000 r.p.m.

**TORQUE**  
120 cmg


**VOLTAGE**  
9-14v d.c.

**DRILL ONLY £8.79**  
(p&p 35p)

**STAND £4.40**  
(p&p 35p)  
Inc. VAT

(Together 50p p&p)

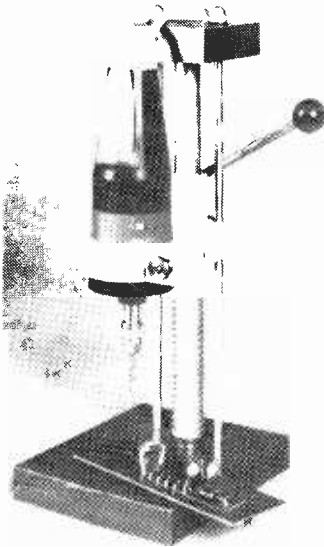Send a 9" x 4"  
SAE for illustrated  
leaflet and order form  
to:



## PRECISION PETITE LTD.

119A HIGH STREET, TEDDINGTON, MIDDX.

TEL. 01-977 0878  
(24-hour answering service)

# Switching problems? Rely on Zettler.

Producing 30 basic types of relay and 15,000 variants with regard to contact stacks, terminals, energizing current and contact material, Zettler is among the largest manufacturers of electro-mechanical components.

Our product range comprises:  
Low profile (platform) · Timing · Miniature · Low contact capacity · Hermetically sealed · Stepping · Mains switching · Latching · Contact stacks · Solenoids



### Miniature Extra Heavy Duty Relay AZ 230

Capable of Switching High Power in spite of small physical size.  
Contact: 1 Changeover.  
Contact Material: Silver Cadmium Oxide.  
Rating: 3.5 kVA, 16 A, 250 V AC max.  
Dielectric Strength: 2.5 kV rms.  
Coils: 5 V DC - 110 V DC.  
Size: 35.5 x 19 x 30.2 mm.  
Printed Circuit Mounting.

We resolve your switching problems rapidly and expertly. Please contact us for further details.



**ZETTLER** Zettler UK Division  
Brember Road

Harrow, Middx. HA2 8AS Tel. (01) 422 0061

A member of the worldwide ZETTLER electrical engineering group, est 1877

WW-048 FOR FURTHER DETAILS



## Audio Connectors

Broadcast pattern jackfields, jackcords, plugs and jacks.

Quick disconnect microphone connectors  
Amphenol (Tuchel) miniature connectors with coupling nut.

Hirschmann Banana plugs and test probes  
XLR compatible in-line attenuators, and reversers.


Low cost slider faders by Ruf.



**Future Film Developments Ltd.**  
90 Wardour Street  
London W1V 3LE  
01-437 1892/3

WW-026 FOR FURTHER DETAILS

## 8 DECADE RESISTANCE BOX

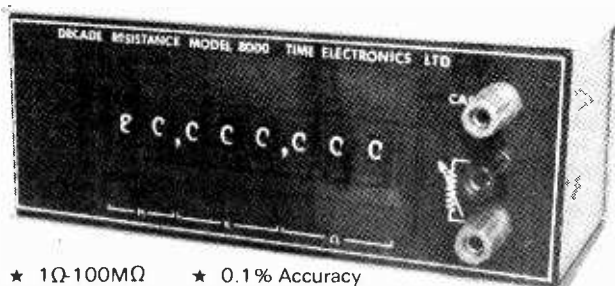

- ★ 1Ω-100MΩ      ★ 0.1% Accuracy
- ★ Colour coded digits, Ω yellow, KΩ white, MΩ red

**TIME ELECTRONICS LTD.**  
Botany Industrial Estate Tonbridge, Kent  
Tel. Tonbridge (0732) 355993

WW-015 FOR FURTHER DETAILS

# PROFESSIONAL POWER AMPLIFIER MODULES



FEATURES :  
SHORT & OPEN CIRCUIT, IMPEDANCE  
OVERLOAD, MISMATCH AND THERMAL  
PROTECTION. ONLY 5 EXTERNAL  
CONNECTIONS REQUIRED.  
FULL 2 YEAR GUARANTEE.

## •NEW•100w MODEL

	JPS 80 price (£18.75)	JPS 100 price (£23.50)	JPS 150 price (£29.85)
Power Output	70watts RMS 7.5 ohms	110 watts RMS 7.5 ohms	170 watts RMS 7.5ohms
Frequ. Response	10-30 kHz - 0.5dB	10-30 kHz - 0.5dB	10-30 kHz - 0.5dB
Slewing Rate	7.3V per microsec.	8V per microsec.	8.4V per microsec
T.H.D.	0.05% @ 1kHz	0.05% @ 1kHz	0.05% @ 1kHz
Damping Factor	200	400	400
Hum & Noise	115dB below 70 watts	115dB below 110 watts	115 dB below 170 watts
Input Sensitivity	0dB(0.775V) 70 watts	0dB(0.775V) 110 watts	0dB(0.775V) 170 watts
Input Impedance	47k	47k	47k
Power Requirement	± 35Volts	± 45Volts	± 55 Volts
Overall Dimens.	5.8" Long x 3" Wide x 1" High.	5.8" Long x 3" Wide x 1" High	4.8" Long x 3" Wide x 1" High Heat Sink 8" x 5" x 1"

For industrial usage the frequency response of the amplifiers can be extended down to DC + 0dB-0.2dB Input Impedance & Sensitivity can be modified to suit particular requirements.

### POWER SUPPLIES

PS60 powers 1 JPS60 price £12.30  
PS100 powers 1 JPS 100 price £14.10 PS100/2 powers 2 JPS100 price £18.65  
PS150 powers 1 JPS 150 price £17.48 PS150/2 powers 2 JPS150 price £23.43  
All Prices Are Subject To 8% VAT

**BELMONT HOUSE - STEELE ROAD**  
PARK ROYAL - LONDON NW10 7AR  
TELEPHONE 01-961 1274



WW - 092 FOR FURTHER DETAILS

**we've got  
microprocessors  
covered**

Microprocessor technology is making a tremendous impact on the electronics industry. Since its birth in 1971, it has revolutionized the microprocessor market. All over the world, electronics design engineers are faced with the challenge of determining how microprocessors can be used most effectively.

- Scope of *MICROPROCESSORS*:
- hardware design and development
  - architecture and system design
  - languages, software code and microprogramming
  - applications
  - education
  - standards, interfaces and markets

*MICROPROCESSORS* will be published quarterly from September 1976.

Annual subscription price (first issue) £20.00 in the UK and £26.00 (\$67.60) overseas.

Advertisement rates	1 insertion	4 insertions
Whole page (255 x 177mm)	£200	£150
Half page	£125	£100
Quarter page	£75	£60

**the new international quarterly journal covering all aspects—hardware, software and applications—of this new technology**

# microprocessors is the success story of 1977

*MICROPROCESSORS* was launched as a quarterly journal in September 1976 to meet the challenge posed by the enormous growth of microprocessor applications in the electronics industry

the response was tremendous, and as this growth continued into 1977 *MICROPROCESSORS* is expanding — from February 1977 it is published alternate months

in fact, the only thing about *MICROPROCESSORS* that is not expanding is the price — an annual subscription (six issues now) still costs £20.00 in the UK and £26.00 (\$67.60) overseas

<b>Advertisement rates</b>	1 insertion	4 insertions
Whole page (255 x 177mm)	£200	£150
Half page	£125	£100
Quarter page	£75	£60

For further details, contact:  
John A. Godley  
Advertisement Manager  
*MICROPROCESSORS*, Dorset House, Stamford Street, London SE1 9LU  
Telephone: 01-261 8359/8503  
Telegrams/Telex: Microsors, Bisnespres London 25137

**microprocessors keeps pace with the technical developments. Devoted solely to the hardware, software and applications of microprocessors and microcomputers, it is international in outlook and readership**

To: IPC Science and Technology Press Limited, IPC House, 32 High Street, Guildford, Surrey, England GU1 3EW  
Telephone: 0483-71661 Telex: Scitec Gd 859556  
Please send me further details about *MICROPROCESSORS* and a subscription order form

Name \_\_\_\_\_  
Organisation and address \_\_\_\_\_  
Signature \_\_\_\_\_ Date \_\_\_\_\_

MWW1

**PROJECT 80 AUDIO MODULES**  
P25 £4.95. Z40 £5.75  
Project 8050 £18.95

**BI-PAK AUDIO MODULES**  
S450 tuner £20.95. AL60 £4.60.  
PA100 £14.95. MK60 Audio Kit  
£31.95. Teak 60 £12.95. Stereo 30  
£16.95. SPM80 £3.95. BMT80 £3.62.  
PS12 £1.75. T538 £3.15. Send sae for  
free data

**SAXON ENTERTAINMENTS  
MODULES**  
SA1208 £20.50. SA1204 £14. SA608  
£13. PM1201/8 £12. PM1202/8 £19.  
PM1201/4 £12. PM1202/4 £19.  
PM601/8 £12.

**JC40 AMPLIFIER**  
New integrated circuit 20W amplifier  
chip with pcb and data £4.45.

**FERRANTI ZN414**  
IC radio chip £1.44. Extra parts and pcb  
for radio £3.85. Case £1. Send sae for  
free leaflet

**BATTERY ELIMINATORS  
MILLENNIA KITS**  
5 Transistor highly stabilized power units.  
Switched 1 to 30V in 0.1V steps. Send  
sae for free leaflet 1 Amp kit £12.45. 2  
Amp kit £14.95. Cases £2.95.

**RADIO MODELS**  
50mA with press-stud battery connectors.  
9V £3.75. 6V £3.75. 4½V £3.75.  
9V+9V £5.45. 6V+6V £5.45.  
4½V+4½V £5.45.

**CASSETTE MAINS UNITS**  
7½V with 5 pin DIN plug 150mA  
£3.95.

**3-WAY MODELS**  
Switched output and 4-way multi-jack  
Type 1 3/4½/6V at 100mA £3.20.  
Type 2 6/7½/9V at 150mA £3.30.  
**FULLY STABILIZED MODEL £6.45**  
Switched 3/6/7½/9V 400mA Stabi-  
lized.

**CAR CONVERTORS**  
Input 12V DC. Output 6/7½/9V DC 1  
Amp Transistor stabilized £5.10.

**PRINTED CIRCUIT KIT**  
Make your own printed circuits. Contains  
etching dish, 100 sq ins of copper clad  
board, 1lb ferric chloride, etch resist pen,  
drill bit and laminate cutter £4.25.

**SINCLAIR CALCULATORS,  
WATCHES AND POCKET TV**  
New Sinclair Pocket TV £165. Cam-  
bridge Scientific £8.95. Oxford Scientific  
£13.30. Mains units £3.20. Grey watch  
+ bracelet £16.45. White watch  
£13.95.

**SINCLAIR IC20**  
IC20 10W+10W stereo amp kit with  
printed circuit £4.95. PZ20 Power supply  
for above £3.95. VP20 Control and  
preamp kit £8.55.

**JC12 AMPLIFIER**  
6W IC audio amp with free data and  
printed circuit £2.25.

**DELUXE KIT FOR JC12**  
Volume and tone controls and extra parts  
for the pcb Mono £2.39. Stereo £5.25.

**JC12 POWER KIT**  
Supplies 25V 1Amp £3.95.

**JC12 PREAMP KITS**  
Type 1 for magnetic pickups, mics and  
tuners Mono £1.50. Stereo £3.00. Type  
2 for ceramic or crystal pickups Mono  
88p. Stereo £1.76.  
SEND SAE FOR FREE LEAFLET

**S-DECS AND T-DECS**  
S-DeC £2.24  
T-DeC £4.05  
u-DeCA £4.45  
u-DeCB £7.85  
16 dif IC carriers  
with sockets £2.05

**BATTERY ELIMINATOR KITS**  
100mA radio types with press-stud  
battery terminals. 4½V £2.10. 6V £2.10.  
9V £2.10. 4½V+4½V £2.80. 6V+6V  
£2.80. 9V+9V £2.80.  
100mA cassette type: 7½V din plug  
£2.10.  
**Stabilized 8-way types:** transistor  
stabilized to give low hum 3 / 4½ / 6 /  
7½ / 9 / 12 / 15 / 18V 100mA model  
£3.50. 1 Amp model £6.50.  
**Heavy duty 13-way types:** 4½ / 6 / 7 /  
8½ / 11 / 13 / 14 / 17 / 21 / 25 / 28 /  
34 / 42V 1A £4.95. 2A £7.95.  
**Car converter kit:** Input 12V DC. Output  
6 / 7½ / 9V DC 1A regulated £1.95.

**SWANLEY ELECTRONICS**  
DEPT. WW, PO BOX 68, 32 GOLDSSEL ROAD, SWANLEY, KENT BR8 8TQ  
Mail order only. No callers. Post 30p on orders under £2.23, otherwise free. Prices include  
VAT. Official orders welcome. Overseas customers deduct VAT


# click

**Light on the scene.**  
Local lighting just where you want it with Click's elegant, adjustable Spotlight or snake-arm Reading Lamp.

**Tidy wires.**  
With Click you can hide all your leads and wires inside the uprights, with a neat, snap-in cover strip.

**Keeping it steady.**  
With shelves fixed firmly to the wall, you eliminate floor vibration problems.

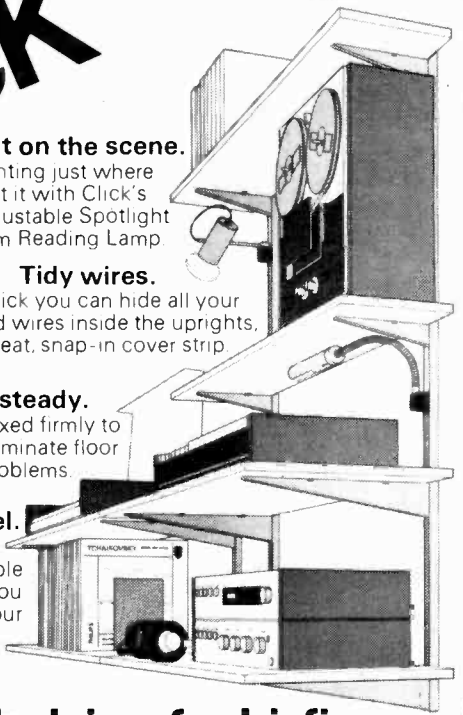**Finding a level.**  
Click brackets are infinitely adjustable for height so you can always get your shelves level.



**Shelving for hi-fi.**  
**We've solved the problems.**

**FREE** Post this ad. with your name and address for a 10-page leaflet to **Click Shelving Ltd.**  
Lowmoor Rd, Kirkby in Ashfield, Notts, NG17 7LH

WW-029 FOR FURTHER DETAILS

## WHAT IS IT?



IT'S —  
**A QUARTZ DIGITAL CLOCK**  
Hrs. Mins. AM/PM Day, Date  
**AN ALARM CLOCK**  
4 Alarm Memories  
**A STOPWATCH**  
To 9 hrs. 59 mins. 59.9 secs.  
**A CALCULATOR**  
Time and Date calculations  
ANOTHER WORLD FIRST FROM CASIO

**THE CQ-1**  
ONLY 1" x 2½" x 5½". ONLY 5.2 OUNCES  
ONLY £29.95 (R.R.P. £35.95)

**NEW** 1977 Casio Casiotron Watches  
8 functions and backlight  
Stopwatch. Dual time zones

Arguably the best watches in the world — at any price. Certainly the most versatile.

**R188** (R.R.P. £75.95) £58.50  
**S168** (R.R.P. £89.95) £68.50  
**S158** (R.R.P. £99.95) £78.50  
(Illustrated)  
Other CASIOTRON watches from £38.50



**NEW** Fairchild Timeband L.C.Ds.  
Battery Hatch for Self-change  
Free Replacement Battery  
Lower prices — Higher quality

5+4 functions. Round watch on strap  
**TC411**, Chrome £25.95. **TC410**, Gold £28.95.  
5+4 functions. Illustrated  
**TC413**, Chrome £31.00. **TC412**, Gold £33.95.

**NEW. TIMEBAND DIGITAL ALARM CLOCK** with snooze button £14.95  
Send 10p for our ILLUSTRATED CATALOGUE. Probably the WIDEST RANGE of the BEST watches at the LOWEST prices. Accurist, Ibico, National Semiconductor, Optim, SEIKO Texas, etc. Also LADIES' Watches.

**TEMPUS**  
Dept. W.W.  
19-21 Fitzroy Street  
Cambridge CB1 1EH  
Telephone: 0223 312866

## AMPLIFIER MODULES

25-100 W rms


### FROM TAMBA ELECTRONICS

LOW COST QUALITY POWER AMPLIFIER MODULES,  
POWER SUPPLIES & MIXERS FOR HI-FI, DISCO, P.A.  
GROUP & CLUB APPLICATIONS

**TAM1000** 100 watts rms into 4 ohms, 65v supply £9.80

**TAM500** 50 watts rms into 4 ohms, 45v supply £7.50

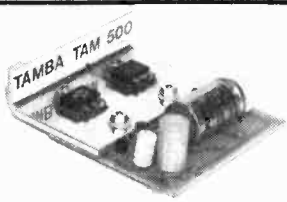**TAM250** 25 watts rms into 8 ohms, 45v supply £4.75



20-20,000HZ ± 1dB  
 SILICON CIRCUITRY THROUGHOUT  
 High sensitivity (100mV 40K)  
 Low distortion (typically 0-1%)  
 Low profile (1in. high x 3½ x 3in.)  
 Four simple connections  
 Glass fibre P.C.B.

High grade components used throughout e.g. Texas, Mullard, R.C.A., Plessey, etc.

**POWER SUPPLIES:**  
For one TAM 1000 £9.80  
For one or two TAM 250/500 £7.50  
(Carr. 50p on supplies)

**MODULAR MIXER PRE-AMP £6.50**

60 mm slider volume  
 Full range bass & treble controls  
 Built-in supply smoothing  
 Operates from main supply

Modular style anodised aluminium fascia  
 High & medium sensitivity inputs  
 Form up to 10 channel systems  
 Accepts a wide variety of inputs


**ADD 8% VAT TO ALL PRICES**  
except TAM 250 & Mixer Modules (12½%)

Access & Barclaycard accepted  
Write or telephone (01) 684 0098.  
Callers welcome COD 60p extra

## TAMBA ELECTRONICS

Bensham Manor, Road Passage, Bensham Manor Road, Thornton Heath, Surrey.

## FROM E.S.E.

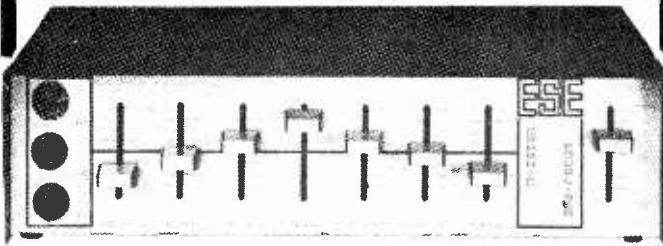

A full frequency range graphic equaliser **YOU** can afford !!

**For JUST £38.85 plus VAT**

You can tune out all unwanted noises at **seven** different frequencies!

Bring all your recordings, P.A. discos, lead guitar, bass guitar, organ, **anything** amplified to life at the touch of a slider !!

No more annoying amplifier noises — just clear, true sound! Frequencies from 60 Hz to 10 kHz! Cut or boost each frequency by maximum of 15 dB!

Hi and lo gain inputs.

Powered by just two PP3 batteries which last for ages. Or mains powered unit available. £49.95 plus VAT

Try it and you'll buy it — it will change your concept of sound. Trade enquiries welcomed.

**Condensed Technical Spec**

Max. output: terminated to 600Ω, -10 dB > 1.6 volts peak to peak, 2.5 volts R.M.S.

Signal to noise ratio: input terminated with 47K resistor. All filters at max. better than -70 dB.

Frequency response: All filters at central better than ± 2 dB.

Filter slope: Better than ± 13 dB per octave.

Filter ranges: Max. ± 15 dB at 60, 180, 480 Hz. 1, 2, 4, 5 and 10 kHz.

To: E.S. Electronics, 2 Upper Fant Road, Maidstone, Kent. Please send me  1,  2,  3,  4,  5 of your Graphic Equalisers. I enclose cheque or postal order for £ having added £1.50 for p. & p. on each item ordered and V.A.T. I understand that two batteries are included.

Name .....

Address .....

Tel. ....

WW—027 FOR FURTHER DETAILS

# CATRONICS WW TELETEXT DECODER

Our kit contains all the printed circuit boards and components necessary to build the complete decoder. The power supply and video switching circuitry are normally installed within the television cabinet and the main decoding control and memory circuitry in a separate cabinet positioned on top of the television.

**PRICES (INCLUDING VAT) ARE AS FOLLOWS:**

	Standard version using 2513	New version with Texas X887	Post & Packing
Set of 5 PCBs	£20 70	£20 65	30p
Component Kit (incl. PCBs)	£120 95	£133 70	£1 00
Add-on Unit for lower case	—	—	—
PCB only	£2 70	—	—
Component Kit (incl. PCBs)	£13 75	—	—
Cabinet	£14 85	£14 85	75p

PLATED THROUGH hole PCBs are available for TEXAS version only at additional cost of £27 00

A reprint of the series of articles is available at £1 50+ large 14p SAE (included free in complete kit)

**COMPONENTS ALSO AVAILABLE SEPARATELY — SAE for price list.**  
**READY BUILT & TESTED DECODERS also available at £241.87 + £3 Carr.**

## MOBILE AERIALS

**BIG ECONOMY NEWS!**

A 'must' for all users of Commercial Radio

Catronics stock a wide range of whip type aerials and a variety of bases, including types that **do not require a fixing hole in the car.** We can, therefore, supply virtually ANY frequency aerial for mounting on ANY car! These aerials are particularly suitable for MINICabs, Breakdown Trucks and other RADIO-CONTROLLED service vehicles.

The range of frequencies extends from 50MHz to 476 MHz  
**ALL AT THE MOST COMPETITIVE PRICES**

Write for illustrated leaflet **CATRONICS LTD (Dept 724)**

# Catronics

Communications House,  
20 Wallington Square,  
Wallington, Surrey

WW—724 FOR FURTHER DETAILS

The All-Electronics Show,  
Grosvenor House, Park Lane, London, W.1.  
19th - 21st April.

# We're name dropping!

- |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                          |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                 |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                             |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| <p>Advance Micro Devices<br/>AMP of Great Britain Ltd<br/>Arcolelectric Switches Ltd<br/>Avdel Ltd<br/>Avo Ltd<br/>Belix Company Ltd<br/>Bell &amp; Howell Ltd<br/>Berg Electronics Ltd<br/>C. Brandauer &amp; Co<br/>Brandenburg Ltd<br/>Britec Elesta Ltd<br/>British Central Electrical Co<br/>Bryans Southern Instruments<br/>Cliffpalm Ltd<br/>Comark Electronics Ltd<br/>Compstock Ltd<br/>Consort Power Sales<br/>Coutant Electronics Ltd<br/>Cramer Components<br/>Crow of Reading Ltd<br/>Data Laboratories Ltd<br/>Datron Electronics Ltd<br/>Davu Wire &amp; Cables Ltd<br/>Diamond H Controls Ltd<br/>Digital Devices Ltd<br/>Dymar Electronics Ltd<br/>Electron<br/>Electronic Engineering<br/>Electronic Equipment News<br/>Electronics Industry<br/>Electronic Visuals Ltd<br/>ENI Power Systems Ltd<br/>Erie Electronics Ltd<br/>European Electronic Contact<br/>Exel Electronics Ltd<br/>Farnell Instruments Ltd<br/>Ferranti Connectors<br/>Ferranti Semiconductors<br/>Fieldtech Ltd<br/>Fluke International Corp</p> | <p>T. Foxall &amp; Sons Ltd<br/>GEC Semiconductors Ltd<br/>Gemini<br/>Giltech Components Ltd<br/>W.L. Gore &amp; Associates Ltd<br/>Gould Advance Ltd<br/>Hartley Measurements<br/>Havant Instruments Ltd<br/>Highland Electronics Ltd<br/>Hunting Hivolt Ltd<br/>Ichthus Instruments Ltd<br/>Imhof Bedco Ltd<br/>Intel Group of Companies<br/>Intima Electronics Ltd<br/>ITT Component Group<br/>ITT Electronic Services<br/>ITT Microprocessors<br/>Journal of ATE<br/>Kemo Ltd<br/>KGM Electronics Ltd<br/>Labhire Ltd<br/>Lambda Electronics Ltd<br/>Lan Electronics Ltd<br/>F.C. Lane Electronics Ltd<br/>Lascar Electronics<br/>Lawtronics Ltd<br/>Lemo U.K. Ltd<br/>Littelfuse (GB) Ltd<br/>Littex<br/>Lipa &amp; Isostat (GB) Ltd<br/>J.J. Lloyd Instruments Ltd<br/>Malden Electronics<br/>Molex Ltd<br/>New Electronics<br/>Nortronic Associates<br/>Normalair Garrett<br/>Oakleigh Engineering<br/>Oxford Electronic Instruments</p> | <p>Philcom Electronics Ltd<br/>Phoenix Electronics Ltd<br/>Pinnacle Electronics Ltd<br/>Plastronics Ltd<br/>Plessey Aerospace<br/>Plessey Semiconductors<br/>Plessey Traffic &amp; Instrumentation<br/>Powertron Ltd<br/>Practical Electronics<br/>Pye Unicam Ltd<br/>Raytheon Semiconductors<br/>Reading Windings Ltd<br/>Redpoint Ltd<br/>Ritro Electronics Ltd<br/>Ross Courtney<br/>Roxburgh Electronics<br/>R.S. Components Ltd<br/>S.A.S.C.O.<br/>Semiconductor Specialists<br/>Setab Electronics<br/>Siliconix Ltd<br/>Sprague Electric U.K.<br/>H.W. Sullivan Ltd<br/>Symot Ltd<br/>Synchro Services<br/>Tektronix U.K. Ltd<br/>Teledyne Semiconductor<br/>Telequipment<br/>Telonic Altair<br/>Texas Instruments<br/>Toko U.K. Ltd<br/>Unimatic Engineering Ltd<br/>Variohm Components<br/>Vero Electronics<br/>Walter Logan &amp; Co Ltd<br/>Wavetek<br/>Weir Electronics Ltd<br/>Zettler U.K.</p> |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|

# You'll come?



## CROFTON FOR USED VIDEO EQUIPMENT

Used Video Equipment bought and sold daily. If we do not have what you want, we enter your requirements on our register and advise you when it is available.

U.H.F. Modulators supplied for connecting a camera directly to a domestic TV or Philips V.C.R. Camera Kits for the enthusiast also in stock.

Fujinon lens available

Repairs of all types of Video equipment undertaken

**WHATEVER YOUR VIDEO REQUIREMENTS FIRST CONTACT CROFTON**

**CROFTON ELECTRONICS LTD.**  
35 Grosvenor Road  
Twickenham  
Middx. TW1 4AD 01-891 1923

WW—036 FOR FURTHER DETAILS

## Get mixed up with SOUNDEX

This year 6-2 mixer



Floating transformer with inputs	Each with 5 modes	RSA & pan-pot.	PPM to BS 4297	All-metal case
----------------------------------	-------------------	----------------	----------------	----------------


**Plus: Pre-fade listen, break jacks on four channels, A-B tape monitoring, Built-in 1KHz line-up osc., XLR-type connectors, 24-volt power input.**

**For broadcasting and recording. less than £400 plus VAT**
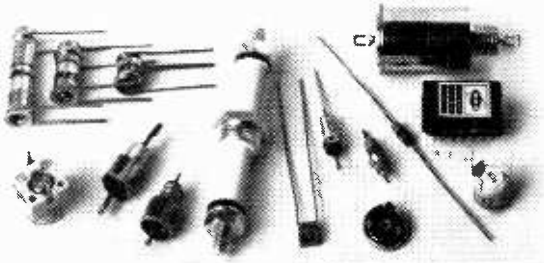
## SOUNDEX LIMITED

728 High Road, Leytonstone, London. 539-4347  
 WW—087 FOR FURTHER DETAILS





## FOR PROFESSIONAL COMPONENTS, SAY ERIE

Erie Technological Products Inc. with manufacturing locations at Erie, State College and Carlisle in Pennsylvania U.S.A., Trenton in Ontario Canada and Nogales in Mexico, offer an unequalled range of electronic components for the professional market.

Product ranges manufactured include—  
 Monolithic Ceramic Capacitors (Monoblocs) Rectangular and Tubular moulded, and tubular glass sealed.  
 Trimmer Capacitors (ceramic, air, plastic, glass and quartz).  
 'Transcap' Disc, feedthru, and tubular ceramic capacitors, button micas, plastic film capacitors.  
 Low pass filters, custom design filter connectors and multi section filters.  
 H.V. rectifiers, and multiplier assemblies.  
 High voltage power supplies.

For further information contact—

**ERIE ELECTRONICS LIMITED**  
 Resistor Division  
 South Denes, Great Yarmouth, Norfolk.  
 Tel: 0493 56122 Telex: 97421

Components **ITT**

WW—047 FOR FURTHER DETAILS

## TIME + FUEL + EFFORT = MONEY

You can effectively reduce costs by the installation of a STORNO mobile radio system.

To investigate further, write, telephone or telex to

**Storno**  
 RADIO COMMUNICATION SYSTEMS

Storno Limited, Frimley Road, Camberley, Surrey.  
 Telephone: Camberley (0276) 29131 Telex: 858154

WW — 089 FOR FURTHER DETAILS

## SCRUMPI

Bywood's Evaluation Kit for the SC/MP microprocessor system. The kit contains MPU chip, 256 x 8 bit RAM, 2 4 bit I/O latches, 24 LED lamps and drivers, 16 data and control switches, all IC sockets, all associated components, PCB and cable. The switches allow you to program the 256 x 8bit RAM and then execute the program in that RAM. Several operating modes allow for ease of programming and testing. SCRUMPI can be extended to access up to 64K bytes and can easily be interfaced to RAM, EAROM, PROM, Keyboard, VDU, Printer, etc. Kit requires +5, -7v @ 200mA. Kit price £64.81 + VAT.

**SCRUMPI EXTENDER CARD.** Available early 1977 this PCB contains interface to 1K PROM, 1K EAROM, 512 RAM, plus device controls. Supplied with or without chips, write for further details.

RAMs, PROMs, EAROMs, Floppies, Printers, Keyboards, Interfaces, VDU systems, Power Supplies and even consultancy. We can set you up in micro-processors with very little trouble and with very little pain.

For expert advice on hardware or software or even if you want to know the difference, or to order any of our products (25p to £5000) ring us on 0442-62757, our technical people don't bite.

### PAYMENT TERMS

Cash with order, Access, Barclaycard (simply quote your number and sign). Credit facilities to accredited account holders. Pro-forma invoices can be issued.

**BYWOOD**

BYWOOD ELECTRONICS

68 Ebbens Road Hemel Hempstead HP3 9RD  
 Tel 0442 62757

## HVS VIDEO PROCESSORS

for Industry, Education, Research



Fast, non-contact measurement of position and size, using input from standard CCTV cameras

Automatic visible-flaw detection

Graphical and message displays on standard CCTV monitors.

Interfaces for hard-wired and computer systems

**VP 101 / 102** Video Target Locators  
 (for automatic positioning systems).

**VP 103** Video Target Height / Position Indicator

**VP 104** Visible Flaw Detector

**VP 105 / 106** Video Level Indicators

**VG 101** Bar Graph Generator  
 (displays on CCTV monitor)

Specials designed and manufactured

Further information from

**HAMPTON VIDEO SYSTEMS LTD.**  
 Heath Road, Twickenham TW1 4BN  
 Tel: 01-891 1974

WW—067 FOR FURTHER DETAILS

**INTERFACE**  
INTERNATIONAL  
Consulting Telecommunications Engineers  
*sole agents for*  
**COHERENT** Speech Plus telegraph multiplex equipment  
Telephone signalling equipment  
Telegraph and data modems up to 1800 baud

**INTERFACE**  
QUARTZ DEVICES LTD.  
World-wide exporters of crystals & filters  
Manufacturers of DIP crystal oscillators  
from 10kHz to 20MHz  
*sole agents for*  
**FILTRONETICS** LC & crystal filters from 10Hz to 100MHz  
**STATEK** Ultra miniature low frequency crystals  
**ELECTRO DYNAMICS** High volume timing crystals

**INTERFACE**  
29 Market Street, Crewkerne, Somerset England TA18 7JU  
Telephone (0460) 74433 Telex 46283 inface g

WW-071 FOR FURTHER DETAILS

## The Teletext decoder you don't have to modify your set for!



Your tv set needs no modification whatsoever! You just plug the decoder's output into your aerial socket. Our Teletext decoder has its own mains power supply, works with any 625-line receiver, monochrome or colour, and to make assembly particularly easy, the design uses four *p.c.b.s* which plug in to a main 'mother' board. Also, to simplify alignment, the very latest receiver techniques are used in the i.f. strip. All *p.c.b.s* will be made available through *Television* magazine's Reader's P.C.B. Service.

Part 1 of the Teletext decoder is in our March issue on sale now. It covers fundamentals and power supply details. Part 2 in the April issue begins the logic section.


Take up the March issue out now

# Television

April issue on sale Monday March 21

45p

## JOYSTICKS

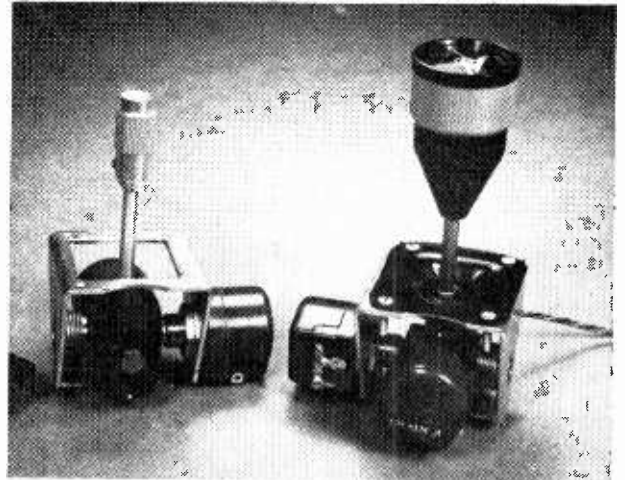

Precise, reliable, long-life Joystick Control Units, in single, dual or triple axis forms. Sprung to centre, or held by adjustable friction locks. Choice of wirewound, cermet or plastic film potentiometers (all standard 3/8" bush types) — or rotary switches.

Already in quantity production for remote control, TV games, electric wheelchairs, audio control panels, etc., etc. Any quantity from one-off to hundreds per month. Typical one-off prices: Single axis £4.50. Dual £6.50. Triple £11.00 + VAT.

### TELEVISION GAME JOYSTICKS

We have finalised the design of an ULTRA LOW COST dual axis Joystick for the home television game market, and wish to arrange mass production for a large scale manufacturer of such games, in the UK or overseas.

## FLIGHT LINK CONTROL LTD.

Bristow Works, Bristow Road  
Hounslow, Middlesex, 01-570 4065

WW-086 FOR FURTHER DETAILS

### TELERADIO SPECIALISTS IN DESIGNS by John Linsley Hood

Example: 25 to 75 watt. Very Low Distortion HIGH FIDELITY STEREO AMPLIFIER D.C. Coupled T.H.D. hardly measureable.



£73  
+ TAX

Supplied as a Kit of parts or in ready assembled module form.

Also available: Phase Locked Loop, F.M. Tuner; Millivoltmeter; Audio Signal Generator; T.H. Distortion Analyser; F.M. Signal Generator/Wobulator.

Send SAE for comprehensive illustrated lists and up-to-date prices INCLUDING BROMLEY AND BAILEY DESIGNS

### TELERADIO ELECTRONICS

325 Fore Street, Edmonton, London N9 0PE

Telephone: 01-807 3719

Closed Thursdays

## carbon film resistors

£2:50 +VAT per 1000!

1/4 W 5% TOL E24 RANGE



SUPPLIED ONLY IN MULTIPLES OF 1000pcs per OHMIC VALUE  
MIN. ORDER £25 WHILE STOCKS LAST

SEND FOR LISTS & SAMPLE OTHER ITEMS AVAILABLE

PBRA LTD THREE ELM LANE GOLDEN GREEN TONBRIDGE TN11 0LH  
phone HOPFIELD (073274) 345

WW-038 FOR FURTHER DETAILS
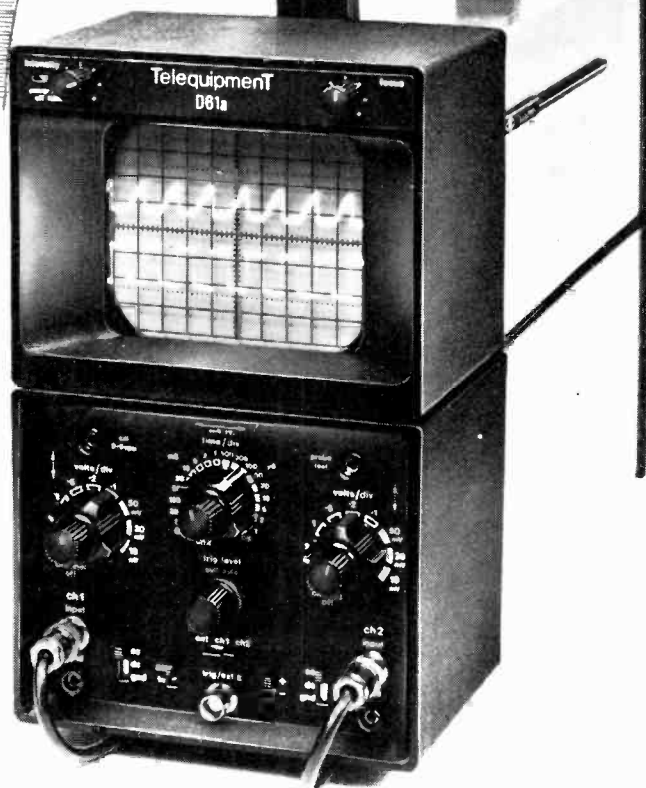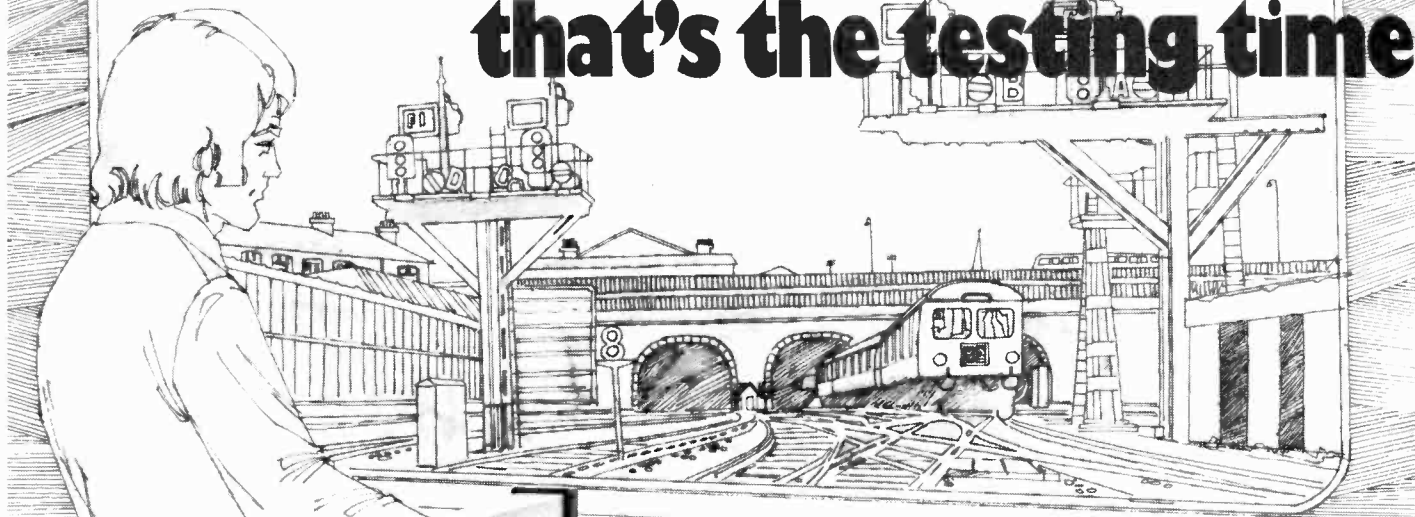
# When so much depends on the signal that's the testing time



## The dual trace D61a

The D61a from Telequipment is a versatile 10MHz dual trace model particularly suited to radio and TV servicing or for general laboratory or classroom work. The dual trace facility includes automatic selection of 'chopped' or 'alternate' modes and an XY capability. A large viewing screen, and simple but effective triggering make the D61a ideal for the busy service engineer.

Signals play an important role in the efficient running of many systems essential to our modern society. Telequipment's range of inexpensive oscilloscopes are designed for the effective display and interpretation of such signals in many different disciplines.

The Telequipment range includes two especially lightweight mains-operated 'scopes, the S61 and D61a, which offer a unique combination of ease of operation, carrying convenience and generous performance.


If signals are your interest, then you should know more about these lightweight 'scopes from Telequipment.

**TELEQUIPMENT** 

Tektronix U.K. Limited,  
P.O. Box 69, Beaverton House, Harpenden, Herts.  
Tel: Harpenden 63141. Telex: 25559.

## & the S61 single trace

The Telequipment S61—a rugged 5MHz single beam 'scope featuring ease of operation and efficient triggering using the absolute minimum of controls. Viewing is enhanced by a large 5 inch CRT screen. In the auto-mode, the sweep free-runs so that in the absence of a signal you still see the trace. Its simplicity of operation makes it ideal for general industrial purposes or for use by non-technical personnel.

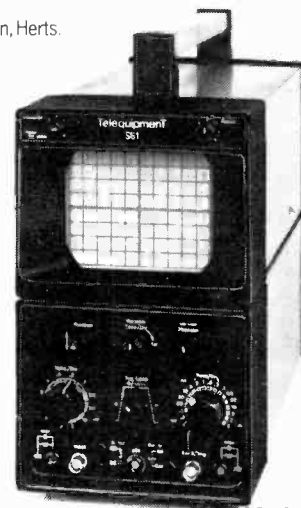

DDL 6445

WW—078 FOR FURTHER DETAILS

# wireless world

Electronics, Television, Radio, Audio


APRIL 1977 Vol 83 No 1496

## Contents

- 35 Time, gentlemen, please  
36 NRDC surround-sound system by *M. A. Gerzon*  
39 News  
40 Characteristics and load lines — 5 by *S. W. Amos*  
44 Wireless World amateur radio station  
45 Sensitive metal detector by *D. E. O'N. Waddington*  
48 H.F. predictions  
53 New of the month  
Bullock's boardroom and the engineer  
Britain pioneered the integrated circuit  
Vmos devices "middle of this year"  
57 Education by radio in Honduras by *M. K. Bates*  
60 Literature received. 100 years ago  
61 Circuit ideas  
Simple noise generator  
Variable band-pass filter  
Ripple eliminator  
65 Viewdata — 3 by *S. Fedida*  
70 World of amateur radio  
73 Electronic rhythm unit — 2 by *A. Battaiotto and G. Ronzi*  
76 Letters to the editor  
The Warden Report  
Current dumping amplifier  
Advanced pre-amplifier design  
79 Broadcast stereo coder by *T. Brook*  
83 Power semiconductors by *M. R. Sagin*  
93 New products  
96 Just for the record by *A. D. Foster*

APPOINTMENTS VACANT

INDEX TO ADVERTISERS

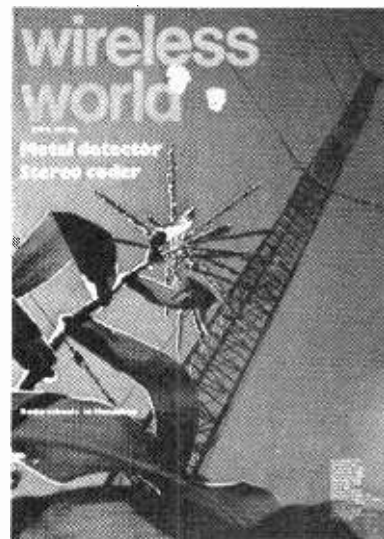

Front cover, showing the medium wave aerial at Radio-lándia, Comayagua, Honduras, introduces the article on education by radio in that country (page 57).

Photographer Paul Brierley

## IN OUR NEXT ISSUE

### Electrolytic capacitor tester.

Enables the value of an electrolytic capacitor to be measured automatically and the result displayed directly by meter. Leakage is also indicated.

### Two-stage linear amplifier.

A discussion of the design of solid-state 50W and 300W linear amplifiers for the h.f. band (1.6-30MHz).

**Radio in the '80s**, a look forward to sound receiver design and the ideal set of the future by the BBC's chief engineer of radio broadcasting.

ISSN 0043 6062

Current issue price 35p, back issues (if available) 50p, at Retail and Trade Counter, Paris Garden, London SE1. By post, current issue 55p, back issues (if available) 50p, order and payment to Room 11, Dorset House, London SE1 9LU.

Editorial & Advertising offices: Dorset House, Stamford Street, London SE1 9LU.

Telephones: Editorial 01 261 8620; Advertising 01 261 8339.

Telegrams/Telex. Wiworld Binspres 25137 London. Cables. "Ethaworld, London SE1.

Subscription rates: 1 year: £7.00 UK and overseas (\$18.20 USA and Canada). Student rate: 1 year, £3.50 UK and overseas (\$9.10 USA and Canada).

Distribution: 40 Bowling Green Lane, London EC1R 0NE. Telephone 01 837 3636.

Subscriptions: Oakfield House, Perymount Rd, Haywards Heath, Sussex RH16 3DH. Telephone 0444 59188. Subscribers are requested to notify a change of address. © I.P.C. Business Press Ltd, 1977

**ibpa**  
International Business  
Press Ltd 1977

**ABC**  
MEMBER OF THE ASSOCIATION  
OF BUSINESS PRESS EDITORS





## The Test of Time

Critics were most generous in their praise when the Shure V-15 Type III pickup cartridge was introduced. The ultimate test, however, has been time. The original engineering innovations, the uniquely uniform quality and consistent performance reliability of the V-15 Type III have made it THE classic choice as the source of sound for the finest music systems, both here and abroad.

Consider making the relatively modest investment of a new cartridge to upgrade the performance of your entire hi-fi system. Why not ask Shure Electronics Limited for their recommendation?

Shure Electronics Limited  
 Eccleston Road, Maidstone ME15 6AU  
 Telephone: Maidstone (0622) 59881

The original manuscript by J. S. Bach shown is reproduced by kind permission of The British Library.

WW-010 FOR FURTHER DETAILS

I am at present using

\_\_\_\_\_ Arm or Unit

\_\_\_\_\_ Cartridge

\_\_\_\_\_ Amplifier

\_\_\_\_\_ Name

\_\_\_\_\_ Address

Please recommend the best Shure cartridge to upgrade my system.



# wireless world

## Time, gentlemen. Please!

**Editor:**  
TOM IVALL, M.I.E.R.E.

**Deputy Editor:**  
PHILIP DARRINGTON  
Phone 01-261 8435

**Technical Editor:**  
GEOFFREY SHORTER, B.Sc.  
Phone 01-261 8443

**Assistant Editors:**  
MIKE SAGIN  
Phone 01-261 8429  
RAY ASHMORE, B.Sc., G8KYY  
Phone 01-261 8043  
JOHN DWYER  
Phone 01-261 8620

**Production:**  
D. R. BRAY

**Advertisement Controller:**  
G. BENTON ROWELL

**Advertisements:**  
PHILIP NOSSEL (*Manager*)  
Phone 01-261 8622

LEO KEMBERY  
Phone 01-261 8515

OWEN BAILEY (*Classified Advertisements*)  
Phone 01-261 8508 or 01-261 8423

JOHN GIBBON (*Make-up and copy*)  
Phone 01-261 8353

**Publishing Director:**  
GORDON HENDERSON

When this issue of *Wireless World* appears on the news stands the deadline for submissions to the Home Office on British policy on frequency reallocations for the 1979 WARC will be only six weeks away. (See *News of the Month*, March p.37). Yet a few months ago even this much consultation seemed out of reach. The Home Office is to be congratulated on reversing its policy of selective consultation and giving the public a chance to have their say. It could be argued, indeed, that the process might have begun much earlier had the electronics industry and its representatives been less acquiescent in the Home Office's reluctance to encourage public intrusion. Even though the discussions to which the discreet trustees we referred to in December found they had an exclusive entrée were on matters of public concern far beyond their immediate interests, they made, at first, no effort to press for a programme that might dilute their own bargaining strength.

But it is for the electronics industry, singly and collectively, to put its own house in order. The immediate need is to make sure that the 1979 package is a fair reflection of the views of all those with an interest in the allocation of frequencies. The Home Secretary's statement is only a beginning. Indeed it contains a surprising admission of the inadequacy of what he has craftily called "the preliminary phase" of the work for the conference: although, he says, a substantial measure of consultation with users and manufacturers has already taken place, during the next phase "those known to have an interest will be specifically invited to comment." One wonders how "substantial" the measure of consultation during the preliminary phase could have been.

One hopes, too, that equal weight will be given to the public's views as to those "specifically invited." This can only be the case if the public is as well informed as those "known to have an interest," yet we have not received any details of the Home Office proposals for disseminating the contents of the Warden reports and any others relevant to the WARC. If the "wider programme of consultation" is to be anything more than an empty political gesture these reports must be made public.

The ten days following the publication of the next issue of *Wireless World* will not give enough time to read the available material, to consult colleagues, and to draft a considered proposal. The consultation period should be extended, just as the Annan committee extended theirs. An extension to the end of the year would give officials a clear year to collate and prepare the British case. Is that so much to ask?

# NRDC surround-sound system

Michael Gerzon reveals the thinking behind system 45J

by Michael Gerzon, M.A., *Mathematical Institute, Oxford*

**This article gives a feel for how it has proved possible to evaluate the whole range of possible methods of encoding and decoding surround-sound based on fundamental psychoacoustic principles. Although the full development was highly mathematical, the basic principles underlying the Ambisonic or NRDC 45J system\* of surround-sound are described without mathematics, this new system being the best possible according to the methods used.**

Up to now, surround sound system design has to a considerable degree been based on guesswork as to what signals fed to an array of loudspeakers will produce a "desirable" directional affect. As an exhaustive experimental evaluation of the directional effect of arbitrary crosstalk patterns for even just a square speaker array involves consideration of a six-parameter family of crosstalk configurations, and as even small variations of the crosstalk pattern can produce significant alterations of directional effect, it would be necessary to do experiments for about 10<sup>6</sup> different crosstalk patterns before one could say that a system could be optimized purely on the basis of experimental data. This is impracticable.

A very general theoretical framework has been developed<sup>1</sup> to assist in maximizing the information that can be deduced from limited experimental tests on human directional psychoacoustics. Certain aspects only of this psychoacoustic framework are discussed in this article.

At low frequencies, the information reaching the brain consists of the sum of the inputs to the two ears, i.e. an omnidirectional or "pressure" sound pick-up and the difference of the inputs to the two ears, i.e. a sideways-pointing figure-of-eight or "velocity" pick-up, Fig. 1. Most low frequency (<700Hz) theories of hearing assume that only the interaural phase is used to determine direction, which is equivalent to saying that only those components of the sideways figure-of-eight pick-up that

are in-phase or out-of-phase with the pressure signal components are used by the ears. In practice the 90°-phase components of figure-of-eight pick-up do affect localization quality toward the top end of this low frequency range, and produce an effect called "phasiness."

In practice, the head may rotate, so that the forward-pointing figure-of-eight pick-up of sound information is also used to determine sound direction. The relative intensity of in-phase figure-of-eight signals in the forward and sideways direction defines a vector pointing in the apparent sound direction according to Makita's theory and is susceptible to calculation as described in reference 4. The length of this vector

(divided by the pressure amplitude) should be one for real-world sounds, and so decoders should be designed with a pressure-to-velocity ratio assuring this requirement for all reproduced sound directions at low frequencies, in addition to ensuring correct Makita localization. It is an incorrect velocity-vector length that makes the side image reproduction so poor in conventional "discrete" quadraphonics.

If there is too high a phasiness, it is clear that this can be reduced for a given decoder design by subtracting from the figure-of-eight signals a suitable amount of 90° phase-shifted pressure signal. In practice, the amount of unwanted 90°-shifted figure-of-eight information varies with sound direction, so that phasiness compensation to reduce phasiness in one direction will tend to increase it in the opposite direction. Nevertheless, it is possible to use this technique to give a subjectivity optimized phasiness, as shown in Fig. 2.

The block diagram of Fig. 2 is a psychoacoustically optimized decoder consisting of a phase-amplitude matrix producing pressure, forward and sideways velocity and 90° phase-shifted pressure signals from the input channels; the design of the phase-amplitude matrix depends on the encoding system.

Fig 2: Block diagram of decoder satisfying the main psychoacoustic requirements. Shelf filters are all-pass types designed to have identical phase responses, and make the decoding matrix varying frequency according to the frequency-dependent properties of human hearing.


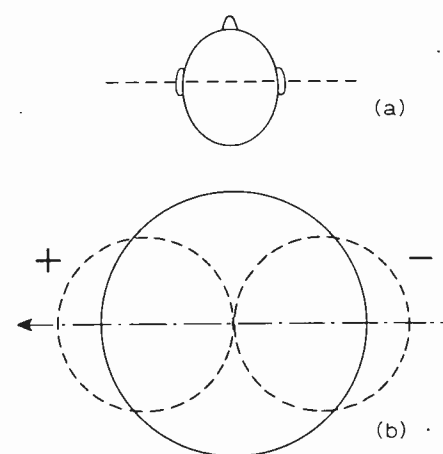


Fig 1: Pressure and velocity (figure-of-eight) pick-up characteristics of the sum and difference of the inputs to the two ears of a listener at low frequencies.

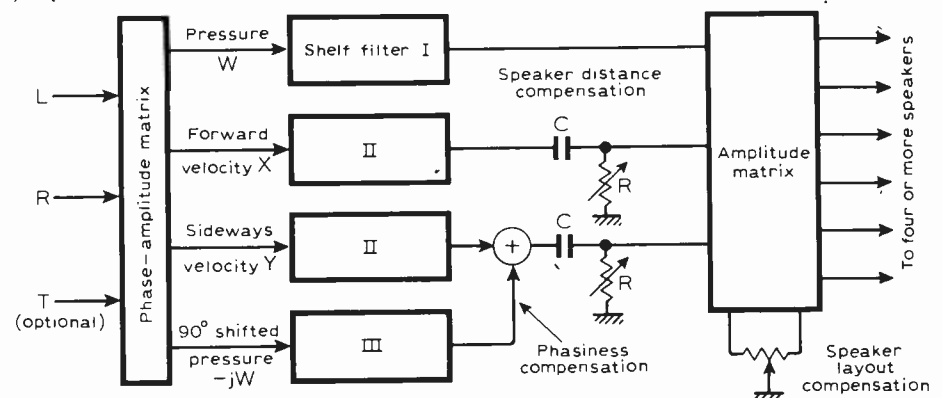

\* System 45J is the subject of a UK-section AES meeting to be held on 12 April at the IEE, Savoy Place, 19.00h. Title is "Hearing and surround-sound," by P. B. Fellgett, M. Gerzon and T. Takagi.

The shelf filters are frequency-dependent gains that permit adjustment of the relative velocity and pressure gains so that at low frequencies the velocity-vector length is correct, and at higher frequencies other psychoacoustic requirements, described later, are satisfied. The "distance compensation" is high-pass RC filtering of velocity, typically  $-3\text{dB}$  at  $20\text{Hz}$ , to compensate the bass boost of the velocity signals produced at the listener by the curved sound field (caused by finite loud-speaker distance). It is mainly the phase response of this filter that is psychoacoustically important. The output amplitude matrix produces speaker feed signals, dependent on the speaker layout used, that create correct pressure and velocity at a central listening position.

At higher frequencies, about  $700$  to  $5\text{kHz}$ , a different class of theories of hearing take over. In these theories localization is via signal energy, and is determined by drawing a vector pointing to each speaker having length equal to the energy of a sound from that speaker. The sum of these vectors is a vector pointing in the intended sound direction, which direction is the "energy vector localization." The length of this vector, divided by total energy (energy vector magnitude) is  $1$  for real-world sounds, and should be as large as possible in decoders for good localization.

There is a transitional frequency band,  $250$  to  $1.5\text{kHz}$  over which both classes of theories may apply, and it is important that decoders should give both correct pressure/velocity and energy localizations as far as possible over this transitional range. This is ensured by designing decoders to give Makita and energy vector localizations that are identical at all frequencies; this may be ensured for many types of speaker layout (rectangle, hexagon, etc.) by a suitable design of output matrix. The shelf filters in Fig. 2 are then chosen to give optimum velocity magnitude at low frequencies and optimum energy vector magnitude at high frequencies. Note that this design procedure involves designing not only optimum low and high frequency decoding matrices, but an optimal variation of the matrix over the transition frequency range.

One result that emerges from this theory is a remarkable mathematical theorem to the effect that the optimal accuracy of reproduction of images in non-speaker directions via a rectangle of speakers can be obtained *only if the four speakers are fed with not more than three information channels*; it may be shown that  $-L_B + L_F - R_F + R_B$  should always be zero for best results. Experiment confirms the theory.

Given that we have a means of designing decoders for optimal psychoacoustic results for any encoding system capable of producing suitable pressure and velocity signals, the aim is

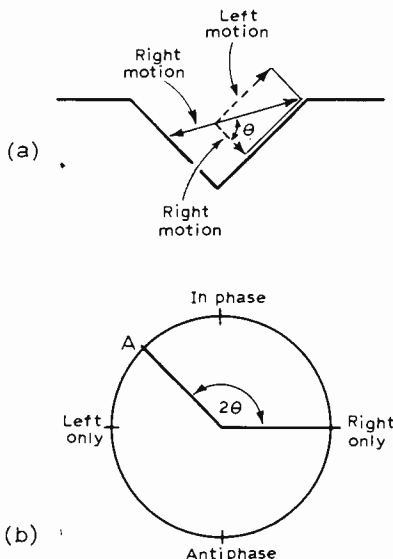


Fig 3: Angle  $\theta$  of stereo stylus motion in record groove corresponds to an angle  $2\theta$  on a circle representing possible stereo positions.

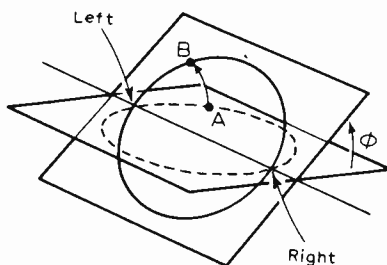


Fig 4: Circle point A goes to point B on sphere by a rotation by angle  $\theta$  equal to the phase lead on the left channel.

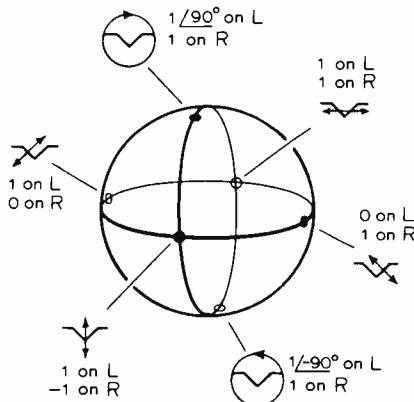


Fig 5: Typical stylus motions (for sine wave signals) and left and right channels gains corresponding to various points on the energy sphere.

then to find the best encoding system, i.e. the one whose optimized decoder gives better results than for all other encoding systems.

It is possible to classify mathematically all systems with not more than three channels that are capable of satisfying the Makita, energy vector and velocity magnitude requirements via suitable decoders. This classification involves about 40 pages of mathematics, but can be solved exactly. The theory involved also gives the detailed

parameters of decoders that optimize the reproduced psychoacoustics of the directional effect for every sound direction.

The requirements on surround-sound performance of such systems include the following.

- The two baseband stereo signals L and R must be decodable for surround directional reproduction in a way satisfying all the basic psychoacoustic criteria discussed earlier.

- It must be possible to supplement the baseband with a third signal capable of being decoded with improved directional effect. A fourth channel is not required as it can only degrade directional reproduction.

- To achieve high quality from carrier discs, which have certain inherent theoretical limitations determinable by standard information theoretic analysis, it is necessary to bandlimit the subcarriers to a few kHz.

- It is required that satisfactory decoders be designable for the case when the third channel is bandlimited, not only in directional effect, but also in flat reproduced frequency response in all encoded directions. The directional effect requirement for such "2½ channel" use means that, as the third channel is attenuated the Makita (and hence energy vector) localization of a three-channel decoder should remain unaltered.

- Within these above constraints, the two channel decoding should be capable simultaneously of low phasiness for front-stage sounds, good localization at the left and right side positions, and with a uniform reproduction of ambience information around the listener on "natural" ambient recordings.

A way of describing the two-channel baseband encoding is the "energy sphere" (ref. 2) which represents the relative phase and amplitude gain of each sound on the two channels as a point on a sphere. A sound recorded on the two groove walls of a stereo disc (Fig. 3), without the use of phase shifters is represented by a point A on the horizontal circle of this sphere, at an angle from the right-most point of the circle twice as big as the angle made by the stylus motion from the right-channel-only direction of stylus motion. In this way all in-phase and out-of-phase lines of stylus motion are mapped to points around a circle. If the left channel is now made to phase-lead one right channel by a phase angle  $\phi$ , then the point B on the sphere representing the method of encoding is also obtained from A by rotating the circle about its left/right axis by an angle  $\phi$  as shown in Fig. 4. Stylus motions and left and right channel phases and gains corresponding to various points on the energy sphere are shown in Fig. 5.

One may describe a method of encoding by the way its energy sphere point varies with encoded direction. The locus traced out on the sphere as the



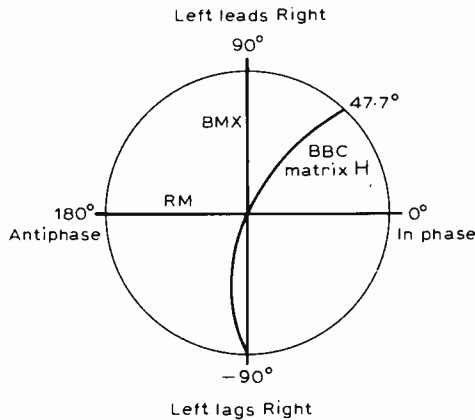


Fig 6: View from right side of energy sphere, showing RM (Regular Matrix) BMX and BBC Matrix H system two-channel encodings. Angles indicated round edge show the phase lead of the left channel.

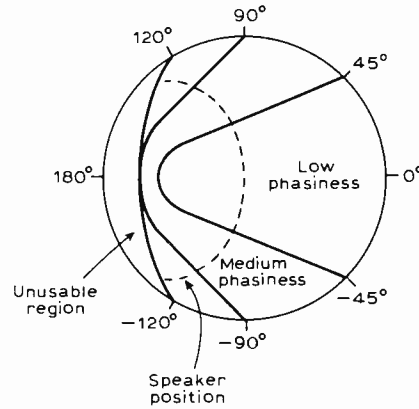


Fig 7: Quality of mono and stereo reproduction shown on energy sphere viewed from right side. "Speaker position" curved indicates appearing to come from one speaker only in stereo.

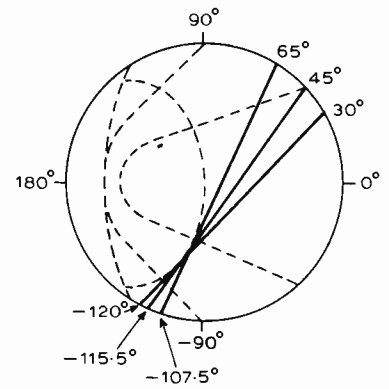


Fig 8: Three possible choices of two-channel encoding system having optimized mono and stereo reproduction.

sound rotates through 360° is shown as the "pan locus" of the encoding system. The best-behaved systems are those in which the left-half and the right-half of the pan locus are mirror images of one another. For such systems, it is convenient to view the locus on the sphere from the right hand side; Fig. 6, shows the side view with various existing system pan loci. The angles round the edge indicate the relative phase lead of the left channel over the right channel, and the centre point represents left-only or right-only.

Fig. 7 gives a rough indication of the acceptability of the mono and stereo quality, as previously discussed. The shaded nearly antiphase region at the back of the sphere must be avoided for direct sounds, both because sound in this region is excessively attenuated in mono, and because the sound is very "phasy" and hard-to-localize in stereo. (It is not always undesirable to have reverberation information in this region, however). Approximate regions of low and medium phasiness effects in stereo are also shown, although the boundaries are not in practice sharply defined. It is possible to have a sensation of unpleasant phasiness for some programme material even when it is all in one low phasiness region, and some material can sound acceptable even in the high phasiness region. In practice, it is found preferable to minimize stereo phasiness for front-sector sounds, even if this means making phasiness marginally worse for rear-sector sounds.

The stereo image must have full stage width. This need not mean the locus passing through the left-only point, but can be achieved as long as the pan locus touches the "speaker position" curve Fig. 7 along which sounds appear to lie in one speaker only in stereo. Thus to get good mono and stereo compatibility, the locus must be moved as far forward as possible, especially for front-encoded sounds, while touching the speaker-position curve.

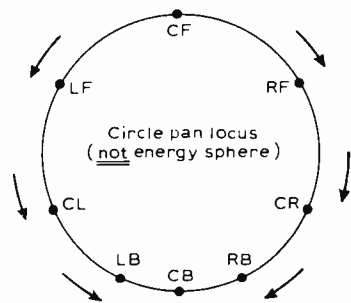


Fig 9: Showing optimized non-symmetric distribution of different encoded directions within the circle "pan locus" of the systems shown edge-on in Fig 8. C<sub>F</sub> stands for "centre-front," R<sub>B</sub> for "right-back," C<sub>L</sub> for "centre-left" and so on. This figure is not a picture of the energy sphere.

Another constraint lies in the requirement for good surround decoding. The effect of using a bent locus, see Fig. 6, rather than a circle locus (whose side view is a straight line!) is that surround decoders give poor side-image localization and it can be proved that this is inevitable for any design made for such systems according to psychoacoustic theory. The asymmetry between side-to-side and front-to-back performance of bent loci means also that ambience reproduction is poor and that 2½-channel decoders cannot give a substantially flat frequency response for all directions of encoding. For these reasons, a circle-locus system must be chosen; otherwise surround reproduction quality inevitably must be degraded.

Pulling a circle locus as far forward as it will go on the sphere while touching the speaker position curve yields possibilities shown in Fig. 8. As the front-centre interchannel phase angle increases from 30° to 65°, the stereo phasiness becomes progressively worse for front-sector sounds, but better for back-sector sounds, and mono compatibility improves. One can argue indefinitely about which compromise of compatibility properties is best, but we have found that the 45°/-115.5° locus

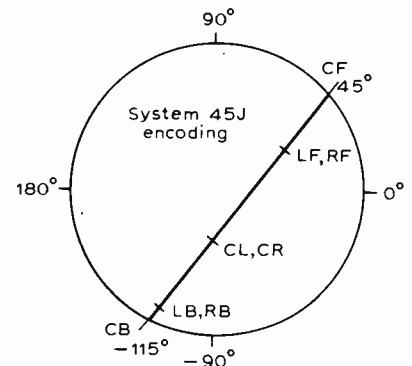


Fig 10: Energy sphere (side view) picture of two-channel version of System 45J encoding.

seems best to satisfy the needs of the widest range of users, including record companies and broadcasters. Moreover, this locus has good performance when used with existing regular matrix (RM) and UMX equipment for decoding. Thus a changeover to this standard should cause minimal disruption, and could simplify the confused market situation by reducing the number of systems on the market.

A further optimization of reproduced surround effect comes from a careful choice of the way different encoded directions are distributed within the circle locus. Low decoded front-stage phasiness in surround may be combined with uniformly reproduced ambience if a sound-azimuth distribution within the circle locus is chosen, as in Fig. 9. This distribution helps widen the stereo presentation for front-stage sounds, thus also giving much better stereo compatibility. The front quadrant of directions alone gives an image filling over 0.8 of the stereo stage in subjective tests. Such "asymmetric circle encoding" requires a careful choice of third-channel encoding to achieve the best 2½-channel decoded results; the mathematics of this is described in reference 4.

The resulting system of encoding, Fig. 10, is called System 45J, and was chosen only after both exhaustive theoretical studies and experimental tests, as well as international discussions within the audio industry. As it is the first system designed based on a complete mathemati-

cal analysis of both system theory and human psychoacoustics, it is possible to say with some confidence that no system appreciably different from it can exceed its performance in optimal surround-sound decoding, so that no further system change is ever likely to be needed for horizontal encoding.

Unlike all previous proposals, System 45J can handle virtually any legitimate requirement in terms of recording philosophy and yet be suitable for listening in mono, stereo, two-channel surround, 2½-channel surround or three-channel surround, giving good results in all modes. There are no sound positions which producers should not use, no incompatibility with types of recording technique such as coincident microphones, and no requirement that variable-matrix decoders be used with their inevitable side-effects.

This choice of encoding system does not prevent equipment manufacturers from using their own decoding philosophy if they desire. For example, both Sansui Variomatrix and the logic decoders can easily be adapted or designed for System 45J. However, if optimum musical results are required, decoders satisfying the maximum number of requirements of human directional psychoacoustics should be used. We have outlined how such decoders may be built\*; and in the near future, a decoder will be publicly demonstrated reproducing sounds via an arbitrary rectangle speaker layout, that can also be hooked up to feed a hexagonal six-speaker layout for an even closer approach to the ideal illusion.

So far, experimental testing has been carried out via about 30 psychoacoustic decoder designs for a wide variety of encoding systems, and a broad spectrum of studio technology developed to get the best possible results. This information will be made available to the industry. The use of System 45J with this technology gives results that are far more convincing and musical, even via two channels, than was the underdeveloped "quadrophonic" approach to surround sound which has now been rendered obsolete by this work. This work was done as a part of the Ambisonic project of the U.K. National Research Development Corporation.

#### References

1. M. A. Gerzon. Surround-sound psychoacoustics, *Wireless World* vol. 80 1974 pp. 483-6.
2. M. A. Gerzon. Geometric model for two-channel, four-speaker matrix stereo systems, *JAES* vol. 23. 1975, pp98-106.
3. M. A. Gerzon. Compatible two-channel encoding of surround sound *Electronic Letters* vol. 11 1975 pp. 615-7.
4. M. A. Gerzon. Optimum choice of surround-sound encoding specification, 56th AES conversion, Paris March 1977

Following articles will give circuit details of a decoder based on these principles and which will decode system 45J and stereo for square, rectangle and hexagon speaker layouts, with distance and psycho-acoustic compensation. — Tech. ed.

## Post Office "holding back technical improvement"

Sixty-one votes prevented Mr Nicholas Ridley from introducing a bill on February 1 to end the Post Office monopoly of the supply of telephone equipment. Seeking leave to introduce a bill he said: "It may be that there are some subscribers who want telephones of different colours from those provided by the Post Office, and they cannot get them. The Post Office monopoly prevents it.

"A more important example is the pushbutton telephone device. We have these in this House, and I can well understand why they have not been allowed outside. If they were unleashed upon the unsuspecting public, dissatisfaction with the Post Office would increase apace. But there is no reason why a really effective push-button telephone should not be offered to subscribers."

Other examples, he said, included automatic telephone dialling equipment, loudspeaking telephones, and more varied answering equipment. "Telephone engineers believe that eventually it will be possible for the telephone connected to one's house to operate as a minicomputer and to give access to one's bank, department store or supermarket direct, and to allow one's meter to be read direct by the telephone. There are all sorts of imaginative, labour saving and exciting devices all within the realms of possibility. But there is one small difficulty — the Post Office is sitting on them, and its monopoly is preventing the proper development of these technical devices."

This criticism also affected the degree of choice available to those subscribers with their own exchanges. His bill proposed that a committee of independent people should check that any equipment developed for the home was compatible with the Post Office network.

The reply to Mr Ridley, the Conservative member for Tewkesbury, a civil engineer and the opposition spokesman on technology and trade from 1969 to 1970, was given by Mr Ian Wrigglesworth, the Labour and Co-operative member for Thornaby and press spokesman for National Giro. He gave a number of reasons why the bill should not be read. The first was that the Carter committee on the future of the Post Office was still sitting, and would probably consider this very point. The second was that the Annan committee was also sitting; "It will no doubt comment on the future of cablevision and on the whole question of common carrier cables."

A third reason he gave was that the testing of each piece of equipment to be

connected to the system would be "a cumbersome, expensive and ineffective process and the consumer would have to bear the costs." Another was that all Mr Ridley hoped to achieve was the creaming off of profitable parts of the Post Office's operations, of which this was one, leaving the Corporation with unremunerative services like the expensively-maintained 'phone boxes. There was already competition among private firms for making small private branch exchanges, special telephones, data transmission and teleprinter equipment provided by the Post Office, though he agreed the range of the equipment so provided ought to be extended. "The Post Office needs to be much less cautious and more aggressive in its marketing and in the number of pieces of equipment that it provides." Joint efforts with manufacturing industry to provide exportable equipment for sale abroad ought to be done through putting pressure on the Post Office.

In the division 175 members voted for the motion, 236 against.

## New hope for solar power

A student working on a PhD thesis on the properties of films at the department of plasma physics at Sydney University appears to have discovered an important way of tapping solar energy. Until now, solar cells have managed to produce temperatures of a maximum of 150 C, but the reports from Australia indicate that the new method is able to achieve 300 C as well as being cheaper than other methods. Details of the method are not yet available, but it appears to be based simply on a characteristic of one film that was tried, with chromium oxide as a main constituent, in converting much of that part of the sunlight it absorbs into heat. The student is a pupil of Dr Charles Watson Monro, the professor of plasma physics, and Professor H. Messel.

News of the development came about a week before the government published its long awaited paper on solar energy (*Solar Energy: its potential contribution within the United Kingdom-Dept of Energy, Energy paper 16, HMSO £3*) and announced that the Department of Energy would be adding £3.6 million to the £2.4 million already being spent by the Industry and Environment Departments in r & d on solar energy. The main areas of the new study will be in domestic water and space heating. Up to half the cost of suitable projects by commercial firms would be supplied.

A lecture on "An experimental energy-saving house" will be given at the IEE, Savoy Place on April 21 at 5.30.

# Characteristics and load lines

## 5 — Non-linear load lines

by S. W. Amos, B.Sc., M.I.E.E.

Part 3 (October 1976) and Part 4 (February) were devoted to linear load lines but in practical circuits load lines can be non-linear for a number of reasons. In this part we shall examine the forms of non-linearity of load lines that can occur and the effect this has on circuit performance.

### A.c. and d.c. load lines

When a load resistor  $R_1$  is capacitance-coupled to a following resistor  $R_2$  there are effectively two load lines, one representing the steady-state or d.c. conditions in the circuit and the other representing the signal-frequency or a.c. conditions: these are sometimes known as the static and dynamic load lines. Because the a.c. resistance in the load circuit is necessarily less than the d.c. resistance, the a.c. load line has a greater slope than the d.c. load line and intersects it at the quiescent point as shown in Fig. 1. As a result the output voltage available from an amplifier is reduced by the connection of  $R_2$ ; in Fig 1 the peak-to-peak value of the voltage is reduced from AB to ab. It is possible that the reduced output may still be adequate for the following stage but the restriction of output voltage is sometimes serious and it is useful to know precisely how great it is. The calculation is easy because the voltage developed across an unshunted load resistor  $R_1$  is  $IR_1$  where  $I$  is the alternating component of the active device output current. For the shunted resistor the output voltage is  $IR_1R_2/(R_1 + R_2)$  in which the reactance of the coupling capacitor is assumed negligible compared with  $R_2$  at the operating frequency. The ratio of the two voltages is  $R_2/(R_1 + R_2)$  which shows that if the shunting resistor is equal to the load resistor the output voltage is halved. To limit the reduction in output voltage to 10 per cent of that developed across  $R_1$  alone,  $R_2$  must not be less than  $9R_1$ . This underlines the requirements, well-known for a voltage amplifier, that the output should be terminated in a high-value resistor.

Fig. 1 also shows the output current waveform as a reminder that there is no corresponding reduction in amplitude as a result of shunting the load. On the contrary the effective reduction in the value of the load resistance increases the current output.

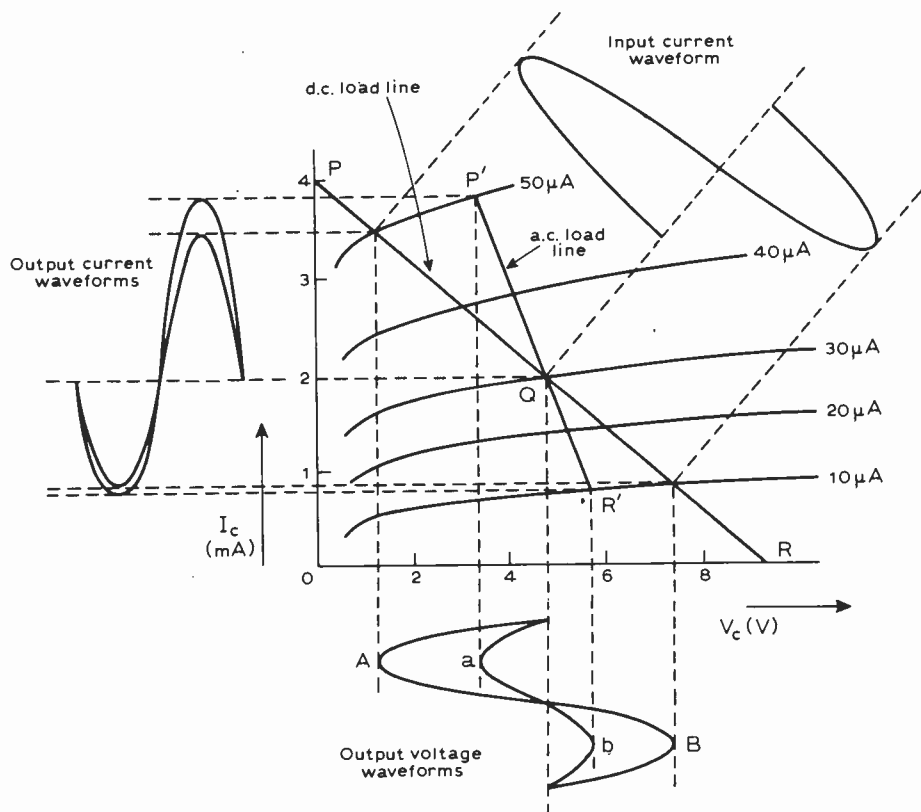


Fig. 1. The reduction in output voltage due to the different slopes of d.c. and a.c. load lines.

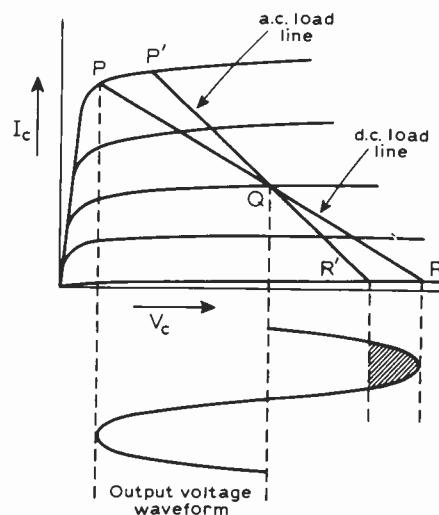


Fig. 2. Clipping of output voltage waveforms as a result of the difference in slope between a.c. and d.c. load lines.

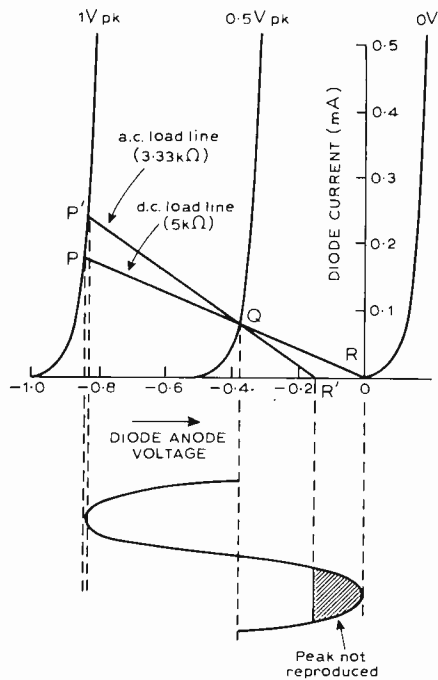


Fig. 3. Clipping of output voltage of a diode detector as a result of the different slopes of the a.c. and d.c. load lines.

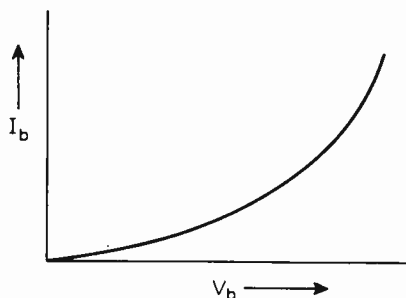


Fig. 4. Relationship between base current and base voltage for a bipolar transistor.

shunt on the diode load. The mechanism of the effect is illustrated in Fig. 3 which shows the anode voltage/anode current characteristics for a diode. These are sometimes known as rectification characteristics and each curve shows the relationship between current and voltage for a particular value of peak input.

It is assumed that the diode feeds a capacitor which charges up to the peak value of the applied signal. Thus for a 1-V peak input signal the diode anode takes up a voltage of -1 V for zero anode current. If current is taken from the diode the anode voltage falls as indicated by the slope of the characteristics. If the signal applied to the diode is amplitude-modulated the peak value varies in accordance with the waveform of the modulating signal and for a 0.5-V peak signal, modulated 100 per cent, the input swings between zero and 1V. The diode load can be represented by a d.c. load line as discussed earlier and PQR shows a load line for 5 kilohms, a value commonly used in transistor a.m. receivers. Q is the quiescent point where

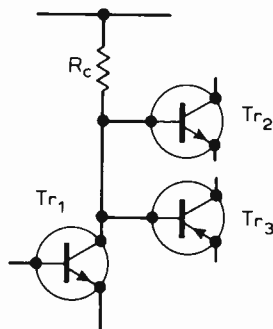


Fig. 5. Skeleton form of a driver feeding a complementary class-B stage.

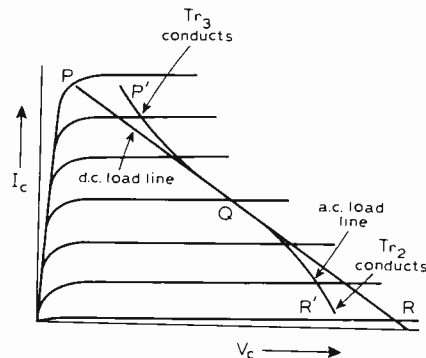


Fig. 6. D.C. and a.c. load lines for the circuit of Fig. 5.

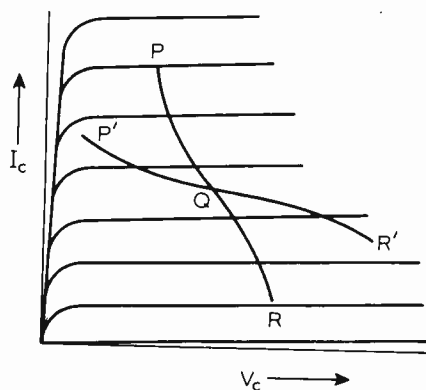


Fig. 7. A.C. load line P'QR' shows the effect of doubling the step-down ratio of the driver transformer feeding a class-B stage.

the characteristic for 0.5-V peak value intersects the load line. In the absence of modulation, therefore, the diode anode has a voltage of -0.38V and the diode current is 0.07mA. When 100 per cent modulation occurs the operating point moves up and down the d.c. load line between the limits of 0.86V (1.7mA) and zero. This represents the performance of the detector if its true load at signal frequencies is 5 kilohms.

In a practical circuit, however, the output of the diode must be applied to the following stage, normally an a.f. amplifier, and this stage has an input resistance which shunts the diode load. Let us assume that this has an input resistance of 10 kilohms. The a.c. load resistance is thus 3.3 kilohms and the a.c. load line therefore has a slope corresponding to this value of resistance and

passes through the quiescent point as shown by P'QR' in Fig. 3. This load line intersects the voltage axis at -0.15V, so clipping one of the peaks of a 100 per cent modulated input to the detector as shown by the shaded area. This represents serious distortion because the upper third of the amplitude range of the signal is not reproduced. The detector can operate reasonably successfully only if the depth of modulation of the input signal is limited to 67 per cent. The tendency in a.m. broadcasting is, in fact, to keep the modulation percentage high so to give a good signal-to-noise ratio. Thus to enable the detector to handle high modulation percentages the shunting effect on the diode load must be minimised and the a.f. amplifier should therefore have an input resistance high compared with the value of the diode load. Perhaps the easiest way of ensuring low distortion would be to interpose an emitter follower between the diode load and the a.f. amplifier.

**Non-linear load resistance**

So far in this series it has been assumed that the loads presented to active devices are purely resistive: the load lines are accordingly linear, showing the direct proportionality between current and voltage for such loads.

If, however, active devices are connected in cascade as in multi-stage equipment the load for one stage is often largely determined by the input resistance of the following stage. For a bipolar transistor the input resistance is not linear but varies with input voltage as indicated by the  $I_b-V_b$  characteristic in Fig. 4. The slope of this curve is low for small values of  $V_b$  showing that the input resistance is high for such values but as  $V_b$  increases the slope increases and the input resistance decreases. For small alternating signals the changes in input resistance may be negligible and it is common in the design of small-signal amplifiers to assume that the input resistance is constant throughout each cycle of input signal. For large signals, however, the variations are significant and must be taken into account in designing circuits. This is particularly true of the input resistance of class-B stages where the transistor is biased near collector-current cut-off and is driven into conduction by the input signal. Because a transistor so biased can amplify only one half cycle of a sinusoidal input, class-B stages in linear equipment are operated in push-pull. This makes the stage symmetrical so that the input resistance for a particular value of positive-going input is the same as for a negative-going input of equal amplitude.

As input increases, however, input resistance decreases. To deduce the effect of such input-resistance variations on the shape of the load line for the driver stage consider the circuit shown



in Fig. 5. The d.c. load line for  $R_c$  is PQR in Fig. 6 and this represents the relationship between  $Tr_1$  collector voltage and collector current in the absence of any shunting effect from the following class-B stage. Q is the quiescent point at which, we shall assume, the two class-B transistors  $Tr_2$  and  $Tr_3$  are almost cut off. The effect of a resistive shunt on  $R_c$  is to introduce an a.c. load line which passes through Q and is rotated clockwise with respect to the d.c. load line to an extent which increases with decrease in the value of the resistive shunt. Thus the rotation is slight for small-amplitude signals (i.e.

for operating points near Q) for which the class-B stage presents a high resistance. The rotation increases however as signal amplitude increases and operating points move away from Q. Thus the a.c. load line has the elongated S shape shown as P'QR' in Fig. 6.

If a sinusoidal signal is assumed applied to  $Tr_1$  base it is possible to deduce from Fig. 6 the waveform of the corresponding collector current and voltage. The curvature of P'QR' is such that it can cause serious distortion of the collector-voltage waveform but this is not generally of importance because it is the shape of the current waveform

which matters and, provided the load line is reasonably steep, there is unlikely to be serious distortion of the current waveform. This is to be expected because a current amplifier should be presented with a low-value load. Such a load ensures that any load-value variations have negligible effect on the output current and that most of the current enters the class-B stage rather than  $R_c$ .

If a transformer is used to couple a class-B stage to the driver stage, the turns ratio can be adjusted to present the driver stage with a desired value of load resistance. As an example consider Fig. 7 which shows at P'QR' the load line representing the input resistance of a class-B stage. If the step-down ratio is doubled, the effective resistance at the primary winding is quadrupled and the driver stage is called upon to deliver twice the voltage swing and one half the current swing. The load line thus rotates anticlockwise about the quiescent point and its new position is at P'QR'.

**Elliptical load lines**

In linear amplification where transformers are used between cascaded stages it is normal practice to make the primary inductance so large that the reactance even at the lowest frequency is large compared with the load resistance. The effective load is then purely resistive and the load line is linear as described earlier.

Suppose, however, that the shunt reactance is not large and absorbs an appreciable fraction of the output current, or that an inductor is connected in series with a load resistor to extend the upper frequency limit as in a video amplifier. How does the reactance so introduced affect the load line?

To determine this consider Fig. 8 which shows the current-voltage relationship for a linear resistor initially free of associated reactance. It is assumed that the resistor is the load of a transistor and the voltage plotted along the horizontal axis is not the voltage drop across the resistor but the voltage at one end of it, e.g. the collector voltage of the transistor feeding the resistor. The other end of the resistor is assumed connected to the positive supply terminal. Thus an increase in the collector voltage means a decrease in the voltage across the resistor and a proportional decrease in the (collector) current through it. If the collector current varies sinusoidally as shown at abcde the corresponding collector voltage ABCDE is inverted with respect to it.

Suppose now that the resistor is shunted by an inductor with a reactance at the frequency in use of twice the ohmic value of the resistor. The sinusoidal current abcde flows in the resistor as before but there is now an additional current (in the inductor) which has half the amplitude of the resistive current and lags it by 90°. This reactive current is shown as a'b'c'd'e' in

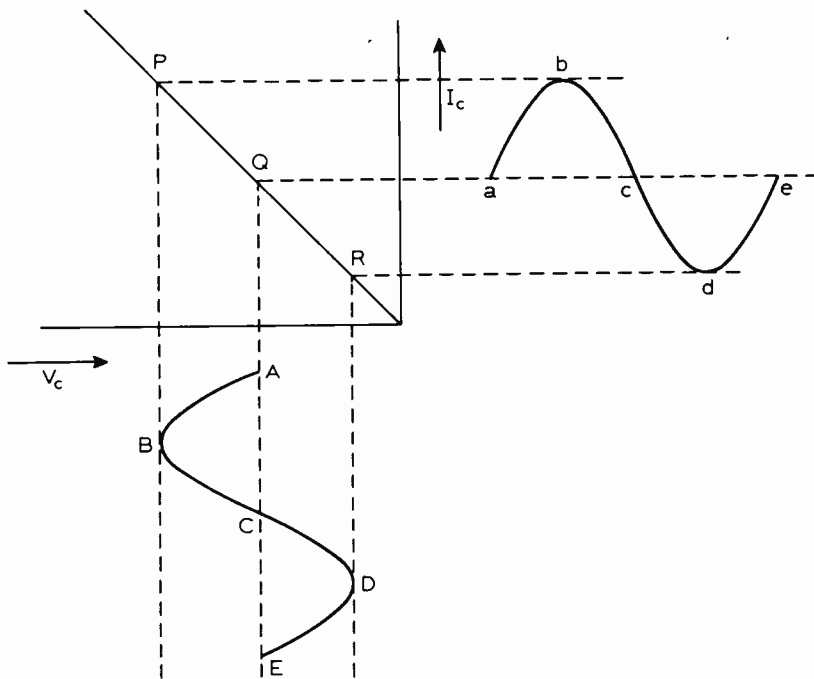


Fig. 8. Current-voltage relationship for a linear resistor.

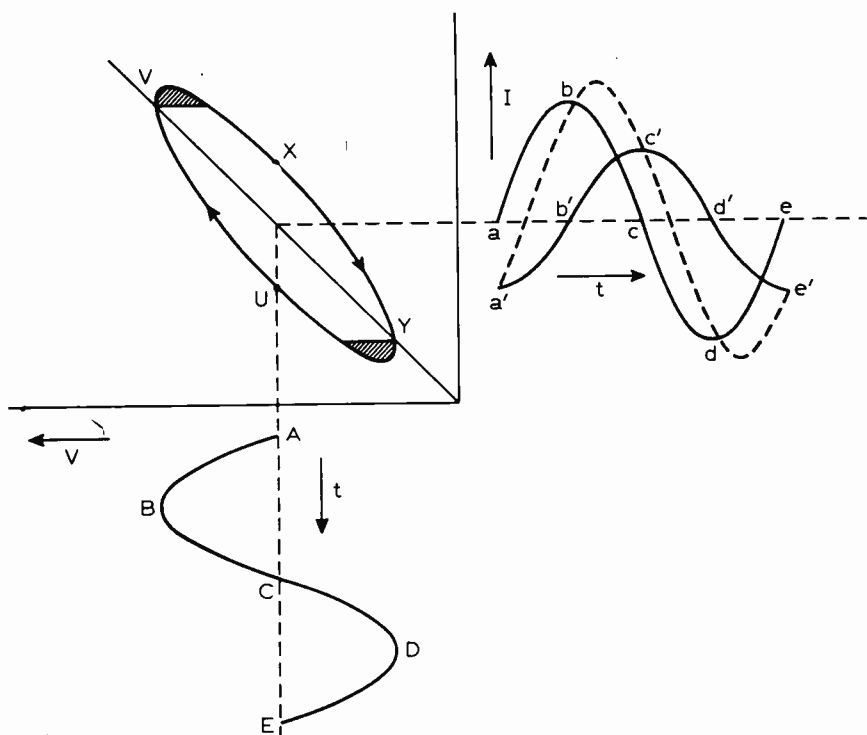


Fig. 9. Derivation of the elliptical load line for a parallel LR combination.

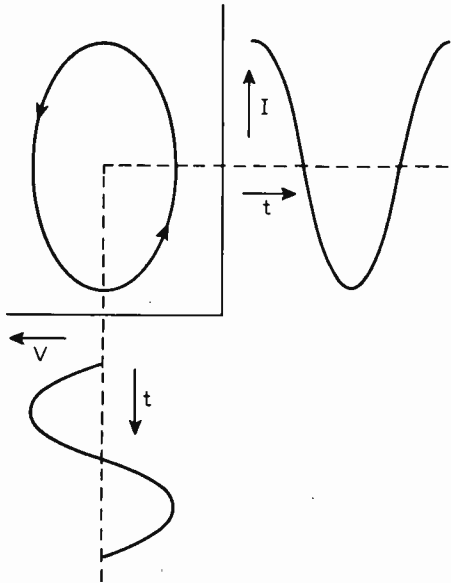


Fig. 10. A purely-reactive load has a load line in the form of a true ellipse. This ellipse and the associated current and voltage waveforms apply to a purely-capacitive load.

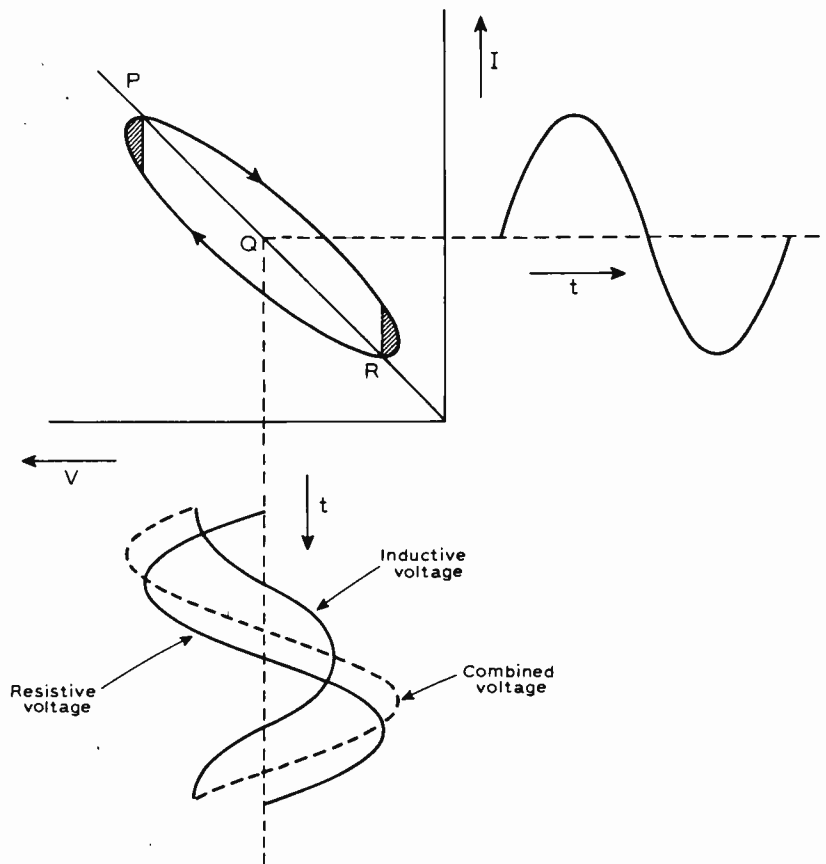


Fig. 11. Elliptical load line for a series LR combination.

Fig. 9. The current in the LR combination, i.e. the output current of the active device, is the sum of  $abcde$  and  $a'b'c'd'e'$ . If we take the datum line  $ace$  as representing zero current, the sum of  $a$  and  $a'$  is at  $a'$ . Similarly the sum of  $b$  and  $b'$  is at  $b$ . By continuing in this way we can deduce the shape of the waveform of the net current. It is shown in dashed lines  $a'bc'd'e'$  in Fig. 9 and is, of course, sinusoidal with a frequency equal to that of the voltage but phase retarded relative to the voltage. The amplitude of this current is in fact approximately 1.12 of that of the resistive current and is  $26.5^\circ$  retarded relative to it. We now know the waveform of the voltage across the LR combination and that of the net current through it. From this information we can deduce the form of the load line in the following manner. The current corresponding to voltage A is at  $a'$ : vertical and horizontal lines from these points meet at U which is therefore a point on the load line. Similarly the current corresponding to voltage B is at  $b$  giving point V on the load line. By continuing in this manner we obtain points X and Y and the next point is back again at U, showing that the load line has the form of an ellipse and that the operating point moves in a clockwise direction around the circumference of the ellipse at the rate of one revolution per cycle of signal.

The elliptical shape results from the interaction of two sinusoidal signals at the same frequency but with a phase displacement between them and can be demonstrated on an oscilloscope by applying the two signals to the X and Y plates: the ellipse is, in fact, one of the Lissajous figures.

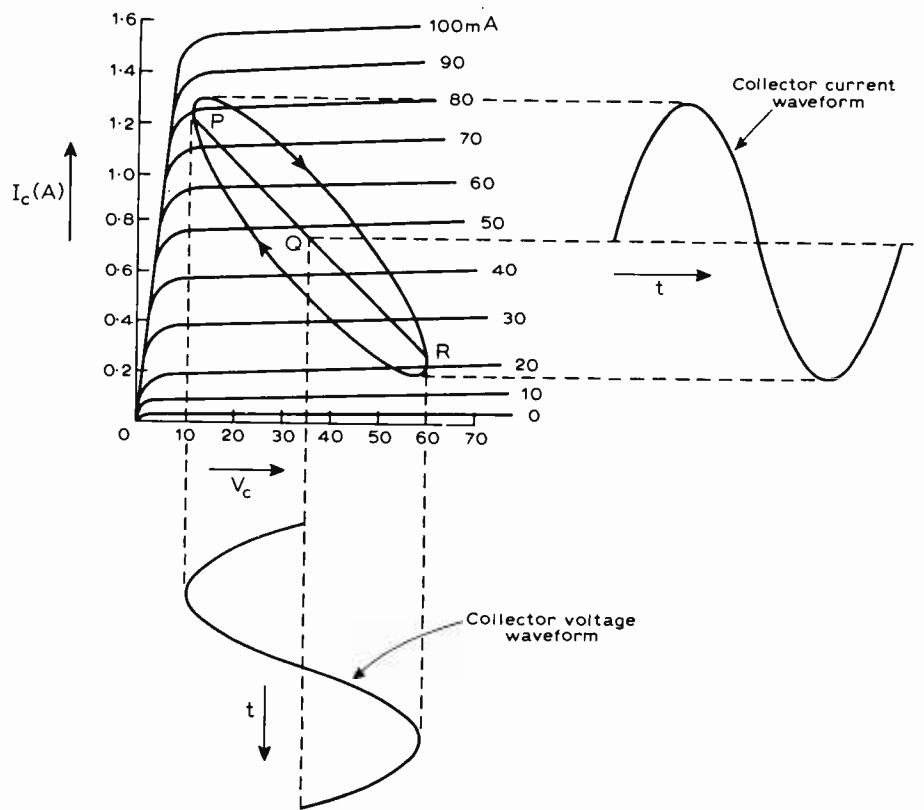


Fig. 12. An elliptical load line superimposed on a set of  $I_c - V_c$  characteristics.

The ellipse shown in Fig. 9 was for a parallel combination of resistance and inductance. For a parallel RC circuit the reactive current is phase advanced on the voltage but a similar elliptical load line results, the operating point this

time moving anticlockwise around the perimeter.

In a series LR combination it is the current which is common to the two components. As shown in Fig. 11 the voltage across the resistor is in phase

with the current; that across the inductor leads the current by  $90^\circ$ . The two voltages are added to obtain the net voltage across the combination and this, together with the current waveform, enables the shape of the load line to be deduced. It is again an ellipse and operating-point rotation is clockwise. A series RC combination gives a similar ellipse but the operating point moves anticlockwise around it.

The "fatness" of the ellipse, i.e. the ratio of the minor to major axis, depends on the phase displacement between the current and voltage in the load. If there is no displacement the ellipse becomes the linear load line VY in Fig. 9. If there is  $90^\circ$  phase displacement, as for a purely inductive or capacitive load, the ellipse has the form shown in Fig. 10. The major and minor axes are now vertical or horizontal and this is a true mathematical ellipse obeying the equation  $x^2/a^2 + y^2/b^2 = 1$ .\*. By suitable choice of scale for the current and voltage axes the major and minor axes can be made equal and the ellipse then becomes a circle. An elliptical load line such as that shown in Fig. 9 is a combination of a true ellipse (representing the reactive component of the load as in Fig. 10) and a linear load line (representing the resistive component of the load). An important point is that the ellipse is not symmetrical about the linear load line but is rotated slightly about the quiescent point in a clockwise direction for a parallel reactance/resistance combination and anti-clockwise for a series combination: thus the resistive load line does not coincide with the major axis of the ellipse.

The shaded areas in Fig. 9 represent the additional current which the active device has to deliver as a result of the reactive component of the load. The voltage swing is unaffected by the addition of the reactive component as would be expected for a parallel combination.

Fig. 11 applies to a series LR combination and the shaded areas here represent the additional voltage which the active device must deliver as a result of the addition of the reactance: the current swing is unaffected.

Curvature of load lines is usually associated with waveform distortion and it might therefore be expected that an elliptical load line (which has pronounced curvature) would also produce distortion. In fact, as shown in Fig. 9, it produces phase shift between the current and the voltage waveforms. This is perhaps clearer in Fig. 12 which shows the same elliptical load line superimposed on a set of  $I_c - V_c$  characteristics. For the particular reactance/resistance ratio chosen (2:1) the collector voltage is phase advanced on

the antiphase condition by  $26\frac{1}{2}^\circ$ . If the load line for a parallel reactance/resistance combination is known only as an ellipse the position of the linear load line representing the resistive component can be found by drawing two vertical tangents to the ellipse at its left-hand and right-hand extremities and by joining their points of contact. (For a series reactance/resistance combination the tangents should be horizontal and touching the upper and lower extremities of the ellipse). The reciprocal of the slope of this line gives the value of the resistance. This construction has been carried out in Fig. 12 and the linear load line PGR corresponds to a resistance of 50 ohms. The shunt reactance is 100 ohms. An input (base)

current swing from 13mA to 83mA gives a collector current swing from 0.15A to 1.25A. The corresponding collector voltage swing is from 60V to 10V. Although the current limits are 0.15A and 1.25A some of this is due to reactance (see Fig. 9) and the useful power output is provided by the swing between 0.2A and 1.2A, the current limits for the linear load line. The single-peak current and voltage values are thus 0.5A and 25V giving the power output as 6.25W.

This has been by no means a complete account of load lines: for example there has been no mention of load lines for push-pull amplifiers. It is hoped, however, that it has proved an interesting introduction to the subject.

## Wireless World amateur radio station

On January 29 *Wireless World's* amateur radio station went on the air. This club station, call sign G8LWW, is licensed to operate in the amateur frequency bands from 144MHz and above (conditionally up to 24GHz). Under the recently-modified licensing conditions this means that *Wireless World* is permitted to operate the modes of fixed, mobile, pedestrian mobile, r.t.t.y. (radio-teletype), television, slow-scan television, facsimile, data and d.s.b.s.c. (double-sideband suppressed carrier). This will also include satellite communications through the amateur satellites Oscar 6 and Oscar 7.

The decision to have a permanent station was made in order that *Wireless World* can participate, in the practical sense, in communications in the same way that it does in the electronics field through constructional projects. This is the first time the journal has had a permanent amateur radio station; the only other time that an amateur station operated from its offices was when *Wireless World* celebrated its 60th anniversary in 1971 with the station GB3WW operating under a special short-term licence (see May 1971 issue).

The station, whose "main address" is at

Dorset House, Stamford Street, London S.E.1, is situated at the top of a nine storey building at about 50m above-sea-level. In due course *Wireless World* intends to design and build its own equipment but until time can be found to carry out this project the station will continue to use tried and proven commercial equipment. Equipment presently in use in the 144 to 146MHz (2 metre) band is the Icom IC201 multi-mode transceiver which provides f.m., u.s.b., l.s.b. and c.w. modes. This 'rig', which uses a v.f.o. to give full 2-metre coverage, also has full facilities for repeater and reverse repeater, an automatic tone burst, break-in on c.w., and v.o.x. (voice-operated switching). The 10W output is fed into a ten-element crossed-yagi aerial mounted twenty feet above the roof of the building on a heavy-duty rotator, and connected for right-hand circular polarization (in preparation for satellite communication). The aerial apparatus and associated equipment was supplied by South Midlands Communications Limited. G8LWW is presently being operated by the licensee, Ray Ashmore, an assistant editor of *Wireless World*, whose own call sign is G8KYY. The station also has available an h.f. (3 to 30MHz) transceiver, the Yaesu Musen FT301, which has been operated from the *Wireless World* station by Ron Leath under his call sign G4ASE. This transceiver, which is capable of delivering the maximum permissible output of 400W, was used with a 40/80m trap-dipole and, after only three QSOs on 80 metres, made contact with SV4KS in Greece.

One disadvantage of the station location is a 31 storey building, part of the IPC complex, directly to the north and only about 100m away from the aerial. Although the effect that this building has on transmission and reception from and to the station has not yet been accurately determined, it represents a line-of-sight restriction of about 12 degrees, which will make contacts to the north of England and Scotland more difficult on 2-metres. However, it is hoped that the favourable "take-off" towards Europe will prove interesting, especially during the summer months when good v.h.f. propagation conditions will be more frequent.



\* This equation applies when the centre of the ellipse is the origin of the rectangular co-ordinate system.

# Metal detector

## B.f.o. circuit using fifth search oscillator harmonic for enhanced sensitivity

by D. E. O'N. Waddington, M.I.E.R.E.

**Metal detectors have fascinated people for a long time and a great many have been designed and built. Some work, but a high proportion have been abandoned as impractical by their disillusioned constructors. This article, in addition to giving the design for a practical metal detector, will explain some of the pitfalls and show how they may be circumvented.**

All the metal detectors known to me use the modification of the magnetic field associated with one or more inductors to locate metal. Three main types are made commercially; b.f.o., induction balance and pulse induction. I will confine my description to the b.f.o., since this is the simplest to implement and, provided that due precautions are observed, it is adequate for most purposes.

Before proceeding any further, however, I think that it is as well to look at some of the legal aspects of metal detectors. Since, under the terms of the Wireless Telegraphy Act 1949 they have been deemed wireless telegraphy apparatus, they come under the jurisdiction of The Home Office who, at present, requires that a licence should be obtained for the use of the detector. Currently, this is £1.20 and permits the use of a "pipe finder" for a period of five years. In addition, the frequency of operation is limited to the range from 16 to 150kHz, with a forbidden band from 90 to 110kHz. In practice, the preferred bands are 85 to 90kHz and 110 to 144kHz. Before a detector may be used it must be "type approved" by the Home Office. Needless to say, the circuit to be described has approval.

With regard to the use of the detector for "treasure hunting" it is as well to observe a few rules:

- Never prospect a known archaeological site. If you do, you will incur the undying wrath of the archaeological fraternity in addition to possibly destroying historical information.
- Report unusual historical finds to your local museum.

- If you find any gold or silver, report the find immediately to the police, who will inform the local coroner. He will hold an inquest to decide to whom the find belongs. (A study of the laws relating to 'treasure trove' will help you to understand your rights.)


- If you find unexploded ammunition or a bomb, mark the place, leave well alone and inform the police.

- Do not leave a mess after excavating your finds.

- The issue of a licence does not absolve the licensee from obtaining any necessary consent before entering on any private property with any apparatus.

The principle of the b.f.o. detector is illustrated in Fig. 1. The outputs of two oscillators, tuned such that there is a small frequency difference between them, are mixed. The difference frequency is selected by a low-pass filter, amplified and fed to a loudspeaker or headphone. When a metallic object is brought near to the search coil, its inductance changes causing a change in the frequency of oscillator 1 and a corresponding change in the difference frequency. Non-ferrous metals will cause the frequency of the search oscillator to increase and ferrous metals should have the opposite effect. I use the word "should" since, in practice, both the shape of the object and its state of decomposition appear

Fig. 1. Block diagram of a simple b.f.o. metal detector.

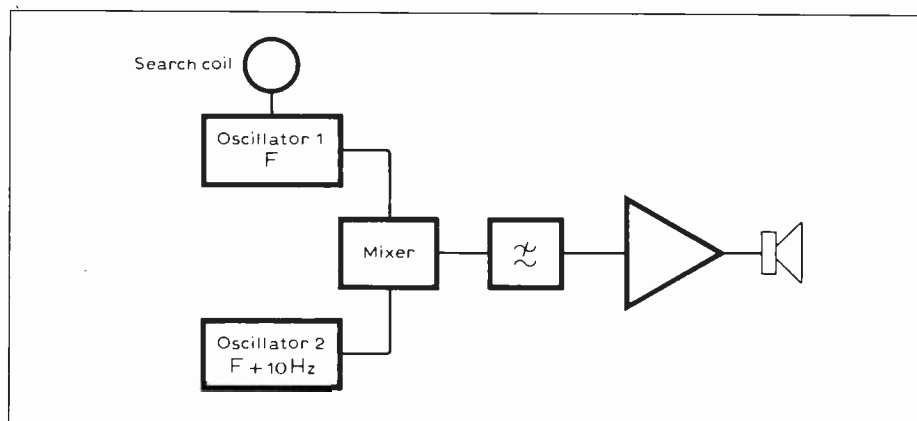

to affect the sense of the change. At first sight, it would appear a simple matter to apply this principle to a practical metal detector but there are a number of problems which need to be overcome before a satisfactory design can be achieved. The first of these concerns the search coil.

The frequency of oscillation will change if the reactance of the coil changes at all. Thus it is as susceptible to capacitance as to inductance changes. Indeed the change in coil capacitance caused by moving it relative to the ground may well exceed the inductance change caused by the object being sought. Fortunately, it is quite easy to minimize this effect by fitting a Faraday screen to the coil. This is done by wrapping the coil with a conductive foil, which is connected to the internal "earth" of the oscillator. There should be a break in the foil so that it does not constitute a short-circuited turn. When I first tried this out, I feared that it would reduce the sensitivity of the coil to metallic objects but measurements showed that the sensitivity was unchanged, while capacitive effects were reduced to negligible proportions. Another cause of spurious frequency change is heat: moving the coil from sunlight to shade can cause a large and fairly rapid frequency change. This effect can be reduced by suitable thermal insulation.

In order to select the best size of coil for the detector I made a series of tests plotting the frequency change caused



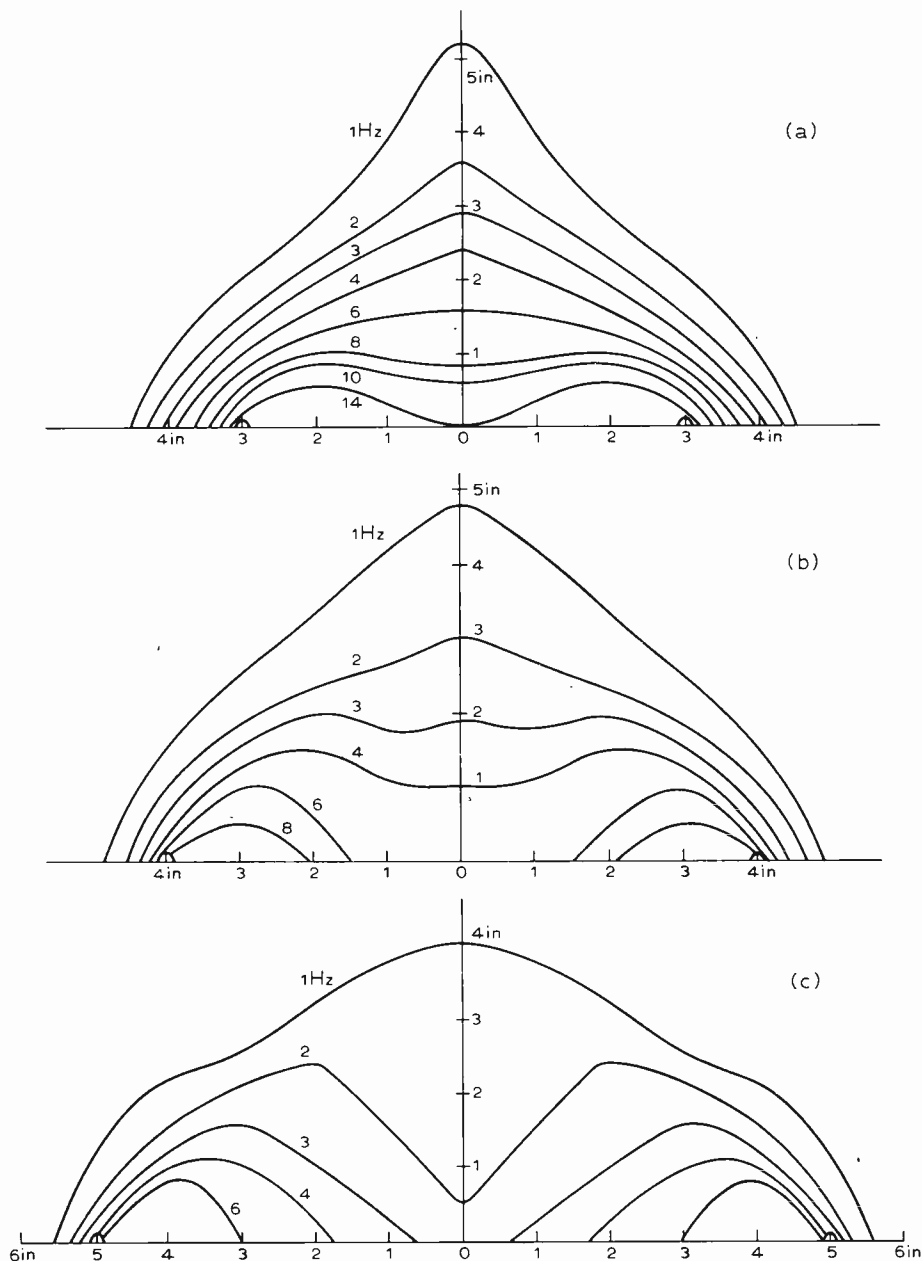


Fig. 2. The lines show the contours of equal frequency change for a 1/2p coin at a frequency of 100kHz with various coil sizes (a) 6" (b) 8" (c) 10"


by a 1/2p coin with various coils. The inductance of the coil does not appear to be an important factor, but the diameter is. The results for 6in, 8in and 10in coils are shown in Fig. 2. They may not be strictly accurate, since the measurement is a very tedious one, but they do show what is to be expected. The important points are:

- The frequency change is very small.
- The sensitivity at the centre of the smaller coils is much the same, while the 10in coil is less sensitive.
- The larger the coil, the larger the sensitive area. However, this is not always an advantage, since it is still necessary to pin point the article being sought and the smaller coil gives a much better "focus". For my own design I have chosen the 6in coil.

The magnitude (or should I say smallness), of the frequency change is

one of the main problems in using a b.f.o. metal detector. One very practical solution is to set the oscillator frequencies such that the frequency difference is very small  $< 10\text{Hz}$ . When this is done a change of one or two hertz is readily discernible. If the frequency difference were of the order

Fig. 3. Block diagram of an improved metal detector.

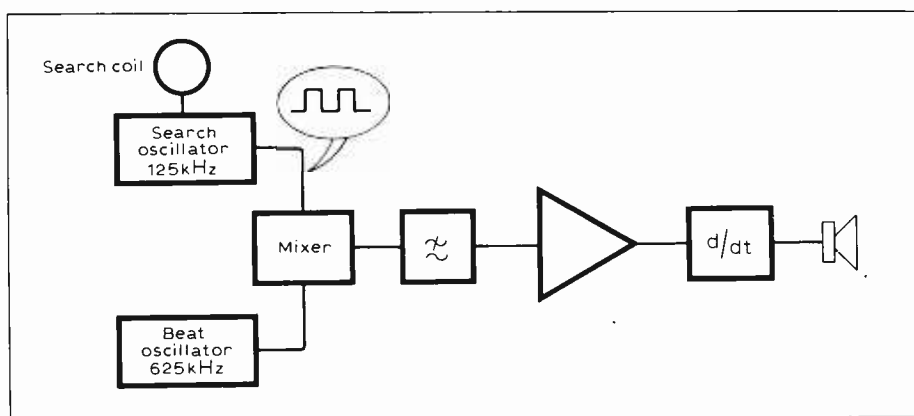

of 250Hz this change could only be heard by a trained listener. Since a normal loudspeaker or headphone does not reproduce low-frequency tones, the low frequency waveform can be converted into a pulse train, which is then easily reproduced.

The sensitivity of the b.f.o. can be increased as shown in Fig. 3. Here the search coil oscillator is operated at a frequency of 125kHz and its output is converted to a square wave, which is rich in harmonics. The beat oscillator runs at a frequency of 625kHz, i.e. five times the search oscillator frequency. Thus, the beat oscillator is mixed with the 5th harmonic of the search oscillator so that any frequency change is multiplied by five. This makes it very much easier to hear a change in frequency, although the susceptibility to drift is much greater. A higher harmonic could be used but it should be remembered that, with a square wave, only odd harmonics are present and the amplitude of the harmonic will be equal to the amplitude of the fundamental divided by the harmonic number. The rather odd choice of frequencies has been dictated by the fact that most constructors will only have a medium-wave radio receiver for setting up purposes and will have no simple means of checking the frequencies. If the beat oscillator is set to 625kHz, the beat note will only be heard strongly if the search oscillator is tuned to an odd sub-harmonic ( $625/5 = 125$  or  $625/7 = 89.286$ ) and the forbidden band from 90-110kHz will be avoided. This precaution is necessary as it is difficult to control all the stray capacities associated with the search coil.

### Design

The circuit of a metal detector based on the above considerations is shown in Fig. 4. I chose the "long-tailed-pair" oscillator for this application because it is easy to design, the tuned circuit needs only two connexions and the output is isolated from the tuned circuit so that the frequency of oscillation is virtually unaffected by loading or signals fed to the output. This last is particularly important for this application, in which it is essential that the oscillators do not lock to each other when the frequency, or in this case, harmonic frequency

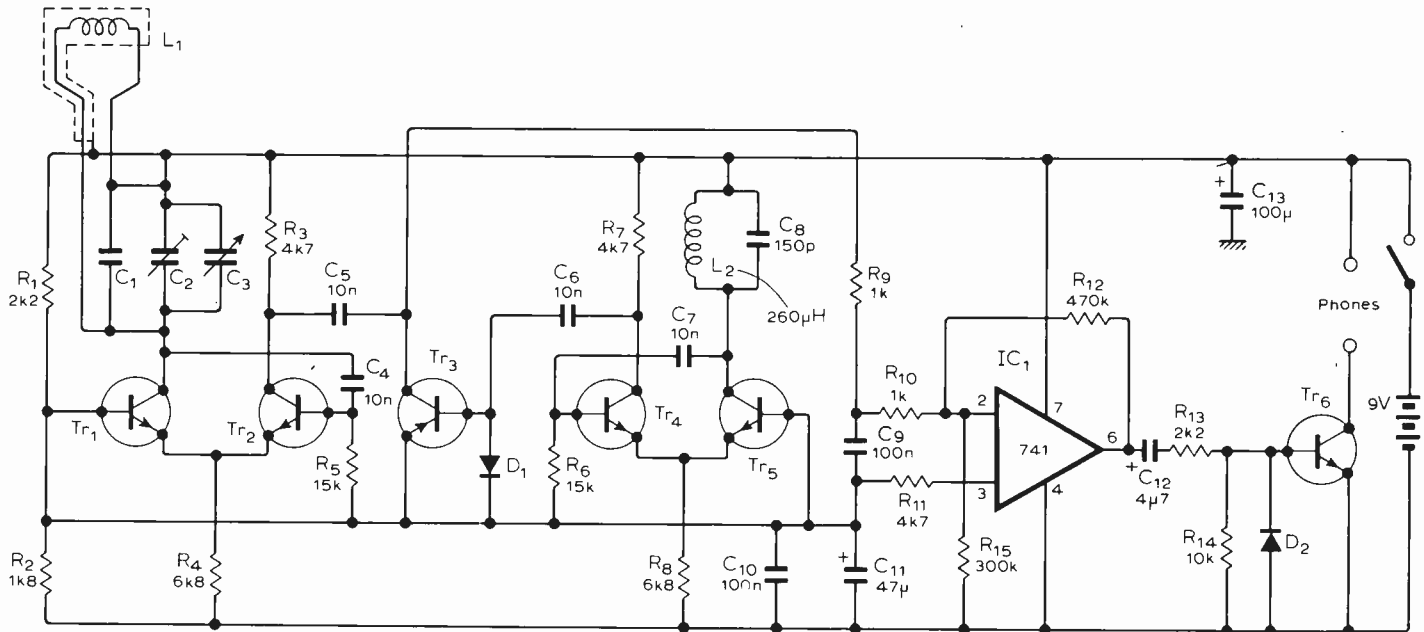


Fig. 4. Circuit diagram for metal detector.

difference is small. The search oscillator uses  $Tr_1$  and  $Tr_2$  with  $L_1$ ,  $C_1$ ,  $C_2$  and  $C_3$  forming the tuned circuit. It will probably be necessary to select  $C_1$  to give the correct frequency, since the Faraday screen and the screened lead add an indeterminate amount of capacitance in parallel with the coil. This capacitance depends upon the physical construction of the coil and the materials used and is rather variable. Coarse tuning is carried out by  $C_2$ , while  $C_3$  is used for fine adjustment. The search oscillator output is taken from the collector of  $Tr_2$  to the mixer  $Tr_3$ . The beat oscillator uses  $Tr_4$  and  $Tr_5$ ;  $L_2$  and  $C_8$  form the tuned circuit, which resonates at 625kHz. The drive to the shunt gate mixer  $Tr_3$  is taken from the collector of  $Tr_4$ . The difference frequency is selected by the low-pass filter, formed by  $R_9$  and  $C_9$  and is amplified by  $IC_1$ , differentiated and then fed to  $Tr_6$ , which drives the phones or loudspeaker. The volume can be controlled by connecting a variable resistor in series with the output.

**Construction**

The layout of the circuit does not appear to be critical - a practical version using matrix board is shown in Fig. 5. Mount the circuit inside a screened box so that hand capacitance does not affect the tuning.

The construction of the search coil is very important. It should be sufficiently robust to withstand rough handling, light, so as to be portable and adequately insulated against temperature change and moisture. I found that the construction shown in Fig. 6 works very well. First cut a ring of about 3/8in plywood as shown. To wind the coil, draw a 6 1/4in diameter circle on a piece of wood. Hammer 3/4in panel pins at about 1in intervals around this circle and then

wind 45 turns of 26 s.w.g. (0.46mm) wire around the pins. Tape the coil in four places to stop it springing undone. Remove the pins. Tape the coil tightly to the underside of the wooden ring, taking care that the ends of the winding come opposite to the tab for the handle. Cover the coil with a second layer of tape. Cut a strip of aluminium cooking foil about 1in wide and tape the coil with it, starting on one side of the tab and finishing at the other. It will probably be necessary to use more than one length of foil, in which case the ends should be overlapped. However take care that the start and finish of the coil do not short to each other. Bind the finish of the coil with 22 s.w.g. tinned copper wire and connect it to one end of the coil and to the screened lead. The other end of the coil is connected to the centre conductor of the screened lead. Cover the coil with a layer of tape. Cut a 1in wide strip of 1/8in thick expanded polystyrene sheet


and wind this around the coil. Cover the whole with another layer of tape. Assemble the coil to the handle and paint it with white waterproof paint.

**Setting up**

The first step is to set the beat oscillator to the correct frequency.

- Short the search coil to disable the search oscillator.
- Switch on and adjust the core of  $L_2$  so that the frequency of the beat oscillator is set to 625kHz. If you have no access to a frequency counter, a medium wave radio receiver may be used. Set the dial of the receiver to 625kHz (480m). If the receiver has an aerial connection, place the aerial lead close to the oscillator, but if it only has a ferrite rod aerial it will be necessary to place the receiver close to the oscillator. This setting up must be carried out with the detector circuit mounted in its screened box with the lid off. Tune for maximum signal. Remember that you will be looking for an

Fig. 5. Layout of circuit, using pin board (no copper tracks).

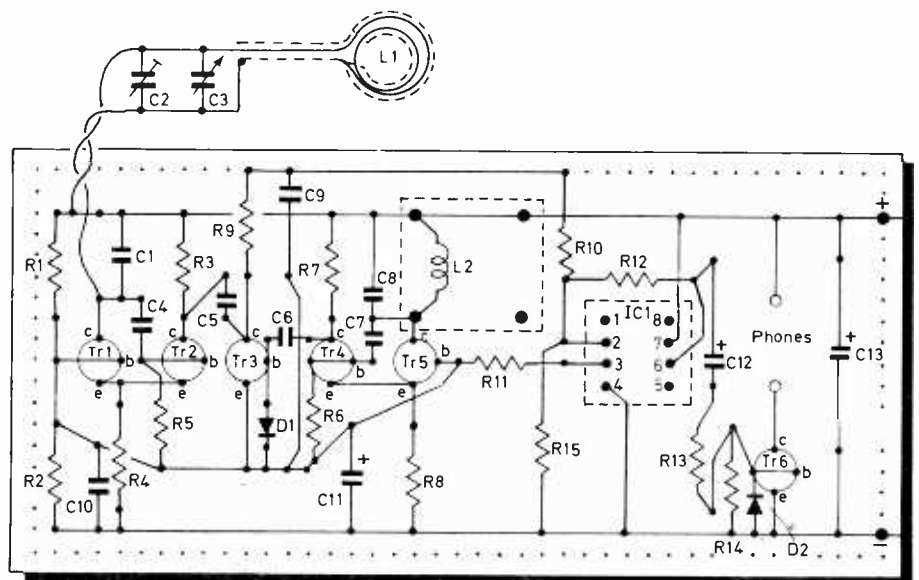

# HF predictions

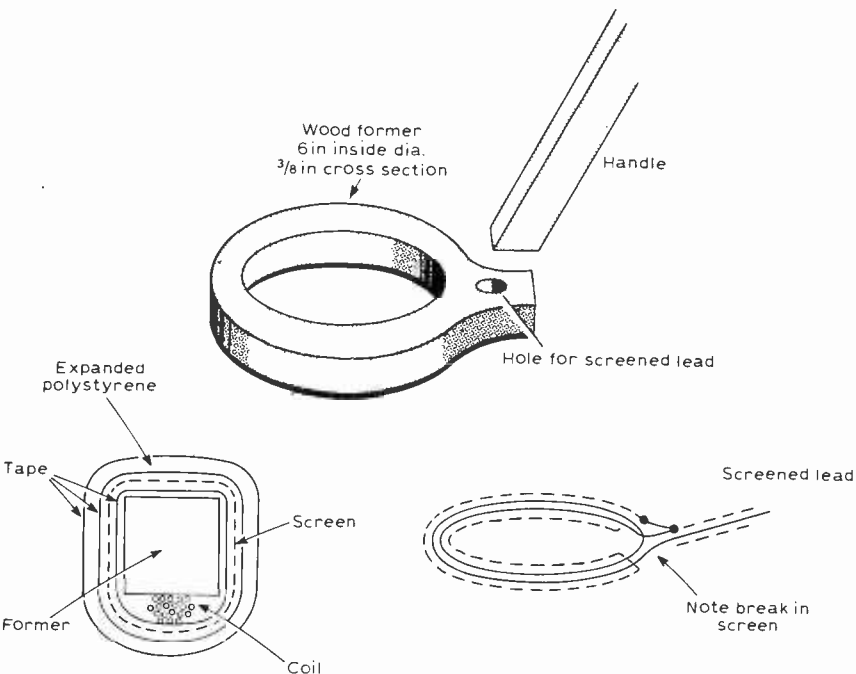


Fig. 6. Coil construction.

unmodulated carrier, so that only hiss will be heard. However, you can check whether you have the correct carrier by shorting the coil. The next step is to set the search oscillator to the correct frequency.

- Remove the short from the search coil.
- Set both the coarse and fine controls to mid-travel.
- Fit a 470pF capacitor for  $C_1$ .
- Adjust  $C_2$  and check that a beat note can be obtained. If necessary increase the value of  $C_2$  by 100pF.
- When a beat note is heard, check the frequency of the search oscillator as follows:

(a) Short the beat oscillator tuning coil.  
 (b) Using the receiver near the search coil, look for the harmonics of the search oscillator which should be as shown in Table 1. It is very probable that you will only be able to identify the odd harmonic frequencies.

(c) If the frequencies are too close together, the search oscillator will probably be running at 89.3kHz. Reduce the value of  $C_1$  and repeat the procedure. If possible it is a good idea to select a value of  $C_1$  which gives the correct frequency with  $C_2$  set to mid travel. This will allow for any drift which may occur during the life of the detector.

Table 1

Harmonic Number	Frequency	Wavelength
5	625 kHz	480 m
6	750 kHz	400 m
7	875 kHz	342.85 m
8	1000 kHz	300 m
9	1125 kHz	266.67 m
10	1250 kHz	240 m
11	1375 kHz	218.18 m
12	1500 kHz	200 m
13	1625 kHz	184.615 m

**PARTS LIST**

**Resistors**

- 1 2k2 All resistors 1/4W ±5%
- 2 1k8
- 3 1k
- 4 6k8
- 5 15k
- 6 15k
- 7 1k
- 8 6k8
- 9 1k
- 10 1k
- 11 4k7
- 12 470k
- 13 2k2
- 14 10k
- 15 300k




**Capacitors**

- 1 560pF polystyrene (see text)
- 2 150pF variable
- 3 10pF variable
- 4 0.01µF disc ceramic
- 5 0.01µF disc ceramic
- 6 0.01µF disc ceramic
- 7 0.01µF disc ceramic
- 8 150pF polystyrene
- 9 0.1µF 100V P.E.T.
- 10 0.1µF 100V P.E.T.
- 11 47µF 10V electrolytic
- 12 4.7µF 10V electrolytic
- 13 100µF 10V electrolytic

- $Tr_1$  2, 4, 5, 6 BF238, BC108 or equivalent
- $Tr_3$  BC308, BCY72 or equivalent
- $D_{1,2}$  1N4148
- $IC_1$  LA741C
- $L_1$  see text
- $L_2$  49t 0.28mm wire or Mullard Vinkor LA1157 (260-H)

Predicted disturbed days are 1st to 3rd and 17th to 24th of the month.

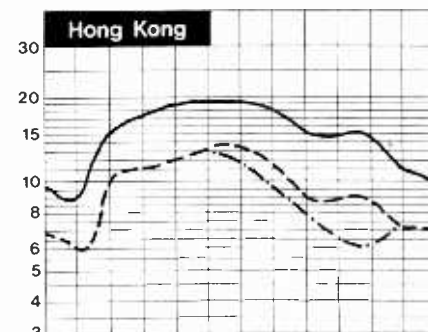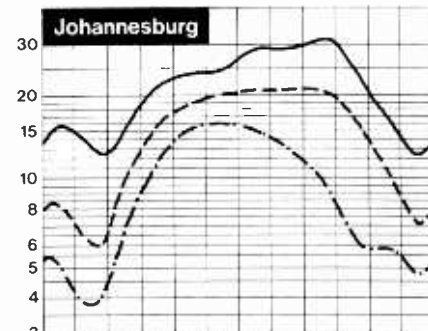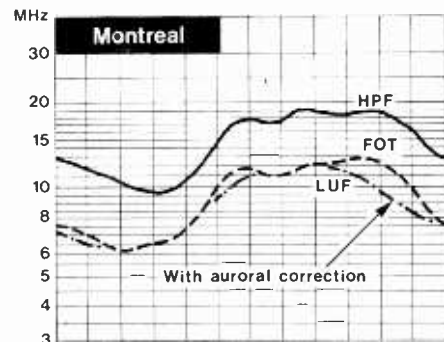Seasonable trend and low solar activity combine to produce FOTs and LUFs which give a restricted choice of time and frequency for reliable day to day communication. The charts show that this restriction is particularly severe for circuits having both terminals in the northern hemisphere.









# The new Maplin Catalogue is no ordinary catalogue...

**Hundreds of fascinating new lines**

**Several major new projects to build**

**MAPLIN ELECTRONIC SUPPLIES**

**BATCH SAVINGS!**

**SUPERSONIC SAME DAY SERVICE!**

**QUALITY COMPONENTS FAST!**

**HUNDREDS OF FASCINATING NEW LINES**

**Several major new projects to build**

**Integrated Circuit Pocket Book**

**Television Servicing Handbook**

**110**

**Hi-Fi**

**Radio Electronics**

The book section contains over 150 titles of books about electronics, radio, TV, Hi-Fi etc. Browse through the pages and choose from some of the best titles around including a superb set of books that will teach you electronics by experimentation! (foot of catalogue page 142)

**HUNDREDS OF PHOTOGRAPHS AND ILLUSTRATIONS**

**Super Discount Scheme - saves you pounds!**

Pages 59 to 61 of our catalogue show you our range of Veroboards and S-Decos or if you prefer to make your own pcb's a range of etching systems including the novel Dato etch-in-a-bag system, plus printed circuit transfers for that professional finish to your boards.

SEND THIS COUPON FOR **YOUR** COPY OF OUR CATALOGUE ON APPROVAL! Price 50p - SEND NO MONEY NOW.

Please rush me a copy of your brand new 1977/78 catalogue by return of post. Only if I am completely satisfied that it is worth every penny, will I send 50p within 14 days of receipt. If I am not satisfied, I may return the catalogue to you within 14 days without obligation. I understand that I need not purchase anything from your catalogue should I choose to keep it

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

\_\_\_\_\_

\_\_\_\_\_

Maplin Electronic Supplies P.O. Box 3, Rayleigh, Essex, SS6 8LR

**DON'T DELAY  
POST COUPON NOW  
IT COULD BE THE BEST 50p YOU'VE EVER  
SPENT**

Catalogue includes a very wide range of components: hundreds of different capacitors; resistors; transistors; I.C.'s; diodes; wires and cables; discotheque equipment; organ components; musical effects units; microphones; turntables; cartridges; styli; test equipment; boxes and instrument cases; knobs, plugs and sockets; audio leads; switches; loudspeakers; books; tools - **AND MANY MANY MORE.**



\* Our bi-monthly newsletter keeps you up to date with latest guaranteed prices - our latest special offers (they save you pounds) - details of new projects and new lines. Send 30p for the next six issues (5p discount voucher with each copy).

# MAPLIN

**ELECTRONIC SUPPLIES**  
**P.O. BOX 3, RAYLEIGH, ESSEX SS6 8LR**

Telephone: Southend (0702) 715155  
Call at our shop 284 London Road, Westcliff-on-Sea, Essex  
(Closed all day Monday) Telephone Southend (0702) 47379

# News of the Month

---



---

## CEI split again

---



---

The Council of Engineering Institutions has attacked the government's believed intention to hold an enquiry into the engineering profession. Sir Charles Pringle, the chairman, has told the Prime Minister in effect that such an enquiry would cause a further period of uncertainty just as the CEI was sorting itself out after its two years of dissension. But although at least half a dozen of the CEI's 15 members are said to share Sir Charles Pringle's objections to an inquiry, among the larger institutions there is a feeling that Sir Charles has spoken out of turn. All the signs are that yet another big row is brewing.

The CEI reached their attitude after a council meeting on February 10. They say that in opposing the enquiry they were reflecting the IEE and the IMechE though these bodies had also said that if there were an enquiry they would want it to include certain topics. The CEI say their attitude is that an enquiry is unnecessary but that they would cooperate if one were held.

It appears, however, that the two senior institutions take a more positive attitude to the putative inquiry. On 27th January they wrote to Mr Eric Varley saying that they would welcome it, and that it should cover: the education and training of engineers; how that education met the needs of industry; a study of compulsory registration in other countries; a study of how compulsory registration might be applied in the UK, and the allocation of certain jobs in industry to professional engineers.

The CEI say publicly there is merely a difference of emphasis between themselves and the IEE and IMechE, but we are told reliably that the CEI sent a letter to the two institutions, after they sent their letter to Varley, asking for an open apology for putting forward their point of view outside the auspices of the Council. From the other side, the dissenting Institutions have been so angered by the CEI's public pronouncements that they would now like the enquiry to review the CEI itself.

---



---

## Radar simulator for the RAF

---



---

A simulated timebase and echo generator (STEG) is to be added to the airborne early warning mission trainer at RAF Lossiemouth. The STEG will generate fifteen controllable radar targets on the AEW trainer displays as well as "own" aircraft movement, sea clutter, Indicate Friend or Foe, thermal noise and a blind arc. The simulator, which is portable, can also superimpose radar echoes on to a background picture derived from a video recording of an actual mission. Operators learn to spot unidentified radar echoes and to guide interceptor aircraft on to the intruders.

Four hand-held keyboards are connected to the simulator by flexible leads. The keyboards first set the STEG to match the radar parameters and then to set up and control the targets and other effects. Marconi, who make the device, say the system is one of many applications of STEG, which can be coupled to any continuously rotating pulse position indicator radar display via an interface.

---



---

## Components helped again

---



---

Electronic components is one of the five industrial sectors singled out by the Chancellor of the Exchequer, Denis Healey, and the Industry Secretary, Mr Eric Varley, for special help as part of an experiment "to see whether there is scope for the government to act as a catalyst in bringing about, in concert with both sides of the industries concerned, a more rapid improvement in performance. . . ."

Because each industry sector is different the approach will be different in each case, but Healey and Varley say in their memorandum to the National Economic Development Council, responsible for bringing together the necessary elements to the working of the Government's industrial strategy, that "One possible approach would be to begin in the case of each sector with a general wide-ranging meeting with both management and trade unions in that sector together with the members of the Sector Working Party, under the chairmanship of the appropriate minister. This meeting would identify the main issues to be tackled. Thereafter, we envisage that it would be useful to hold discussions with individual firms or, if particular subjects lend themselves to more broadly based consultations, with groups of firms, to pursue these issues." Companies would be asked for their views, particularly on

the sector working party reports but also on the whole range of Government policies.

An element of the Government's as yet vague proposals especially welcome to the components chiefs will be that although in the current economic circumstances resources are limited, "to the extent that public money is needed to solve the problems of the five sectors set out above (or those of other sectors) or, indeed to push forward the work on industrial strategy generally, the resources will within reason be available."

The proposals also follow news of a £20 million aid scheme for the components industry, which *Wireless World* reported last month. Still further help is expected from the European Commission (see WW News, March p48).

---



---

## Students for industry

---



---

Sponsored students may get an extra £500 a year from their employers without a reduction in the local authority grant under a scheme outlined by the Education Secretary, Mrs Shirley Williams, in the Commons on February 3. From September 1977, she said in a written reply, "payments by employers to students whom they wish to sponsor, or by institutions who wish to give scholarships of up to £500 per annum will not be taken into account in the assessment of mandatory awards by local education authorities. This will be in addition to the amount of income disregarded under the present arrangements which is £185 per annum and now under review for the academic year 1977/8."

At present a local authority, in assessing a student's income for making a grant, does not take into account the first £185 per annum of income, any holiday earnings, or various pensions and benefits. Later in the year changes in the rates and conditions applying to mandatory awards, including the £185, will also be announced.

Currently about 7,200 undergraduate students and 2,600 postgraduates are fully supported by employers rather than by a grant. About a third are supported by industrial or commercial concerns and the rest by Government departments. Normally an employer makes a choice between giving a student £185 on top of his grant or paying him a salary greater than the grant would have been. About 400,000 students in Britain receive grants totalling £382 million, according to the Department of Education and Science, though this includes a controversial £107 million supplied by parents or spouses. In 1974-75 a Department survey showed that about half the students on mandatory grants did not get all the parental contribution, or £90 for each student underpaid.

---



---

## Bullock's boardroom and the engineer

---



---

Lord Bullock himself has acknowledged that the proposals the majority of his committee agreed after a year's work may never be carried out. But he is not discouraged. The vigour of the debate since his report was published on January 26 has shown that the call for greater involvement of workers in company policy decisions which affect them has suddenly become a political issue. It is likely to remain so.

Among those who gave evidence were the Association of Professional Scientists and Technologists, the Business Equipment Trade Association, the CEI, the Electrical, Electronic, Telecommunication & Plumbing Union, EMI, GEC, Philips Electronic and Associated Industries, and the United Kingdom Association of Professional Engineers. The EETPU expressed the strongest opposition to the representation of trade unions on the board because they saw a conflict between collective bargaining and such representation: "It is not the responsibility of work people to manage the enterprise . . . It is essential that trade unions retain their independence." The EETPU thought that the job of the trade unions was, through collective bargaining, to "consider, contest and oppose, if necessary, the exercise of managerial prerogatives," but Bullock, unimpressed, says unions and management "have the same objective: to enable employees to participate in decision-making in the enterprise in which they work."

Reading the report makes you no wiser about the future role of the engineer, the scientist or the technician in the proposed new democratic boardroom. It is a fact of modern industrial organisation, however, that their skills and experience are badly needed.

Most of what Bullock says that is relevant to engineers is about middle management.

### Staff associations count

"Some people have suggested to us that managers and other professional groups play a particularly important role in the running of companies and often occupy a unique position between the board and other employees – at one point representing the company in discussions with employees and at another being employees themselves – and they have argued that a special seat on the board should be reserved for these groups. Provided that professional and managerial employees are organised collectively, as increasingly many of them are, we can see no reason why they should not be represented on the board amongst the employee representatives. But we do not think that a special seat should be reserved for them on the board by law." Bullock explains that it would be unfortunate to

give the impression that some employees had a special, and therefore higher, status in the eyes of the law.

Bullock adds that there is no objection to a staff association or professional association or any other employee organisation not affiliated to the TUC from being represented on the board provided it is independent of the company but recognised by it.

### Trade Unions

So if the Bullock proposals are implemented the degree to which technicians and engineers will be able to contribute to the better running of their companies will be largely dependent on the extent to which they are involved in trade unions. The Confederation of British Industry has made clear its bitter opposition to Bullock on just these grounds, saying that trade unions speak for only half the workforce. The true picture is, however, a great deal more complicated than the CBI makes out. Trade union membership is not distributed evenly throughout industry, and the smaller the firm the less likely it is to be unionised.

Of the total workforce, it is true, 50.4% are members of a union. But in manufacturing industry membership is 62%, and if enterprises with less than 200 workers are left out of account the proportion jumps to 89%. In the Post Office and telecommunications the figure is 87.9% and in metals and engineering 69.4%. Bullock's proposals, if adopted, would only affect enterprises employing more than 2,000. In the others, according to Bullock, trade unions represent only 20% of the workforce, and it is because of this that these firms have been excluded from the proposals.

Against that, these smaller companies represent 11 million of the 18 million people employed in the private sector, and two thirds of the total number of enterprises. It seems true that small firms are becoming less important – the 1968 census of production showed that firms with over 2,000 employees then represented only 21% of the enterprises – but it also seems that the Bullock idea is not to extend industrial democracy to workers in the small firms, where the majority of work is done. The CBI has not been heard to complain about that.

### Unionised engineers

On the other hand, trade unionism is still a more potent force among the wearers of blue than white collars. The qualified engineer is generally regarded as a white collar worker and as such if he is a member of a union, he is one of 4.3 million, whereas his manual union colleague is one of 7.5 million. Engineers, therefore, stand less chance than manual workers of getting into the boardroom if Bullock is adopted. But the report also notes the increasing rate at which white collar workers have joined trade unions. Since 1948, union membership among white collar

workers has increased 117%, while manual union membership has increased 0.1%. In the four years to 1974 union membership among manual workers actually fell 1.3% but rose 19% among those off the shop floor.

### The 'Y' element

For the moment, a much more likely opening for engineers lies in the proposal that a third element should balance the shareholder and union representatives. This third element, the Y in the now famous 2X + Y formula, has to be an uneven number greater than one, must be less than a third of the whole board and its membership must be agreed by the other two elements. The system, says the report "will provide an important means by which special experience and expertise can be brought into the boardroom from *inside and outside the company* . . . It may be, for example, that there will be someone in the company itself – among senior or middle management – who both sides agree could be a useful addition to the board."

### The industry view

The electronics industry has identified itself with the CBI's view of Bullock. The Electronic Engineering Association told *Wireless World*: "Our input on that will be done through the CBI." Latest figures are not available but a quick check of 39 of the companies in the EEA shows an average number of employees of around 9,6700. Many of these are companies with a large number of subsidiaries with activities across the whole range of electronics. A council meeting of the British Radio Equipment Manufacturers' Association on February 10 decided that the attitude of many of their members would be decided by parent companies here or abroad, many of them in the EEA.

### Size of firms

According to figures for the third quarter of 1976 at the Business Statistics Office at Newport, 48 enterprises in telegraph and telephone equipment employ 73,100 people; 252 enterprises in radio and electronic components employ 126,700; 37 computer firms employ 44,300; and 132 firms in radio, radar and electronic capital goods employ 90,400. No figures are available for the number of employees in the broadcast receiving and sound reproducing equipment sector.

### Does it matter?

Membership of the EEC, for which the CBI must hold itself largely responsible, commits us to some form of worker participation in the boardroom. However, the National Enterprise Board has, since the report was published, dropped its commitment to putting worker directors on its board, and the Prime Minister agreed with the CBI in February that the Bullock proposals need not be implemented as long as there is greater consultation below board level.



## V.m.o.s. devices "middle of this year"

American Microsystems (AMI) say devices which use their patented v.m.o.s. technique will be available commercially around the middle of 1977. "We are currently in the process of bringing them into production," said AMI's president and chief executive Glenn E. Penisten at a press conference in February.

He described the device as a "short channel n.m.o.s. structure fabricated in v-shaped grooves which entered the silicon surface." Advantages included vertical current paths, higher current density, and higher gain bandwidth than was possible with other devices. It was possible to get 285 dies from each 3in wafer of silicon with a side length of 145 mils each. In line with the general tendency for a reduction in the memory cell area per bit, such devices could be used to store 16kbits of information and this could be increased to 65k "before 1980". Mr Penisten told *Wireless World* that the speed of the devices was "approaching bipolar speeds, the 40ns kind of category." AMI also say the speed is less dependent on temperature change, and could work well at "enhanced ambient temperatures of 70°C." Although others might be producing discrete products using the technique AMI were further ahead, they say, in optimising "the speed/power relationships." It had been thought that v.m.o.s. was a dead-end technology because it could not be scaled (reduced in size to lower silicon consumption), but, said Penisten, that was wrong. "Our product is a product that has been scaled and scaled again." The first commercial product, a 1K static memory would be available "probably by mid-year."

## Goldring falls with the pound

A receiver was appointed on February 3 for Goldring, which in 1973 was trading so strongly that it offered 1.5 million 10p shares at £1.17 each and closed the offer oversubscribed. The day before the receiver, Mr Christopher Morris of Touche Ross, was appointed they were down to 8p.

Goldring was heavily dependent on the home market. About 85% of its business was in the UK, according to the *Financial Times*, and this had a number of effects. The first was that when VAT was increased to 25% they suffered more than firms like Garrard, which now exports something like 70% of its output. At one time Goldring stopped producing almost completely and relied on selling Swiss Lenco turntables, for which they had an agency. Another effect was that when

the pound started to fall this Lenco equipment became uncompetitive in the market they relied on.


Another blow was that Lasky's stopped selling Goldring equipment when the Japanese put the marketing pressure on direct-drive turntables. While a belt-driven model might have withstood this, Goldring's rim-driven turntables were too far behind the times. They could not rely on the kind of business BSR had so successfully built up, supplying turntables for fitting to other sound systems. BSR turntables can even be found in audio systems imported from Japan, as in the case of Crown, now imported by York Electronics. Goldring also imported Toa public address equipment, which had been affected by import restrictions.

To add to everything else Goldring's premises at Leytonstone were compulsorily purchased by Walthamstow council, and they were faced with the disruption and cost of moving to Bury St Edmunds, still a matter of dispute with Walthamstow council. Cost control was not too strict, and they spent £100,000 there in offices alone, according to one account. Although staff had been reduced from 298 to 179 during 1975, effecting a reduction in the wage bill from £466,772 to £427,622, directors fees went up around £200 to £46,629. In the same year, the Barclay's bank overdraft jumped from £3,650 to £160,746, and the company borrowed a further £200,000 from the family of Mr E. Sharf, the president.

According to an informed source the receiver has now recovered the money owing to Barclay's and it now remains to get back the Sharf money, after which the future of the company seems grim indeed. Most of the money so far obtained has been won by selling off the considerable stock at a low price and keeping staff on while there are enough parts in the store to make more. The main value of the Goldring name will rest on the pickup cartridges and styli, and it has been suggested that Sharf will eventually buy the goodwill of the possibly liquidated firm. Toa have wasted no time in setting up Toa (UK) Ltd, and C. E. Hammond have already taken over the Lenco agency.
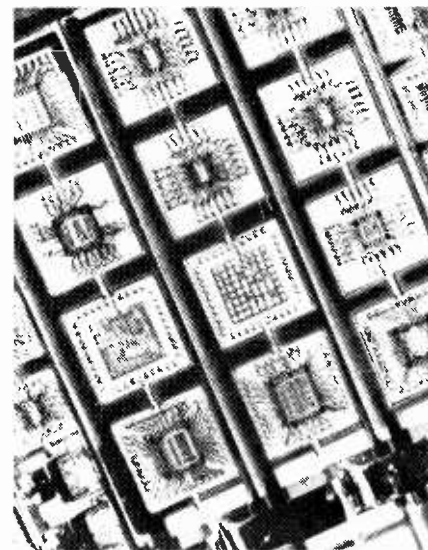
## "Britain pioneered the integrated circuit"

Mr G. W. A. Dummer, formerly superintendent of applied physics at the Royal Signals and Radar Establishment, has no doubt that Britain was the pioneer in the invention of the integrated circuit, though not the inventor in the full sense of the word. In a letter to the American journal *IEE Spectrum* (December 1976) he distinguishes between the pioneer "who thinks of it,"



**Liquid-cooled logic.** Current mode logic circuits used in Honeywell's new 66/85 computers. Honeywell say the elimination of transistor storage time makes each chip five to seven times as fast as t.t.l., using half the power: One 3in square micropackage there are up to 110 chips, "almost as much circuitry as a standard 12in square circuit board." At the back of each micropackage a liquid cooled heat exchanger eliminates the need for system air cooling. The exchanger is an oxidised copper diaphragm which, when pressurised by liquid flowing behind it, conforms to the surface of the micropack. Each board has 12 micropacks arranged in four columns of three. The coolant is pumped in parallel through each column. The liquid is cooled in an air-cooled radiator cabinet with an air blower. If the cooling system fails the computer shuts down automatically.

the experimenter "who makes a working model" and the exploiter "who develops and produces it." He writes: "The pioneering stage was certainly that of the Royal Radar Establishment (RRE) in Great Britain. It must be remembered that the "solid circuit" idea was no flash in the pan, but the result of six years' work on miniaturization. The model shown to US military and other visitors at the United Kingdom Symposium in 1957 was intended to indicate my views on the logical future of component miniaturization techniques." The real inventors of the integrated circuit, in Dummer's opinion, were "Noyce and his dedicated team at Fairchild."

As a result of reporting the 1957 UK symposium under the title "Solid Circuits," *Wireless World* (Nov. 1957 issue) subsequently ran into a spot of bother with the lawyers of Texas Instruments because TI, at a date somewhat later than the report, had decided to use "Solid Circuits" as a trade name for their devices (before the term "integrated

*Continued on page 92*

## Binaural broadcast

### First announced BBC programme

From a preliminary analysis of listeners' letters, a large majority of respondents got a sound sensation outside of the head when listening to "Oil Rig" on headphones, says the producer, Richard Imison. The Radio 3 programme was made with "binaural" microphones intended for headphone listening and was the first announced broadcast of its kind in the UK. After reading the first 500 letters, Mr Imison said about a third had experienced good all-round perception, but of the remaining two-thirds, a majority had good sound except within an arc of around  $\pm 45^\circ$  of centre front, and a significant minority found everything in front and nothing behind. The programme, auditioned for the press six days before transmission on 8th February, was a 75-minute distillation of 37 hours of interviews and sound effects from a North Sea oil rig.

An interesting choice of location, this, for while life on an oil rig may possibly make for good journalism, its remoteness from everyday life did perhaps make it a little difficult to relate it to reality, acoustically. But it wasn't difficult to discover the weak point of the technique, that is, in portraying frontal sound images, a widely recognised problem with such binaural techniques.

One found the background sensation to be good and generally located outside the head, though almost always taking place behind. Three kinds of speech were heard. Studio-produced mono narration which, as it was fed to both channels equally, appeared in the head. On location, speech was either in the head or out of the head and elevated but never in front (for those at the audition anyway).

The two sensations were produced

with two different microphone techniques. One used a 10-in diameter perspex disc with two forward-pointing eccentric omnidirectional microphones mounted either side to correspond with ear-to-ear spacing. This was used in the interview of the cook, but gave too much ambient noise on most interviews. The alternative was to mount microphones on the head of the speaker in "stethoscope" fashion — hence an in-head image.



One sometimes found it disconcerting when the out-of-head speech, clearly directed at the listener, didn't come from in front where one would have liked it to come from. This lack of centre front speech is not so upsetting on special demonstrations that are intended to startle, such as on the Sennheiser dummy head recording, but it can spoil the illusion where a speaker is addressing you constantly from behind or the sides — in real life one would quickly turn to face the speaker.

### Why dummy heads weren't used

This disc baffle arrangement came about after three years of experiments by BBC Radio using first the Neumann artificial head and then the Sennheiser (both pictured on page 336 September 1974 issue). They say the heads were subject to countless tests involving hundreds of tapes, starting with a large, dead studio and going on to other studios and the open air, with different kinds of material including test sequences, plays, outside broadcasts, music.

They found that while the Neumann head was "convincing" and impressive on headphones, it had quality shortcomings on loudspeakers, in particular a steep roll off at 5kHz. The Sennheiser head and "stethoscope"-type microphone arrangement brought a

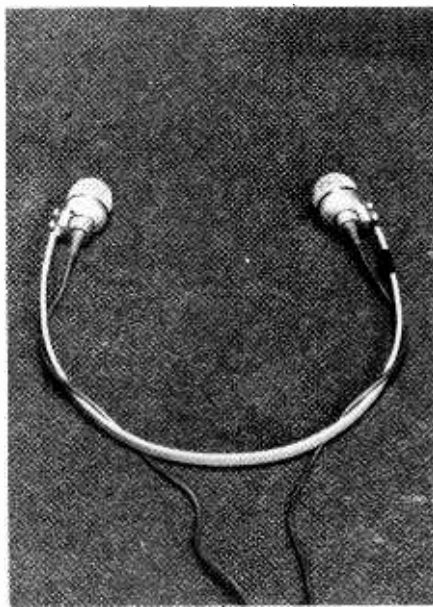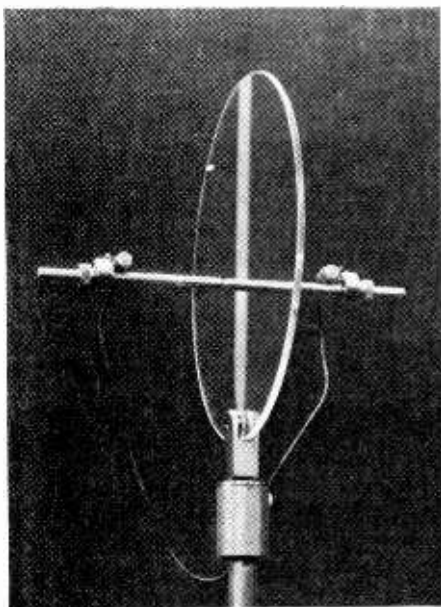*The baffle and (right) "stethoscope" microphone pairs described in the text.*



response up to 15kHz, but the top was "edgy" and "rather hard" and the quality was not the best. Results with this arrangement on a real head were "a little better with the 'stethoscope' mikes but not good enough," commented Richard Imison. "Not really up to broadcast standards".

This was the point where an alternative had to be found; in fact the project was nearly abandoned, recalls Richard Imison. Derek Taylor of programme operations then found that good results could be obtained using better quality microphones in stethoscope fashion — Sony omnidirectional ECM50's were mounted on a headband with wind-shield and worn at the ears.

Because of the obvious limitations of this technique, checks were then made to see how much an artificial head actually contributed, starting with a head-sized carpet baffle between ear-spaced microphones (with and without plasticine pinnae!). Directional properties of the set up didn't seem any worse. In Derek Taylor's words "As long as the mics were about ear distance apart, with a baffle between to give the correct path length, the directional effects were not significantly different. Model ears or baffles behind the mics did not seem to help in resolving front-to-back confusion." Richard Imison agrees: there is "no significant difference" between the techniques tried as far as front localization is concerned. (They also agree that there isn't much difference in results between closed and open-type headphones either.)

Front-to-back ambiguity, it is argued, occurs with single, transient live sounds anyway. For continuous or longer live sounds one's head has more of a chance at assessing direction, either by unconscious minute head movements or by conscious larger movements, and the poor frontal localization with headphones is thought to be due to loss of such clues.

The BBC have obviously reached a point where they want to experiment with a large audience. But the data from listeners will have to be carefully interpreted as it seems far more likely that those who were impressed with the technique — say on account of well-defined images — would respond more readily than those for whom the technique was disappointing.

The ear-spaced microphone with baffle arrangement was made into more permanent form, as in the photograph, and used for the Oil Rig programme, as well as on other occasions including a proms recording. The prom recording, as with others, was not nearly so effective on loudspeakers though BBC personnel found it as good as the conventional stereo recordings, in some cases better. In simple informal preference tests between conventional and binaural stereo over loudspeakers, the binaural version was the preferred one. — GBS.



# Education by radio in Honduras

A case study in electronics technology in a developing country

by Michael K. Bates\* B.A. (Eng. Tripos, Cambridge)

**Electronics technology is at such a level of sophistication that few countries can sustain their own electronics industry. Nevertheless radio is an effective means of communication the world over and it has had a significant impact on developing countries. In studying a particular application in Honduras, the author draws lessons about the suitability of present technology for use in other developing countries.**

Honduras, Central America, is reputedly the second poorest country in the Western Hemisphere. Although Honduras is less than half the size of the UK, its population density is low since the total population is only three million, of whom nearly all are Spanish-speaking Catholics; over two million eke out a subsistence living in rural areas and are known as *campesinos*, or peasant farmers. Most of the land is mountainous, containing small but fertile valleys. The wide strip of highly productive land on the Caribbean seaboard is mostly owned by foreign banana companies.

Communications systems within the country are on the whole ineffective: not even all the major towns are linked by paved roads, many villages are accessible only on foot or horseback, telephone links are over-subscribed and unreliable, and both the circulation of newspapers and the coverage of television are mostly confined to the cities. But radio has proved to be highly suitable and is the dominant medium for mass entertainment, dissemination of information and passing of messages. The success of radio broadcasting is largely due to an influx of cheap portable transistor radios, ownership of which is often regarded as an indication of social status, and this may account for the range at which the average transistor set is audible. Most broadcasting is on a private commercial basis from nearly one hundred local radio

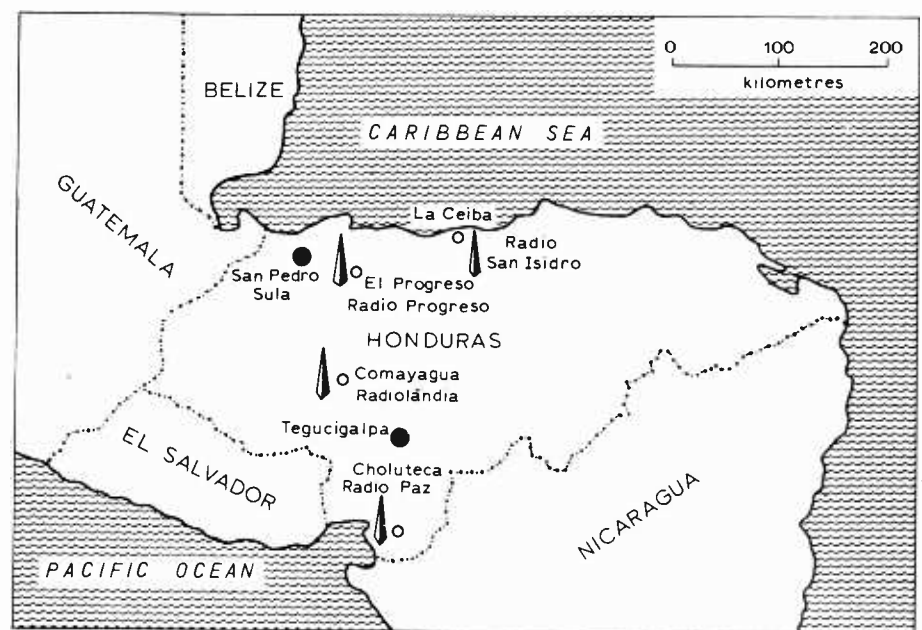


Fig. 1. Map of Honduras showing locations of radio stations mentioned in the text.

stations transmitting in the 540 to 1600kHz band, although use is also made of the 60m short-wave band and the standard v.h.f. f.m. band.

## Radio schools

Although education is free in Honduras and primary school is, in theory, compulsory it is evident that few *campesinos* benefit from it: most have been to school for perhaps only a year or two and over 65% are illiterate. There are obvious difficulties in sparsely populated areas in bringing together enough pupils to make a conventional school viable, especially if the aim is education of working adults. Use of radio can, however, offer a solution to problems like these.

The system of radio schooling prevalent in Latin America originated in Colombia in 1947, when Radio Sutatenza went on the air with a 100W transmitter and just forty-five pupils. The idea proved successful and the organization grew rapidly, until today

the station controls four transmitters with a combined output of over 750kW. Meanwhile radio schools were started in fifteen other Latin American countries, including Honduras.

The radio schools of Honduras have grown up under the auspices of *Acción Cultural Popular Hondureña* (ACPH), a non-government independent development agency which is financed from voluntary sources. There have been considerable problems in achieving autonomy from the influences of commercial enterprise, political forces and more recently a sector of the Catholic Church, partly because ACPH relies on agreements with sympathetic radio stations to buy air-time for transmission of the schools classes: hence, its effectiveness is closely linked to the progress of these stations.


Experimental education of adults by radio began in 1959 with broadcasts from Radio Católica in Tegucigalpa, the capital, and grew successful to encompass 700 school groups by 1964. After several years of organizational problems, the system was re-vitalised in 1969 with the opening by foreign priests of

\*Volunteer radio engineer with the Catholic Institute for International Relations from September 1974 to December 1975 as part of the British volunteer programme.

Radio Paz, in southern Honduras, and the acquisition the following year of Radio Progreso in the north by Jesuits. As well as transmitting schools programmes, then as now recorded in the ACPH offices in Tegucigalpa, both stations followed normal commercial schedules. Plans for more comprehensive coverage of the country developed, and in 1974 surplus equipment was bought in the USA and shipped to Honduras for in-country construction of transmitters and studio facilities with local help. However this scheme has not reached fruition due to diverging aims of ACPH and the Catholic Church, a situation which has also caused Radio Católica to cease passing schools classes. Some expansion of the network was nevertheless achieved in 1975 with a low power short-wave installation at Radio San Isidro, La Ceiba, and complete new studios and transmitters for medium and short wavebands at Radiolândia, Comayagua. But these gains were offset by the closure of Radio Paz in June 1975 by the military government, following struggles over land tenancy in the east of the country, and attempts to regain the broadcast licence have so far only brought prevaricative responses.

The current disposition of facilities illustrates the wide spread of techniques which occurs in any technology in Honduras, ranging from the relatively sophisticated to the unbelievably crude. At the more impressive end of the spectrum, Radio Progreso broadcasts via a new Gates/Harris 5kW pulse-width modulated transmitter on

Fig. 2. Transmitter construction in workshops at Radio Paz, Cháuteca. On the right is the completed transmitter for Radiolândia; in the centre is a copy of it under construction; on the left is a BC610 US surplus being converted for short wave broadcasting. Note the tin bath, used to supply cooling water for a dummy load during necessarily brief transmitter tests at full power.

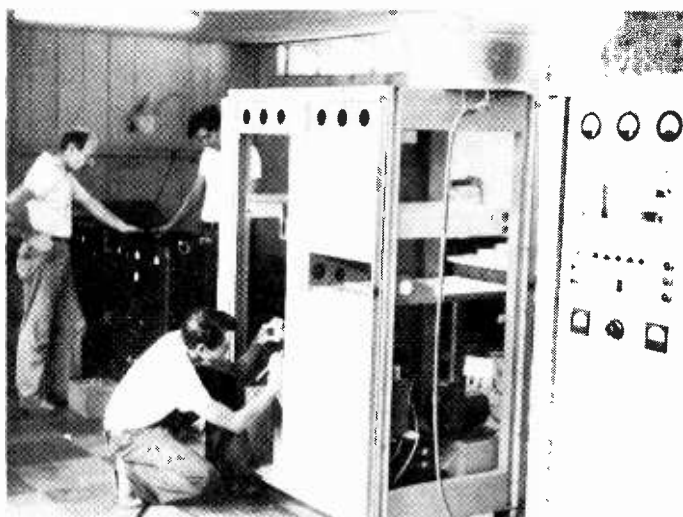

1110kHz, with a modified 10kW Collins on 4920kHz; on both frequencies there are back-up transmitters, a rare achievement for a Honduran station. Radio Paz transmitted on 990kHz using a modified Contel unit with 4-1000 tetrodes in the modulator and 3-1000 triodes in the final, and the locally constructed transmitter for Radiolândia draws from the same series of valves but with a single anode-modulated zero grid bias 4-1000 on the r.f. side to deliver 1.5kW on 1460kHz. For short-wave broadcasting at both Radiolândia and Radio San Isidro BC610 transmitters are in use, boosted to 500W with a final 833, a good robust valve which has been known to withstand accidental use as a light bulb. Even surplus equipment like this looks elegant alongside some home-made transmitters, which have been seen to use wood blocks to support and isolate transformers and domestic light switches on the control panel. It will be noticed that transmitter powers are all fairly low: 10kW is the legal upper limit and Honduran stations are at the moment spared the spiral of ever-rising powers. Despite the higher radio noise levels under tropical conditions, most areas are served well by their local transmitters and there is little adjacent or co-channel interference even at night.

On the studio side, there is such a range of equipment in use as to prohibit more than a mention here. The radio schools central recording studio is well equipped with a double turntable sound mixing desk, two Magnecord professional recorders, three Ampex series 600 machines and two high-speed tape duplicators. So too Radio Progreso has an impressive line up of Ampex 351 recorders in two fully interchangeable control rooms serving three studios. However, at the other end of the scale, the type of station with "mic and two decks" (one of them probably non-operational) is common.

#### Broadcasting policy

Radio Schools classes are broadcast from 4 p.m. to 6 p.m. Monday to Friday

with supplementary material on Saturday including news and current affairs for *campesinos*. These programmes are followed by some 1200 community school groups involving about 22,000 students which means that, with their families included, the broadcasts affect some 100,000 people, around 5% of the rural population. Each group is guided by a *monitor* who will be a local *campesino* with approximately one month's training at one of a number of regional centres. The *monitor* also plays an important part in a feedback path of opinion via a regional co-ordinator to the production team in the capital. Instruction is given in reading, writing and basic arithmetic, progressing to geographical and cultural knowledge, but at all stages there is practical advice on agriculture, health and home management. However it is the teaching method which is significant. Education follows the idea, originated in Latin America, of "conscientization", a very pragmatic philosophy intended to create a critical awareness of one's environment and capabilities within it, with emphasis on democratic and co-operative processes as means of achieving communal aims. Hence it is not so much a "handing downwards" of information but rather a combined search by students and teachers in the context of a localized community to find solutions to very real practical problems.

The importance of employing local radio stations is noteworthy. Firstly the schedules of classes need to differ in various parts of the country to accommodate variations in the tending of crops. Secondly there is a chance for the local radio station to become the focal point in a community and give a sense of identification to those living around it, through their knowing personally the announcers, being able to participate in discussion programmes, or merely by hearing their own record dedications.

Fig. 3. A typical radio schools class, making use of a primary school out of normal school hours.





Fig. 4. An exercise in Handwriting for a Honduran campesino.

### Operational problems

Operation of a radio network in a developing tropical country brings its own special difficulties not normally encountered here. There are frequent troubles with the *campesino* transistor radios which are often subjected to extreme conditions of heat or mechanical abuse, such as use as a temporary seat in a bus with doubtful suspension driven along a rocky dirt road. Sometimes a little "home servicing" is attempted too, with the aid of the first implement which comes to hand, normally a machete, and often the back of the set is lost and the loudspeaker cone is eaten by cockroaches.

Broadcasting stations also suffer from the climatic conditions. Ventilation can be a major difficulty: at the Radio Paz transmitter in Choluteca, admittedly one of the warmest parts of the country, shade temperatures in March and April regularly exceed 40°C, and even after increasing the size of blowers it was necessary to run the transmitter without sides and play a domestic fan on the modulator chassis. Concurrent with temperature problems are often those of high humidity: a particularly bad case is in La Ceiba, where the damp salt-air has affected even the BC610, designed for military and tropical use. During the wet season, lightning strikes cause frequent disruption of service and damage to transmitters and for this reason a folded unipole (caged) aerial configuration, in which the base of the tower is earthed, has been adopted for m.w. radiation at both Radio Progreso and Radiolândia.

The studio equipment is not normally subjected to such extreme conditions, but in studios without air conditioning there are problems of overheating in turntable and tape-recorder motors, and much valve equipment such as line amplifiers and compressors has to be blown. Fluctuations in mains voltage

can also be troublesome; for example the Radiolândia transmitter shows a tendency to trip out on the surge caused by a local factory shutting down at the end of the day.

Many stations have no technical staff and hence no regular maintenance, repairs being effected only when breakdown occurs. In a country dependent on agriculture rather than industry and technology, the whole environment is non-scientific and there are few technicians and engineers of any description. There appear to be several reasons for this. The social circumstances of most families tend to inhibit rather than encourage a child's natural curiosity; the education system, for those who benefit from it at all, is biased towards learning by rote rather than from exploratory and logical deduction processes, and Honduran technicians experience particular difficulty in fault diagnosis. For those few privileged enough to go on to higher education, most seeking technical studies would travel to the U.S.A. or Mexico, and perhaps not return. Latin American technicians encounter additional problems with language, as a large proportion of service manuals and specification sheets are in English only. Nevertheless, the enthusiasm and capacity for hard work of those trying to better themselves is an inspiration. Moreover most Hondurans are capable with their hands and adept at improvisation with what materials and knowledge they possess.

### Electronics technology for developing countries

One of the dilemmas which developing countries face is whether to accept certain totally imported technologies,

such as electronics, or to manage without them. The extent of radio ownership leaves no doubt that radio broadcasting is both desirable and successful in Honduras, yet even an organization like the radio schools, trying to go its own way to suit the needs of its own people, has to accept the technology of the industrialized countries and the way in which it is administered.

Furthermore, there is no half-way stage in radio, no "intermediate" technology. Other branches of engineering, for example transport, can be upgraded by better techniques while remaining within the framework of traditional styles: the wooden wheels and axles of an ox-cart can be replaced by pneumatic tyres and a suspension system without a complete changeover to use of a tractor and trailer. But there is no parallel process in radio, which is not a development of a traditional method of communication but a totally new science. It is hard to simplify a transmitter beyond a basic valve-driven anode-modulated circuit, yet at present this remains as incomprehensible to most Hondurans as ampliphase, Doherty or pulse amplitude systems: it is just another proverbial "black box".

So how suitable is present day electronics technology for developing countries such as Honduras? Despite the extent and importance of radio systems in such countries, little equipment is manufactured specifically for their needs and often standard equipment is unsuitable without modifications such as tropicalized components or additional cooling. At times equipment cannot be set up correctly or maintained through lack of test gear and spares: an example is an ampliphase transmitter imported into Honduras which has never given optimum performance. On the other hand, confusion is caused when a range of test equipment is specified which is not normally used

Fig. 5. Radio schools classes are often held in ordinary campesino houses such as this one near Choluteca.



outside a laboratory; the list of "required equipment" for tape-head alignment on one model of recorder included a valve voltmeter, a low-distortion oscillator and a spectrum analyser. The station concerned did not possess even a multimeter.

Nevertheless, the Latin American broadcast equipment market is booming; a periodical is produced, in English and Spanish, for free distribution to any radio personnel requesting it, and many of the larger electronics companies now have agencies in Central and South America.

Bearing in mind the possible size of the market for electronic and radio goods in developing countries, it seems appropriate to consider some of their basic requirements. It would indeed be a noteworthy advance if there were available a cheap, simple, foolproof transistor radio, in a tough impact-resistant case with firmly secured back and control knobs, with reliable battery contacts and protection against incorrect battery insertion. Suitable circuitry might include integrated circuit i.f. and a.f. stages and ceramic filters, with servicing simplified to the level of quick circuit-block replacement or perhaps even a complete change of encapsulated, throwaway electronics. The criteria of low cost, robustness under exacting conditions and misuse, reliability and ease of servicing by non-expert personnel also apply to broadcasting equipment, appearing more important than high performance and sophistication of design. Such ideas as solid-state relays, ball-race bearings lubricated for life, modular construction but with far more attention given to connectors, and generously rated components immediately suggest themselves. A plea might well be added for VU meters with flexible pointers and unbreakable end-stops.

Current technology can adequately satisfy these requirements if suitable production and marketing policies are adopted. Future demands from developing countries are likely to be for television as well as radio equipment in ever-increasing quantities, but understanding and ability to use the technology can only come slowly. In the meantime, these countries require the sort of equipment which can be used successfully in the present environment. The Honduran *campesino* needs his indestructible transistor radio for entertainment and for education, and must hope that progress in electronics technology will move towards providing it. And there might even be something in it for us.

#### Acknowledgements

Thanks are due for the considerable assistance provided by R. J. Levey, engineer for ACPH; P. G. Nairne, now with the British Council; and the Catholic Institute for International Relations.

# One hundred years ago

No, *Wireless World* was yet a thing of the future in 1877, but the groundwork for the development of the electronic twentieth century was being laid and already, a hundred years ago, an impressive list of theoretical and practical invention was in existence. Computers, relays, transformers, diaphragm microphones, motors, fuel cells had all been made and the theory of wave propagation was well advanced.

In April 1877, Thomas Alva Edison filed a U.S. patent application for the design of the carbon microphone, which immediately took precedence over the efforts of Reis (diaphragm type — 1860) and Bell (magnetic — 1875). The "other end" of a speech communication system was attacked by E. W. Siemens, who applied for a German patent on the moving-coil loudspeaker in December, 1877. The device used the now-familiar motor with a circular coil moving in a radial field.

A rather more publicized centenary this year is the invention by Edison of the phonograph (or gramophone) using tin foil wrapped round a hand-cranked cylinder. This patent was applied for in December, 1877.

Moving on to fifty years ago, 1927 was an important date in the history of the cinema

when the first really effective "talkie" film, "The Jazz Singer", with Al Jolson, was a tremendous success. The Western Electric sound system — the Vitaphone — used 16in disc turntables driven at 33½ r.p.m. from the same constant speed motor system as the film projectors. But this method of synchronism was soon to be supplanted by the "sound track" (sound-on-film system) introduced in the same year by Fox Movietone News. On a quieter and somewhat less distorted note, but highly significant to audio engineering, was the invention in 1927 of the negative feedback amplifier by H. S. Black of Bell Laboratories.

These are just a few of the significant inventions described in a new book "Electronic Inventions 1745-1976" by G. W. A. Dummer just published by Pergamon Press at £4.00. This contains mainly brief accounts of important inventions in electronics but also has some interesting graphs showing historical trends. For example, it shows that in the 200 years from 1745 to 1945 some 106 electronic inventions originated in Europe against 66 in the same period in the USA; but in the mere 31 years from 1945 to 1976 the situation was reversed with 32 inventions for Europe and 85 for the USA.

## Literature Received

Power supply price list is now available from Weir, including bench types, a unit for use with microprocessors and a range of card supplies. Weir Instrumentation Ltd, Durban Road, Bognor Regis, Sussex ..... WW401

Video cassette recorder control unit is made by Crow of Reading for use with the Ampex ACR-25. A leaflet describes the function of the unit, which is designed for remote control of the programmed recorder. Crow of Reading Ltd, PO Box 36, Reading, RG1 2NB ..... WW402

Demonstration panels for teaching electronics are produced by Taran International. The panels take the form of large mimic diagrams with the circuit printed on the front, the components being plugged in. A leaflet can be obtained from Raynham Road, Bishop's Stortford, Herts CM23 5PG ..... WW403

Component lead forming machinery from Eraser International is described in a "Wyber" catalogue. Hand-operated and automatic forming and cropping tools are illustrated and several implements for cleaning printed boards are described. Eraser International Ltd, 2/3 Hampton Court Parade, East Molesey, Surrey KT8 9HB ..... WW404

Prices of measuring instruments in the Electroplan catalogue are brought up to date in their February 77 list, which briefly describes additions to the range from Advance, Solartron, Weston, Bryans, Telequipment and Systron-Donner. Electroplan Ltd, PO Box 19, Orchard Road, Royston, Herts SG8 5HH ..... WW405

Printed-circuit manufacture by the Nevin group is the subject of a new brochure, which includes a wall-chart of board design information, protective finishes and metric conversions. Nevin Electric (Holdings) Ltd, Arkwright Road, Poyle Trading Estate, Colnbrook, Bucks SL3 0HJ ..... WW406

Connectors in the Amphenol range include the r.f. types to DEF standards — the 27GB Subminax, the 31GB series quick disconnecting connectors and the 82GB 'C' weatherproof type. A set of data sheets covering all these is now obtainable from Amphenol Ltd, Thanet Way, Whitstable, Kent CT5 3JF ..... WW407

Distance measurement techniques over a period of 5000 years are illustrated on a new wall-chart from Tellurometer, which has been involved in only the later, microwave methods of measurement. Tellurometer, Oakcroft Road, Chessington, Surrey KT9 1RQ ..... WW408

Capacitors and semiconductor devices by RIFA are fully described in a catalogue, now available. A very full range of capacitors is offered and the semiconductors are rectifiers, timers and driver/interface circuits. Rifa, Fac. S-161 11 Bromma, Sweden ..... WW409

Power supplies by Gardners are detailed in a series of recently published leaflets. Chargers for nickel-cadmium cells, 50Hz d.c.-to-a.c. inverters, regulators and d.c.-to-d.c. converters are all described and the leaflets can be obtained from Gardners Transformers Ltd, Christchurch, Dorset, BH23 3PN ..... WW410

Speaker drive units, crossovers, materials and accessories for loudspeaker construction are listed in a new catalogue, obtainable from Badger Sound Services Ltd, 38(a) St Andrews Road South, St Annes, Lytham St Annes, Lancs FY8 1PS at 10p per copy.

Pressure transducers of various types are made by Bell & Howell who describe them in four bulletins. Types covered are: thin-film types, high-output versions with amplifiers, marine and industrial transducers with electronics in a bulkhead-mounting case and flameproof transducers. Bell & Howell Ltd, Electronics and Instruments Division, Lennox Road, Basingstoke, Hants RG22 4AW ..... WW411


General electronic components, instruments, kits and books are all listed in the Maplin 1977 catalogue, available at 50p from Maplin Electronic Supplies, PO Box 3, Rayleigh, Essex SS6 8LR.

# Circuit Ideas

## Voltage/current meter switch

The circuit arrangement shown enables a single pole two way switch to be used in place of the two pole, two way type which is usually required when one meter indicates both current and voltage. Resistors  $R_1$  and  $R_2$  are the meter shunt and series resistances respectively. The change of output voltage due to  $R_1$  being switched in and out will usually be negligible if the circuit is included in the feedback loop of a stabilised power supply.

S. V. Essex,  
London W.14.

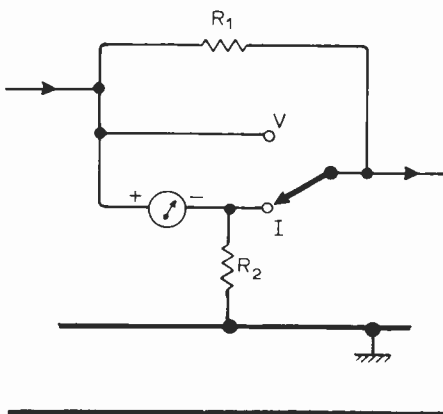


## N-stable multivibrator

This circuit produces a fixed number of pulses when triggered. Applications include number indicators, frequency multiplication, and number loaders. A monostable feeds a gated astable and, by adjusting the frequency control of

the last mentioned, between two and thirty pulses can be obtained. This has been realised using a single CD4001 i.c. A pushbutton can be used instead of a trigger pulse for manual circuits.

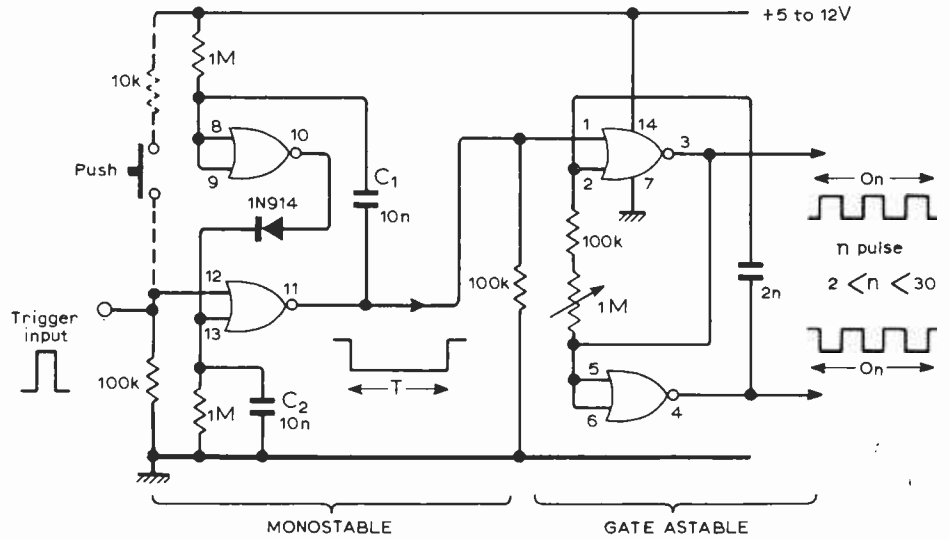Dr K. Padmanabhan,  
University of Madras,  
India.



## Variable band-pass filter


Sometimes it is required to have a high-Q, bandpass filter which is adjustable over a wide frequency range without an appreciable change in Q, or more particularly, without the loop-gain becoming greater than unity which causes oscillation. With this circuit the centre frequency can be adjusted over a 100:1 range whilst maintaining  $Q > 100$ , and over smaller frequency ranges, a Q of up to  $10^4$ . In addition, a two-phase output is also available.

Two cascaded all-pass networks, B and C, each have a  $0^\circ$  to  $180^\circ$  phase variation, and unity gain at all frequencies. This cascade is driven from a third operational amplifier whose feedback signal is the sum of the input

and output of the all-pass network. The sum becomes zero when there is exactly  $180^\circ$  phase shift over the cascade, and thus the overall gain approaches half the open-loop gain of amplifier A. At other frequencies the gain tends towards unity.

Because the frequency determining components only affect the overall phase-shift and not the gain, there is a no danger of having a loop-gain greater than unity. If the two-phase output or large frequency range is not required one R can be fixed. The Q is adjusted by  $R_2$ , and with the values shown gives the circuit a 20Hz to 2kHz range.

J. M. Worley,  
Colchester,  
Essex.

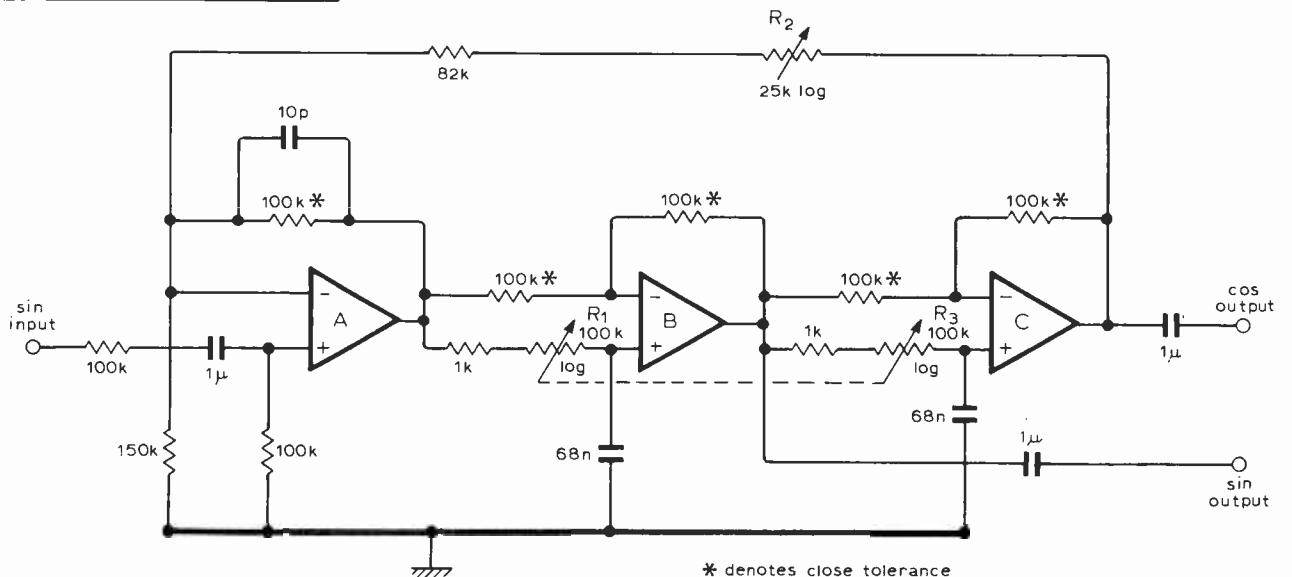




## Ripple eliminator


This shunt regulator circuit virtually removes all mains ripple without using a large capacitor, and is inherently short-circuit proof. The regulator is ideal as a stabilized supply line for audio preamplifiers and other applications where a precise voltage level is not important but freedom from ripple is. The circuit's simplicity is due to silicon transistors which can operate at very

low levels of collector-emitter voltage. The zener diode should be operated with enough current to make its dynamic resistance significantly less than  $R_1$ . Transistor  $Tr_3$  may be a power type or a Darlington. The Miller capacitor should be large enough to stop high frequency oscillations.

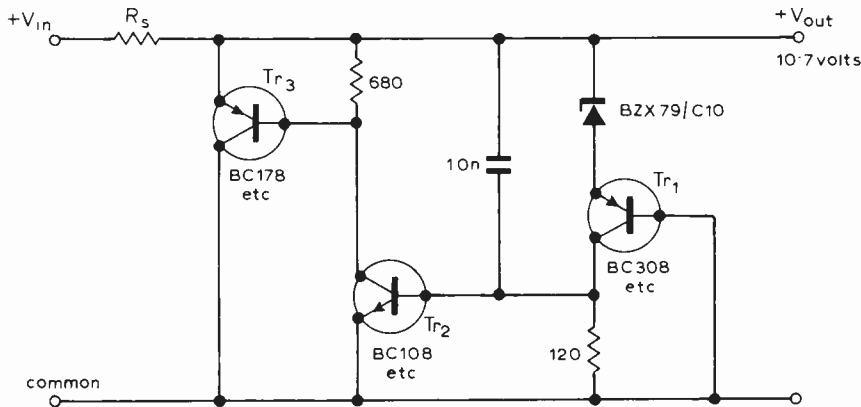P. S. Bright,  
Christchurch, New Zealand.



## Earth warning indicator

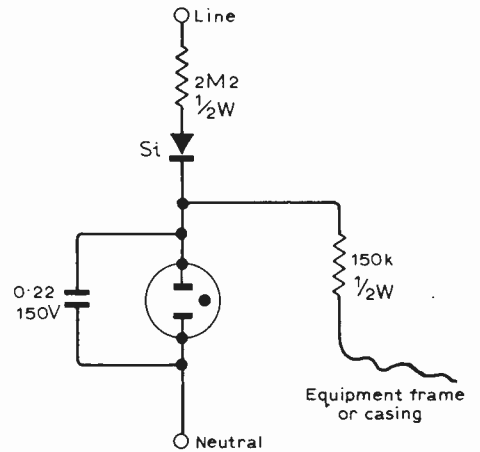

This simple circuit gives a warning if the earth wire is disconnected from the chassis of an instrument. It is particularly useful for oscilloscopes which may be left in a hazardous state when the earth wire is purposely disconnected to avoid hum loops etc.

The neon is normally extinguished, and flashes if the earth is not connected.  
R. H. Troughton,  
Gatwick Airport, Surrey.


## Simple noise generator

Phase-lock loop techniques, for the recovery of low level information from noisy signals, have become increasingly important. This note describes a simple noise generator in which both signal and noise levels are continuously and independently variable from zero to maximum. The only point requiring care is the positioning of the transformer to avoid 50Hz hum. The voltage doubler supply may be replaced by any convenient configuration. The input

impedance is approximately 500Ω. Four stages of gain have been used to minimize instabilities and provide the maximum noise amplitude without reaching the limits of output excursion. The a.c. coupling between stages eliminates offset compensation and provides low frequency roll-off. High frequency roll-off is determined by the gain of each stage and varies slightly with the noise level control. Output noise is essentially "white" from below 50Hz to above 5kHz. This range was selected as appropriate to demonstrate

the recovery of a 500Hz signal from noise of similar frequencies. The circuit will operate at maximum noise output into a load of 1.5kΩ. For smaller load impedances, the noise level must be reduced or the 1000μF power supply capacitors increased to prevent oscillation.

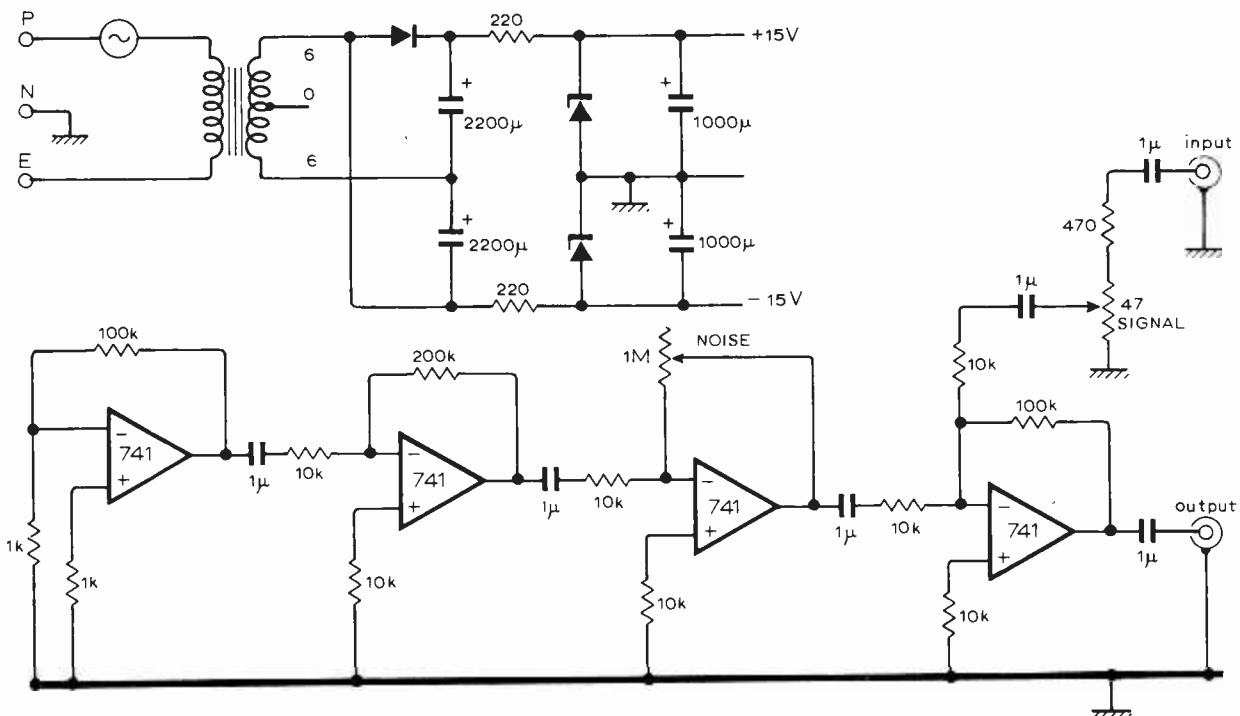The author wishes to acknowledge the contributions of Dr T. G. L. Shirtcliffe, Mr J. E. Nixon and Mr P. D. Turner to the project.  
J. E. Morris,  
University of Wellington,  
New Zealand.



# We complete the open circuit in your money supply.

In almost any industry these days, the gap between invoicing and getting paid is widening so fast it's causing cash flow problems even for sound companies.

It's the creditability gap.

It affects the quality of work and frustrates plans for improving productivity and profits through expansion. It prevents good companies from forging ahead.

Here's the professional answer to the problem.

Alex. Lawrie will bridge your creditability gap by converting up to 75% of your invoices into ready cash - immediately. You inject it into your business - immediately. And together, you and Alex. Lawrie generate a sound cycle of money supply.

Let's face it, if you've got a good business going in this critical economic climate, you have no alternative but to protect it. Phone the Alex. Lawrie Regional Manager and talk to him now. Or send for details.



**Alex. Lawrie  
Factors Limited**

**London Region:** (01) 626 0484 **Northern Region:** Manchester (061) 834 7415 **Midland Region:** Banbury (0295) 51126

**Southern Region:** Southampton (0703) 22968 **Belfast Branch:** (0232) 22350


**Scottish Offices:** Glasgow (041) 221 3637 **Edinburgh** (031) 226 4599

**Registered Office:** Beaumont House, Beaumont Road, Banbury, Oxfordshire OX16 7RN.

Gould Advance offer a comprehensive range of generators – and every one's a winner.

Take the J3A and J4A Test Oscillators, for example. Both feature a choice of four different outputs, and both give you outstanding performance at a very modest price.

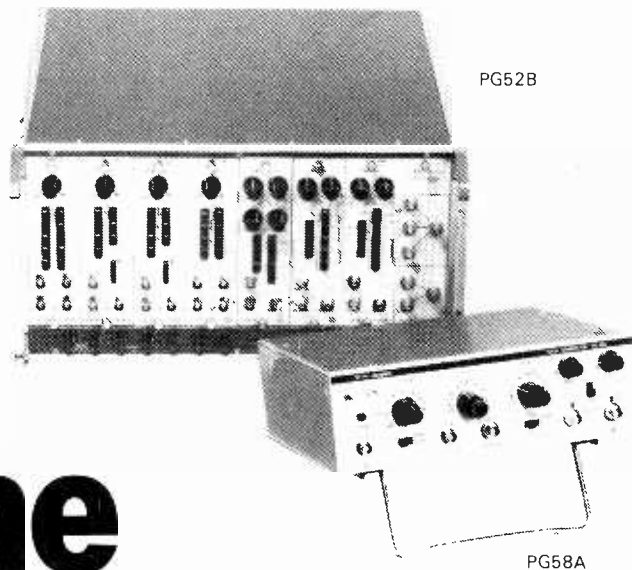Then there's the SG200 RF Signal Generator, offering 7 ranges from 160 kHz to 230 MHz, and excellent frequency stability with fine setting to within 1 kHz.



# The Generation Game

There are Pulse Generators too. The PG58A, for instance: an inexpensive general-purpose instrument providing single or double pulses as well as square

waves. And the PG52B; not really one instrument, but up to eight modular units in one Main Frame. There are twelve modules to choose from, enabling you to generate an extremely wide range of pulses and pulse patterns. And if you need still more versatility, there's a 16 bit Word Generator and a Gate Module to provide even more complex pulse patterns.

Look into the Gould Advance range for yourself. You'll find that it's hard to beat for price, performance and reliability. In fact, we've guaranteed every instrument in the range for no less than two years. Didn't we do well!

**Gould Advance Limited**,  
Instrument Division, Roebuck Road,  
Hainault, Essex IG6 3UE.  
Tel: 01-500 1000 Telex: 263785



**GOULD ADVANCE**

WW-073 FOR FURTHER DETAILS

# VIEWDATA

## 3 — Operation of the system: terminals and codes

by S. Fedida, B.Sc. (Eng), M.Sc., F.I.E.E., A.C.G.I. *Post Office Research Centre*

**Part 1 of this series, in the February issue, gave an introduction to Viewdata, with mentions of earlier systems. Part 2, in the March issue, dealt mainly with applications. This article now describes the overall arrangement of the system, the codes used and the Viewdata terminal.**

Fig. 1 gives an overall view of a Viewdata connection. The home terminal, shown at the bottom left hand side, comprises a domestic television set, a telephone instrument, a Viewdata adaptor and a keypad. The actual assembly is shown in Fig. 2. Two types of keypads proposed are shown in Figs. 3 and 4. The basic keypad is Fig. 3; this provides the ten numerals, \* and  $\#$  symbols and keys for automatic dialling, if installed. Fig. 4 is an alphanumeric keypad. This contains in addition to the above, the complete upper case alphabet, punctuation marks and symbols like £, %, /, arithmetic and algebraic symbols and cursor control characters. A typical Viewdata terminal for the office, the Viewdataphone, is shown schematically at the bottom right hand side of Fig. 1. This consists of a Viewdata terminal and a self-contained telephone instrument. A typical Viewdataphone was shown in the March issue. The Viewdata computer is shown at the top of Fig. 1, notionally connected to a variety of data banks, either direct or through the switched telephone network.

As mentioned in the February issue communication between the terminal and the Viewdata computer is at a rate of 1200 bits/s from computer to terminal and 75 bits/s in the opposite direction. More details of this arrangement will be given later.

In order to establish a connection to the Viewdata computer the user dials the telephone number of the computer as for a normal telephone call. When the connection is established the computer generates a high pitched tone (frequency 1300Hz) which is heard in the telephone receiver. The user then presses a button marked "data" on the telephone set, which switches the telephone line from the telephone set to a modem (modulator-demodulator). The telephone receiver is then set by the


side of the cradle. Once contact is established, the computer transmits a first frame, which requires the user to enter a user number. When this has been done Viewdata offers the first index (shown in the February issue, p. 32).


The action is now transferred to the keypad. On this the user keys-in his user number and any further responses. Suppose the user wishes to obtain information about entertainment activities for a given day of the week. The

user may enter the entertainment page direct by keying \*3230 $\#$ . An example of one of the pages in the entertainment sequence was Fig. 6 in the February issue. In later models of the terminal, use is made of the calling key on the keypad. This calls the Viewdata computer automatically and switches over to the modem without the user's intervention. The keypad may then be used as previously.

The design philosophy of Viewdata which has been dealt with in the first

Fig. 1. Overall picture of connections in Viewdata, showing the telephone system at the top and the home and office terminal at the bottom.

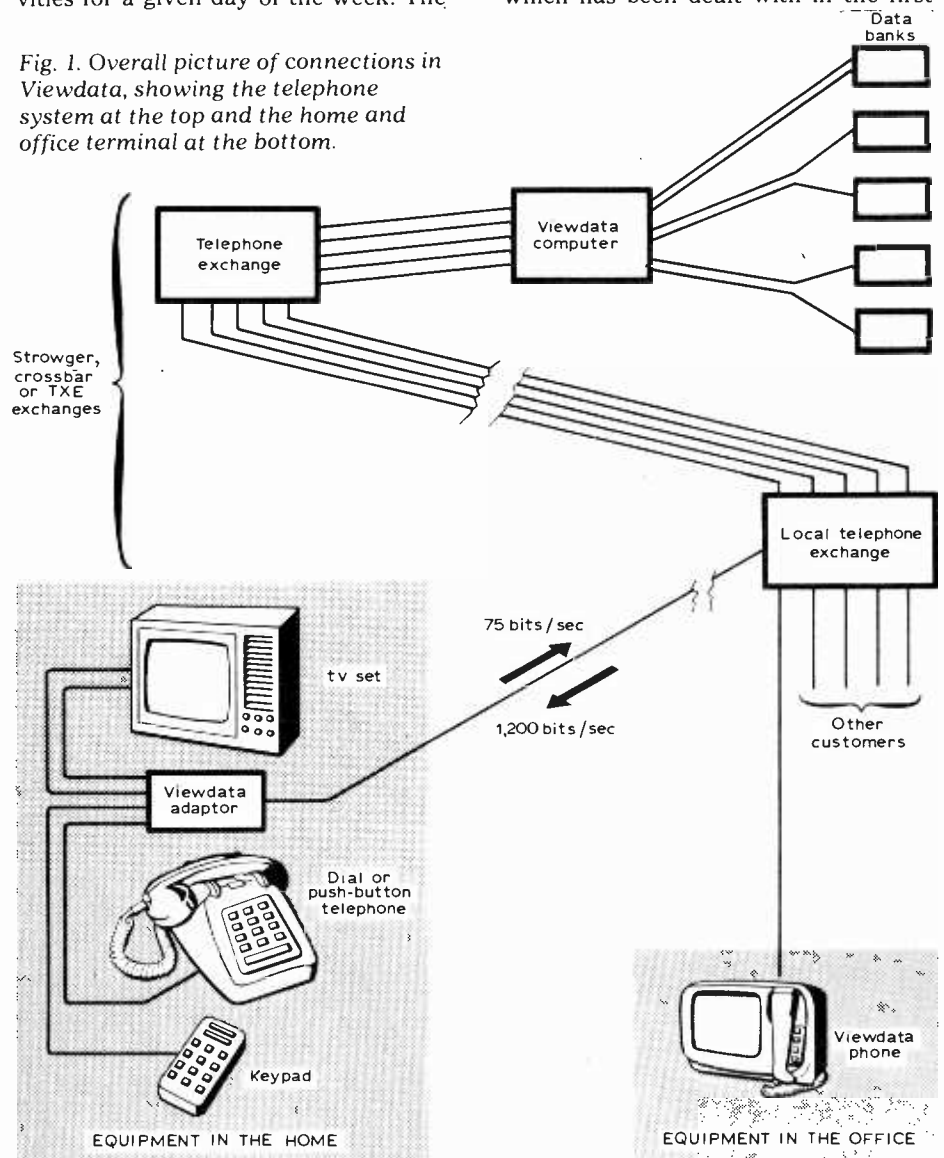

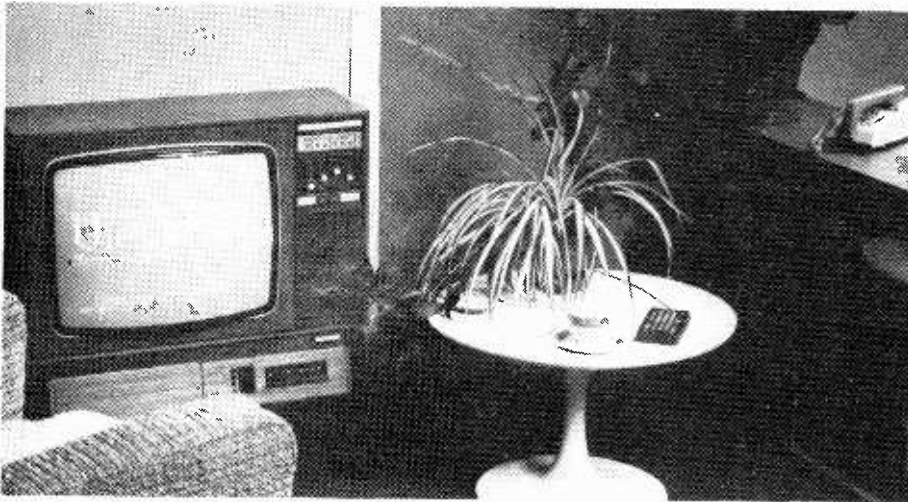

▲ Fig. 2. Home terminal for Viewdata, with television set, telephone (right) and keypad on the table.


two parts of this article referred to the need to keep the cost of Viewdata down to very low levels, both on the terminal side and on the computer usage side. Indeed, unless the cost of using the computer facility is kept substantially below that of using current computer time-sharing systems, the whole project may not become viable. This therefore postulates the use of a distributed computer system, so arranged that the majority of users may have access to a nearby computer centre, at the cost of a local telephone call for the connection plus a correspondingly modest charge for the use of the computer and the information provided.

The resulting network is typically as shown in Fig. 5. Users are within a local call distance of their computer centres, shown as rectangles. A cluster of local computer centres is grouped under the control of a regional centre for the purpose of data gathering and distribution. A national data centre controls the operation of the whole system and distributes to each regional centre new information, news and data updates. Regional centres also accept information of regional or local interest and distribute this to the local centres.

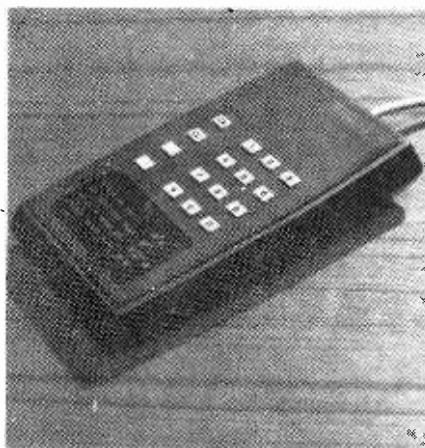**The Viewdata terminal**

**Display format.** The display format of Viewdata is identical with that of teletext, i.e. a page consists of 24 rows of 40 characters each, each character being generated by a 5 × 7 matrix with upper and lower case, character rounding, graphics symbols and colour. Thus a great deal of the electronics in a terminal may be common to Viewdata and teletext, the differences being primarily concerned with the additional functions needed in Viewdata, the different modes of transmission applicable to these two systems and the different constraints appertaining to the different communications media involved.

In the case of Viewdata the data enters the terminal via the telephone line at relatively low speed, and, as the probability of data corruption is quite low, little is needed for the purpose of error detection and correction. Indeed, extensive Viewdata tests have been



▲ Fig. 3. Basic keypad used in a Viewdata terminal, providing ten numerals and a few other keys.

carried out over the past two years from a large number of centres in the UK and on the Continent. In all these tests the public switched telephone network was used to connect up to the experimental Viewdata system based at Martlesham, near Ipswich, and transmission difficulties have been very rare.

The character codes used for Viewdata and teletext are also identical,


except for the actual codes transmitted over the line, where a slight change is made to comply with International Standards Organization recommendations.

The table of codes used for Viewdata is shown in Figs. 6, 7 and 8. Fig. 6 shows the joint Viewdata and teletext codes for alphanumeric characters only. This differs from earlier versions in the following characters:


Column	Row	Was	Is now
5	11	[	←
5	12	\	½
5	13	]	→
5	15	-	≠
6	0	-	-
7	11	:	¼
7	12	i	
7	13	:	¾
7	14	-	÷

Note: The top, left-pointing, arrow is used as an assignment statement; the lower, right-pointing, arrow means "go to"; and the sign ≠ is used as a terminator and for special functions. Note also that the arithmetic operator × (multiply) used in Viewdata is shown as x (lower case x), while the minus sign (-) is code 2/13 and the exponentiation sign is code 5/14 shown as ↑.

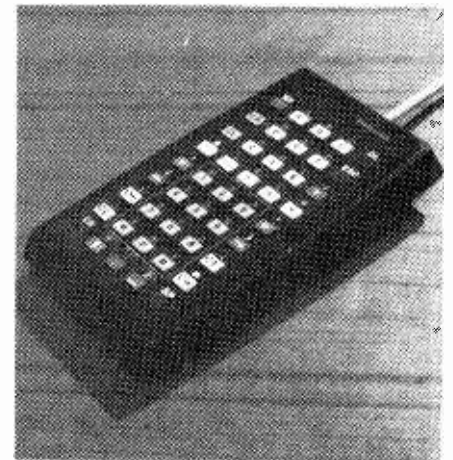▼ Fig. 4. More elaborate, alphanumeric, keypad with a variety of other symbols.



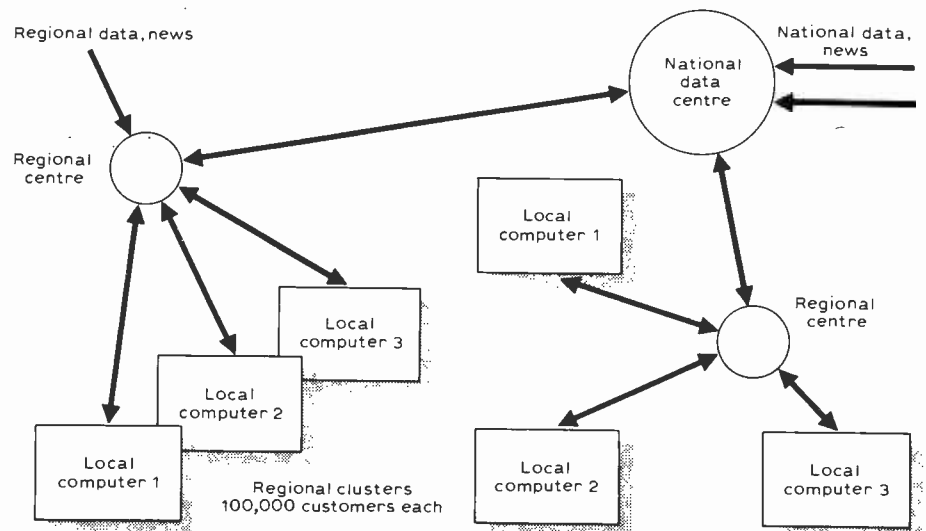▼ Fig. 5. A distributed Viewdata network, showing local computers, regional centres and national data centre.





Bits	b <sub>7</sub>	b <sub>6</sub>	b <sub>5</sub>	b <sub>4</sub>	b <sub>3</sub>	b <sub>2</sub>	b <sub>1</sub>	Col	Row
	0	0	0	0	1	1	1	0	0
	0	0	1	1	0	0	1	1	1
	0	1	0	1	0	1	0	1	2
	0	0	0	0	0	0	0	0	3
	0	1	0	0	0	0	0	1	4
	0	1	0	1	0	0	0	1	5
	0	1	1	0	0	0	0	1	6
	0	1	1	1	0	0	0	1	7
	1	0	0	0	0	0	0	0	8
	1	0	0	1	0	0	0	0	9
	1	0	1	0	0	0	0	0	10
	1	0	1	1	0	0	0	0	11
	1	1	0	0	0	0	0	0	12
	1	1	0	1	0	0	0	0	13
	1	1	1	0	0	0	0	0	14
	1	1	1	1	0	0	0	0	15

▲ Fig. 6. Codes for alphanumeric characters only, as used in both Viewdata and teletext.

Fig. 7 shows the graphics and control characters use in teletext, as at September 1976\*, the conventions being as before, that is:

1. All character rows start in the "steady", "alphanumeric white" and "unboxed" condition without control characters.
2. Control characters shown are displayed as spaces, but control whether alphanumeric or graphic characters are displayed and what colour is used.
3. Alphanumeric characters in columns 4 and 5, i.e. all of the upper case letters and a few others, may be displayed next to graphic symbols without an intervening space.

While the intervening space convention following a control character is essential in teletext, it has been accepted in Viewdata for the sake of uniformity, although it is not really essential and imposes undesirable constraints on the page format.

Additional control characters have recently been added to teletext to provide enhanced display facilities. The "intervening space" convention is somewhat modified and made less onerous, although not all its undesirable effects are eliminated.

The new control characters, which may be applied equally in Viewdata are in four groups:

**Contiguous/separate graphics.** Codes 1/9 and 1/10 in teletext, 5a/9 and 5a/10 in Viewdata. This provides the choice of graphics symbols filling the whole of a character rectangle, or only six discrete and separate dots.

**Normal height/double height.** Codes 0/12 and 0/13 in teletext, 4a/12 and 4a/13 in Viewdata. This provides for the optional display of alphanumeric characters in the standard size, i.e. within the normal char-

\*Broadcast Teletext Specification. Published jointly by the Broadcasting Corporation, Independent Broadcasting Authority and British Radio Equipment Manufacturers Association.

Bits	b <sub>7</sub>	b <sub>6</sub>	b <sub>5</sub>	b <sub>4</sub>	b <sub>3</sub>	b <sub>2</sub>	b <sub>1</sub>	Col	Row	0a	1a	2a	3a	6a	7a
	0	0	0	0	1	0	1	0	0	(NUL)	(DLE)				
	0	0	0	1	0	0	1	1	1	alpha <sup>n</sup> red	graphics red				
	0	0	1	0	0	0	0	0	2	alpha <sup>n</sup> green	graphics green				
	0	0	1	0	0	0	1	0	3	alpha <sup>n</sup> yellow	graphics yellow				
	0	1	0	0	0	0	0	0	4	alpha <sup>n</sup> blue	graphics blue				
	0	1	0	1	0	0	0	0	5	alpha <sup>n</sup> magenta	graphics magenta				
	0	1	1	0	0	0	0	0	6	alpha <sup>n</sup> cyan	graphics cyan				
	0	1	1	1	0	0	0	0	7	alpha <sup>n</sup> white	graphics white				
	1	0	0	0	0	0	0	0	8	flash	conceal display				
	1	0	0	1	0	0	0	0	9	steady	contiguous graphics				
	1	0	1	0	0	0	0	0	10	end box	separated graphics				
	1	0	1	1	0	0	0	0	11	start box	(ESC)				
	1	1	0	0	0	0	0	0	12	normal height	black background				
	1	1	0	1	0	0	0	0	13	double height	new background				
	1	1	1	0	0	0	0	0	14	(S0)	hold graphics				
	1	1	1	1	0	0	0	0	15	(S1)	release graphics				

Fig. 7. Codes for graphics used in teletext.

Bits	b <sub>7</sub>	b <sub>6</sub>	b <sub>5</sub>	b <sub>4</sub>	b <sub>3</sub>	b <sub>2</sub>	b <sub>1</sub>	Col	Row	0	1	2a	3a	4a	5a	6a	7a
	0	0	0	0	1	0	1	0	0	NUL							
	0	0	0	1	0	0	1	1	1	DC1			alpha <sup>n</sup> red	graphics red			
	0	0	1	0	0	0	0	0	2	DC2			alpha <sup>n</sup> green	graphics green			
	0	0	1	0	0	0	1	0	3	DC3			alpha <sup>n</sup> yellow	graphics yellow			
	0	1	0	0	0	0	0	0	4	DC4			alpha <sup>n</sup> blue	graphics blue			
	0	1	0	1	0	0	0	0	5	ENQ			alpha <sup>n</sup> magenta	graphics magenta			
	0	1	1	0	0	0	0	0	6				alpha <sup>n</sup> cyan	graphics cyan			
	0	1	1	1	0	0	0	0	7				alpha <sup>n</sup> white	graphics white			
	1	0	0	0	0	0	0	0	8	BS	CAN		flash	conceal display			
	1	0	0	1	0	0	0	0	9	HT			steady	contiguous graphics			
	1	0	1	0	0	0	0	0	10	LF			end box	separated graphics			
	1	0	1	1	0	0	0	0	11	VT	ESC		start box				
	1	1	0	0	0	0	0	0	12	FF			normal height	black background			
	1	1	0	1	0	0	0	0	13	CR			double height	new background			
	1	1	1	0	0	0	0	0	14		cursor home IS <sub>2</sub>			hold graphics			
	1	1	1	1	0	0	0	0	15					release graphics			

Fig. 8. Control and graphics codes used in Viewdata.

acter rectangle or stretched vertically to double height, the width of each character and the intervening spaces between characters remaining the same.

**Black background/new background.** The background colour of the character rectangle is normally black. Whenever the new background control character 1/13 in teletext or 5a/13 in Viewdata occurs, the display colour then obtaining is adopted as the new background colour.

**Hold graphics/Release graphics.** Codes 1/14

and 1/15 in teletext, 5a/14 and 5a/15 in Viewdata. This allows a limited range of abrupt display colour changes in a row whereas normally there is at least one space between rectangles with different display colours in the same row.

The graphics and control characters in Viewdata are show in Fig 8, but before these are looked at in detail, the use of a cursor in Viewdata should first be explained.


**Cursor.** The cursor in Viewdata is a symbol which shows up on the display as a bright rectangle, filling the space of an upper case alphabetic character. It may be switched on and off, as required, by a switch on the terminal or on the keypad, or by remote control from the computer. It may also be moved anywhere over the display either manually by using special keys on the keypad or by remote control from the computer.

The cursor has many functions.

Bits	b <sub>7</sub> b <sub>6</sub> b <sub>5</sub> b <sub>4</sub> b <sub>3</sub> b <sub>2</sub> b <sub>1</sub>	Col Row	0	1	2	2a	3	3a	4	4a	5	5a	6	6a	7	7a
			0	1	2	2a	3	3a	4	4a	5	5a	6	6a	7	7a
	0 0 0 0	0	NUL		SP		0		@		P		-		p	
	0 0 0 1	1	DC <sub>1</sub>	!		1		A	alpha <sup>n</sup> red		Q	graphics red	a		q	
	0 0 1 0	2	DC <sub>2</sub>	"		2		B	alpha <sup>n</sup> green		R	graphics green	b		r	
	0 0 1 1	3	DC <sub>3</sub>	£		3		C	alpha <sup>n</sup> yellow		S	graphics yellow	c		s	
	0 1 0 0	4	DC <sub>4</sub>	\$		4		D	alpha <sup>n</sup> blue		T	graphics blue	d		t	
	0 1 0 1	5	ENQ	%		5		E	alpha <sup>n</sup> magenta		U	graphics magenta	e		u	
	0 1 1 0	6		&		6		F	alpha <sup>n</sup> cyan		V	graphics cyan	f		v	
	0 1 1 1	7		,		7		G	alpha <sup>n</sup> white		W	graphics white	g		w	
	1 0 0 0	8	BS	CAN	(	8		H	flash		X	conceal display	h		x	
	1 0 0 1	9	HT	)		9		I	steady		Y	contiguous graphics	i		y	
	1 0 1 0	10	LF	*	:			J	end box		Z	separated graphics	j		z	
	1 0 1 1	11	VT	ESC	+	;		K	start box	←			k		¼	
	1 1 0 0	12	FF	,	<			L	normal height	½		black background	l		½	
	1 1 0 1	13	CR	-	=			M	double height	→		new background	m		¾	
	1 1 1 0	14		.	>			N		↑		hold graphics	n		÷	
	1 1 1 1	15		/	?			O		⌘		release graphics	o			

◀ Fig. 9. Complete set of Viewdata codes. columns 2a, 3a, 6a and 7a for graphics and columns 4a and 5a for the controls.

▼ Fig. 10. Block diagrams of (a) a Viewdata terminal and (b) a teletext terminal, showing video connections to the television set.

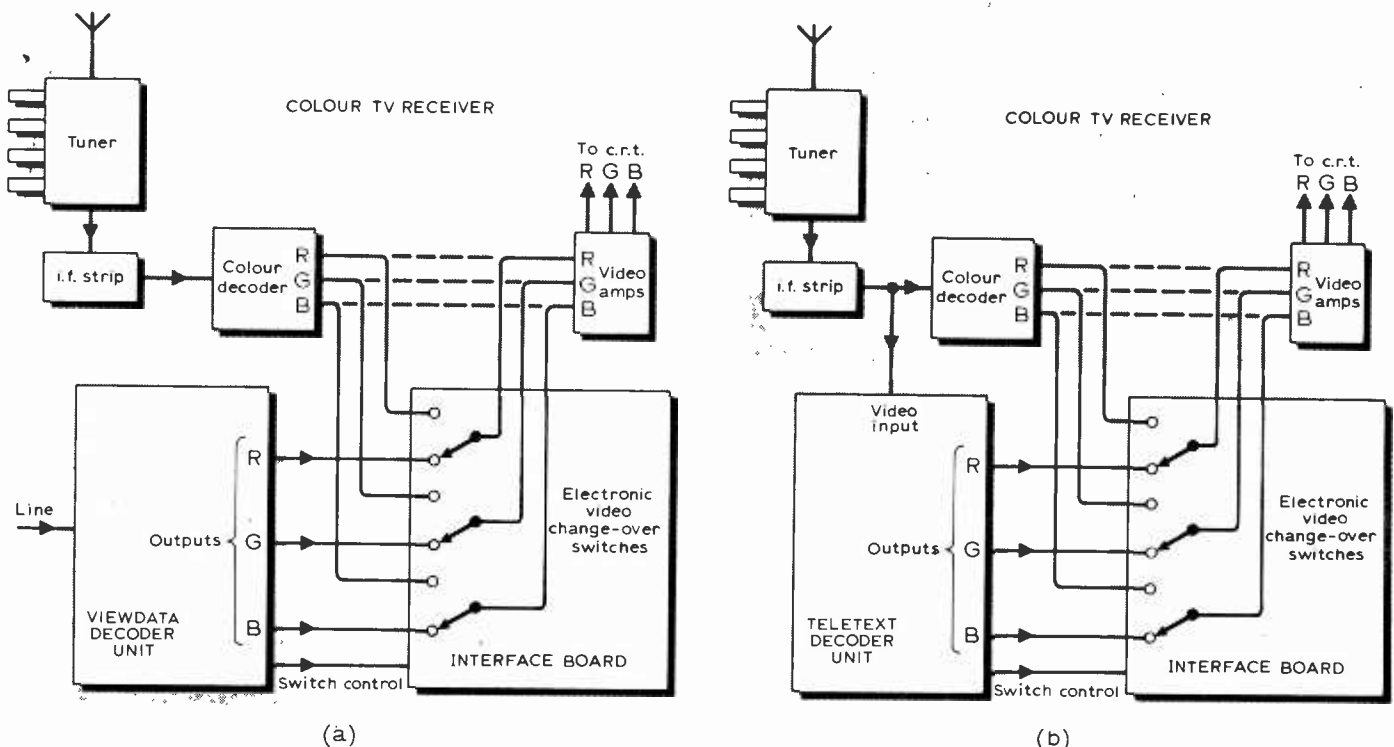

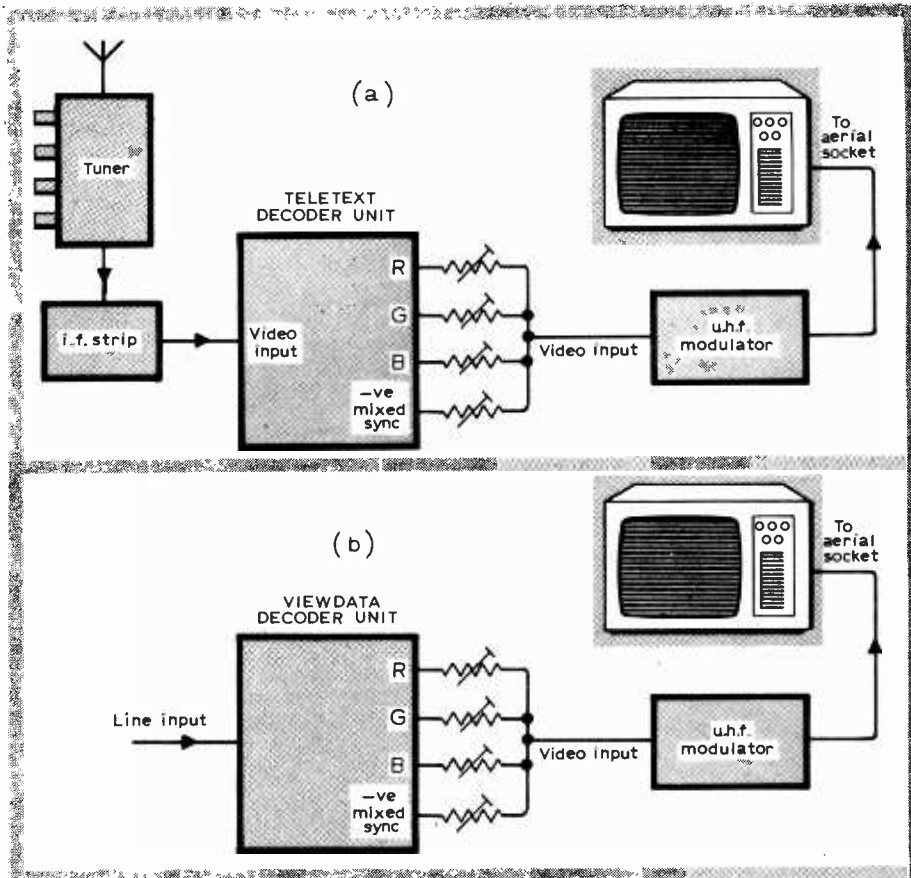


Fig. 11. Block diagrams of (a) a teletext terminal and (b) a Viewdata terminal, showing r.f. (u.h.f.) connections to the television set.

Basically it gives a visual indication of the position on the screen at which the next character sent by the computer will be displayed. When the computer sends a new page of information to the terminal, it first sends a code which returns the cursor, whether visible or not on the display, to the "home" position which is at the top left-hand side of the display. Thereafter, as each character is entered, the cursor is moved one character position to the right. The position of the cursor, whether this is switched on or off, is recorded by two counters, a character counter and a row counter, which maintain at all times a knowledge of the position at which the next character is to be displayed (and entered on memory). Thus we talk of the cursor as if it were a real entity, whether or not it is displayed.

By moving the cursor by means of the controls available (see below), the computer may position it to where the next character is to be entered. Thus it is not necessary to send a series of spaces where one or more blank lines are required, or where a row of characters is shorter than the full length of the line. The cursor also enables the computer to overwrite a portion of a display without having to first erase and retransmit the whole page.

The cursor may also be used at the terminal for editing purposes, e.g. when composing messages or doing calculations, or to point at a feature of the display it is desired to manipulate. In this context the cursor is a powerful communication channel between com-

puter and user which resembles a pointer (but more about this later).

Control characters in columns 0 and 1 must comply with ISO7 for line transmission and so far 15 have been allocated. Additional characters in the same columns may be allocated in future as more facilities are included.

The control characters which have so far been allocated in the experimental system undergoing pilot trials are:

Col/row	Name	Function
0/1	NUL	None-used for timing purposes
0/5	ENQ	Code sent by computer to terminal to initiate automatic terminal identification
0/8	BS	Back-space. Moves cursor one character position to left
0/9	HT	Horizontal tab. Moves cursor one character position to right
0/10	LF	Line feed. Moves cursor one line position down
0/11	VT	Vertical tab. Moves cursor one line position up
0/12	FF	Form feed. Erases screen and moves cursor to top left hand side of screen (position 1)
0/13	CR	Carriage return. Moves cursor to first position on same line
1/1	DC1	Device control 1
1/2	DC2	Device control 2
13	DC3	Device control 3

Combinations of these characters will be used to switch on tape recorders and hard copy devices remotely

- 1/4 DC4 Device control 4. Used to switch off both tape recorder and hard copy unit
- 1/8 CAN Cancel. Used to delete line of character. This code is used only from terminal to computer
- 1/9 ESC Escape. Used to indicate to terminal that the character following is from another set of control codes (in this case the control code set 2a to 7a of colours or graphics)
- 1/10 IS2 Home. Returns cursor to character position 1 on screen (top left hand side)

**Graphics characters.** The graphics and colour control characters for Viewdata are shown in Fig. 8 columns 2a, 3a, 6a, 7a for graphics and 4a and 5a for the controls. For line transmission the control characters of 4a and 5a are always preceded with ESC (code 1/11). On receipt of this code the terminal reverses the polarity of bit 7 from 1 to 0, thus restoring compatibility with teletext and places the characters in store.

The graphics characters in columns 2a, 3a, 6a and 7a are fully compatible with teletext and are treated in the same way when displayed. The complete set of Viewdata codes is shown in Fig. 9.

**Block diagram of terminal.** A block diagram of a Viewdata terminal is shown in Fig 10 (b). This shows the interconnection between the Viewdata decoder and the video amplifier of the colour tv receiver. An interface board contains the electronic switch which provides the changeover from tv reception to Viewdata. The input to the Viewdata decoder unit is, of course, the telephone line. By contrast Fig 10 (a) shows the teletext decoder connections (*Wireless World*, December 1975, pp. 563-566). The input to the teletext decoder is obtained from the i.f. input.

Fig 11 shows a similar set of connections where the entry to the television set for display purposes is the aerial socket of the tv receiver. In Viewdata only (b) a u.h.f. modulator has to be added, whereas for teletext (a) an additional tuner and i.f. strip must be provided. Hence the considerably greater attraction of a built-in decoder in the case of teletext.

(To be continued)

**The journal you like**

*Wireless World's* average circulation last year was up 4,604 copies to 69,220 per month, according to the Audit Bureau of Circulations. Overseas readers, in countries from the USSR and USA to the Falklands and Seychelles, bought 21,000 of these. On average, for the past eight years 200 more readers have joined our circulation each month.

# World of Amateur Radio

## Space and propagation

Martin Sweeting, G3YJO, of the University of Surrey's Oscar telecommand station reports that early this year one of the NiCad cells in the upper half of the Oscar 6 spacecraft (launched in 1972) "took a turn for the worse" and may fail completely; if this happens it is likely that the battery will be irretrievably damaged. He appeals for strict adherence by all amateurs to the operating schedules if Oscar 6 is to survive the year. Additional telemetry information received from the satellite would be welcome and should be sent to: UOS-AMSAT, Department of Electronic Engineering, University of Surrey, Guildford, Surrey. Incidentally, the UK FM Group (London) state that many amateurs in the Thames Valley area have been puzzled by the 144.8MHz wideband transmissions from the UOS-AMSAT telecommand station, G4DVT, at Guildford. This station operates daily for up to 25 minutes at a time, repeating every 100 minutes between 0530 and 2300 GMT.

GB3LBH, the 10GHz beacon station at Romford, Essex recently increased power and now uses a 200mW Gunn oscillator on 10.1GHz; it is regularly received at distances up to 25km including some obstructed paths; this beacon may be used for studies being carried out, by students at Imperial College. A 144MHz beacon (possibly 9H3ML) may be set up in Malta. The 1.3GHz beacon at Andover (GB3AND) with a power of 5 watts e.r.p. has been heard in Devon.

28MHz c.w. and s.s.b. activity periods are now being run by the RSGB on the first Sunday of each month (1200-1800 GMT, 28.0 to 28.1 and 28.5 to 28.6MHz). A new 28MHz beacon is expected to be set up at Lannion in Brittany, France, with the callsign F3THF on 28.227MHz; it also hoped that 50MHz beacons may be established at Lannion and also at Gibraltar as part of a new series of 50MHz transatlantic tests.

It is now thought likely that the

minimum of Sunspot Cycle 20 was reached during July 1976 with a maximum for Cycle 21 predicted around 1981.

## Licence totals

The Radio Regulatory Department of the Home Office are currently distributing (as renewals fall due) the new form of amateur licence (see February issue). Two reasons are given for the changes: "(1) To give you greater flexibility to pursue each aspect of amateur radio without having to apply to us each time for authority to do so; (2) we, in turn, expect to be able to keep within the Government's staff ceiling over the next few years while maintaining the issue of amateur licences without undue delays."

On January 1, 1977 the number of new-style Class A and B licences were: Class A 15,956; Class B 6202; total 22,158.

How the number of old-style licences built up to over 29,000 during the past few years is shown below:

	end- 1968	end- 1971	end- 1974	end- 1976
Class A	13,082	14,082	15,304	15,956
Class B	1,352	3,012	4,966	6,142
Class A/M	2,589	2,666	3,424	4,173
Class B/M	132	545	1,549	2,463
Class F/M	-	-	-	23
Television	186	214	277	318
<b>Totals</b>	<b>17,341</b>	<b>20,502</b>	<b>25,520</b>	<b>29,075</b>

## Amateur TV News

Mr R. C. Hills, G3HRH, Chief Engineer (Transmitters) of the IBA, is the new President of the British Amateur Television Club. He succeeds Mr R. S. Roberts, G6NR, who recently completed his four-year term of office. BATC has recently published a new 110-page book "A guide to amateur television" (non-members £1.75 post paid from BATC, 64 Showell Lane, Penn, Wolverhampton, Staffordshire).

P. Blakeborough, G3PYB, is constructing a vision transmitter for 1296MHz in addition to his 100-watt 625-line transmissions in the 432MHz band. Alan Morris, G4ENS, of Luton is trying to raise interest in proposals for an amateur tv beacon on 432MHz and later a 1296MHz repeater capable of handling tv signals.

## U.H.F. aerial gain

Des Clift, VK2AHC (formerly G3BAK) who has operated on every available band from 1.8MHz to 10GHz has commented in *Electronics Australia* on the problems of reproducing aerial designs from constructional articles, noting that the element dimensions given by different constructors for the same bands often show surprising differences. For 1296MHz he has attempted with only moderate success to build 8-over-8 skeleton slot array; 34-element long Yagi; four square helix; conical reflector with dipole feed, etc.

Arrays for 5.8 and 10GHz which can more readily be based on dishes have proved more successful.

The problem of obtaining gains (reference dipole) of above about 14dB on 432MHz is underlined in the results of the 10th national antenna-gain measuring contest held in the United States last year. The leading designs were: eight times 16-element Yagi (K2CBA) 16.1dB; four times 13-element wooden-boom Yagi (K2UYH) 16dB; G3JBL-type 28-element long quad-loop Yagi (K1LOG) 15dB; 15-element W0EYE-type Yagi (K1LOG) 11.8dB. On 1296MHz a 7ft dish aerial (WA2FGK) registered a gain of 24.3dB; a G3JBL-type 28-element long quad-loop Yagi (K2UYH) 17.1dB.

Such events indicate that many amateurs have an inflated idea of the forward gain of their aerials, possibly due to high front/back ratios.

## In Brief

The death has occurred of Austin Forsyth, OBE, G6FO, for many years editor of *Short Wave Magazine*. Before the war he operated from Newport, Monmouth and for a time from North Devon; more recently from Mads Morton, Buckinghamshire. . . . A working party is being set up by the RSGB "to study the whole Society in depth with a particular relation to the organisation of the Society's headquarters, the organisation of Council and its committees and the inter-relation between HQ, Council and Committees". . . . Seychelles now use the prefix S7, and the prefix S8 has been allotted to Transkei. . . . A mountain top in the Antarctic has been named "Cima Radioamatori" by a recent Italian expedition that kept in daily touch with northern Italy with the help of a number of Italian amateurs. . . . Endorsements for five-band operation are now made by the RSGB for the British Commonwealth Radio Transmission Award, the British Commonwealth Radio Reception Award and the DX Listeners' Century Award. . . . The ARRL National Convention for 1977 is being held (June 3-5) in Canada at the Sheraton Centre Hotel, Toronto; special get-togethers are planned for visiting British and "ex-G" amateurs. . . . Attention was drawn last September to the attractions offered by crystal ladder filters for the home construction of s.s.b. filters. Now, after extensive investigation of this type of filter, J. A. Hardcastle, G3JIR, has reported: "If a single outstanding factor were to be chosen from all the measurements which have been made, it would be that it is almost impossible not to produce a filter of some sort, if guidelines are followed. This should be sufficient to encourage even the most hesitant to try to construct their own crystal filters."


PAT HAWKER, G3VA

# On the bench or in the field.

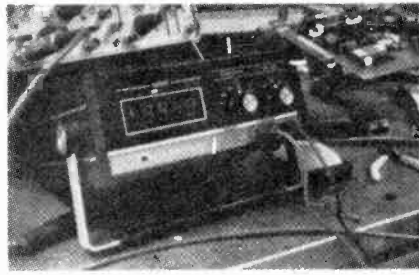**Model 1455. 4½ digit accuracy, stability, resolution. £260**

Here is a 4½ digit DMM that won't tie you down. It's Data Precision's Model 1455, the 4½ digit bench instrument that goes into the field with you.

The 1455 gives  $\pm 0.02\%$  reading  $\pm 0.01\%$  f.s.,  $\pm 1$  digit basic accuracy for 6 months. A five function multimeter with large ½" high, 7 segment planar display and 100% overrange, it measures 100  $\mu\text{V}$  to 1000 VDC, 100  $\mu\text{V}$  to 500 VAC, 100 milliohms to 20 Megohms; AC and DC current 1 microamp to 2 amps, AC response, 30 Hz to 50kHz. These



are specs you'd expect from lab units costing twice as much. But the extraordinary 1455 gives you still more. With its built-in rechargeable NiCd battery, it is completely portable, meaning you can have this in-lab accuracy, anywhere you go.

The 1455 incorporates Tri-Phasic™ Conversion Cycle and our patented Isopolar™ Referencing, just two Data Precision


exclusives that enable us to offer you this kind of accuracy, flexibility and dependability for £260

For versatility and value you won't find anywhere else, carry off a Data Precision Model 1455. Or for the same specs and features in a unit designed for line use only, we offer our Model 1450 for only £240. They're both a lot of multimeter.



**Farnell  
International**

Farnell International Instruments Ltd  
Wetherby West Yorkshire LS22 4DH  
Telephone 0937 3541 Telex 557294

 **DATA PRECISION®**  
...years ahead



WW — 056 FOR FURTHER DETAILS



# When did you last buy your Ford direct from Henry?

Even if you could get a car straight off the Dagenham production line, chances are it wouldn't be the model or colour you wanted.

And the same limits on choice apply if you're buying electronic instruments and power supplies direct from the manufacturer.

If you deal direct with ITT Instrument Services though, it's a different story.

We select the best instruments from all the manufacturers' ranges

available. We stock them in depth. And we fully document them in a comprehensive catalogue available for the asking.

No account to open (if you have one with ITT Electronic Services, then you have one with us), no second bests to put up with.

Just phone, write or telex over your order.

Then sit back and admire our easy handling and remarkable turn of speed.

To: ITT Instrument Services,  
Edinburgh Way, Harlow, Essex.  
Telex 81525.  
Please send me your instrument  
and power supply catalogue.

Name \_\_\_\_\_  
Company \_\_\_\_\_


Address \_\_\_\_\_  
\_\_\_\_\_

Tel. No: \_\_\_\_\_

## **ITT** instrument services

Our catalogue features the full range of Racal counter timers and the 9913 and 9915 frequency meters. It's a range that uses l.s.i. technology to bring you the ultimate in reliability combined with the features you need for your measurement requirements. They're all stocked in depth and can be with you before you can say 99!
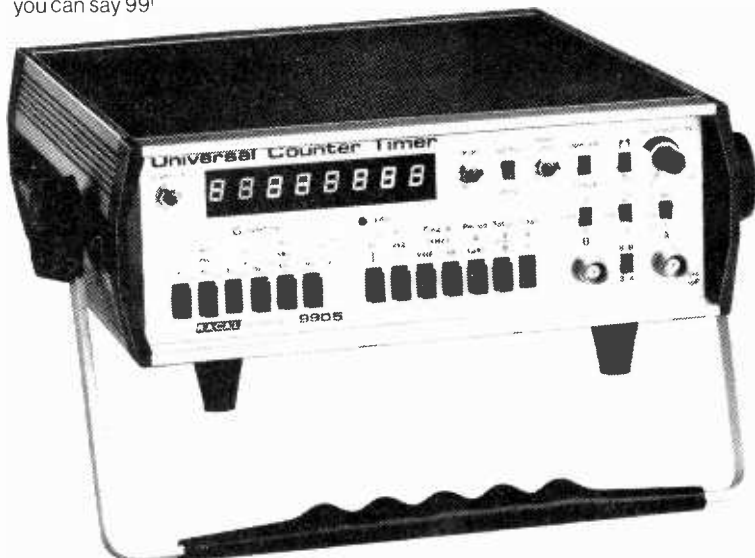
# The only way to buy. Harlow (0279) 29522



WW — 093 FOR FURTHER DETAILS

# Electronic rhythm unit

## Interfacing the M252 and M253 circuits, described in the March issue

by A. Battaiotto and G. Ronzi, *SGS-Ates Application Laboratory, Agrate, Italy*

So that the rhythm section may be inserted into an electronic organ, a signal must be available which indicates whether one or more keys on the organ key board have been played. This signal, which we call the key played, starts the rhythm section. When a key is played the rhythm section can be arranged to start at the beginning of the bar (touch or key operation), i.e. the playing of a key removes the reset from the clock and from the M 252 or M 253.

Alternatively it can be arranged to start at any point in the bar (continuous or silent operation) i.e. the rhythm generator runs continuously, but its output is enabled by the "key played" signal. In continuous operation, therefore, the down-beat indicator is indispensable as it allows the first key to be played when the bar begins.

A third method (continuous free running) allows the unit to operate without playing any of the keys. This is done simply by selecting a rhythm on the push button array of the rhythm section. Neither the touch key nor the continuous silent key must be on when this method is used.

Fig. 11 illustrates the insertion of the electronic rhythm section into an organ. The two parts within dashed lines are details of the rhythm section, of interest for the connections to the keyboard of the organ.

### Rhythm section with 15 rhythms and 9 instruments

This rhythm section, realized with the M 252AA, is programmed with 15 different rhythms in such a way that each rhythm can use up to a maximum of eight of the nine instruments available, Fig. 12. The 15 rhythms programmed are the waltz, jazz, waltz, tango, march, swing, foxtrot, slow rock, pop rock, shuffle, mambo, beguine, cha cha, bajon, samba and bossa nova, and can be brought in one at a time by means of the key board. The instruments available are the bassdrum, snare drum, claves, high bongo, low bongo, conga drum, long cymbals, short cymbals and maracas.

The three controls are volume, tone and tempo. In addition, a switch allows the rhythm to be started at the begin-

ning of the bar or stops the rhythm. The assembly is carried out on two printed circuits, one contains the sound generators and preamplifier, and the other contains the supply, the M 252AA, the variable clock generator and the monostable circuit for driving the down-beat lamp.

The circuit can be divided into four parts, the sound generators, the variable clock generator, the down-beat monostable and the encoder. Operation of the M 252AA has already been described in the first part, but some further details will be given toward the end of this description.

### Sound generators

The generators are designed to reproduce as faithfully as possible the sounds made by percussion instruments. They

can be divided into two broad groups, namely, sounds consisting of damped, sinusoidal waves, like drums, and those consisting of damped white noise, like cymbals.


In the first category we can include the bass drum, high bongo, low bongo, conga drum and the claves, for which the basic circuit is shown around the twin-T parts of Fig. 13.

This circuit is a simple twin-T oscillator with active c.m.o.s.\* element kept slightly below the point of oscillation by the pre-set resistor. To obtain the effect of different frequency instruments you only have to select the right values for the capacitors. The potentiometer also regulates the length of the damping, so that longer or shorter sounds can be obtained.

The command from the M252AA is applied at points BD, HB, etc. As the M252 produces a square wave, the RC

\* A discrete-component oscillator circuit is available on request.

Fig. 11. Connections for incorporating into electronic organ. Rhythm unit parts are within shaded enclosures.

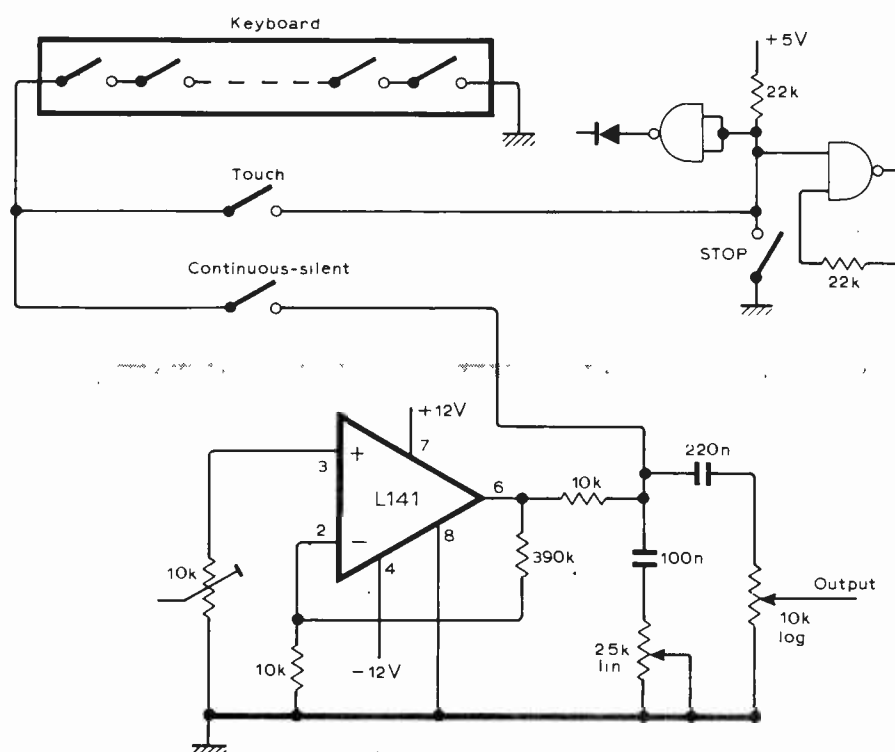


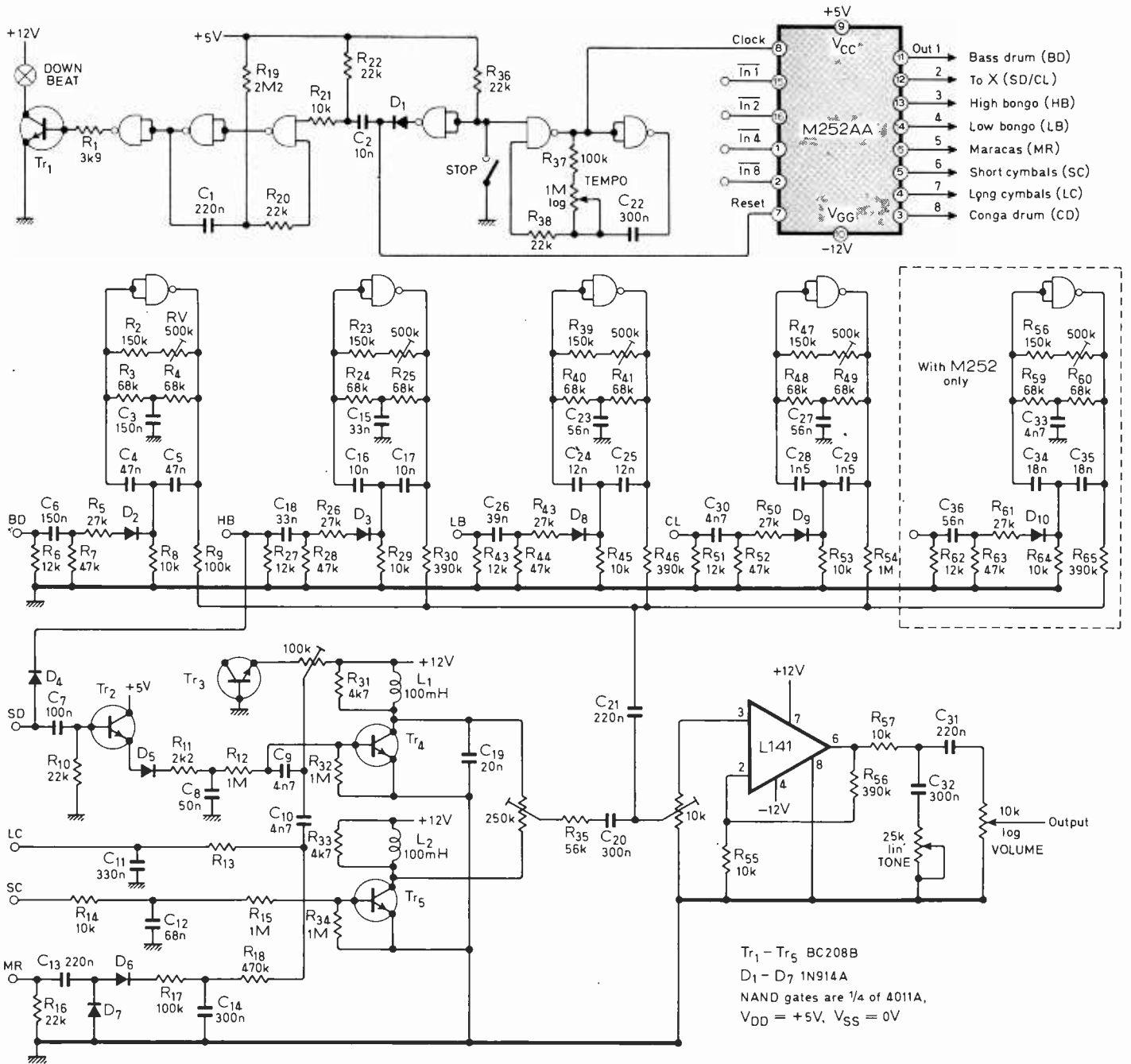


Fig. 12. Use encoder circuit of Fig. 13 with this M252 15-rhythm unit. (Rhythm selection details for M253 circuit will appear in part 3.) Circuit includes twin-T oscillators.

Below is show a conventional three-rail power supply circuit for rhythm generator.

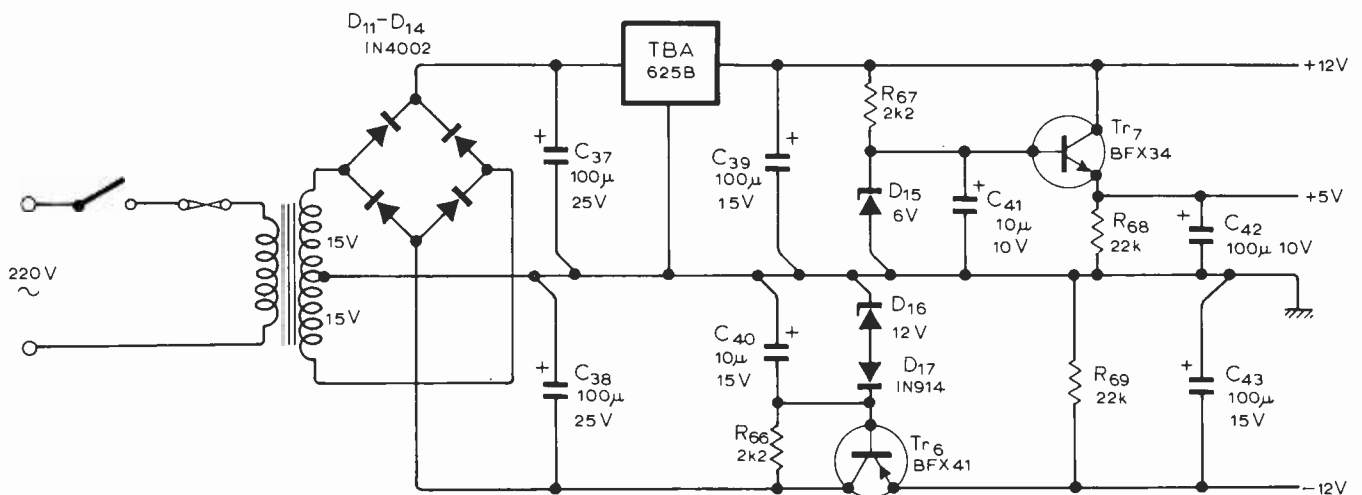

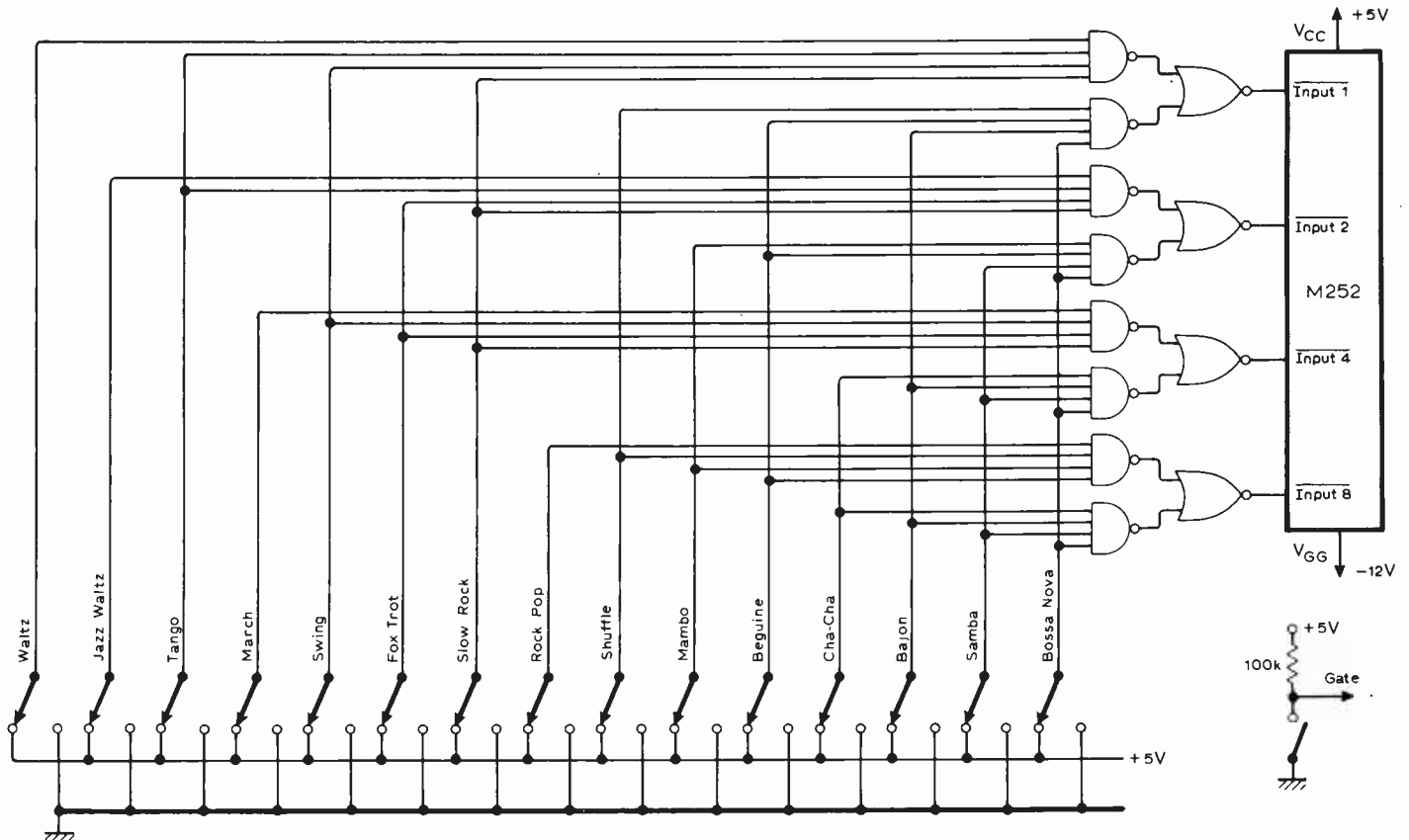


Fig. 13. In c.m.o.s. encoder for use with M252 rhythm unit single-pole switches can be used with resistors if desired. (See part 3 for M253 rhythm selection.)

differentiator (e.g.  $C_6$ ,  $R_7$ ) must be introduced so that a fairly short pulse arrives at the oscillator, which should not interfere with the damping of the oscillation but should be sufficient to activate the oscillator itself. Resistors  $R_{27}$ , etc, keeps the input at earth in the absence of a command, otherwise it would remain floating since the outputs of the M252AA are open-drain types.

In the second category are the long cymbals, short cymbals and maracas, for which the basic circuit is shown bottom left in Fig. 13. Transistor  $Tr_2$  charges the capacitor  $C_8$  during the short command pulse. This capacitor then discharges through  $R_{12}$  and the base of  $Tr_4$ .

The white noise produced by the zener effect of the base-emitter junction of a transistor is applied at the base of  $Tr_4$ . during the discharge of  $C_8$ , therefore, transistor  $Tr_4$  can amplify this noise. The level of amplification, however, will follow the discharge curve of  $C_8$  and therefore a damping effect of variable length will be obtained according to the values of  $C_8$  and  $R_{12}$ .

The inductor and the capacitor at the collector of  $Tr_4$  allow partially selective amplification to be obtained so that some harmonics can be boosted and an effect more similar to the instrument being simulated can be obtained.

Almost all the instruments used in this rhythm section start immediately with maximum amplitude and decrease exponentially. The only exception is the maracas simulator, whose signal increa-

ses progressively and then decreases like the others. This effect was achieved by means of the integrator-differentiator circuit which allows controlled amplification of the white noise. The snare drum is obtained by adding a signal of the second type, i.e. a metallic sound, to a drum sound. Each sound starts on the positive edge of the control pulse.

**Variable clock generator\***

The clock generator is realized with two c.m.o.s. gates and the tempo regulated by means of a potentiometer. When closed, the switch sets the generator in such a way that the output remains at 1 and at the same time the M252AA is reset. By opening this switch the bar begins i.e. the output immediately goes to 0 so generating the negative edge necessary to cause the first command pulse or pulses to be produced by the M252AA, according to the rhythm selected.

**Down-beat\***

This too is made with two c.m.o.s. gates. The down-beat pulse supplied by the M252AA is too short to light a lamp. Also it occurs at the end of the bar whereas the lamp should be lit at the beginning. This monostable, Fig. 12 top, which starts on the negative edge i.e. at the beginning of the bar, operates with an auxiliary transistor in such a way that the lamp lights for a sufficient period of time to indicate the beginning of each bar.

\* Alternative clock generator and downbeat circuits have been designed using t.t.l., h.l.l. and discrete components. Copies are available from editorial office.

**Encoder†**

Circuit, Fig. 13, uses HBF4012A four-input NAND gates, and HBF 4001A two-input NOR gates. If simple single-pole switches are to be used rather than an array of two-way switches, 15 resistors of 100kΩ must be inserted as indicated.

**Rhythm section with 12 rhythms and 8 instruments**

An alternative rhythm section was realized with the M253AA in which 12 different rhythms are programmed, each rhythm being able to drive simultaneously a maximum of seven out of the eight instruments available.

The 12 rhythms programmed are the tango, waltz, shuffle, march, slow rock, swing, pop rock, rumba, beguine, cha cha, samba and bossa nova. These rhythms can also be combined; two more can be selected simultaneously.

The instruments are the same as for the preceding unit with the exception of the conga. The adjustments too are equivalent, and the assembly is simply carried out on two printed circuit boards (£6 inclusive from M. R. Sagin, 23 Keyes Road, London NW2).

The sound generators, variable clock generator and monostable for the down-beat, are the same as for the M252 rhythm section.

The keyboard has the function of connecting the snare drum or the claves to the third output of the M253AA, according to the rhythm selected.

† Alternative encoder circuits are possible using mechanical switching, a diode matrix or t.t.l. gates. Copies of circuits may be obtained from the editorial office.

To be concluded

# Letters to the Editor

## THE WARDEN REPORT

Having read your leading article "WARC talk" (December 1976) and the follow-up article "Who is warden over the Wardens" (January issue), we feel it might be informative to your readers to learn of the mobile radio industry's reaction to these two articles.

We should confirm that the EEA were given an opportunity to examine carefully the Warden report, an industry working party was set up and its view of the report was placed before the Home Office Mobile Radio Committee.

The industry was critical of many sections of the report but all companies supported, *inter alia*, that part of the Warden report which called for additional spectrum for land mobile services.

It should be emphasised that this report was probably the first of its kind with anything like its depth, and was a major contribution to the understanding of the many factors which affect the use of the spectrum by all mobile radio users.

Subsequently, one of our member companies has produced a report (the Pannell report) which presents a view supported in large measure by the industry and demonstrates that something like 100MHz, is required between now and 1999. [See leader in February issue — Editor.]

It is quite understandable for a regulating department to take a rather conservative attitude but, as they are aware of the views of the users and the industry, we have confidence that the Home Office strategy at WARC will result in these views carrying considerable weight.

In conclusion, we ought to point out that your "Warden" article is misleading in three matters. Mr Warden has not, as far as we are aware, (a) completed a report on broadcasting; (b) reached the conclusion that there was "no further need for any allocation to mobile radio above what it had already got"; (c) said that "any further channels which did become available should go to the Post Office" — indeed, we understand that the Post Office were asked to go to 12.5kHz channel spacing and to prove further need for more spectrum.

We trust this will be helpful in explaining the EEA view on this very important matter. J. W. Carlton, Chairman, Mobile Radio Committee, Electronic Engineering Association, London WC2.

## CURRENT DUMPING AMPLIFIER

The recent controversy on the current dumping amplifier (December 1975 issue and subsequent letters) has not come up with any consensus as to whether it is just an elegant method of applying feedback or whether there is an element of feedforward in it. It can be shown quite easily that with an amplifier of finite open loop gain (and consequently finite feedback), the current dump trick achieves much more than feedback alone possibly could. An expression is derived below for the current dump configuration given by Mr Walker and Mr Albinson in *Wireless World* (Dec. 1975), but the amplifier considered has a finite open loop gain and a finite input impedance. With these constraints, and assuming an arbitrary non-linear transfer function for the current dump block, an expression can be derived wherein it can be shown that the error in the current through  $Z_4$  is exactly compensated for by the current through  $Z_1$  provided the conditions given in equation 4 are satisfied.

$$V_{o1} = A(V_{in} - V_i) \tag{1}$$

$$V_i = (Z_1 || Z_3 || Z_{in}) \left( \frac{V_{o1}}{Z_3} + \frac{V_{in}}{Z_{in}} + \frac{N(V_{o1})}{Z_2} \right) \tag{2}$$

$$V_L = (Z_L || Z_4) \left( \frac{V_{o1}}{Z_1} + \frac{N(V_{o1})}{Z_4} \right) \tag{3}$$

Simplification yields the combination required to make  $V_L$  independent of  $N(V_{o1})$

$$\text{i.e. } \frac{Z_1 Z_2}{Z_3 Z_4} = \frac{1}{1 + \frac{1}{A} \frac{Z_3 || Z_4}{Z_1 || Z_2 || Z_3 || Z_4}} \tag{4}$$

For an infinite gain op-amp, equation 4 reduces to Walker's original form. To confirm this result an amplifier was made with a variable open loop gain (A). This variation in open loop gain was obtained in an elegant manner by connecting a potentiometer across the compensating terminals of the operational amplifier used. The circuit was designed to have minimum distortion for an open loop gain of approximately 52dB, corresponding to 20dB of feedback. Fig. 2 shows the results which confirm that increasing feedback beyond a particular value makes the distortion figure worse. In fact with all the current dump elements removed and the same amount of feedback (20dB), the distortion measured 3.1% against the null reading of 0.4%. This should remove any doubt about the effectiveness of the method, and Mr Walker and Mr Albinson of the Acoustical Manufacturing Company should be congratulated on innovating a most elegant method for removing distortion and for eliminating thermal problems associated with the output stages of high power audio amplifiers.

D. M. Divan and V. V. Ghatge, Philips India Ltd.

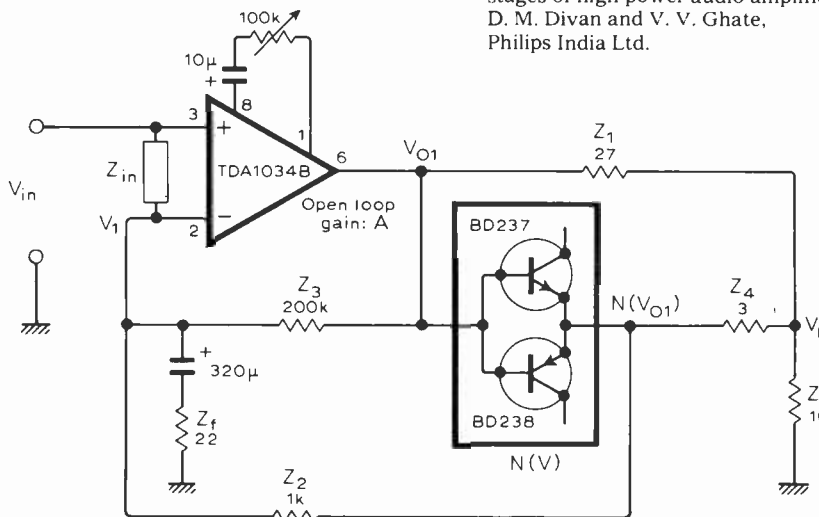


Fig. 1

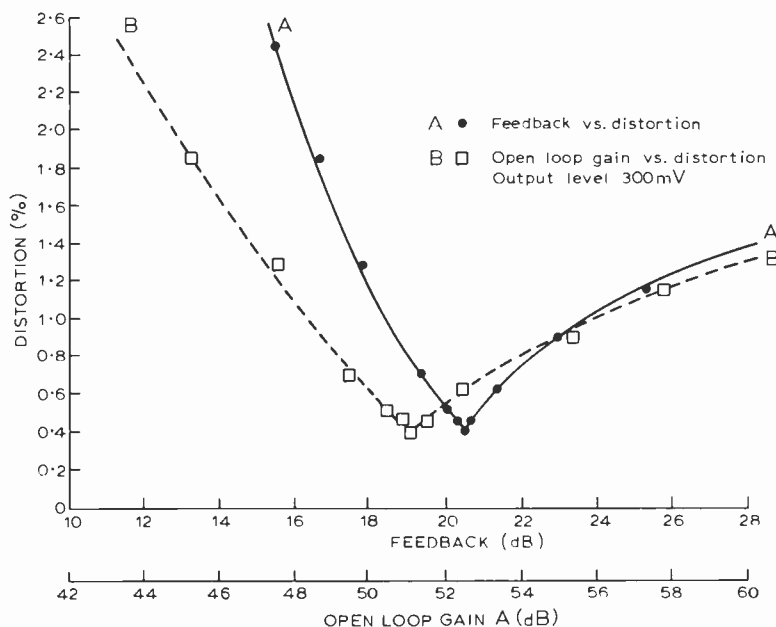


Fig. 2



## ADVANCED PREAMPLIFIER DESIGN

The letter from Mr Watts in your February issue and the answer from Mr Self is notable for two factors — the abrasive language of the former's criticism and the surprisingly temperate reply from the latter. Frankly, I, too, could find much to fault in the design but, of course, there are ways of expressing it, aren't there?

My main criticism of Mr Self's design is that it is over-engineered, conceived by a hi-fi enthusiast who apparently has not been too involved in the costing process when putting together the elements of a circuit. The principle of Occam's Razor is also the essence of good design technique. He has also overlooked the simple facts of life — that despite the extremes to which one may go in designing equipment of this type, the aberrations that are inherent in all programme sources available to the domestic user are likely to be far greater than those introduced by even the most modestly designed reproducing equipment.

But Mr Watts is guilty of worse errors, in dealing with pure theory, opinion, and dressing it up as fact. Let me take one example — and since he seems to invite challenges, here's another from me. If he is able to produce for me a *high grade pickup cartridge* capable of the sort of amplitude linearity input when correctly loaded that he insists should be observed in the equalised input stage and will deliver consistently peaks in excess of 200mV, then there is £5 ready in my hand for any charity he cares to name.

Reg Williamson,  
Norwich.

## AURAL SENSITIVITY TO PHASE

As comment on the two letters in the February issue may I summarise some comment that I have made many times on the subject of the effects of phase shift in a monaural channel?

If a wideband speech or music signal is fed into a transmission system the system design must ensure that the low frequency components and the high frequency components arrive at the output end at about the same time. Clearly there will be some loss in sound quality if the low frequency components arrive today and the high frequency components arrive tomorrow. Thus there must be a limit to the differences in the transmission time that can be allowed. The CCIR standards define the permissible differential time delays for high quality systems, typically the 5kHz components may be delayed by around 5 milliseconds with respect to the 1kHz reference signal before a quality change is noticeable.

If we (mistakenly) choose to express this permissible time delay as a phase shift, it is some 9000 degrees, that is, the start of the 5kHz component can be delayed by about *twenty five cycles* before the shift is aurally noticeable. The wave shape at the system output then bears no relation to the waveshape at the system input.

If anybody has any evidence that time delays inside the CCIR values can result in

obvious differences in sound quality then the data should be produced as a contribution to the art. Our own work appears to show that if a skilled listener has the opportunity to listen repeatedly to a signal while the time delay is switched in and out of circuit, he will eventually come to detect a shift of about 3 milliseconds (rather than 5 milliseconds quoted above) but these observations only serve to confirm that the delay limit specified by CCIR is a reasonable choice for the ordinary situation where repeated comparison is not possible.

James Moir,  
James Moir & Associates,  
Chipperfield,  
Herts.

## DISTORTION AND THE EAR

After reading D. Self's article, "Advanced preamplifier design" in your November issue, I feel obliged to comment on the general attitude to audio amplifier design taken by the majority of WW contributors. At the core of this approach is the assumption that any loss of realism, originating from amplification within the reproducing train, is a direct function of t.h.d. Consequently with each new design appears detailed analysis of t.h.d. performance but, from the user's point of view, the lack of any comparative listening test is painfully obvious.

A striking example of the ear's dissimilarity to a t.h.d. meter would be the attempted measurement of distortion from an audibly inferior preamplifier of a sinewave signal recorded on disc. Wow and tracing distortion combine to swamp the amplifier's contribution by orders of magnitude, but the amplifier's imperfections are all too obvious through the reproduction of voice or music from the same source.

If an accurate model of the human audio processing path existed, it would be possible to design with confidence circuits that introduced the theoretical minimum of audible colouration. Unfortunately, this model does not exist and any major advancement in amplifier quality can only be achieved through extensive, practical listening comparisons of all types of active devices and circuit configurations.

After experimenting for several years in this direction and through the careful analysis of designs proved to be audibly superior, the one common factor to emerge is an appreciation of the ear's uncanny ability

to detect high order distortion products under heavy masking by low order products and noise. In essence, the ear will react favourably to 1st order distortion products in the order of one per cent, provided all higher order products are virtually non-existent. Although it has been long accepted that the ear does favour colouration derived from low order products, the relative weighting ratio (for a given degree of colouration) has never been established and I believe has been consistently under-estimated.


If one applies this theory to high quality amplifiers, the design rules are radically altered. Bipolar transistors become virtually useless in low level stages because of the complex exponential transfer characteristic. Negative feedback (even locally applied) tends to be a disadvantage because innocuous low order distortion products are converted to lower level, but audibly more apparent, higher order ones (Ref. Scroggie) and the output impedance of devices becomes a significant source of distortion. Space allows no further elaboration but a simple example of this alternative approach is given in the form of a unity gain buffer stage. Anyone interested in conducting a comparative listening test (on a high quality stereo system) between this circuit and the standard emitter-follower may find the lack of correlation between measured t.h.d. and audible colouration interesting.


A. King,  
Glenroy,  
Victoria, Australia.
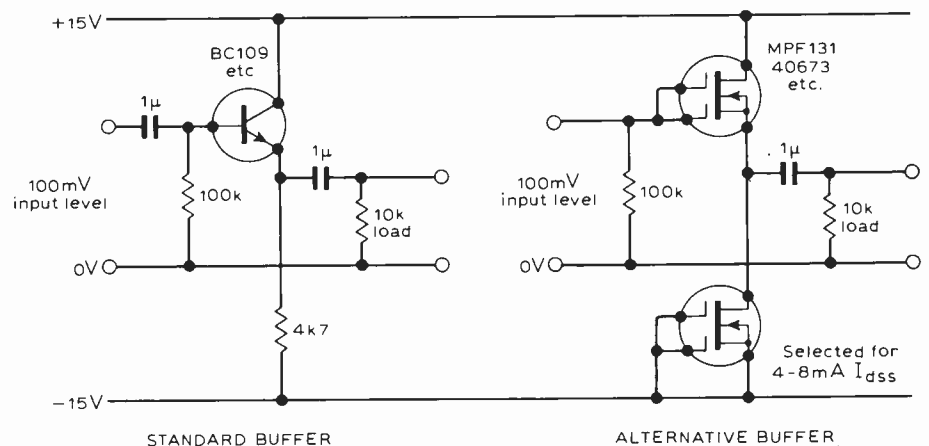
## LINEAR PHASE LOUDSPEAKERS

As Mr Gorman pointed out in his letter in the February 1977 issue, the arguments arising from the advocacy of linear phase loudspeakers have generated much interest, heat and correspondence. May I be allowed to add to the last by enquiring of your other correspondents what importance should be attached to the position of the listener who has set up his linear phase loudspeakers in the normal stereophonic configuration?

In the diagram (overleaf) I shall assume that two linear phase loudspeakers (which I assume may be regarded as point or at most line sources) have been situated at points A and B of an equilateral triangle ABC of side, say, 2 metres. The listener being conscientious (and also being a point receiver) situates himself at C. Unfortunately before he can begin to appreciate the benefits of a linear



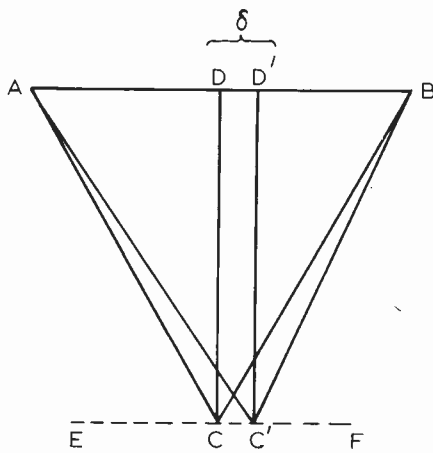

phase configuration, a malevolent deity displaces him a small distance  $\delta$  metres along the line EF to C'. Trivial geometry shows that in these circumstances there is a difference in path lengths  $AC' - BC'$  equal to

$$\sqrt{3+(1+\delta)^2} - \sqrt{3+(1-\delta)^2} \approx \delta \text{ metres.}$$

Thus, assuming a speed of sound of, say, 330m/s, a displacement of 10cm will produce approximate cancellation of a steady signal of wavelength 20cm, i.e. a frequency of 1.65kHz, and will do funny things to the phase of signals near that frequency.

Of course the listener should not have allowed himself to be displaced from point C, but the malevolent deity who is also cunning provided him with two ears placed about 20cm apart. Thus the poor listener (who, being conscientious has avoided the trap of inducing phase distortion by, say, wagging his head from side to side) is left in the position that the only way he can effectively enjoy the linear phase of the stereophonic set-up is to block-up one of his ears and locate the other at C.

N. G. Shipley,  
London, EC4.

## AMPLIFIER DESIGN

There is clearly an interesting disputation in the making regarding pre-amplifiers between Messrs Watts and Self (February letters). I particularly note that both seek upwards of 40dB overload margin. Why? There is no point in it unless the main amplifier and the loudspeakers could also handle 40dB overload. But in a real world what would happen? If such a sound level could be produced it is more than likely to permanently damage the ears, a fearful consequence of some such little *faux pas* as dropping the pickup.

Reality calls for a limitation of peak power and that limitation is best achieved by a means which minimises the resulting and inevitable distortion. More by accident than design valve amplifiers working in Class A had that useful property.

Mr Sundqvist (February issue) is now spelling out for us the details of i.m. distortion and it is becoming more generally apparent that transistor design needs far greater thought and attention to detail if i.m. and other distortion is to be kept at innocuous levels. In particular he is making us aware of the danger of feedback over several stages of undefined bandwidth in that a transitory condition will arise of a maximum signal at some point where feed

back has failed, for an instant, to reduce the signal to its normal working level. Several cures were suggested including a generous overload margin.

May the current vogue and justifications for large overload margins arise from a possible subconscious reaction to hearing i.m. distortion which is then irrationally justified in terms of some supposed large transient output from the pickup? How in a practical world would this transient find its way on to the record, and if it could be present will not the normal mechanical constraints ensure it is never produced? Why in fact does virtually all discussion of high fidelity reproduction assume no significant defects in the recording amplifiers etc? Were this really true there are, and have long been, practical designs for near perfect reproduction amplifiers.

Be that as it may; the recordist does not, indeed he dare not, shrink back from some means of volume compression even if it be no more than simple manual control. That is his tool for avoiding the overload situation and if he has done his job properly may I ask what distressing signal, capable of upsetting a pre-amp, can come off a record via a pickup?

The truth of the situation is more likely that pre-amps are generally badly designed and, transistors being deceiving little beasts, they react in ways that are not expected. Mr Self would not have it that the first part of his pre-amp was, as Mr Watts claimed, a phase shift oscillator, but I can safely say from recent practical experience that similar arrangements are quite capable of oscillating at h.f. or l.f. and showing h.f. oscillation on part of an l.f. cycle when fed with a normal sine wave. They have in fact mutual conductances far beyond those of valves, and these increase more or less directly with current flow and have no clear inbuilt limiting mechanism as has a valve, which limits in most circuits just as soon as the grid becomes positive. Without limiting, a transistor may well start an h.f. oscillation; the circuit comprising *inter alia* stray reactances, in which its own widely variable capacitances will figure. This of course may establish a form of blocking oscillator. If the crucial reactances are within the transistor chip the designer has a fearsome problem on his hands.

Here Mr Watts chooses a policy of avoidance by using an i.c. in the no doubt well founded belief that these have been the subject of such exhaustive designing processes, so that they may be marketed as being vice free, that he needs fear no unwanted side effects. Mr Self attacks on the grounds that i.c.s have greater noise, which seems to be yet another airing of the irrational oversight of the way in which noise in later stages is lost in the amplified noise from earlier stages.

However, the most intriguing feature of Mr Self's design and defence concerns the 1 n 5 capacitor from base to emitter of the input transistor. Why not to earth, if as claimed, it is an r.f. bypass? May the truth be that by some chance it is solving some instability problem? Certainly by trying out a number of preamp designs I have learnt to realise RIAA stages are exceedingly prone to strange problems. But then a warning was issued by J. Linsley Hood in the September 1971 issue of *Wireless World* concerning two, let alone three, transistor high gain circuits. Perhaps we do not learn and continue to fall into the same traps.

C. Streatfield,  
Poole,  
Dorset.

## NORTH SEA COMMUNICATIONS

I have read with interest your report in the December 1976 issue (p.44) of Mr L. Buttriss's talk to the World Offshore Oil Conference.

How easy it is to knock those who are pace setting and breaking new ground and who occasionally fall short of the standards which Mr Buttriss sets. Considering that Mr Buttriss's organisation is only following along behind others who are in the front line, as it were, I suppose he is in a very good position to develop hindsight, which as we all know is a splendid quality.

If Mr Buttriss was a little nearer the front line action he might recognise the difficulties with which the British Post Office have had to cope, not to mention systems designers like my organisation whose clients found themselves at the mercy of a takeover exercise near to Mr Buttriss.

It is always easy to generalise on the failings of others, unspecified of course, but not always the wisest policy if your livelihood depends to a large extent on the said others.

W. T. Brown,  
Macclesfield,  
Cheshire.

## TALKING BOOKS APPEAL

A few years ago you were good enough to publish an appeal for servicing volunteers for the British Talking Book Service for the Blind. As a result many new volunteers were enrolled.

As the service has expanded so has the need for servicing volunteers and I would ask anyone who can repair a simple tape recorder, and can spare a little time, to contact the address given below for further details.


These Talking Books mean a lot to the blind people who use them and their gratitude for the help given by servicing volunteers amply compensates for the loss of a few hours spare time.

The address to contact is: British Talking Book Service for the Blind, Nuffield Library, Mount Pleasant, Wembley, Middx. HAA 1RR. Telephone: 01-903-6666  
A. J. Smale,  
London N21.
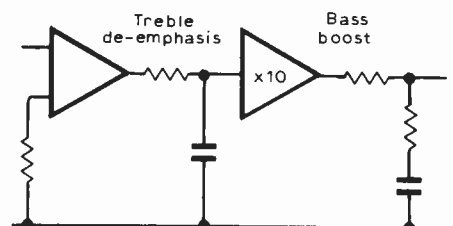
## Corrections

The diagram below was inadvertently omitted from Mr Graham Nalty's letter in the February issue on the Advanced Pre-amplifier Design.

Also, the heading "Re-invention" was omitted from Mr K. H. Green's letter (top of page 60). Apologies to Mr Nalty, Mr Green and our readers.



# Stereo coder

## 1 —Choice of method/oscillator stability

by Trevor Brook

**A practical design for a high quality coder suitable as a test instrument is described. Apart from the audio filtering, inductors have been avoided and a compact board layout produced. A v.h.f. unit for servicing checks on receiver performance could also be used by demonstration showrooms to feed programmes of their own choice to stereo tuners.**

**Part 1 examines the stereo multiplex system and establishes tolerance limits for signal components. Channel separation is considered as this would assume increased importance if a matrix system of surround sound broadcasting were adopted. Part 2 gives construction and alignment details for the coder and Part 3 gives modifications to the Portus and Haywood decoder to provide a low distortion reference decoder.**

Work on this coder started originally out of curiosity as to whether an inductorless design would be possible. Early experiments were promising and the design has been pursued to give performance of broadcast quality.

The specifications of stereo coders now in use at both national and independent local radio transmitters are given in Table 1 and most existing coders have similar figures. Particular objects of this design are to improve crosstalk at the higher audio frequencies and achieve mid-frequency distortion better than 0.05%.

### Stereo signal specification

The modulating signal in the Zenith-GE pilot tone system is defined as

$$0.9 \left( \frac{A+B}{2} + \frac{A-B}{2} \sin 2\pi f_c t + 0.1 \sin \pi f_c t \right)$$

where A is pre-emphasized left channel, B is the pre-emphasized right channel, and  $f_c$  is 38kHz.  $\frac{1}{2}(A+B)$  is called the sum or M signal, and  $\frac{1}{2}(A-B)\sin 2\pi f_c t$  is called the stereo difference or S signal, and is a double sideband suppressed-carrier signal.  $0.1\sin \pi f_c t$  is the pilot signal at 19kHz.

Substituting the maximum values  $A=+1$  and  $B=+1$  or  $-1$  gives the maximum amplitude of 90% for the M

and S signals respectively. Monophonic receivers continue to produce only the M signal as audible output thus giving the system its compatibility.

### Decoding

To retrieve the stereo information involves a decoder which can take the form in Fig. 1. The reduction in channel separation if a decoder adjusted to


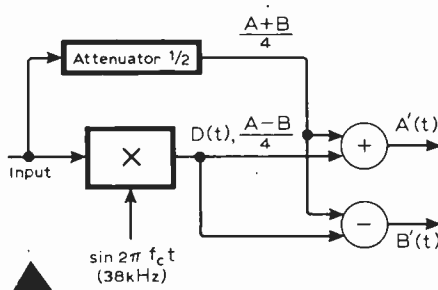


Fig. 1. How the stereo multiplex signal can be decoded. After de-emphasis the A' and B' outputs become left and right channels.

decode a perfect multiplex signal is presented with signals having the five following departures from ideal is shown in Fig 2:

- amplitude error between the M and S signals
- phase error between the M and S signals
- phase error in the pilot relative to the 38kHz suppressed carrier. The requirement for pilot phase accuracy is substantially less than for M/S phase accuracy
- amplitude error of one sideband only of the S signal, typical of the h.f. loss

Fig. 2. Inherent crosstalk of the multiplex signal plotted against  
 1) Amplitude error between the M and S signals  
 2) Phase error between the M and S signals  
 3) Error in pilot phase  
 4) Amplitude imbalance between the sidebands of the S signal  
 5) Phase shift in a sideband of the S signal

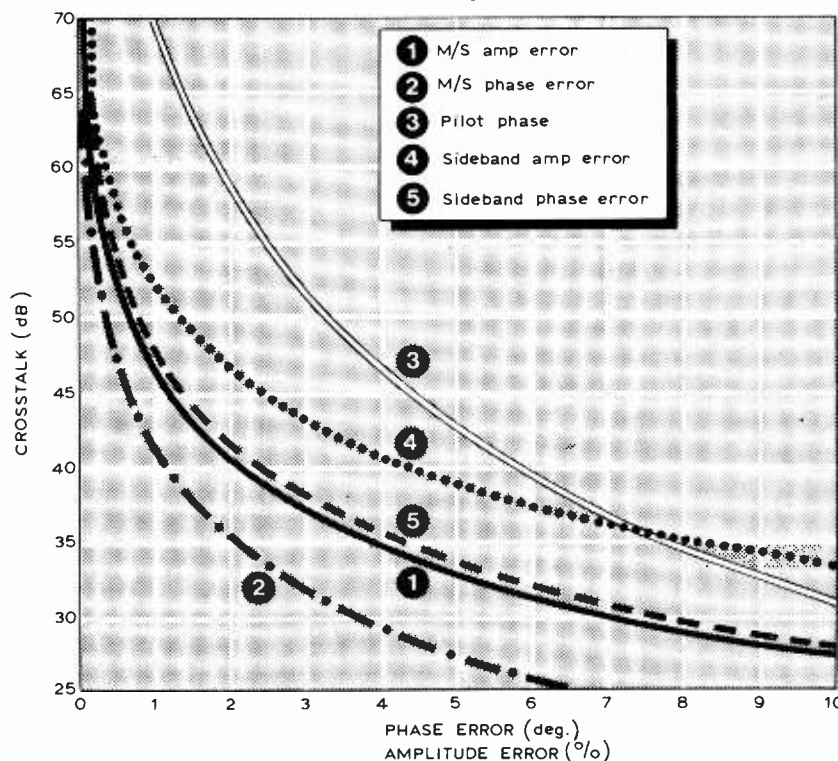

**Table 1. Some parameters of the broadcast coders in use today.**

	BBC	IBA
Amplitude response $\pm 0.5\text{dB}$ $\pm 1\text{dB}$	60Hz — 10kHz 40Hz — 15kHz	50Hz — 15kHz —
Channel separation	100Hz — 10kHz $\geq 40\text{dB}$ 10kHz — 15kHz $\geq 36\text{dB}$	400Hz — 5kHz $\geq 48\text{dB}$ 30Hz — 15kHz $\geq 42\text{dB}$
Harmonic distortion (1kHz)	0.3% at 2dB above peak level	0.5% at peak level
38kHz leakage	$< 40\text{dB}$	$\leq 40\text{dB}$

encountered in receivers

— phase error of one sideband only of the S signal.

For reasonably high channel separation, say better than 45dB, the above effects may be considered as algebraically additive. It is evident that extremely stringent amplitude and phase performance requirements are set for a coder intended to give high channel separation.

Another problem in the multiplex system is distortion. Apart from the usual harmonic and intermodulation distortions, spurious beat tones can be produced in the decoded outputs. This is the result of intermodulation between the various components of the stereo signal and, though predominantly a receiver problem, could also be caused in the signal generation method or in a coder's output amplifier. Beat tone distortion is worst at the higher audio frequencies and subjectively produces an unpleasant 'splashing' sound on sibilants. Most stereo receivers will give clearly audible low- or mid-frequency beats on the 10 and 14kHz bursts during the BBC stereo test zone transmissions even though these tones are not at full level. On mono reception of a stereo signal the effect is not noticeable except on very poor receivers. Fig 3 shows the beat tone possibilities in both mono and stereo reception.

**Generating multiplex signals**

There are two principal ways of producing the coded stereo signal. The first and almost universal are switching methods, while the second is the matrix method where the individual signal components are generated separately and then added together.

Conceptually the simplest and also a common way of switch encoding is to switch between the A and B signals with a diode ring or similar device driven by 38kHz, Fig 4. For a square wave switching signal the following output is produced

$$\frac{A+B}{2} + \frac{A-B}{2} \cdot \frac{4}{\pi} \left| \sin 2\pi f_c t \right. \\ \left. + \frac{1}{3} \sin 6\pi f_c t + \frac{1}{5} \sin 10\pi f_c t + \dots \right|$$

The snag is that sidebands around odd harmonics of the switching frequency are present in the output and, more difficult, the required difference signal

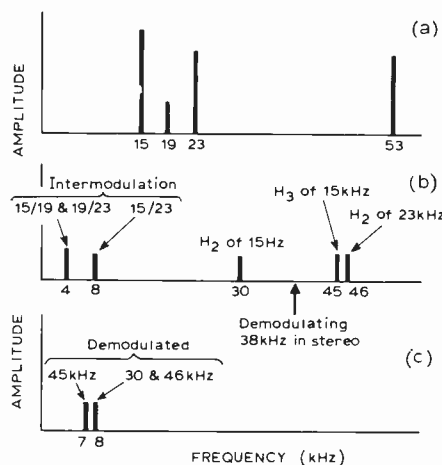


Fig. 3. Principal possibilities for production of beat tone distortion in any receiver (b) whenever a composite stereo signal (a) undergoes intermodulation distortion. Additional tones are produced in a stereo receiver (c).

has too high an amplitude. To remove the components above 53kHz as well as reduce the S amplitude by  $\pi/4$  requires a filter with the amplitude characteristic shown in Fig 5, and a linear phase response at frequencies below 53kHz! Broadcast quality coders typically use ten or so inductors in such a filter. Other switching arrangements can avoid the necessity for S amplitude correction and in other respects switching coder performance is largely determined by switching time and 1:1 accuracy of the 38kHz square wave. Whatever low-pass filter is required practical realisations need careful alignment involving several interdependent adjustments and

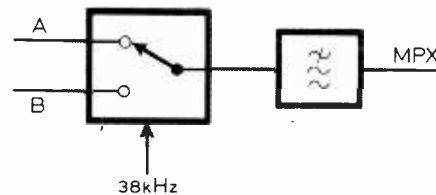


Fig. 4. Basic arrangement for the switch encoding method. Switch would typically be a ring of diodes or f.e.t. switch driven by the 38kHz square wave.

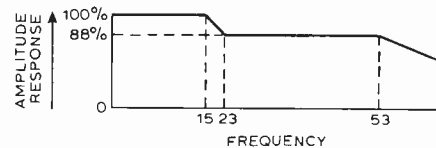


Fig. 5. Desired characteristic for the filter in the simple switch coder, Fig. 5. A linear phase response is required up to 53kHz.


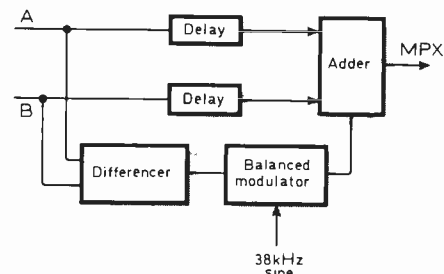


Fig. 6. Block diagram for the matrix coding method.

deficiencies in the filter make such coders susceptible to all the forms of signal degradation listed earlier. A complete switching coder design has been published by Mack<sup>1</sup> and the virtues of diode cross modulator circuits for applications including coding stereo extolled by the same author<sup>2</sup>.

The matrix form of coding is shown in Fig 6. A point to note is that the 38kHz fed to the multiplier in this case is a sine wave. Another alternative would be to use a conventional switching multiplier

Fig. 7. Complete block diagram of the coder described.

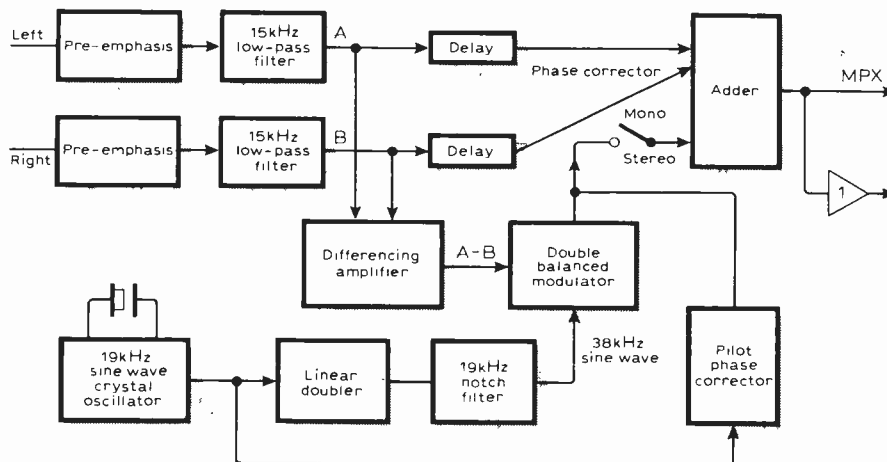

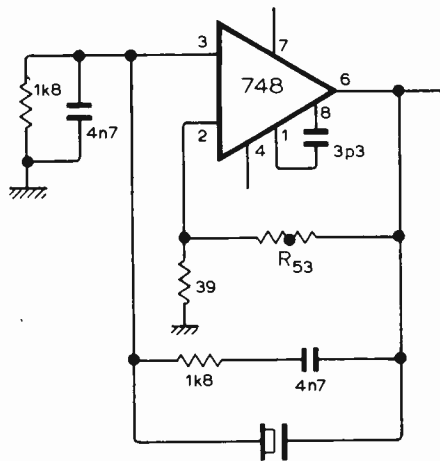


Fig. 8. Thermistor-controlled oscillator with the R53 bead running at 205°C, and a resistance of 82 ohms.

fed by a square wave, filter out the difference signal from the odd harmonic components, and then feed it to the adder. With the matrix arrangement in the diagram the last three degradations can be made negligible so crosstalk performance mainly rests on achieving good gain stability and phase matching between the sum and difference signal paths.

However, some new problems arise with this form of coder. The linearity of the multiplier to audio frequencies will have an effect on beat tone distortion performance and in a practical design there is the danger of impurities on the 38kHz producing further beat tone outputs. Common to all forms of coder is the need for a low distortion 19kHz pilot of correct phase and good stability, and audio pre-emphasis and filtering to limit the bandwidth of A and B signals to 15kHz.

**Choice of matrix method**

With an instinctive loathing of inductors and poor prospects at the time of realising a sensible active filter meeting the stringent phase and amplitude requirements while introducing negligible noise and distortion, the matrix approach looked more promising. Using the matrix principle only the first two signal degradations should be apparent and to meet a target channel separation of 55dB implies an M/S amplitude error of less than 0.18% and an M/S phase error better than 0.1°.

The block diagram of the coder is shown in Fig 7. Both 19 and 38kHz sine waves are required in this coder and starting with a 19kHz sine wave which is then doubled using a linear multiplier to square its input (a sine-wave squared equals a single wave of double frequency plus a d.c. term) and produce 38kHz of correct phase involves less filtering than starting with a square wave at a higher frequency (38, 76 or 152kHz) and dividing down.

If the coder is to be fed from any practical signal source other than a distortionless audio signal generator then the 15kHz filters are essential to

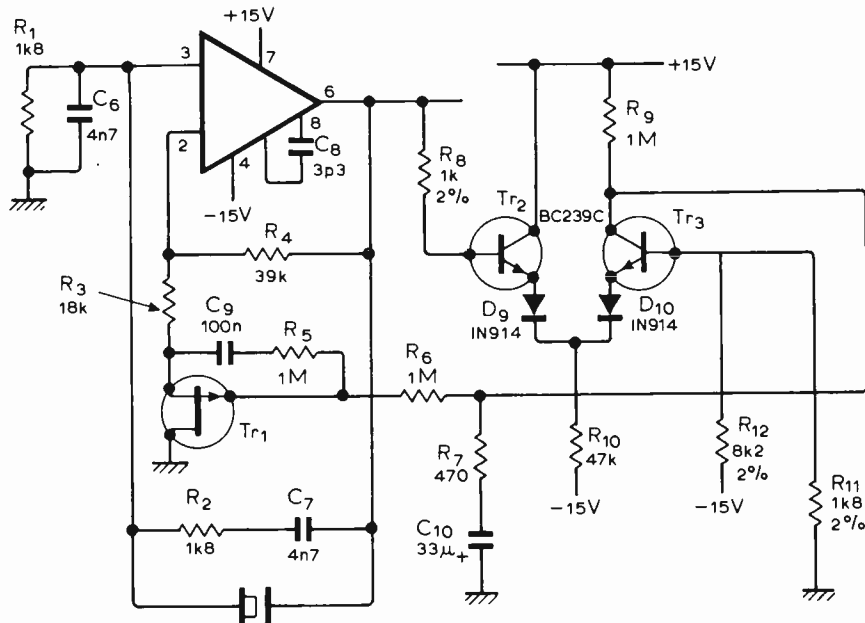


Fig. 9. Oscillator with improved amplitude/temperature drift. Tr<sub>2</sub> and Tr<sub>3</sub> form a long-tailed pair comparator and R<sub>5</sub>, R<sub>6</sub> equalize the signal voltages across the f.e.t. to linearize it and reduce distortion of the sine wave output.

prevent gross beat tone effects due to ultrasonic components on the audio inputs. It is desirable that rejection of frequencies of 19kHz and above be at least 45dB so this means that when pre-emphasis is in use, giving around 20dB boost at 19kHz, a filter attenuation of 65dB is required by 19kHz. If a passband ripple of only 1dB is allowed this implies the enormous attenuation rate of 200dB/octave between 15 and 19kHz.

Fortunately two cascaded Toko filter blocks can exceed the requirements in a very small space and at reasonable cost. The drawback of a filter with such violent attenuation so close to the passband is that there is little hope of achieving a linear phase characteristic and this is a deficiency common to all stereo coders. Part 2 includes a spectrum analyser photograph of the present filter response and a graph of measured phase shift.

The audio difference is derived and fed via the balanced modulator to the output adder while the sum signal is produced by feeding equal amounts of A and B directly to the output adder. The longer route of the difference signal means that it is slightly delayed at the adder compared to the A and B components and at the higher audio frequencies this would amount to a significant phase shift between the M and S components, hence the phase correctors inserted in the A and B lines to the adder.

Because the linear doubler used to produce 38kHz is not a perfect device some leakthrough of 19kHz may occur, particularly at extremes of the temperature range, so a 19kHz rejector

is placed before the multiplier's carrier input. The pilot must also arrive at the output adder at the correct amplitude and phase and a small phase shift is required to equal the time delay through the doubler, amplifier, notch filter and balanced modulator. To provide balanced outputs a straightforward unity gain inverter is fed from the adder output.

Power supplies are entirely conventional, producing plus and minus 15 volts at around 100mA. Power take off points are provided for running the clipping amplifier and v.h.f. oscillator described later.

**19kHz oscillator**

The accepted frequency tolerance for the pilot tone is ±2Hz so crystal control, if not essential, is certainly desirable. As a sine wave is required anyway it seems sensible to start with a sine wave crystal oscillator. This is something which often gives circuit designers a problem but a reliable inductorless circuit is easily formed at low frequencies by building a Wien bridge oscillator around the correct frequency and then putting the crystal across the series element of the bridge. Easy starting with reliable crystal lock is the result.

The standard thermistor amplitude control method, Fig 8, proved adequate for an early prototype, but even running the bead as hot as permissible, 200 deg C, still means that its operating point is determined roughly 9 parts in 10 by the oscillation voltage and 1 part in 10 by the ambient temperature. With this circuit I measured an amplitude drift of -0.02dB/deg C over the range +10 to +40 deg C and distortion was below 0.05%. Evidently some form of amplified control was needed to improve this drift figure tenfold and allow maintenance of good channel separation over a wide temperature range.

The circuit evolved is in Fig. 9 where an f.e.t. replaces the thermistor as the




gain control element but with linearizing components to maintain the distortion performance. Linearizing is achieved by equalizing the gate/drain and gate/source signal voltages and is done by  $R_5$  and  $R_6$ . The f.e.t. is also only allowed to contribute a small amount of the total resistance between pin 2 of the i.c. and common, and this fraction is determined by  $R_3$  in the source lead. Linearizing produces distortion better than 0.05% compared with around 0.4% without.

Transistors  $Tr_2$  and  $Tr_3$  form a long tailed pair which compares the oscillator amplitude with a direct reference voltage. Resistor 8 prevents loading of the oscillator output by changes in  $Tr_2$  input impedance over each cycle. The direct error voltage feeds the f.e.t. gate after filtering ( $R_7, C_{10}$ ) to remove oscillator components. The two transistors are identical types and mounted together so that their two base-emitter junctions provide temperature compensation; the use of a matched pair in a single can does not seem to be justified. Stability of the d.c. reference is assured by using low temperature coefficient resistors for  $R_{11}$  and  $R_{12}$  as well as a stabilized negative line.

Though a square wave oscillator followed by a filter could have produced similar amplitude stability simply by defining the voltage excursion of the square wave generator there is a unique advantage in the method described. Namely, the long-tailed pair comparator need not look at the oscillator output directly; it could look at the level of 38kHz which feeds into the multiplier and thus act as a servo, taking up gain drift in the doubler, amplifier and notch filter.

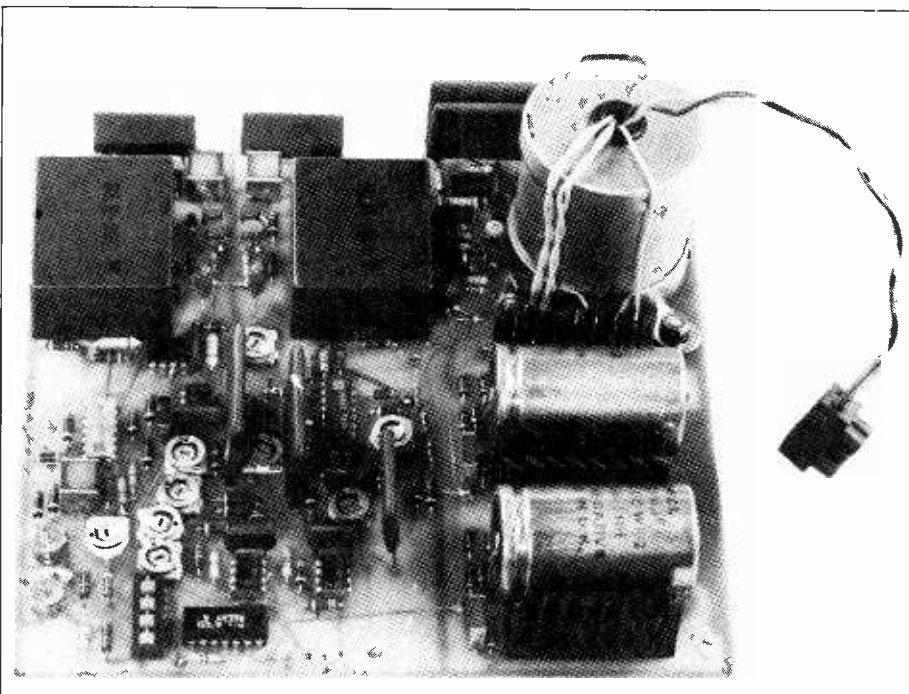Printed boards (a total of three) are available for this encoder for £7.50 inclusive from M. R. Sagin, 23 Keyes Road, London NW2.



**Appendix**

**Inherent crosstalk arising from deficiencies in the coded signal.**

Crosstalk is expressed relative to the full level on the decoded channels when  $A = B = 1$  as this is the most convenient reference when making measurements.

*Amplitude error between the M and S signals.*

Ignoring the pilot signal and considering an error  $\delta$  so that the composite signal becomes

$$\frac{A+B}{2} + \frac{A-B}{2+\delta} \sin 2f_c t$$

i.e. S is low in level if  $\delta$  is positive. After multiplication in the decoder, considering only the 38kHz component of the reinserted carrier waveform

$$D(t) = \left[ \frac{A+B}{2} + \frac{A-B}{2+\delta} \sin 2\pi f_c t \right] \sin 2\pi f_c t$$

Adding  $\frac{1}{4}(A+B)$  to give the decoded A signal, and considering only baseband components gives

$$\frac{A+B}{4} + \frac{A-B}{2(2+\delta)}$$

Related to peak level,  $\frac{1}{2}B$ , fractional crosstalk is  $\frac{\delta}{2(2+\delta)}$ .

*Phase error between M and S signals.*

Suppose  $A = 0, B = 1$  and  $B(t) = \sin 2\pi f_B t$ . If a delay of  $\delta t$  exists on the S signal, the composite signal is

$$\frac{\sin 2\pi f_B t}{2} - \left( \frac{\sin 2\pi f_B (t + \delta t)}{2} \right) \sin 2\pi f_c t.$$

After decoding, adding  $\frac{1}{4}(A+B)$ , i.e.  $\frac{1}{4}\sin 2\pi f_B t$ , and neglecting non-baseband components, the decoded A signal

$$\frac{1}{4} \sqrt{(1 - \cos 2\pi f_B \delta t)^2 + \sin^2 2\pi f_B \delta t}$$

$= \frac{1}{2} \sin \pi f_B \delta t$ , so that fractional crosstalk is  $\sin \pi f_B \delta t$ .

*Error in pilot phase.*

Suppose pilot is 0.1  $\sin f_c (t + \delta t)$ , so in the decoder the regenerated 38kHz is  $\sin 2\pi f_c (t + \delta t)$ .  $D(t) =$

$$\frac{1}{2} \frac{A+B}{2} + \frac{A-B}{2} \sin 2\pi f_c t \sin 2\pi f_c (t + \delta t).$$

Add  $\frac{1}{4}(A+B)$  and neglecting non-baseband terms the decoded A signal is

$$\frac{A}{4} (1 + \cos 2\pi f_c \delta t) + \frac{B}{4} (1 - \cos 2\pi f_c \delta t).$$

and fractional crosstalk is  $\sin^2 \pi f_c \delta t$ .

*Amplitude imbalance between the sidebands of the S signal.*

If  $A = 0, B = 1$  and  $B(t) = \sin 2\pi f_B t$  and a sideband imbalance exists then the composite signal is

$$\frac{\sin 2\pi f_B t}{2} - \frac{\cos 2\pi (f_c - f_B) t}{4} + \frac{\cos 2\pi (f_c + f_B) t}{4 + \delta} \quad A1$$

Considering only baseband terms

$$D(t) = -\sin 2\pi f_B t \left[ \frac{8 + \delta}{8(4 + \delta)} \right].$$

Adding  $\frac{1}{4}(A+B)$  the decoded A signal is

$$\sin 2\pi f_B t \left[ \frac{\delta}{8(4 + \delta)} \right].$$

and fractional crosstalk is therefore

$$\frac{\delta}{4(4 + \delta)}$$

*Phase shift in the upper sideband of the S signal.*

Taking equation A1 but for a phase error in the  $(f_c + f_B)$  component, signal is

$$\frac{\sin 2\pi f_B t}{2} - \frac{\cos 2\pi (f_c - f_B) t}{4} + \frac{\cos 2\pi (f_c + f_B) (t + \delta t)}{4}$$

$$D(t) = \frac{1}{8} \left[ \sin 2\pi f_B t \cdot \cos 2\pi (f_c + f_B) \delta t + \cos 2\pi f_B t \cdot \sin 2\pi (f_c + f_B) \delta t \right] - \frac{\sin 2\pi f_B t}{8}$$

and the decoded A signal is  $\frac{1}{4}\sin(f_c + f_B)\delta t$ , giving a fractional crosstalk of  $\frac{1}{2}\sin(f_c + f_B)\delta t$ .

**References**

1. Z. Mack, Stereo service generator (in German). Circuit of a switching type coder is given. *Funk-Technik* 1968 p.532.
2. Z. Mack, Comparison of transformerless ring-modulators and cross modulators. *Radio and Electronic Engineer* vol. 44 1974 p.407.

# Power semiconductors— 2

## A survey of devices, technologies and applications

by Mike Sagin, Assistant editor *Wireless World*

Over recent years much development has taken place in the power semiconductor field. Conventional devices are getting larger, quicker and more efficient, and several new devices have been introduced to the design engineer. These semiconductors allow far more freedom in the design of a power control system provided that they are used correctly. This article covers the various types of device currently available and outlines applications, together with future developments.

### Thyristors

Thyristor is the generic name for a semiconductor bistable switch which has at least four semiconductor layers. The most common type, the silicon controlled rectifier, was first introduced

in the 1950s and was used to replace thyratrons and mercury-arc rectifiers. Since then it has undergone much development to produce devices which can switch 1000A or 1000V in one microsecond, withstand voltages up to 4kV, handle r.m.s. currents up to 2.5kA, and operate at frequencies up to 5kHz. Several types of construction are now used, all of which have very definite advantages and corresponding disadvantages. Because designers have to "rob Peter to pay Paul" s.c.r.s are designed for specific applications.

The basic s.c.r. as shown in Fig. 1(a) is a half way device whose bistable state depends on a positive feedback loop. When the s.c.r. is forward biased it can be switched from a high to low impedance state by making the gate positive with respect to the cathode. This action is analogous to a complementary pair of

internally connected transistors as shown in Fig. 1(b). A regenerative situation exists when the positive feedback gain exceeds unity. Under reverse bias, the s.c.r. behaves like a p-n junction rectifier. The switching characteristics of a typical reverse blocking s.c.r. are shown in Fig. 2 and the important ratings and characteristics are shown in table 1.

In general, for high operating voltages, the p-n-p-n structure must be thicker and possess a higher resistivity. Unfortunately, this increases the voltage drop, which reduces the current rating. High frequency performance is also degraded because the rate of rise in current ( $di/dt$ ) rating is reduced and the turn-off time increased, due to a larger stored charge in the structure. Another important factor which determines the voltage rating is the surface condition

Table 1  
Important ratings and characteristics

<b>Off-state</b>	
$V_{DRM}, V_{DSM}$	Peak repetitive and non-repetitive voltages (V)
$I_{DRM}$	Peak current (mA)
<b>On-state</b>	
$V_{IM}$	On-state voltage (V)
$I_{IAV}$	Mean on-state current (A)
$I_{IRM}, I_{ISM}$	Repetitive and non-repetitive currents (A)
$I_H$	Holding current (mA)
<b>Trigger</b>	
$V_{GT}, I_{GT}$	Gate trigger voltage (V) and current (mA)
<b>Reverse bias</b>	
$V_{RRM}, V_{RSM}$	Peak repetitive and non-repetitive voltages (V)
$I_{HRM}$	Peak current (mA)
<b>Thermal</b>	
$R_{th}$	Thermal resistance (deg C/W)
$T_j$	Junction temperature (deg C)
<b>Turn-on</b>	
$t_{gt}$	Turn-on time
$dI/dt$ on	Rate of rise of current (A/s)
<b>Turn-off</b>	
$t_g$	Turn-off time (s)
$dI/dt$ off;	Rate of fall of current and
$dV/dt$ off	rise of reverse voltage in turn-off (A/s, V/s)
$dV/dt$	Rate of re-application of forward blocking voltage (V/s)

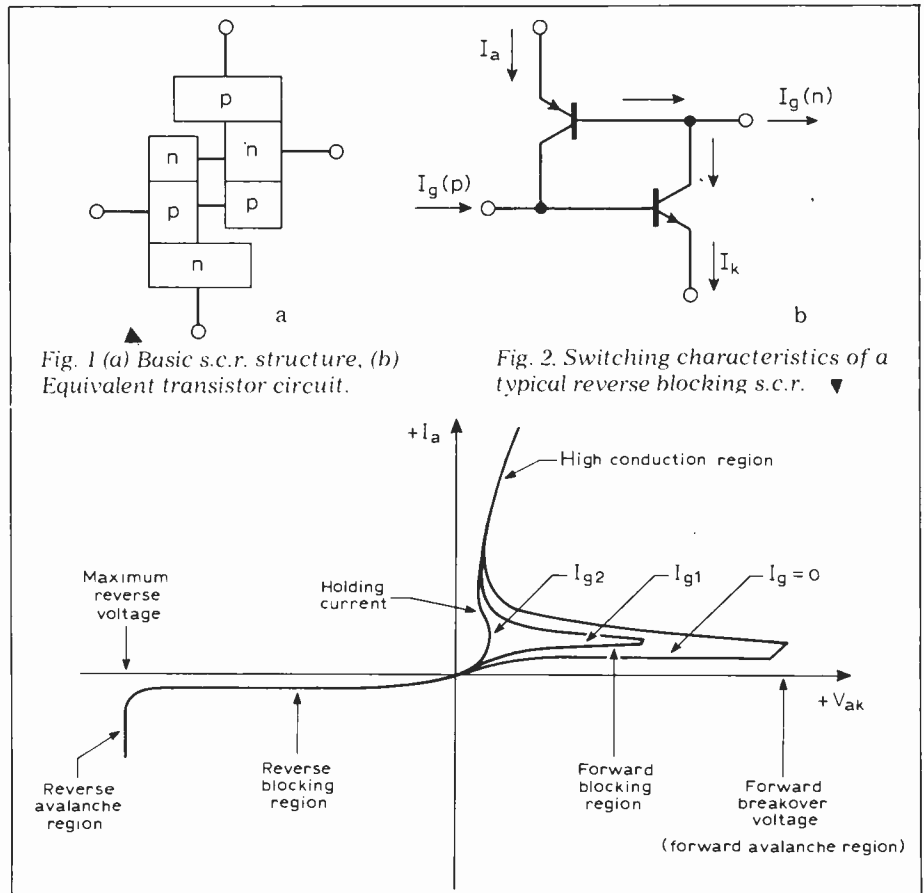


Fig. 1 (a) Basic s.c.r. structure, (b) Equivalent transistor circuit.


Fig. 2. Switching characteristics of a typical reverse blocking s.c.r.

where the p-n junction meets the silicon surface. Surface contouring or bevelling allows higher voltage operation by reducing the electric field in the depletion layer at the surface of the silicon pellet.

The allowable current through a device depends mainly on the conducting area. Silicon slices of 50mm diameter are now used in high power s.c.r.s and larger devices are being produced in the laboratory.

**Switching performance** has received much attention because of the  $di/dt$  problems which have been encountered. The turn-on process of a s.c.r. is two dimensional because the structure has an electrical resistance across the silicon wafer. Switching is initiated near to the gate electrode and the conducting area spreads outwards until a uniform current density is established. If the build-up of load current is too fast, localized "hot-spots" are created which can damage the device. This problem is most acute in the early point-gate structure, shown in Fig. 3. The area initially turned on is very small and is dependent upon the amplitude of the gate signal. An obvious progression was the centre gate, shown in Fig. 4. This type of construction is widely used in consumer and light industrial s.c.r.s and allows  $di/dt$  ratings up to  $100A/\mu s$  when using gate pulses of 1-2A. The next development to improve the switching performance was the amplifying gate s.c.r. — see Fig 5. This type of structure may be considered as two radial s.c.r.s with a common anode connection. When a positive gate signal is applied, current flows into the p region beneath the gate contact and across the p-n junction at the nearest point to the gate. This forward biases junction J4 and current flows into a metallized region which overlays the outside edge of this junction. The gate-pulse current then re-enters the p region and crosses the p-n junction J3 at the nearest point. Because the length of the auxiliary s.c.r. inner cathode edge is shorter than the main s.c.r. inner edge, the current density at J4 is higher than J3. This ensures that the auxiliary s.c.r. switches before the main section. When the auxiliary s.c.r. has switched, most of the anode current flows in the lowest impedance circuit to the cathode lead which includes the inside edge of the main s.c.r. The equivalent circuit is shown in Fig. 5(b).

Although this structure greatly improves the  $di/dt$  ratings, further developments have produced the distributed amplifying gate s.c.r. shown in Fig. 6, and the interdigitated amplifying gate s.c.r. — Fig. 7. These are extensions of the basic amplifying gate device in which the length of the main s.c.r. cathode switching edge has been increased to reduce the spreading distance. Although this appears to be the answer to all power switching

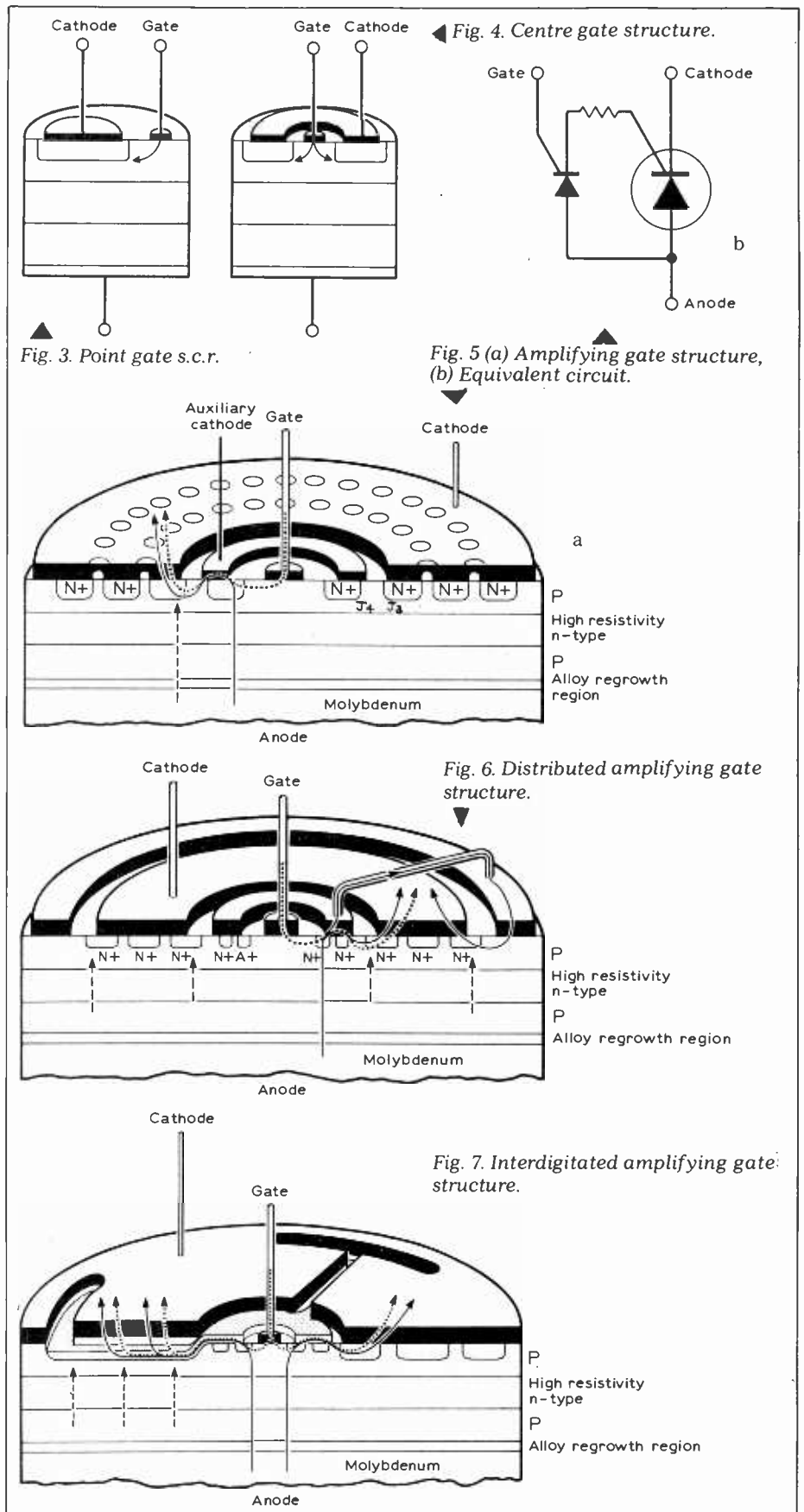


problems, "Peter" is effectively robbed again because as the surface area of the distributed gate increases, so the main cathode area, and hence, anode current carrying area decreases.

A second rating which effects the switching performance is the  $dv/dt$ . Rapidly rising voltage waveforms and high junction temperature can cause

spurious triggering of an s.c.r., due to the capacitance of the p-n junction and the leakage current from the gate junction. The effect is one of increased gate sensitivity. This brought about the shorted-emitter structure which uses partial shorting links between the gate and cathode junction, to produce the same effect as placing a resistor

Continued on page 87



# International Rectifier makes the most of semiconductors

... to make the most of your circuit and equipment performance!

From a discrete diode to a complex circuit function ... from minimum to maximum power where solid state electronic and electrical power conversion and control are involved, we have the experience.


Since 1947, the year the semiconductor industry was born, we've chosen to specialise in those areas where our sophistication and high technology make a big difference. When we make a product, we make the most of it. The most in technology ... the most in performance ... the most in configurations ... and the most in reliability. So check our areas of specialisation, and keep us in mind when you begin your next design.

*You too, can make the most of it with IR semiconductors.*

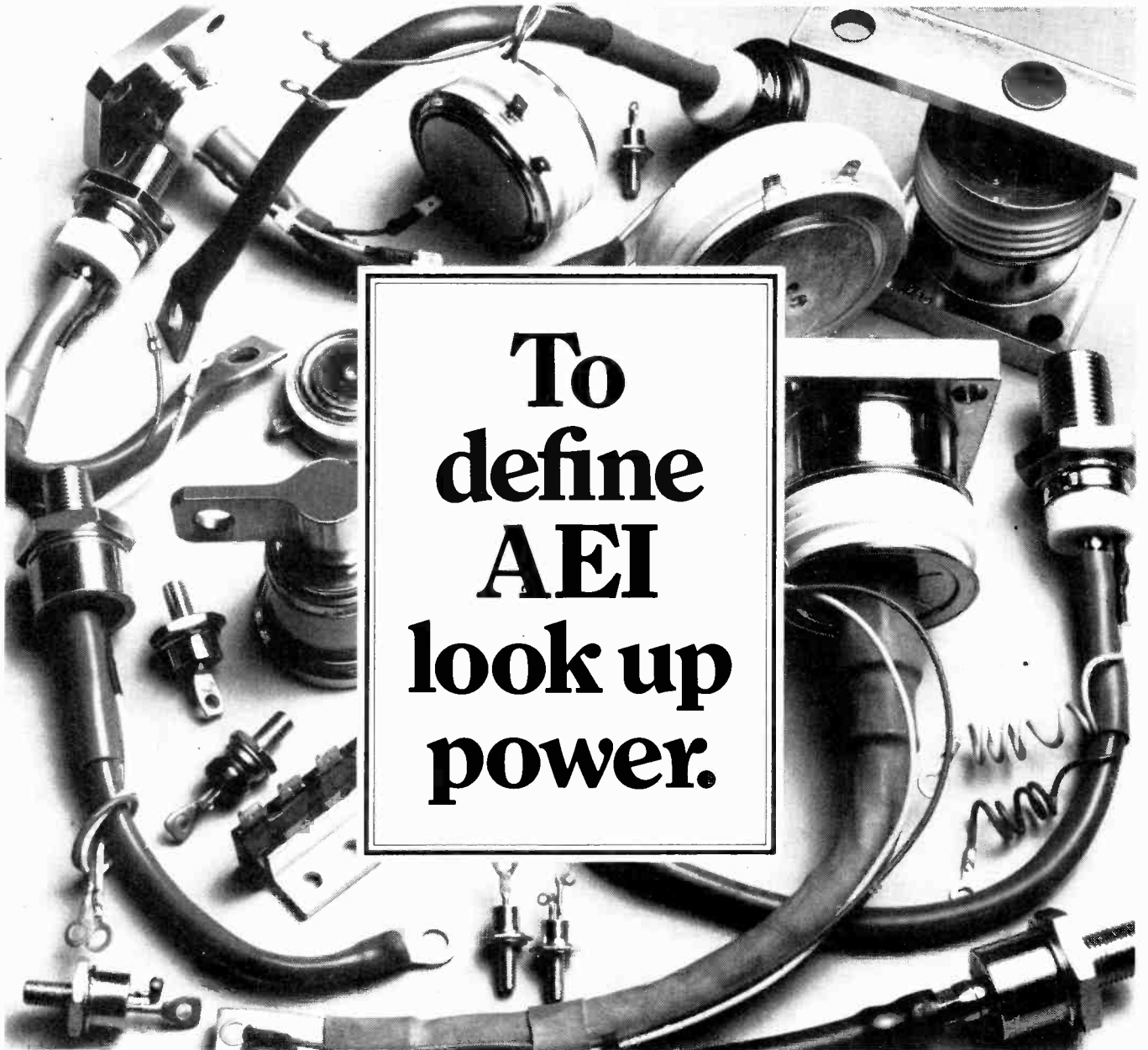**INTERNATIONAL RECTIFIER**

HURST GREEN OXTED SURREY RH8 9BB TELEX RECTIFIER OXTED 95219 TELEPHONE OXTED 3215/4231





**To  
define  
AEI  
look up  
power.**

**POW'ER** *n.* ability to do or act;

AEI Semiconductors Limited manufacture a wide range of industrial diodes and thyristors from 1 amp to well over 1,000 amps. AEI are acknowledged experts and have the experience to make power semiconductors for a wide range of applications. AEI's wealth of technological expertise ensures that reliability is the keyword of their product range. AEI are proud of their reliability and proud of their name. To AEI's customers this ensures that, whatever the requirement, the best device is specified and supplied.

**Low Power Thyristors**  
**Medium Power Thyristors**  
**High Power Thyristors**  
**Low and Medium Power Inverter Thyristors**  
**High Power Fast Switching Thyristors**  
**A.C. Controllers**  
**Low and Medium Power Diodes**  
**High Power Diodes**  
**Voltage Regulator Diodes**  
**Plastic Power Microcircuits**  
**Thyristor and Rectifier Assemblies**  
**BS 9300 types**

**AEI**  
**SEMICONDUCTORS**

**The symbol of power:**

**AEI Semiconductors Limited**  
 Carholme Road, Lincoln, England.  
 Telephone 0522-29992, Telex 56163.

Part of GEC Electrical Components Group

WW — 099 FOR FURTHER DETAILS



between the gate and cathode. The only disadvantage of this type of construction is the slightly increased firing requirements.

The turn-off time for a s.c.r. will determine the maximum operating frequency of the device. During the turn-off period the excess minority charge must either be swept out by an electric field or must decay by recombination within the silicon before the s.c.r. will block a forward voltage. For rapid decay more recombination centres must be introduced. One method of achieving this is gold diffusion during fabrication. The introduction of gold impurities does, however, reduce the voltage and current ratings, and gate sensitivity.

**Construction.** The heart of a thyristor is its multi-layered pellet of alternate p and n-type semiconductor material. The pellet structure may be fabricated in several ways, depending on the characteristics and complexity of the device. The most popular fabrication methods are alloy diffusion, full diffusion and planar diffusion. The first two methods use large-area p-n-p wafers which are formed by gaseously diffusing p type impurities simultaneously into both faces of a thin n type wafer. Where specific device characteristics are required, a second diffusion step is used to complete the all-diffused p-n-p-n structure. To do this, each p-n-p wafer is selectively marked on one side and diffusion takes place through the windows in the mask. The finished wafers are then diced into individual pellets. In the manufacture of some higher power s.c.r.s where only one pellet is available from the wafer, the original p-n-p wafer is converted into a pellet structure before the final n region is added. In this construction the alloying technique is used to fuse a gold-antimony layer into each p-n-p pellet — see Fig. 8.

Planar structure describes a type of device where all of the p-n junctions are on a single surface of the pellet. In this construction a thin layer of silicon dioxide is grown over the wafer before diffusion starts. This prevents contamination of the silicon surfaces. Because the planar construction requires more silicon per amp, the process is normally used for low current devices where many pellets can be cut from a single wafer.

Encapsulation of the s.c.r. pellet has played an essential role in the progressive increase of power ratings. All s.c.r. characteristics are temperature sensitive and provision must be made to conduct away heat generated in the silicon. The older, more traditional method is to hard solder the pellet between a pair of thermally matched plates, one of which is then soldered to a copper stud. The stud serves as one terminal and the thermal conducting path. A newer method of encapsulation for devices rated at above about 150A is the pressure contact system. This

replaces the solder joints between the silica pellet and the plates and, in turn, relieves much of the thermally induced stress on the pellet. This system is the only practical method for encapsulating pellets of more than 1 inch in diameter. An even more recent development in pellet encapsulation is glass passivation. A thin coating of low temperature glass is fused on to the silicon chip and performs the same function as the silicon dioxide layer used in the planar diffusion process. Glass passivation is a post-diffusion process and is superior to  $\text{SiO}_2$  because it can be applied in thicker coatings, which also allow higher voltage ratings. Another advantage of glass passivation is the hermetic seal it produces which allows simple plastic packages to be used instead of the hermetic metal containers.

Future devices will no doubt have improved voltage and current ratings especially with the development of more uniformly doped silicon. As mentioned earlier, 50mm diameter silicon is now commonly used in high current s.c.r.s. Larger diameter slices are already well advanced and will shortly be used in commercial devices.

**Triacs**

A bidirectional triode thyristor, commonly called the triac, is basically two

s.c.r.s connected back to back. These devices are mainly used for a.c. power control and are generally restricted to lower power applications. The structure of a typical glass passivated triac is shown in Fig. 9. Seven steps are necessary in the construction of such a device and the process begins with an n type high resistivity silicon wafer which has p layers deeply diffused into both sides. Silicon-dioxide diffusion masks are grown, and p<sup>+</sup> regions are defined and diffused into the wafer. A second diffusion mask is grown, and n<sup>+</sup> regions are defined and diffused into the wafer. A silicon-dioxide etch mask is grown and defined. Grids and gate moats are etched into the wafer and the glass passivated layer is then applied in these grids and moats. Finally, contact areas are opened on the wafer and nickel-lead-tin solder metallization is applied. The wafer is then separated into pellets.

The triac can be triggered by either a positive or negative gate signal regardless of the voltage polarity across the main terminals of the device. The triggering mechanism and current flow within the triac is shown in Fig. 10. Gate trigger polarity is always referred to terminal 1, and the potential difference between the two terminals is such that gate current flows in the direction indicated by the dotted arrows. Because

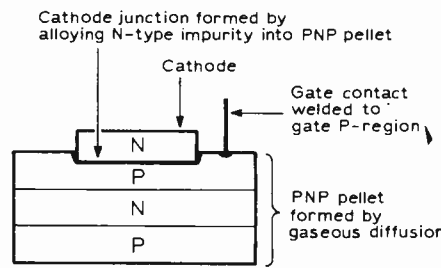


Fig. 8. Alloy-diffused pellet formation.


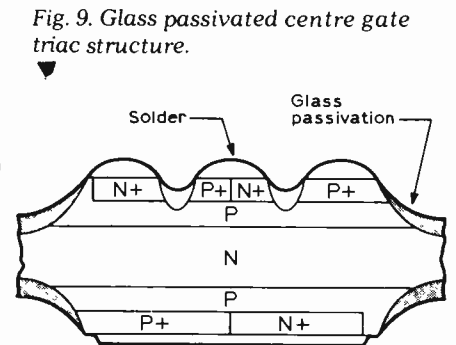
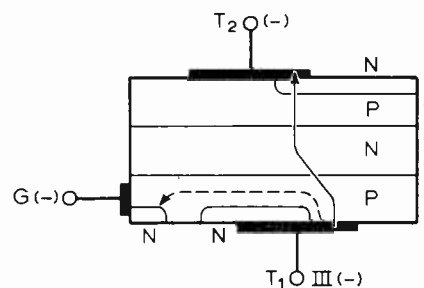
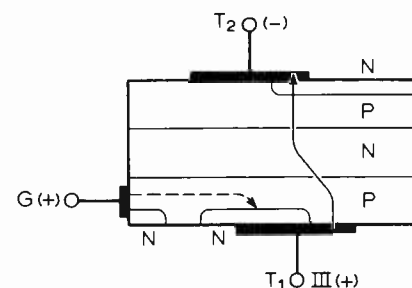
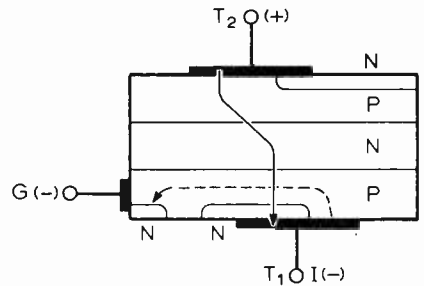


Fig. 9. Glass passivated centre gate triac structure.

Fig. 10. Current flow in a triac. Dotted lines show the direction of gate current.

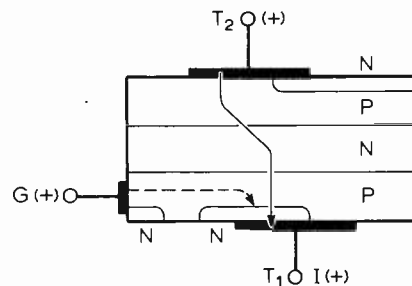

the direction of current flow influences the gate trigger current, the gate requirements differ for each of the four modes. The operating modes in which the main current is in the same direction as the gate current require less trigger current than those in which the main current opposes the gate current.

Unlike s.c.r.s, turn-off times are not associated with triacs because of the physical structure of the device. The ability of a triac to commute a fixed value of current is an important characteristic, which is known as the commutating  $dv/dt$  capability of the device. In a.c. applications a triac must

switch from the conducting state to the blocking state at each zero-current point. This action is called commutation. If the triac fails to block the circuit voltage, control of the load power is lost. Commutation for resistive loads presents no special problems because the voltage and current are in phase. For inductive loads, however, the current lag causes an applied voltage, opposite to the current and equal to the peak of the a.c. line voltage, across the triac after the zero current point. The maximum rate of rise of this voltage which can be blocked without the triac reverting to the on state is the

commutating  $dv/dt$  capability of the device, and is specified in volts per microsecond for the following conditions. The maximum rated on-state current  $I_{T(RMS)}$ , the maximum case temperature for the rated value of on-state current, the maximum rated off-state voltage ( $V_{DROM}$ ) and the maximum commutating  $di/dt$ .

The addition of a series capacitor and resistor "snubber" network across the triac reduces the commutating  $dv/dt$  of a circuit and is often used for inductive loads. The sizes of these components vary with the load but typical values are 100 ohms and 0.1 $\mu$ F. Table 2 shows

*Continued on page 91*



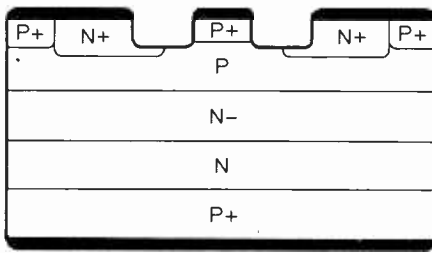


Fig. 11. Asymmetrical s.c.r. junction structure.


Fig. 12. Practical circuit for an induction cooker hob. For further details see RCA application note number AN-6456.

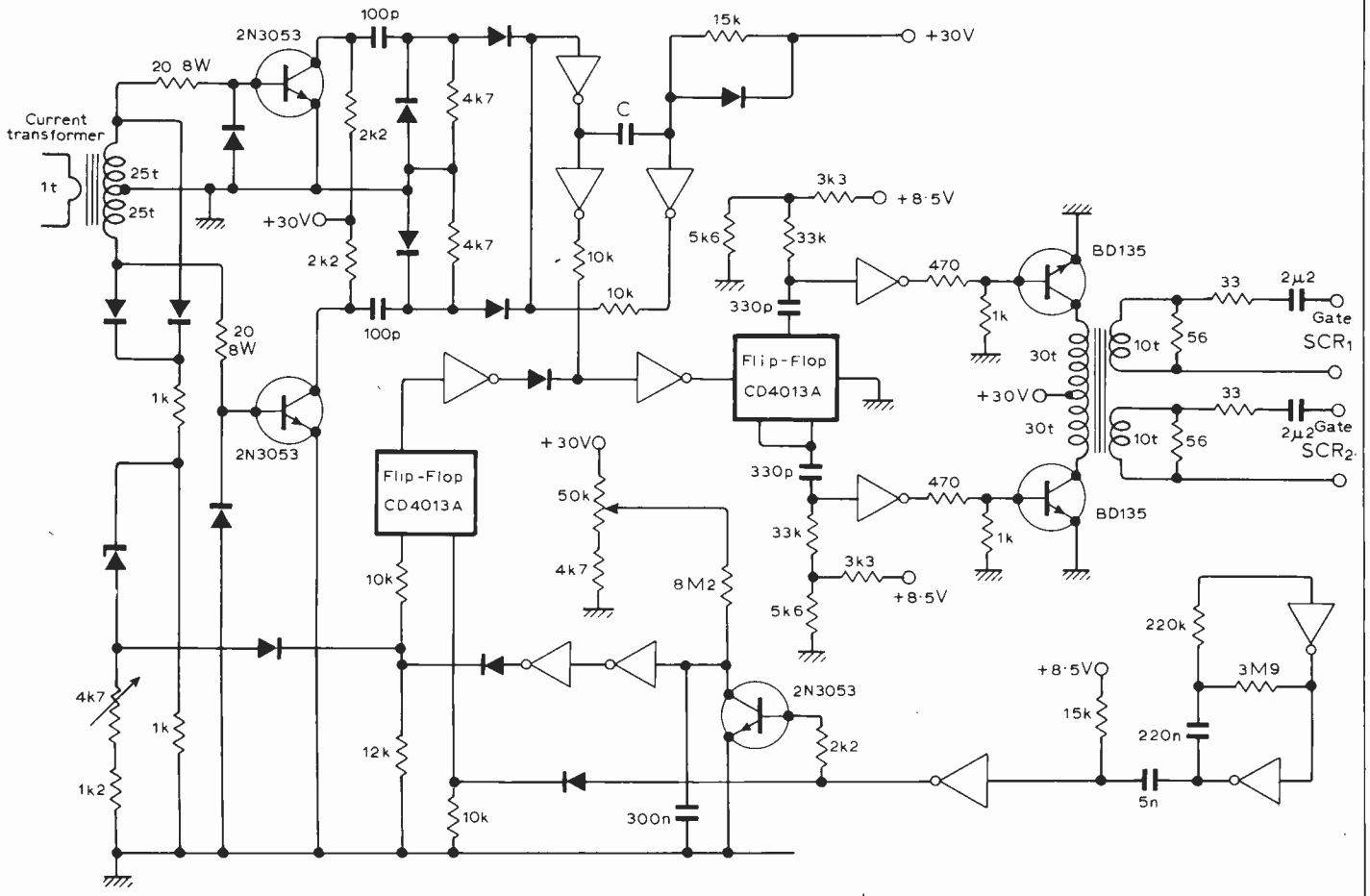
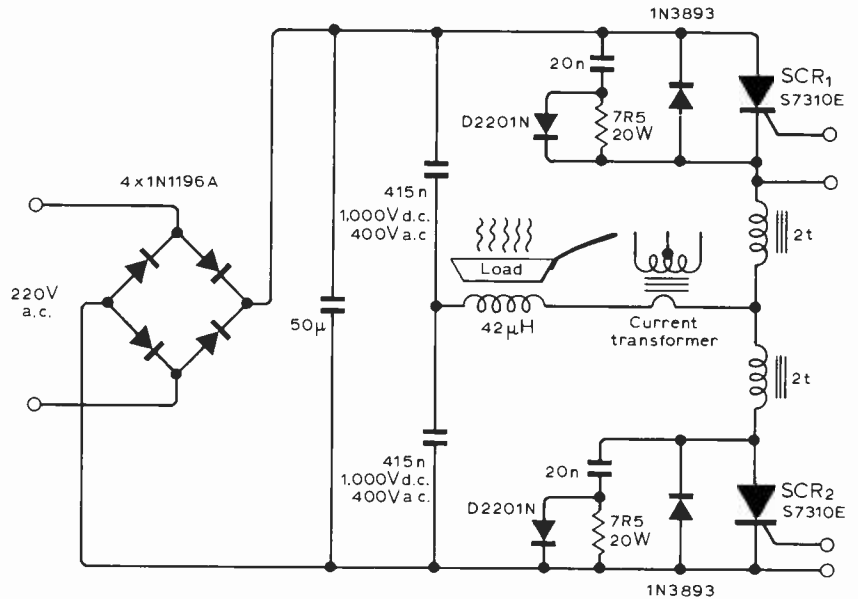
# Six power levels in high speed switching



**400W**  
ESM 1000  
and 2060  
TO-83

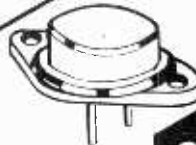

**250W**  
BUX 20 to 25  
TO-3  
modified



**150W**  
BUX 10 to 15  
TO-3



**120W**  
BUX 39 to 45  
TO-3



**70W**  
BUX 59 to 65  
TO-66



**40W**  
BUX 49 to 55  
TO-39

In high speed switching, the Sescossem Division of Thomson-CSF is ready for every industrial and professional application. Main application areas are: static converters operating on 24V/48V/110V batteries, and static converters operating on 110V/220V mains motor speed controls. Write for technical data.

Voltages from 90V to 500V (BUX series);  
from 100V to 200V (ESM series)

Current from 1A to 150A

Frequency up to 50kHz



**THOMSON-CSF**

**Available from these Thomson-CSF distributors:**

- Spenco Electronics (Phoenix) Ltd., Kelvin Industrial Estate, East Kilbride, Scotland. (035 52 36311).
- Phoenix Electronics (Portsmouth) Ltd., 149-141 Havant Road, Drayton, Portsmouth, Hants. (070 18 73441).
- Concorde Instrument Company, 42 Cricklewood Broadway, London NW2. (01-452 0161).
- Lock Distribution, Neville Street, Middleton Road, Oldham Lancs OL9 6LP. (061 652 0431).
- Barlec Ltd., 219 London Road, East Grinstead, Sussex. (0342 24383).
- Omni Components Ltd., 59 Vastern Road, Reading, Berks. (0734 594834).

Thomson-CSF United Kingdom Ltd., Ringway Hse., Bell Road, Daneshill, Basingstoke RG24 0QG. Tel: 0256 29155

WW — 096 FOR FURTHER DETAILS

# Pinnacle hold the power of GENERAL ELECTRIC (U.S.A.)



Power Transistors  
Tunnel Diodes  
Unijunctions  
Optoelectronics  
Rectifiers  
SCRs

Triacs  
GE-MOV Varistors  
Power Modules  
SCR Commutating &  
Computer Grade  
Capacitors



## THE HOUSE OF POWER

Pinnacle Electronic Components, Electron House, Cray Avenue, St. Mary Cray, Orpington, Kent. BR5 3QJ. Phone: 71531 Telex: 896141  
WW-068 FOR FURTHER DETAILS

Table 2

**Commutating di/dt for various currents and frequencies.**

Commutating di/dt A/-s	Sine wave Amperes r.m.s.	Operating Frequency Hz
141	40	400
88	25	400
21.1	40	60
13.2	25	60
17.6	40	50
11.0	25	50

commutating di/dt for various currents and frequencies.

**Asymmetrical silicon controlled rectifier**

A recently introduced device from RCA, known as an a.s.c.r., has been specially designed to achieve high dv/dt and di/dt capabilities. A gold dopant is diffused into the a.s.c.r. pellet to achieve fast turn-off capability but, as discussed earlier, gold doping tends to increase turn-on time and decrease di/dt capability. Special techniques are used to overcome this problem. The structure of an a.s.c.r. is shown in Fig. 11. It differs from a conventional s.c.r. in that an additional n-type layer is inserted between the p<sup>+</sup> and n<sup>-</sup> regions. This new layer is doped so that it increases the forward blocking voltage of the device. The reverse blocking voltage, which is a function of the n<sup>-</sup>/p<sup>+</sup> junction, is much lower than in conventional s.c.r.s and is about 15V. The dv/dt capability of the a.s.c.r. is also increased with the introduction of a p<sup>+</sup> ring at the edge of the pellet.

Asymmetrical s.c.r.s can be used in fast switching applications at frequencies up to 35kHz. A recently developed circuit uses these devices in an induction cooker hob. A high-frequency generator is used to supply an alternating current to a flat coil under a working surface. When an iron or steel utensil is placed above the induction coil, high-frequency currents are induced into the pan which generates heat. A functional circuit for such a unit is shown in Fig. 12. This design offers an output of 1275W, and a typical efficiency of 80%.

**Gate turn-off s.c.r.**

Gate turn-off devices (g.t.o.) are also four-layer, three-junction structures as shown in Fig. 13 but, unlike the s.c.r., they can be turned off by the application of a negative gate pulse. The g.t.o. can be turned on in a similar way to the conventional s.c.r. by making the gate positive with respect to the cathode. As positive current is applied to the gate, the voltage/current relationship resembles that of a forward-biased p-n junction until the point is reached where regeneration takes over to switch the structure on. The g.t.o. incorporates the regenerative properties of the two-transistor model of a

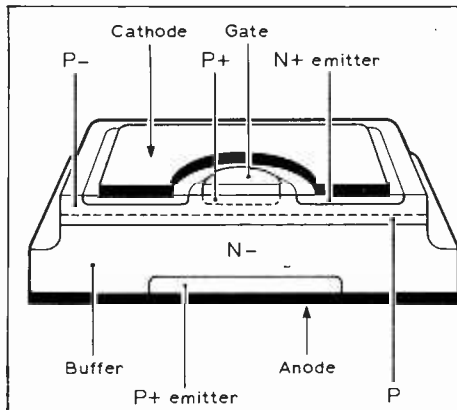


Fig. 13. Gate turn off s.c.r. structure showing centre gate and double p base layer.

Fig. 14. Anode current rise time versus gate drive current.


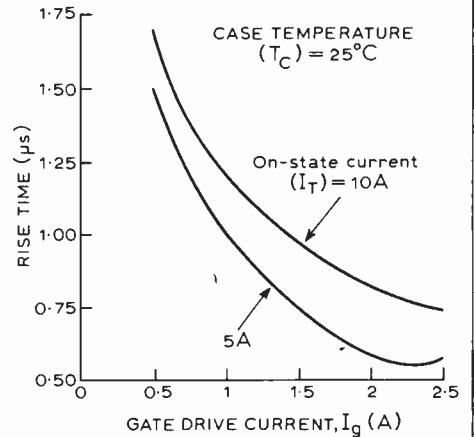


Fig. 15 (a) Gate turn off s.c.r. in the on-state and, (b) during turn off. The high density filament forms a non-regenerative region.

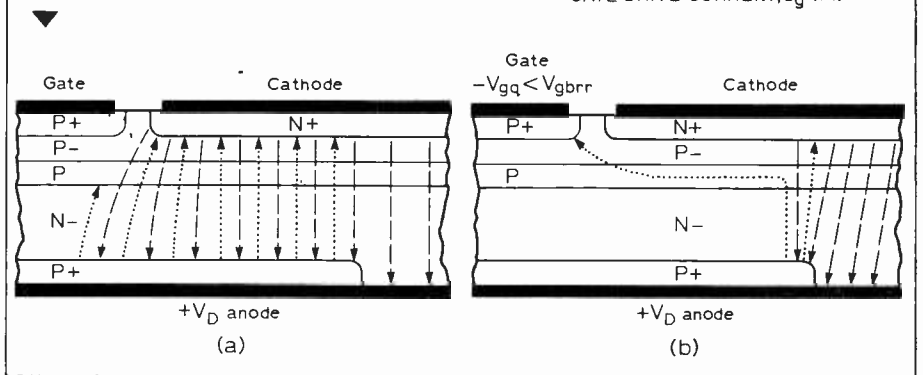

s.c.r., but the loop gain is reduced to allow turn-off control at the gate. In effect, turn-on in a g.t.o. is similar to that of a desensitized s.c.r. and, if sufficient gate drive is applied during turn-on, satisfactory performance can be achieved. The effect of increased values of gate-current on anode-current rise time for two values of on-state anode current, is shown in Fig. 14. The on-state voltage of the g.t.o. is a function of the regenerative properties of the device, so the transient on-state voltage drop can be reduced by the use of an increased gate drive.

During the turn-off process, the conducting electron/hole plasma is deflected from an area close to the gate, which has the highest negative potential, to the most remote area beneath the cathode, which has the least negative potential, see Fig. 15. In the on-state the device conducts uniformly over the entire cathode area. Upon application of a negative bias to the gate, the plasma is squeezed into a high-density filament. This filament is deflected into a non-regenerative three-layer section and cannot sustain itself.

The structure has a centre-gate geometry and a double-layer p base

which allows a low lateral resistance. This low resistance causes a very small voltage drop from the negative gate current. The g.t.o. is surrounded by a non-regenerative section in which the final phase of the turn-off cycle takes place. Device dimensions are about 3 × 3mm and this size allows a continuous current operation up to 15A and a forward blocking voltage of above 600V.

**Gate-drive techniques.** For the best switch-on rise times a positive gate current of between 0.5 and 1A with at least a two microsecond pulse width is recommended by the manufacturers. Also, a pulse of -70V between the gate and cathode for the duration of the turn-off interval is advised. Fig. 16 shows gate drive systems that may be used when a negative voltage source of 70V is not available. In circuit (a) the resistor causes unnecessary dissipation during switching and in circuit (b) an inductor is substituted to reduce the dissipation. The configuration shown in (c) is the best method of switching the g.t.o. The peak value of the reverse gate current carried by the switch in Fig. 16 is approximately half the maximum



Continued from page 55

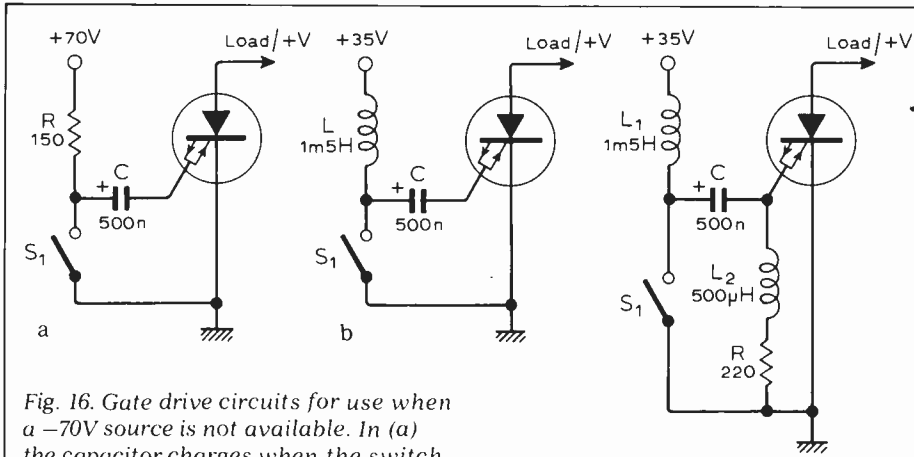


Fig. 16. Gate drive circuits for use when a -70V source is not available. In (a) the capacitor charges when the switch is opened and gate current turns the g.t.o. on. When the switch is closed the charged capacitor acts as a source of negative potential. In (b) when the switch is closed the g.t.o. is turned off by the capacitor and the extra energy stored in the inductor. In (c) when the

switch is opened the g.t.o. is turned on because of stored energy from  $L_1$  and the increased drive provided by the stored energy in  $L_2$ . When the switch is closed the g.t.o. turns off because of the negative voltage from the capacitor.

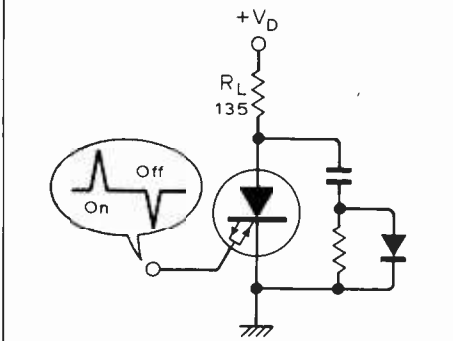


Fig. 17. Typical d.c. switch. The capacitor and resistor form a "snubber" network.

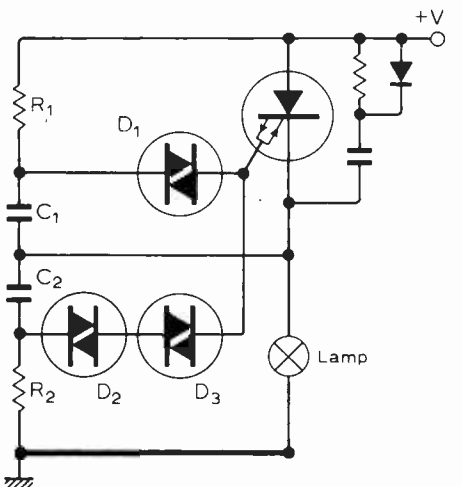
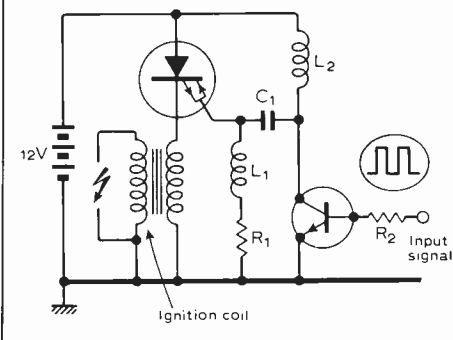


Fig. 18. Lamp flasher circuit. The on and off times can be adjusted by the time-constant networks  $R_1C_1$  and  $R_2C_2$  respectively.

Fig. 19. Car ignition circuit.

anode current of the g.t.o. prior to turn off. This current lasts for about 400ns and then decreases to a value less than 0.7A for the rest of the turn-off interval. The switch may be an n-p-n transistor or low voltage s.c.r.

Applications of the g.t.o. are mainly in d.c. circuits, and use in cars will be popular. Particular devices can operate at frequencies up to 30kHz and Fig. 17 shows a circuit suitable for use as a d.c. switch. Fig. 18 shows a circuit breaker or lamp flasher. Diacs  $D_2$  and  $D_3$  are connected in series to provide a maximum peak negative gate voltage of -70V during the turn off period. The RC "snubber" network in parallel with the g.t.o., protects the device against high

dv/dt. The circuit in Fig. 19 illustrates a typical use in a car ignition unit. The input signal can be obtained from the mechanical distributor or from an electronic generator.

In the near future it is expected that new devices will have much lower gate turn-off voltages of around -20V, higher current capabilities, and increased gate sensitivities. Because the g.t.o. can switch higher voltages at greater currents with a semiconductor pellet the same size as a conventional bi-polar transistor, these devices are likely to replace high power transistors in many d.c. switching applications.

To be continued.

circuits" had gained currency). Texas were anxious to establish that what we saw at the symposium was not in fact a working device but a model, and our reporter agreed to sign an affidavit to this effect. This incident demonstrates the Americans' awareness of the possibility of British priority in integrated circuits.

Mr Dummer is author of a new book "Electronic Inventions 1745-1976" just published by Pergamon Press at £4.00. This contains mainly brief descriptions of important inventions in electronics but also has some interesting graphs showing historical trends. For example, it shows that in the 200 years from 1745 to 1945 some 106 electronic inventions originated in Europe against 66 in the same period in the USA; but in the mere 31 years from 1945 to 1976 the situation was reversed, with 32 inventions in Europe and 85 in the USA.

## Time by satellite

A digital clock controlled by a time code transmitted from a satellite has been developed by the US National Bureau of Standards (NBS). Once set by the time code the clock, which uses a simple and cheap microprocessor, continues to keep time in the presence or absence of the satellite signal. The clock was designed to use transmissions from the National Oceanic and Atmospheric Administration's meteorological satellites, which relay information from buoys, automatic weather stations, ships, aircraft and balloons. The time code used dates the information or organises its transmission into sequence.


The clock receives a 100Hz pulse stream and time code information in 30s data frames. "Since each time code frame differs from the previous one by only 30s there is a high degree of redundancy in this data which can be used to improve the signal to noise ratio. The microprocessor stores the received time in random access memory and continually updates it by counting the 100Hz pulse stream." During every time code frame the r.a.m. time is compared with the new time message for errors. The r.a.m. time is assumed to be correct in the case of error in three consecutive comparisons. On the fourth the r.a.m. is assumed wrong and is reset in the next frame.

To counteract noise in the pulse stream the microprocessor crystal oscillator is divided down to 100Hz from 4.096MHz and phase locked to the received pulse stream. The adjustment of the crystal frequency is accomplished with varactor diodes.

# New Products
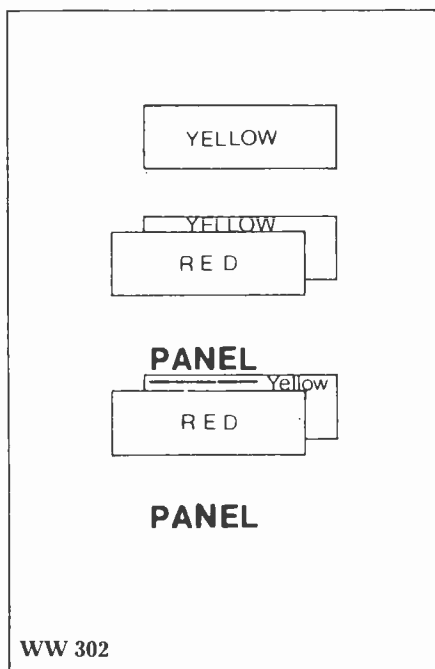
## Graphic transfers

P.c.b. and rub-down acid-resist graphic transfers, manufactured by E. R. Nicholls, includes space bars which enable users to lay transfers level and with the correct letter, word and line spacings. A yellow strip is first placed on to the artwork below the desired position of the wording, and a red straight edge is positioned over it. The space bar of the first character is then lined up on the visible yellow strip so that when rubbed down the character transfers to the artwork and the space bar transfers to the yellow strip. By lining up the space bars of adjacent characters, correct spacings will result. White line spacers are used in a similar way to give correct line spacings. Another important feature is that the transfers contain adhesive only on the character area and not on the surrounding area. Transfers include capitals and lower case letters and numerals in 1/8, 1/4 and 1/2 inch sizes. Prices for complete kits are from £1.00, for the 1/8in set. E. R. Nicholls, 46 Lowfield Road, Stockport, Cheshire, **WW 302**





## Circuit module "time-savers" for development engineers

A range of circuit modules, called Cirblocs, includes power supplies, amplifiers, timers, comparators, count displays, waveform generators, relay drivers and switching and phase control units. All of the units are either ready to use or, by simple wire links and component programming, can be set up to provide desired operating characteristics. The manufacturers, Lascars Electronics Ltd, are a new organisation formed specifically to manufacture and market modules covering the most widely used electronic circuits so that engineers can produce many different electronic systems in the shortest possible time. The managing director of Lascars pointed out that all over the world engineers are spending time hard wiring the same basic types of circuits, during the development stage of their particular system. This range, he claims, offers these engineers a means of saving time by supplying basic, ready to use, circuits, leaving the engineer to devote more time to the development work. Also, he says, fault diagnosis and repair is simplified and complex systems may be constructed without specialised electronic knowledge.

Two of the modules, a power supply and a count-display unit, are illustrated below.

The  $\pm 15V$ , 100mA power supply is suitable for operational amplifiers, and has current, thermal shut-down and output short-circuit protection. Other features include a load regulation of 0.6%, line regulation of 0.13% and an output noise voltage of 0.06V; all of these parameters being typical and measured at 25°C. Five-, 12- and 24-V power supplies are also available.

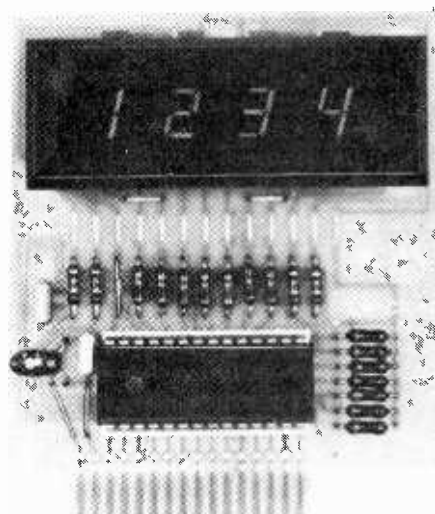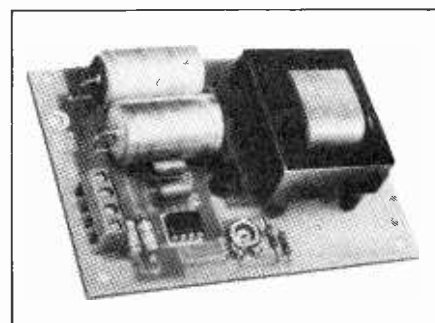The count-display module is a four-digit unit based on the Ferranti ZN1040E i.c. It has a 0.3in red (or green) i.e.d. display and may be supplied with a mounting bezel and filter. If the module is to be fitted in a low-profile instrument it may be divided in two and reconnected with ribbon cable. This unit, which has a t.t.l.-compatible input and requires a 5V supply, features up/down



counting up to 5MHz, a reset zero, a display latch, and "unwanted zero" suppression. An add-on module is also available to convert this count-display into a digital frequency meter with ranges 0 to 9.999kHz and 0 to 99.99kHz.

Full details of the complete Cirbloc range, together with connection instructions and a selection of hand tools, are given in a catalogue which may be obtained from Lascars. All of these products are offered on a same-day basis, if orders are received before 4 p.m. and include no minimum order charges. Lascars Electronics Limited, P.O. Box 12, Second Avenue, Billericay, Essex CM12 9QA. **WW 301**

## Duplex muting unit

Full duplex operation requires the simultaneous operation of both a transmitter and receiver. In order to avoid breakthrough from the transmitter to the receiver the antennae are often geographically spaced, typically 30 miles apart in land-based installations. This is obviously impossible with ship-board installations. The Duplex Muting Unit, which is placed between the receiver and the antennae, eliminates breakthrough by monitoring the nature and level of the r.f. and introducing attenuation for the duration of the

potential breakthrough — imitating the ear by automatically reducing sensitivity when the owner is talking. The unit requires no modifications to existing equipment, is compatible with all receivers without affecting the "type approval" and can represent, it is claimed, a saving of up to 90% against the costs of fitting feeders.

The frequency range of the unit is 0.1 to 30MHz and the insertion loss is typically 1dB. Callbuoy Marine Electronics Limited, 6 Somerset Road, Cwmbran, Gwent NP4 1QX. **WW 303**

## Polypropylene capacitors

Capacitors in the KP72 range have polypropylene dielectrics, instead of polystyrene, and use aluminium foil as electrodes. It is claimed that these capacitors offer a considerable improvement in heat resistance compared to polystyrene capacitors. Nickel silver terminals, welded to the foil electrodes, make the capacitors suitable for r.f. applications. Capacitances range from 100 to 33,000pF in tolerances of  $\pm 10\%$ ,  $\pm 5\%$  and  $\pm 2.5\%$  and are available with working voltages of 63, 160 and 630V. AEG-Telefunken UK Limited, Bath Road, Slough, Berks SL1 4AW.

WW 304

## Miniature variable capacitors

Miniature trimmer capacitors in the Voltronics CP range, from ITT Components, are suitable for tuning circuits up to 5GHz. Two basic capacitance types 2.5 and 9pF, are available and these are tuned by sliding a shuttle from one end of the component to the other. They may be used to facilitate rough tuning of several stages before final tuning. The devices have contact resistances of  $0.005\Omega$ , voltage ratings of 15V d.c. (300V d.c. max. surge) and temperature coefficients of  $\pm 100$  p.p.m./ $^{\circ}\text{C}$ . Minimum life is quoted as 1000 cycles. ITT Components Group Europe, Capacitor Division, Brixham Road, Paignton, Devon TQ4 7BE.

WW 305



WW 305

## Stereo equalizer

The EQ2 stereo equalizer has eleven bands per channel and provides full equalization from 20Hz to 20kHz with a cut or boost of  $\pm 15\text{dB}$  on each band. Each filter has a control which allows an  $\pm \frac{1}{2}$  octave variation of the centre frequency, and tone controls are also provided allowing very low phase distortion equalisations. Balanced inputs provide either unity gain or switched 10dB gain. L.e.d.s are provided to monitor and indicate overload. Frequency response is  $\pm 0.1\text{dB}$  from 20Hz to 20kHz and i.m. distortion is below 0.01% at the rated output of 2.5V r.m.s. Macinnes Laboratories Limited, Macinnes House, Carlton Park Industrial Estate, Saxmundham, Suffolk.

WW 306

## Drive/stepping motors

A series of drive and stepping motors specifically designed for floppy disc drive applications has been introduced by Eastern Air Devices. The standard 1/100 h.p. a.c. drive motor has a high inertia ratio and output speeds of 1500rev/min at 50Hz or 1800 rev/min at 60Hz. This unit is a permanent-split-capacitor synchronous motor with an automatic-reset thermal overload protector.

The stepping motors, sizes 18 and 20, have single or multiple-start lead screws and are available with  $15^{\circ}$  step angles for 3 or 4 phase supplies. These variable

reluctance motors are totally-enclosed bi-directional devices with permanently lubricated ball bearings. Computer Controls Limited, 19 Buckingham Street, London WC2N 6EQ.

WW 307


## Rotary switch

A multi-wafer rotary switch, designated as Type 30, has ground, silicone treated h.f. ceramic wafers for high insulation resistance. The switch, which has a roller-type index mechanism allowing central bush or two-hole mounting, is available with up to 26 shorting and 13 non-shorting positions, with or without stops. Contacts are gold flash on silver plate as standard or hard gold plating as an option, and are protected from dust and solder vapour by transparent plastic covers. Operational life is quoted as 25,000 rotations and the temperature range is  $-40$  to  $+85^{\circ}\text{C}$ . Radiatron Components Limited, 76 Crown Road, Twickenham, Middlesex.


WW 308

## Precision resistors


Wirewound resistors, available from G.E. Electronics Ltd, have standard tolerances of 0.1% and are rated at 0.3W ( $70^{\circ}\text{C}$ ). These resistors, in values from  $10\Omega$  to  $1\text{M}\Omega$ , have temperature coefficients of  $\pm 3$  p.p.m. over the range 0 to  $85^{\circ}\text{C}$  and  $\pm 5$  p.p.m. over the range  $-55$  to  $145^{\circ}\text{C}$ . The components are also available in 0.025 and 0.01% tolerances

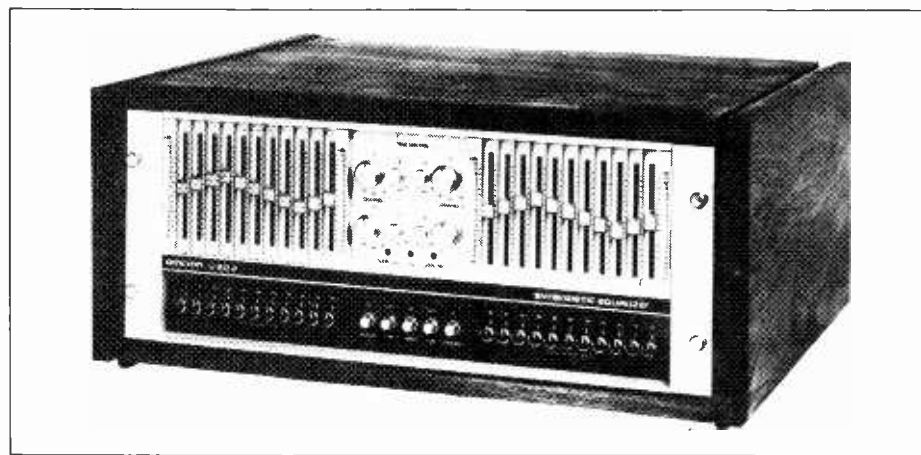

WW 306

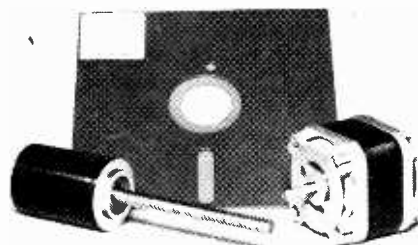

WW 307

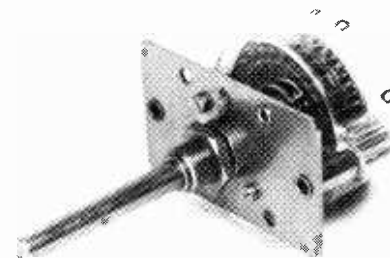

WW 308

and are manufactured and tested to MIL-R93, MIL-Std-202 and DIN40040. G.E. Electronics Limited, 182-184 Campden Hill Road, Kensington, London W8 7AS.

**WW 309**

## Low-cost 5MHz oscilloscope

The S61 oscilloscope is a single trace 5MHz instrument featuring calibrated deflection factors from 5mV/div to 20V/div and sweep rates from 1 s/div to 500ms/div. Simple trigger controls provide a clear, jitter-free trace at all settings and levels over the entire bandwidth it is claimed. A trigger source may be switch selected from either an internal, external, or line frequency. An external X facility is provided for the X-Y display of Lissajous figures and other interactive signals, particularly useful in educational applications. The S61 has an 8 × 10cm screen and is priced at £125 + V.A.T. Electroplan Ltd, P.O. Box 19, Orchard Road, Royston, Herts.

**WW 310**

## General purpose multimeter

The UM11 multimeter, from Poland, has 38 ranges and offers high sensitivities coupled with high input impedances. It has nine direct voltage ranges having input impedance of 100kΩ/V and



**WW 310**

covering full scale values from 150mV to 1500V. Eight alternating voltage ranges, with sensitivities of 31.6kΩ/V, cover the range 1.5 to 1500V. Other ranges cover direct and alternating current, resistance and dBm. The meter is supplied with a leather carrying case and is priced at £39.50. Electronic Brokers Limited, 49-53 Pancras Road, London NW1 2QB.

**WW 311**

## Wheatstone bridge

A Wheatstone bridge, designated as type 2272, enables measurement of resistances from 0.001Ω to 1,000MΩ with an accuracy of ±0.002% between 22 and 24°C or ±0.005% between 18 and 28°C. The load on the unknown resistor is less than 50mW. The bridge, which is equipped with leakage current protection for improved accuracy, is supplied by a built-in power supply and has a zero-indicator having a sensitivity of 150nV/mm. Tettex AG Instruments, P.O. Box, CH 8042 Zurich, Switzerland.

**WW 312**

## U.h.f. attenuators

Variable attenuators in the 67DR range, from AEG-Telefunken, are constant impedance units suitable for use in broadband amplifiers — for example in distribution systems having frequencies 40 to 860MHz. The attenuators are available in three versions: 50, 60 and 75Ω with attenuations from 0 to 20dB.

**WW 311.**



Four mechanical versions, with vertical or horizontal mountings, are also produced for p.c. or conventional wiring boards. AEG-Telefunken UK Limited, Bath Road, Slough, Berks SL1 4AW.

**WW 313**

## V.h.f./u.h.f. amplifiers


A series of high dynamic range, wide-band linear-amplifiers, from the Microwave Semiconductor Corporation, operate over the range 20 to 1000MHz. The amplifiers have outputs of about 25 to 29dBm at the 1dB compression point, with typical gains of 30dB at 1GHz. Typical noise figures are 7.5dB and operating temperatures range from -20 to +70°C. Tranchant Electronics UK Limited, 100a High Street, Hampton, Middlesex TW9w wST.

**WW 314**


## Silent timers

A silent operating elapsed-time control, the Type ET from NSF Controls, is variable from 4 to 30 minutes and has a switch rating of 16A at 240V a.c. The unit has an eddy current brake mechanism and may be produced to customers' specifications for time cycles, mounting, shaft details and other characteristics. Switches are either s.p.s.t. or d.p.s.t. NSF Controls Ltd, Fence Houses, Houghton-le-Spring, Tyne & Wear DH4 5RG.

**WW 315**

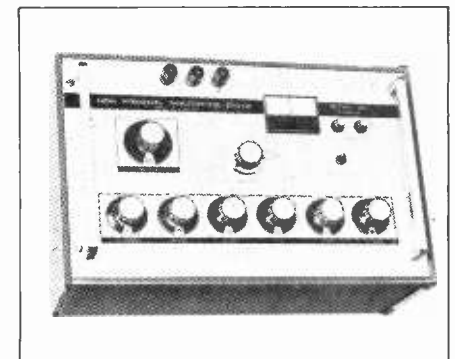

**WW312**

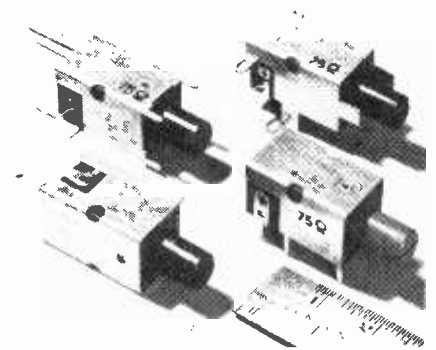

**WW 313**

# Just for the record

## Memories of the early years of recording

by Alan D. Foster

We have already been reminded that the year 1977 marks the centenary of the invention of sound recording. To me, this prompts the very sobering thought that I can clearly remember further than half way back over this period of time.

My earliest recollection of the wonders of recorded sound was at about the age of eight. An uncle of mine had an Edison phonograph and a large number of cylinder records. There may in fact have been less than 30 of them in all, but to me at the time it was a very impressive collection. The model of phonograph he had was a fine machine, all nickel plate and shining black, lavishly decorated in gold. It had two soundboxes, one for making and another for playing records, and must have cost about £10, with records in those days running at around one shilling.

Phonographs were made in a variety of models, the cheaper ones being very simple machines, driven by a key-wound clockwork motor with a fan governor rather like a musical box. These models had the unfortunate habit of slowing down during the run of the record. "Melody in 'F'" could well finish up "Melody in 'E,'" and if the machine were not placed on a perfectly level table, the stylus was prone to jump a groove now and then.

I remember my uncle's bitter complaint that blank cylinders for making one's own records cost more than professionally-made ones but, of course, they could be used over and over again. The record was simply placed on the machine, and a special cutting tool would shave off a thin layer of wax, removing the previous recording. After the application of wax polish and a finish-off with a soft duster, the cylinder would gleam like new all ready to be re-used. About 20 or more recordings could be made before the record became too thin and had to be discarded. Cylinder records were fragile things, sold in flock-lined boxes to protect the relatively soft wax surface. Apart from being dropped on to the floor an untimely end could result simply by forgetfully leaving a record on the machine overnight. In the morning, there could be a gaping crack running right across the face of the record! With the usual overnight fall in room temperature the record would shrink on to the machine cylinder so tightly that it would simply burst.

Although he may have known a good deal about music, my uncle knew a good

deal less about technical matters. I remember him one day standing by the window, closely inspecting a record through a pocket magnifier. "I just can't understand," he said, with a very puzzled expression, "how it is possible to record so many different notes all at the same time." "After all," he reasoned, "There is only one track of vibrations on the record and only one stylus to follow them so how on earth does it work!"

The disc record with which we are familiar today dates from the beginning of this century, yet so well established was the phonograph that both cylinder and disc records co-existed for many years. Edison and other manufacturers were producing cylinder records up to the 1920s until the demand fell off completely in favour of the disc record. The big breakthrough came after 1924, with what nowadays we call electronics. This had a dramatic effect on the recording industry. Technical know-how flourished at a healthy pace and, combined with a widening knowledge of acoustics, records were produced of such quality that some still bear comparison with today's high standard.

### The heavy gang

In the late 20s, The H.M.V. Gramophone Company, as it was then, presented a demonstration of electrical recording at the premises of Rushworth & Dreaper, a leading, long established family music house in Liverpool. The demonstration was arranged in the large, ground floor showrooms, the handsome display of grand pianos and cases of musical instruments being put aside to make room for all the paraphernalia necessary to make a record. This consisted of an amplifier rack, control panel, two recording lathes and a large supply of thick, yellow, wax recording blanks. They even brought along their own power supply in the form of dozens of large lead acid accumulators. I was surprised to see that the record cutting lathes were powered not by an electric motor or even clockwork but by a huge iron block suspended like a clock weight under the cutting lathe. This, I suppose provided the smoothest possible source of power but, amongst the other sophisticated hardware, did look a bit primitive.

The advent of electrical recording gave voice to the silent films of the day. Sound accompanying some early films was recorded on 16in discs, running on a turntable directly coupled to the film

projector. Projectionists of the day found this period in the development of the talkies to be a very tedious one indeed. In order to maintain synchronization between sound and picture, both the film in the projector and the disc on the turntable had to be set at precise starting points. Of course, the inevitable mistake had to happen. Everything was set, the projector and turntable started together. The sub-titles came on the screen, "World Boy Scout Jamboree" followed by the usual credit titles. Meanwhile background music came from the record on the turntable. Everything seemed OK. The projectionist was himself interested in the subject to settle down to watch the film. The music slowly faded as, on the screen, Lord Baden-Powell mounted the rostrum to make the opening speech — and then it happened.

As the chief scout's lips moved there came out, not inspiring words appropriate to the occasion, but the loud sound of a dog barking! Obviously something was radically wrong, but momentarily the projectionist was transfixed by the near perfect synchronization between the movement of Baden Powell's lips and the barking of the dog — "it was uncanny," he said. The record he had put on the turntable was intended to accompany a film of the "Down on the Farm" type. In haste, he had mis-read the film code mark S.O.F. (sound-on-film) for S.O.D. (sound-on-disc). The experience, he said, haunted him for weeks although he did admit to the satisfaction of having caused as big a laugh as Laurel and Hardy. Only the cinema manager wasn't amused.

This state of affairs was fortunately short-lived and ended with the exclusive use of the "Photophone" system. Thereafter, the sound to accompany a film was recorded photographically along the film itself.

As a result of well directed propaganda, I became the proud owner of my uncle's phonograph and what remained of his record collection. Inspired by the demonstration I had seen at Rushworth & Dreaper, I made an electrical recording head from an S. G. Brown Type A earphone. The old machine was given a new lease of life. Gone was the large horn and in its place was a hefty coil speaker, mounted on a large baffle board, driven by a push-pull amplifier. There was no end to my recordings, music and variety from the radio, piano duets with a friend and even the interval signals between programmes (who, I wonder, can remember those?). One day I found my father, glass in eye, closely studying the works of his watch. Its normally good timekeeping had gone completely crazy, he said. I remembered then I had made a record of the chimes of Big Ben which was wont to come booming out of my den at any time of day. Could the "old man" have been setting his watch to the recorded chimes? I often wondered but never asked.



Safe, tough, efficient and versatile – that's our new miniature CX iron.

**Safe** because it is virtually leak-free (leakage current less than  $1\mu\text{A}$ ). Earth it if you like – three core lead. It is made to conform with B.S. 3456 and has a breakdown voltage of more than 4000V.

**Tough** because the handle is almost unbreakable and the ceramic shaft is covered by a stainless steel shaft.

**Efficient** because the element is situated right inside the soldering bit and the heat generated by its 17 watts is not wasted.

**Versatile** because the iron can be used for a wide variety of soldering jobs; with six easily interchangeable, slide-on bits, ranging from  $\frac{1}{8}$ " right down to  $\frac{3}{32}$ " (1mm). It's suitable for small, miniature and micro miniature joints.

Available for 220-250 volts or 100-120 volts. Weight –  $1\frac{1}{2}$  oz (40 gram). Length  $7\frac{1}{2}$ " (19cm). Price – **£3.20** fitted with standard bit  $\frac{1}{2}$ " (2.3mm). Spare bits £0.46; £0.72; £0.84 exclusive of VAT.

Stocked by most of the well-known wholesalers and many retailers. Or direct from us if you are desperate.

Send for colour catalogue from:  
Antex Freepost, Plymouth PL1 1BR

Model X.25 is a general purpose soldering iron, also with two shafts for toughness and perfect insulation. Available for 220-250 volts or 100-120 volts at 25 watts and priced at **£3.20** exclusive of VAT.




Stand model S.T.3 has a chromium plated steel spring, two sponges for cleaning the bits and is priced at **£1.40** exclusive of VAT.



Mayflower House, Plymouth.  
Telephone (0752) 67377/8 Telex 45296  
Giro 2581030

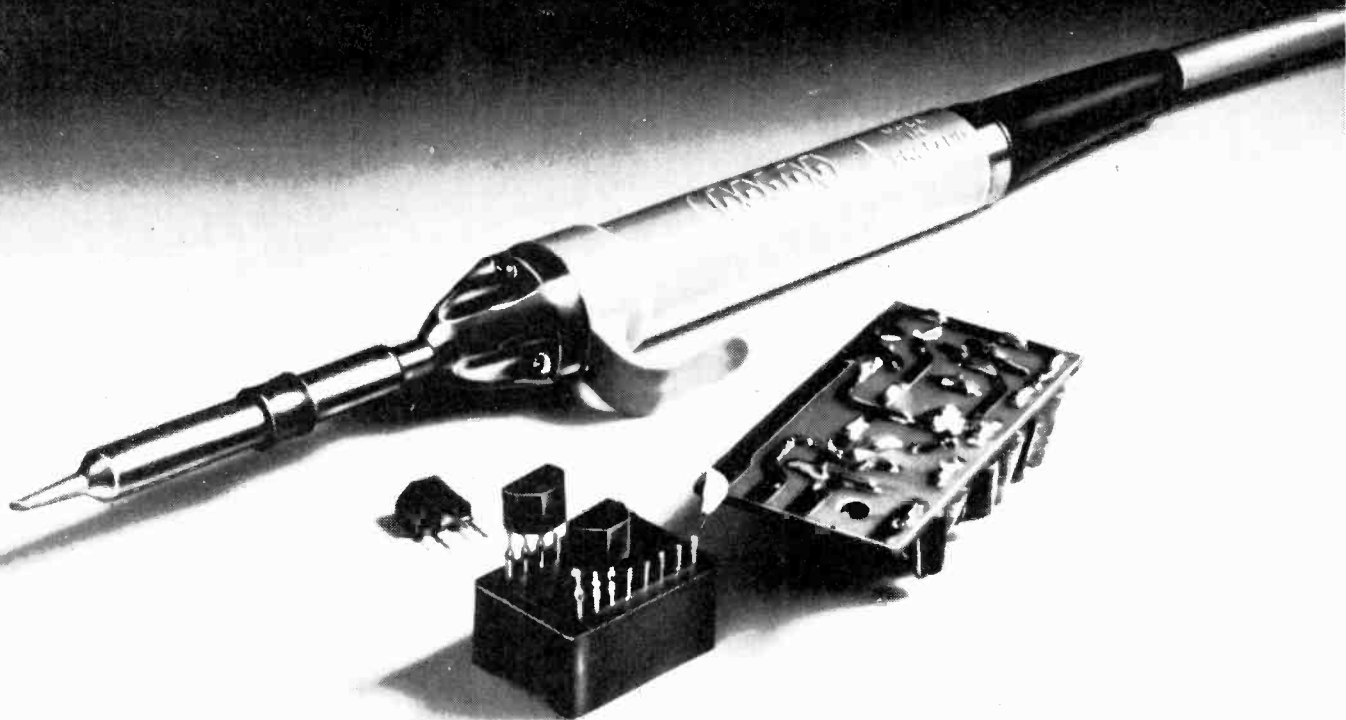**Forget all you've ever read about  
miniaturised soldering irons.  
This is the NEW ANTEX CX.**



# DEMA ELECTRONICS INTERNATIONAL

ELECTRONIC COMPONENTS DISTRIBUTOR FOR INDUSTRY AND HOBBYIST

MONTHLY SPECIALS			
<b>LINEARS</b>	LM 309 K 99 or 3/1 75	LM 556 69 or 3/1 90	<b>MEMORIES</b>
LM 550 50 or 3/1 25	LM 708 18 or 3/1 50	1103 1024 8 Bit Ram MOS 99	1024 8 Bit Ram MOS 135
LM 555 31 or 3/1 85	LM 3900 29 or 3/1 80	7489 (8225) 64 Bit Ram TTL 1.45	1702 2048 8 Bit Ram 6.95
		5203 2048 8 Bit U/Violet PROMS 5.95	
<b>CALCULATOR CHIPS</b>	CT 5002 8 Bit Oper 5001 59 or 3/1 25	CT 5005 12 Digit 4 Func w/Mem 69 or 3/1 50	<b>CLOCK CHIPS</b>
5/25 18 Pin 6 Dlg MUX	5/28 8 Dlg 6 Func + Mem/Conv/ Floating Dec 8 Bit Op 1.20 or 3/1 20	5311 28 Pin BCD 6 Dlg MUX 2.60	5312 24 Pin BCD 4 Dlg MUX 2.25
		5316 4 Digit 12 24 Hr 24 Pin 3.65	7001 4 or 6 Digit Alarm 3.50
<b>TTL &amp; CMOS</b>	Quantity Discounts (any combination) 15.50 Less 10% 51 & Up Less 15%	<b>SCHOTTKY</b>	
		74500 18 or 3/1 50 74522 25 or 3/1 65	74503 20 or 3/1 50 74532 35 or 3/1 90
		74508 28 or 3/1 80 74579 25 or 3/1 65	

TTL 7400 SERIES		NEW LOW PRICES	
7400 £ 0.09	7440 £ 0.11	7485 £ 0.85	74155 £ 0.69
7401 0.09	7441 0.58	7486 0.25	74156 0.69
7402 0.10	7442 0.48	7489 1.45	74157 0.69
7403 0.10	7443 0.48	7490 0.32	74158 0.69
7404 0.13	7444 0.60	7491 0.55	74160 0.89
7405 0.13	7445 0.70	7492 0.35	74162 0.89
7406 0.22	7446 0.80	7493 0.35	74163 0.89
7407 0.22	7447 0.65	7494 0.40	74164 1.05
7408 0.13	7448 0.60	7495 0.45	74165 1.05
7409 0.13	7450 0.12	7496 0.55	74166 1.05
7410 0.09	7451 0.12	74100 0.89	74170 1.65
7411 0.16	7453 0.12	74107 0.23	74175 0.85
7413 0.25	7454 0.12	74121 0.23	74180 0.80
7414 0.22	7460 0.11	74122 0.37	74181 2.00
7416 0.22	7470 0.24	74123 0.45	74182 0.80
7420 0.11	7472 0.21	74145 0.57	74192 0.95
7425 0.23	7473 0.25	74150 0.75	74193 0.95
7430 0.11	7474 0.25	74151 0.59	74194 0.85
7432 0.22	7475 0.35	74153 0.69	74195 0.78
7437 0.25	7476 0.24	74154 1.05	74198 1.20
7438 0.19	7483 0.69		74199 1.70

SCHOTTKY			
74500 24	74504 29	74520 29	74574 29
74502 29	74508 35	74522 29	
74503 24	74510 29	74532 39	

LOW POWER SCHOTTKY			
74LS00 23	74LS20 23	74LS90 1.25	74LS193 1.75
74LS02 23	74LS32 27	74LS93 1.25	74LS197 1.65
74LS04 25	74LS40 33	74LS95 2.10	
74LS08 27	74LS42 1.30	74LS107 .39	
74LS10 23	74LS74 39	74LS164 1.80	

CMOS 4000 SERIES			
4000A £ 0.14	4010 £ 0.36	4023 £ 0.65	4050 £ 0.35
4001 0.14	4011 0.14	4024 0.50	4066 0.46
4002 0.14	4012 0.14	4025 0.14	4069 0.15
4006 0.15	4013 0.36	4027 0.36	4071 0.15
4007 0.14	4014 0.65	4028 0.59	
4008 0.65	4015 0.65	4030 0.36	
4009 0.36	4016 0.38	4035 0.75	
	4020 0.75	4042 0.55	
	4021 0.65	4049 0.35	
	4022 0.14		

LINEARS			
LM300 T099 £ 0.45	340T T092 £ 1.25	739 A DIP £ 0.65	
301 V DIP 0.25	380 A DIP 0.80	741 V DIP 0.22	
302 T099 0.40	381 A DIP 0.90	747 A DIP 0.44	
304 TO100 0.50	550 A DIP 0.55	748 V DIP 0.24	
305 T099 0.45	555 V DIP 0.35	5556 (1456) V DIP 0.95	
307 V DIP 0.38	556 B DIP 0.75	5558 (1458) V DIP 0.45	
308 T099 0.40	560 B DIP 2.45	LM3900 A DIP 0.25	
A DIP 0.59	562 B DIP 2.45	75450 V DIP 1.00	
T099 0.65	565 A DIP 1.40	75451 V DIP 0.23	
T03 1.10	566 V DIP 1.40	75452 V DIP 0.23	
1 pkg 0.59	567 V DIP 1.55	75453 V DIP 0.23	
V DIP 0.75	709 A DIP 0.20	75491 A pkg 0.60	
TO 3 NEG 710 A DIP 0.25	75492 A pkg 0.65	ICL8038 Funct Gen 2.80	
5 2 12 15 100 711 A DIP 0.18		Volt Contr Oscillator, Sine Sq 8864 22 Pin pkg 1.45	
A DIP 1.07	723 A DIP 0.38		
A DIP 1.15			
103 1.50			
12V 1 AMP			

V Mini Dip, A 14L Dip, B 16L Dip, T099 8 Pin Header, TO100 10 Pin Header. Data sheets supplied on request. Add 20p ea. excised as noted.

MEMORIES w/DATA		CALCULATORS & CLOCKS w/DATA	
1101 256 Bit Ram Mos £ 1.30	5002 Cal Chip £ 0.79	5005 Cal Chip 0.79	
1103 1024 Bit Ram Mos 1.25	5225 Cal Chip 1.10	5311 Clock Chip 2.80	
7489 (8225) 64 Bit Ram TTL 1.45	5312 Clock Chip 2.50	5314 Clock Chip 3.45	
82523 Programmable ROM 2.15	5316 Clock Chip 3.95	5316 Clock Chip 3.95	
5260 1024 Bit Ram Low Power 1.45	CT7001 Clock Chip 3.85		
5261 1024 Bit Ram L Power 1.45			
1702A 2048 Bit Ram 11.35			
2102 1024 Bit Status Ram 2.75			

LEDS		TRANSISTORS	
MV 5020 Jumbo Red or Clear £ 0.15	2N 2219A T05 £ 0.42	2N 4124 T092 0.11	
MAN 1 Red 7 Seg 270 1.20	2N 2222 T018 0.17	2N 4126 T092 0.11	
MAN 3A Red Seg 127 0.20	2N 2369 T018 0.11	2N 4401 T092 0.11	
MAN 5 Green 7 Seg 270 1.85	2N 2905A T05 0.43	2N 5225 T092 0.17	
MAN 6 6 Solid Seg 2.60	2N 3227 T018 0.37	2N 5226 T092 0.17	
9 Digit Array Fairchild 37 with clear magnifying lens 2.80			

DISCOUNTS	MIN ORDER	All Items New Branded Guaranteed By DEMA ELECTRONICS
10% on orders over £ 10	£ 2.00	
15% on orders over £ 25		

SEND FOR FREE CATALOGUE

SEND FOR FREE CATALOGUE

**TERMS:** PRICES LISTED ARE BRITISH POUNDS & PENCE. SEND CHEQUE WITH ORDER. ACCESS CARD, BANKAMERICARD, BARCLAY CARD ACCEPTED. (Card # and expiration date requested). TERMS OFFERED TO SCHOOLS & INSTITUTIONS.

POSTAL AND HANDLING CHARGES SHIPMENT VIA AIR MAIL  
 under 4.99 add .45 £ 10 and over  
 5.00-9.99 add .35 No Charge

**DEMA ELECTRONICS INTERNATIONAL**  
 P.O. Box 407 San Ramon, Ca. 94583 USA  
 Cable DEMAEINTL

## You will know about Blind Rivets



Interesting data and application notes on Blind Rivets — yours for the asking

**Blind Rivets, of course are for making permanent joints in sheets, chassis, corners. What if you need a detachable joint? Read on about Anchor Nuts, blind rivets with internal threads.**

To fasten a lid or a panel that has got to come off, you need Anchor Nuts which are used with ordinary screws or bolts.




**Anchor Nuts System J, the high strength threaded insert for sheets and sections up to 0.270" 6.86mm.**



**Anchor Nuts System X, the threaded insert for sheets, plates, sections of unlimited thickness.**
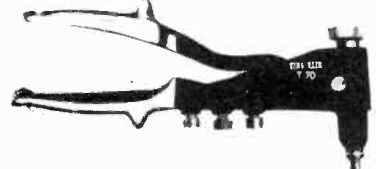
## Anchor Nuts are placed in seconds!

It's quick and easy, done on the job with tools similar to riveters. You can buy a hand tool for around £10 or a



kit in a carrying case with a tool and an assortment of Anchor Nuts for about £22. Anchor Nuts cost around £2-£6 a hundred.



There are kits for all regular thread systems, BA, Metric, Whitworth, UNC, UNF. Data and prices on request.

## HARMSWORTH

HARMSWORTH, TOWNLEY & CO. LTD.  
 HAREHILL TODMORDEN LANCS OL14 5JY  
 Phone TODMORDEN 2601 (STD 070 681 1601)

# SERVICE TRADING CO

## RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries

### WHY PAY MORE?!

**MULTI RANGE METER** A.C. volts 2.5-500 D.C. volts 2.5-500 (Sensitivity 2000 $\mu$ V D.C. & A.C.) D.C. current 0.1/1/10/100 mA Ohms range Sturdy compact moving coil instrument with 21 ranges dimensions 120 x 80 x 44mm Weight 0.32 kg **SERVICE TRADING CO Price £5.50.** Incl. leads anti battery Post 50p (Total price inc VAT & Post **£6.48.**)



**TRIAC** Raytheon tag symmetrical Triac. Type Tag 250/500v 10 amp 500 pW Glass passivated plastic triac. Swiss precision product for long term reliability **£1.25.** P&P 10p (inclusive of date and application sheet) Suitable Diac 20p.

**0 to 60 MINUTES CLOCKWORK TIMER.** Double pole 15 amp 230AC. Contacts (no dial) **£1.50.** P&P 30p

**GALVANOMETER.** 50 micro mirror galvanometer Calibrated 50 0.50 and 0-100 Mfg by Griffin & George Ltd. Offered at fraction of maker's price in original ministry packing **£12.00.** p&p 60p



**HONEYWELL PUSH BUTTON PANEL MOUNTING MICRO SWITCH ASSEMBLY.**

Each bank comprises of a change-over rated at 10 amp 250v A.C. Black knob 1" dia. fixing hole  $\frac{3}{16}$ ". Price one bank **40p.** Two bank **50p.** Three bank **60p.** Min order 5 pieces P&P 50p



**230 VOLT FAN ASSEMBLY** Continuously rated removable aluminum blades Price **£1.25.** Post 50p VAT 12 1/2 %



**21-WAY SELECTOR SWITCH** with reset coil

The ingenious electro-mechanical device can be switched up to 21 positions and can be reset from any position by energising the reset coil 230/240v A.C. operation. Unit is mounted on strong chassis. Complete with cover. Price **£5.50.** P&P 75p



**PRECISION CENTRIFUGAL BLOWERS** (230/240v A.C.)

Mfg by Smiths Industries. Miniature model Series SF 200 Size 95mm x 87mm Aperture 38mm x 31mm 12 c.f.m. **£2.75.** Post 50p Other types available. phone for details. Also available extremely powerful blower mfg by Fracmo.



**FRACMO** 115/230v A.C. 2800/3400 r.p.m. fan type aperture 3" x 2 1/2" VBLA 25/c. Price **£12.00.** Post £1 00

**BLOWER UNIT**

200/240v a.c. precision German built. Dynamically balanced, quiet, con rated reversible. Consumption 60mA Size 120mm dia x 60mm dep Price **£3.50.** Post 50p




**UNISELECTOR SWITCH**

4 bank 25 volt 75 ohm coil. 16-48v D.C. operation. Ex. new equipment **£4.25.** P&P 75p Total price inc VAT **£5.40.**



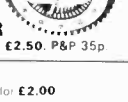**MINIATURE UNISELECTOR**

12v 11 way 4 bank (3 non-bridging 1 homing) **£2.50.** P&P 35p




**MICRO SWITCHES**

Omron roller micro switch type V15 FL 22-1C 10 for **£2.00** post 50p Min order 10 Sub miniature Burgess type V 41 1 10 for **£2.50.** 50 for **£10.00.** post paid Sub miniature Honeywell roller M/S type J 115M 906/F 10 for **£2.50.** post paid **LEVER OPERATED** 10 amp c.o. Mfg by Unimax USA 10 for **£4.00** plus 50p P&P (min order 10).



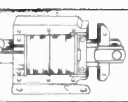**NEW HEAVY DUTY SOLENOID**

Mfg by Magnet Devices 740v A.C. operation approx. 24lb pull at 1.25" Price **£7.00.** P&P 75p



**230-250 VOLT A.C. SOLENOID**

Similar in appearance to illustration. Approximately 1 1/2lb pull. Size of feet 1 1/2" x 1 1/2" x 1 1/2" Price **£1.00.** Post 25p



**24 VOLT D.C. SOLENOIDS**

UNIT containing 1 heavy duty solenoid approx. 25 lb. pull at 1 in travel 2 solenoids of approx. 1 lb. pull at 1/2 in travel 6 solenoids of approx. 4 oz pull at 1/2 in travel Plus 1 24V D.C. 1 heavy duty 1 make relay Price **£3.00.** Post £1 00 **ABSOLUTE BARGAIN**

**240 A.C. SOLENOID OPERATED FLUID VALVE**

Rated 1 p.s.i. will handle up to 7 p.s.i. Forged brass body stainless steel core and spring 1/2 in. b.s.p. inlet outlet Precision made British mfg. PRICE **£2.75.** Post 50p. NEW original packing



**600 WATT DIMMER SWITCH**

Easily fitted. Fully guaranteed by makers. Will control up to 600 watts of all lighting except fluorescent at mains voltage. Complete with simple instructions **£3.65.** Post 25p 1000 watt model **£5.60.** Post 25p 2000 watt model **£9.75.** Post 40p



## VARIABLE VOLTAGE TRANSFORMERS

Carriage extra **INPUT 230 v. A.C. 50/60 OUTPUT VARIABLE 0/260v. A.C.** BRAND NEW. All types. **200W (1 Amp) fitted A/C volt meter** **£11.50** **0.5 KVA (Max. 2 1/2 Amp)** **£14.00** **1 KVA (Max. 5 Amp)** **£18.00** **2 KVA (Max. 10 Amp)** **£30.00** **3 KVA (Max. 15 Amp)** **£38.00** **4 KVA (Max. 20 Amp)** **£60.00**

## LT TRANSFORMERS

0-12v 24v at 1 amp **£2.50** p&p 50p  
0-15v at 1 amp + 0-15v at 1 amp (30v 1 amp) **£2.50** p&p 50p  
25-0-25v at 2 1/2 amp **£4.50** p&p 75p  
0-12v/24v 10 amp **£12.35** p&p £1 50  
0-4v/6v/24v 32v at 12 amp **£13.00** p&p £1 50  
0-12v at 20 amp or 0-24v at 10 amp **£12.40** p&p £1 50  
0-6v/12v/17v/18v/20v at 20 amp **£14.00** p&p £1 50  
0-6v/12v at 20 amp **£11.85** p&p £1 00  
Other types in stock phone in enquiries

## AUTO TRANSFORMERS

Step up step down 0 115 200 230v/140v  
75 watt **£4.20** p&p 80p 150 watt **£6.00** p&p 80p 300 watt **£8.40.** p&p 95p 500 watt **£12.90** p&p £1 25 1000 watt **£19.20** p&p £1 50p

## 300 V.A. ISOLATING TRANSFORMER

115 230 screened primary two separate or 115v for 115 or 230v. Secondary two 115v at 150 V.A. for 115 or 230v output. Can be used in series of parallel connections. Fully tropicalised. Length 13.5cm width 11cm weight 15lbs. Special price **£6.00.** carr £1 00

## RODENE UNISET TYPE 71

**TIMER.** 0.60 sec. 230v A.C. operation. Incorporating a lapse time indicator and repeat facilities. A precision maintained timer ideal for processing timing photography. Weighing mixing etc. Price **£6.00.** p&p 60p



## GENTS 4" ALARM BELL

3-4 1/2 v D.C. Price **£4.50.** P&P 50p



## STROBE! STROBE! STROBE!

### \* HY-LIGHT STROBE Mk. IV \*

\* Latest type Xenon white light tube. Solid state timing and triggering circuit. 230/240 volt A.C. operation. Speed adjustable 1/2 to 1 p.s. Designed for large rooms, halls, etc. Light output greater than many so called 4 Joule strobes. Price **£18.00.** Post 75p. Specially designed case and reflector for Hy-Light **£8.25.** Post 11 00

### \* XENON FLASH GUN TUBES \*

Range of Xenon tubes available from stock. S.A.E. for full details



### \* ULTRA VIOLET BLACK LIGHT FLUORESCENT TUBES \*


\* 4ft. 40 watt £7.00 (halogens only). 2ft. 20 watt **£4.60.** Post 60p (for use in stan. bipin fittings). MINI 12in. 8 watt **£1.75.** Post 25p 9in. 6 watt **£1.40.** 6in. 4 watt **£1.40.** Post 25p Complete ballast unit. Either 6" 9" or 12" tube 230V A.C. op. **£3.50** plus p&p 40p. Also available for 12V D.C. op. **£3.50** plus p&p 40p

### \* BIG BLACK LIGHT \*

\* 400W Mercury Vapour Ultra Violet Lamp. Powerful source of UV P.F. ballast unit is essential with this lamp. Price of bulb and matched ballast unit. **£28.** Post £2 Spare bulb only **£10.** Post 80p
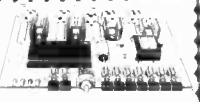
## SQUAD LIGHT

A new conception in light control. Four channels each capable of handling 750 watts of spotlights floodlights or dozens of small mains lamps. Seven programs all speed controlled plus flash modulation effectively giving 14 different displays. Makes sound-to-light obsolete. Completely electrically and mechanically noise free. Price only **£60.00** Post 75p S.A.E. (Footscap) for further details.




## RELAYS

Wide range of AC and DC relays available from stock. Phone or write in your enquiries

## COLOUR WHEEL PROJECTOR
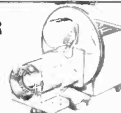
### TYPE P150 INTACHANGE

200/240v a.c. 50Hz 150W lamp complete with oil filled colour wheel and motor plate. Takes intachange accessories and full range of lenses **£32.00.** Post £1 00



## INSULATION TESTERS

### (NEW)

Test to I.E.E. Spec. Rugged metal construction suitable for bench or field work. constant speed clutch. Size L 8 in. W 4 in. H 6 in. weight 6 lb **100 VOLTS** 500 megohms **£40.00** Post 80p **1000 VOLTS** 1000 megohms **£46.00** Post 80p SAE for leaflet



**VAT AT CURRENT RATE MUST BE ADDED TO ALL ORDERS**

**FOR THE TOTAL VALUE OF GOODS INCLUDING POSTAGE UNLESS OTHERWISE STATED**

**ACCOUNT CUSTOMERS MIN. ORDER £10.00**

## GEARED MOTORS

100 R.P.M. 115 lbs. ins.!!

115 lb ins 110 volt, 50Hz, 2.8 amp. single phase split capacitor motor. Immense power. Continuously rated. Totally enclosed. Fan cooled. In-line gearbox. Length 250mm. Dia 135mm. Spindle Dia 15.5mm. Length 145mm. ex-equipment tested **£12.00.** Post £1 50 Suitable transformer 230/240 volt **£8.00.** Post 75p



### 15 R.P.M.

Type SD48 15 r.p.m. 80 lb. ins. Input 100/120 volt A.C. Length incl gearbox 270mm. Height 135mm. Width 150mm. Shaft free 16mm. Weight 8.5 Kilos. BRAND NEW. Price **£10.00.** carr £1 00 Suitable transformer for use on 220/240 volt A.C. **£6.00.** Post 50p

## DRAYTON MOTOR

Type RQR 230/250v 50c. Continuously rated 1 RPM 90lb in. Reversible motor. Twin spindle size 100mm by 140mm by 125mm. Shaft 50mm by 8mm. Weight 2 kilos. New Price **£16.50.** P&P £1 00.



## BODINE TYPE N.C.I. GEARED MOTOR

(Type 1) 71 r.p.m. torque 10 lb. in. Reversible 1/70th h.p. cycle 38 amp. This U.S.A. motor is offered in as new condition. Input voltage of motor 115v A.C. Supplied complete with transformer for 230/240v A.C. input. Price type **£6.25.** Post 75p or less transformer **£3.75.** Post 65p (Type 3) 71 r.p.m. 230 Volt A.C. Continuously rated. Non reversible. **£6.50** Post 75p



6/9 VOLT D.C. GOVERNED 40mm x 40mm Spindle 10mm Dia 2 mm **£1.00** Post Paid Two for **£1.85** Post Paid

24 R.P.M. 230 volt A.C. Continuously rated. Mfg. Mycalex. Ex-equip. Fully tested **£3.85** Post 75p.

1 R.P.M. 230/240 VOLT A.C. SYNCHRONOUS!! Ex-equipment Thoroughly tested and guaranteed. **ONLY £1.50.** Post 20p

20 R.P.M. GEARED MOTOR. 230/240 volt 20 r.p.m. motor **£1.00.** Post 20p

HALF REV. PER HOUR. Sync. Motor 230/240v A.C. Mfg. by Smiths **£1.** P&P 20p

## REVERSIBLE MOTOR 230V A.C.

General Electric 230V A.C. 1.600 r.p.m. 0.25 amp. Complete with anti-vibration mounting bracket and capacitor. O.A. size 110mm x 95mm. Spindle 5/16" dia 20mm long. Ex-equipment tested **£3.00.** Post 50p


## REVERSIBLE MOTOR

AEI 1 1/2 hp continuous rated reversible motor 100/120v A.C. 50/60 cycle 2850 r.p.m. Flange fixing dia 4". length 4 1/2". shaft 1" x 5/16". Price **£3.25.** P&P 75p



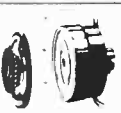
## METERS NEW 90mm Diameter

Type: 65CS D.C. mc. 2.5 10 20 50 amp **£3.00.** Post 20p 100 amp **£3.25.** Post 20p Type: 62T2 A.C. M 1 1 20 50 amp **£3.00** Post 20p 0.300 Volt A.C. M 1 **£3.00** and 300 volt A.C. R.M.C. **£3.25** Post 30p


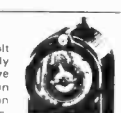
## BENDIX MAGNETIC CLUTCH

Superb example of electro-mechanics. Main body in two sections. Coil section is fixed and has 3/8" sleeve. The drive section rotating on the outer perimeter. When engaged the transmission is extremely powerful. Diameter 1 1/2". Total width 1 3/4". 24V D.C. op. Price **£3.50** plus p&p 45p



## TIME SWITCH

Horstmann Type V Mk II Time Switch 200/250 volt A.C. Two on two off every 24 hours. at any manually pre-set time 30 amp contacts 36-hour spring reserve in case of power failure. Day omitting device. Fitted in heavy high impact case with glass observation window. Built to highest Electricity Board spec. individually tested. Price **£7.75.** Post 50p (Total inc VAT **£8.91.**)



## A.C. MAINS TIMER UNIT

Based on an electric clock with 25 amp single pole switch which can be preset for any period up to 12 hrs. ahead to switch on for any length of time from 10 mins to 6 hrs then switch off. An additional 60 min. audible timer is also incorporated. Ideal for Tape Recorders, Lights, Electric Blankets etc. Attractive satin copper finish. Size 125 mm x 130 mm x 60 mm. Price **£2.25.** Post 40p (Total inc VAT & Post **£2.87.**)



## POWER RHEOSTATS

New ceramic construction vitreous enamel embedded winding heavy duty brush assembly. continuously rated.


25 WATT 10 25 100 150 250 500 1k 1.5k ohm **£1.90.** Post 20p 50 WATT 25 100 500 1k ohm **£2.40.** Post 25p 100 WATT 1 5 10 25 50 100 250 500 1k 1.5k 2.5k 5k ohm **£3.70.** Post 35p **Black Silver Skirted knob** calibrated in Nos 1-9. 1 1/2 in. dia brass bush. Ideal for above Rheostats. **22p** ea.


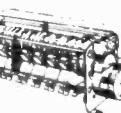
## PROGRAMME TIMERS

230 Volt A.C. Operation 15 or 20 r.p.m. Each cam operates a c/o micro switch. Ideal for lighting effects displays etc. Ex-equip. tested. Similar to illustration

6 CAM model **£5.00**  
9 CAM model **£6.50**  
12 CAM model **£7.50**  
Post 60p. Also available for 50 volt A.C. operation. Prices as above



ALL MAIL ORDERS, ALSO CALLERS AT:

57 BRIDGMAN ROAD, CHISWICK, LONDON, W4 5BB. Phone: 01-995 1560. Closed Saturdays.



## SERVICE TRADING CO.

SHOWROOMS NOW OPEN AMPLE PARKING

PERSONAL CALLERS ONLY

LITTLE NEWPORT STREET, LONDON, WC2H 7JJ. Tel.: 01-437 0576

# SCOPEX 456

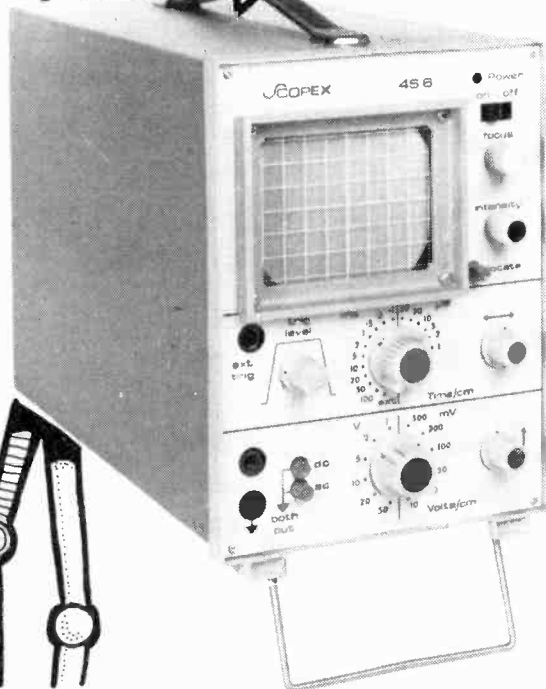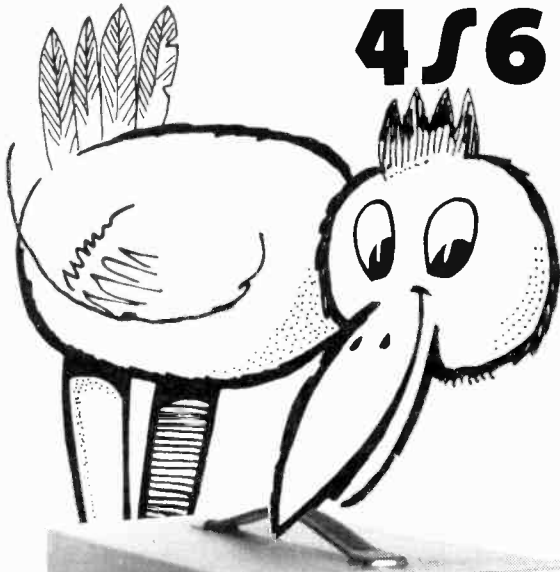

## SINGLE BEAM OSCILLOSCOPE

**45-6** 6MHz Bandwidth.  
10mV/cm Sensitivity.  
1 $\mu$ S/cm-100mS/cm Timebase  
(16 Calibrated ranges).  
Glaireq Non-reflective  
graticule.

**45-6LS...** (£115) Designed for LOW  
SPEED Measurements.  
10 $\mu$ S/cm-1 sec/cm Timebase.

# SCOPEX

SCOPEX Instruments Ltd.  
Pixmore Industrial Estate, Pixmore Avenue,  
Letchworth, Herts. SG6 1JJ (046 26)72771

# £98.00

(ex VAT)

® Regd Trade Mark

WW — 064 FOR FURTHER DETAILS

# THE JAMES SCOTT INDUSTRIAL MICROWAVE RANGE OF EQUIPMENT

The James Scott range of Microwave equipment offers industrial users a greater choice of alternative systems in robust, industrial, cast aluminium housings, for a wide variety of applications.

The range is made up of standard sub-assemblies which can be permuted to suit individual application requirements. Here are some suggested applications for these units.

- TRAIN CONTROL SYSTEMS
- PROCESS CONTROL SYSTEMS
- SAFETY BARRIERS
- INDUSTRIAL ALARM SYSTEMS
- INTRUDER ALARMS
- ROAD VEHICLE SENSING SYSTEMS
- PROXIMITY ALARMS
- SMALL OBJECT COUNTERS
- POSITIONING SYSTEMS
- PRESENCE/DETECTORS
- VIBRATION SENSING SYSTEMS
- LEVEL CONTROLLERS
- DOOR OPENING SYSTEMS

Please write or telephone for further information and technical literature to

**JAMES SCOTT**  
**(Electronic Engineering) Ltd**  
CARNTYNE INDUSTRIAL ESTATE  
GLASGOW G32 6AB Tel: 041 778 4296 Telex 778286

WW — 062 FOR FURTHER DETAILS









# NEW DITTON 22

...the only speaker that could successfully  
come between the famous 15 & 33.

The Celestion Ditton 22 has been added to the popular Ditton series especially for the discerning audiophile who demands large system performance, but cannot accommodate a big loudspeaker.

Utilising an 8 inch bass unit and 5 inch mid-range, specially designed and built by Celestion, plus the impressive HD 1000 dome tweeter, the Ditton 22 is a compact 3 way system capable of

delivering the sort of sound you would normally expect from a much larger loudspeaker.

You don't have to take our word for it-why not audition the Ditton 22 at your local dealer's showroom. We are sure that you will hear what we mean.





Send this coupon for literature or ask your dealer for a demonstration.

Name

Address

07/07/04

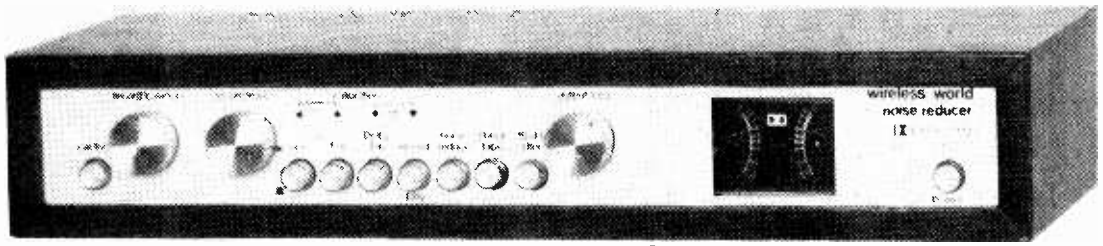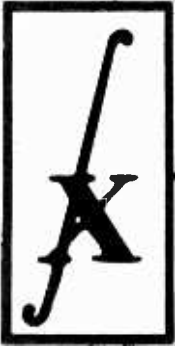Rola Celestion Ltd., Ditton Works, Foxhall Road, Ipswich, Suffolk IP3 8JP.  
Telephone: Ipswich (0473) 73131. Cobles Voicecoil, Ipswich Telex: 98365.



# Wireless World Dolby<sup>TM</sup> noise reducer

Trademark of Dolby Laboratories Inc.

We are proud to announce the latest addition to our range of matching high fidelity units.

### Featuring

- switching for both encoding (low-level h.f. compression) and decoding
- a switchable f.m. stereo multiplex and bias filter
- provision for decoding Dolby f.m. radio transmissions (as in USA)
- no equipment needed for alignment
- suitability for both open-reel and cassette tape machines
- check tape switch for encoded monitoring in three-head machines

### The kit includes

- complete set of components for stereo processor
- regulated power supply components
- board-mounted DIN sockets and push-button switches
- fibreglass board designed for minimum wiring
- solid mahogany cabinet, chassis, twin meters, front panel, knobs, mounting screws and nuts

**Typical performance**

Noise reduction better than 9dB weighted

Clipping level 16.5dB above Dolby level (measured at 1% third harmonic content)

Harmonic distortion 0.1% at Dolby level typically 0.05% over most of band, rising to a maximum of 0.12%

Signal-to-noise ratio: 75dB (20Hz to 20kHz, signal at Dolby level) at Monitor output

Dynamic Range >90dB  
30mV sensitivity.

**PRICE: £37.90 + VAT**

Also available ready built and tested ..... **Price £52.00 + VAT**

Calibration tapes are available for open-reel use and for cassette (specify which) ..... **Price £2.00 + VAT \***

Single channel plug-in Dolby<sup>TM</sup> PROCESSOR BOARDS (92 x 87mm) with gold plated contacts are available with all components ..... **Price £7.20 + VAT**

Single channel board with selected feet ..... **Price £2.20 + VAT**

Gold Plated edge connector ..... **Price £1.40 + VAT \***

Selected FETs **60p** each + VAT, **100p** + VAT for two, **£1.90** + VAT for four

Please add VAT 12½% unless marked thus\*, then 8% applies  
We guarantee full after-sales technical and servicing facilities on all our kits, have you checked that these services are available from other suppliers?



# INTEGREX LTD.


Please send SAE for complete lists and specifications  
**Portwood Industrial Estate, Church Gresley,  
Burton-on-Trent, Staffs DE11 9PT  
Burton-on-Trent (0283) 215432 Telex 377106**

# INTEGREX

## S-2020TA STEREO TUNER/AMPLIFIER KIT

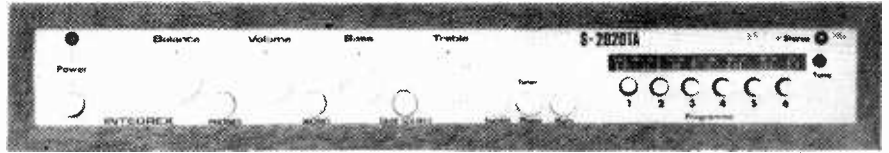**SOLID MAHOGANY CABINET**

*A high-quality push-button FM Varicap Stereo Tuner combined with a 24W r.m.s. per channel Stereo Amplifier.*




**Brief Spec.** Amplifier Low field Toroidal transformer, Mag. input, Tape In/Out facility (for noise reduction unit, etc.), THD less than 0.1% at 20W into 8 ohms. Power on/off FET transient protection. All sockets, fuses, etc., are PC mounted for ease of assembly. Tuner section uses 3302 FET module requiring no RF alignment, ceramic IF, INTERSTATION MUTE, and phase-locked IC stereo decoder. LED tuning and stereo indicators. Tuning range 88–104MHz. 30dB mono S/N @ 1.2µV. THD 0.3%. Pre-decoder 'birdy' filter.

**PRICE: £53.95 + VAT**
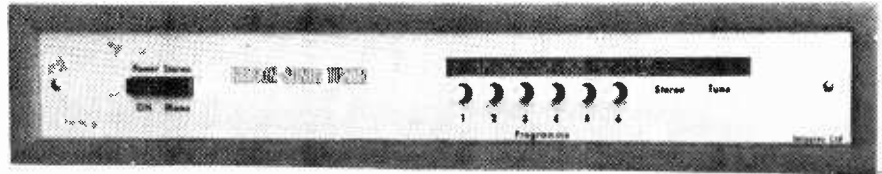
## NELSON-JONES STEREO FM TUNER KIT

*A very high performance tuner with dual gate MOSFET RF and Mixer front end, triple gang varicap tuning, and dual ceramic filter/dual IC IF amp.*



**Brief Spec.** Tuning range 88–104MHz. 20dB mono quieting @ 0.75µV. Image rejection — 70dB. IF rejection — 85dB. THD typically 0.4%. IC stabilized PSU and LED tuning indicators. Push-button tuning and AFC unit. Choice of either mono or stereo with a choice of stereo decoders.

*Compare this spec. with tuners costing twice the price.*

**Mono £29.15 + VAT**

**With ICPL Decoder £33.42 + VAT**

**With Portus-Haywood Decoder  
£35.95 + VAT**

## STEREO MODULE TUNER KIT

*A low-cost Stereo Tuner based on the 3302 FET RF module requiring no alignment. The IF comprises a ceramic filter and high-performance IC Variable INTERSTATION MUTE. PLL stereo decoder IC. Pre-decoder 'birdy' filter*

**PRICE: Mono £26.85 + VAT**

**Stereo £29.95 + VAT**

## S-2020A AMPLIFIER KIT

*Developed in our laboratories from the highly successful "TEXAN" design. PC mounting potentiometers, switches, sockets and fuses are used for ease of assembly and to minimize wiring*

*Power 'on/off' FET transient protection.*



**Typ Spec.** 24+24W r.m.s. into 8-ohm load at less than 0.1% THD. Mag. PU input S/N 60dB. Radio input S/N 72dB. Headphone output. Tape In/Out facility (for noise reduction unit, etc.). Toroidal mains transformer.

**PRICE: £31.95 + VAT**


**ALL THE ABOVE KITS ARE SUPPLIED COMPLETE WITH ALL METALWORK, SOCKETS, FUSES, NUTS AND BOLTS, KNOBS, FRONT PANELS, SOLID MAHOGANY CABINETS AND COMPREHENSIVE INSTRUCTIONS**

<b>BASIC NELSON-JONES TUNER KIT</b>	<b>£14.28 + VAT</b>	<b>PHASE-LOCKED IC DECODER KIT</b>	<b>£4.47 + VAT</b>
<b>BASIC MODULE TUNER KIT (stereo)</b>	<b>£16.75 + VAT</b>	<b>PUSH-BUTTON UNIT</b>	<b>£4.50 + VAT</b>
<b>PORTUS-HAYWOOD PHASE-LOCKED STEREO DECODER KIT</b>			<b>£8.00 + VAT</b>


# HART ELECTRONICS

The Only Firm for Quality Audio Kits
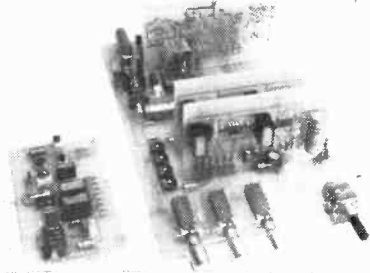
## J. L. Linsley-Hood High Quality Cassette Recorder



Master Board with one Replay Amp removed

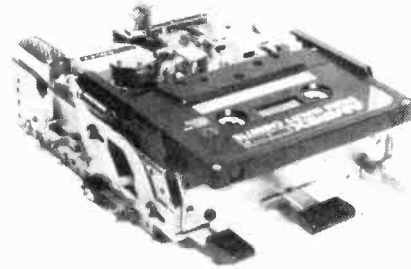

As these circuits in recent issues of "Wireless World" are capable of such an excellent performance we feel that it is not sensible to sacrifice this potential by designing a kit down to a price. We have therefore spent a little more on professional hardware allowing us to design a very advanced modular system. This enables a more satisfactory electrical layout to be achieved, particularly around the very critical input areas of the replay preamps. These are totally stable with this layout and require no extra stabilising components. Many other advantages also come from this system which has separate record and replay amps for each channel plugging in to a master board with gold plated sockets. The most obvious is the reduction of crosstalk and interaction which could cause trouble on a single plane board, with our modular system the layout is compact but there is no component crowding. Testing is very easy with separate identical modules and building with the aid of our component-by-component instructions is childishly simple, but the finished result is a unit designed not to normal domestic standards but to the best professional practice.

**ALL PARTS ARE POST FREE**

Please send 9 x 4 SAE for lists giving fuller details and Price breakdowns.  
A suitable Metalwork and Front Plate is now available

### Penylan Mill, Oswestry, Salop

Personal callers are always welcome, but please note we are closed all day Saturday

**LENCO CRV CASSETTE MECHANISM**

High Quality, robust cassette transport for Linsley Hood Recorder. Features fast forward, fast rewind, record, pause and automatic cassette ejection facilities. Fitted with Record/Play and Erase Heads and supplied complete with Data and extra cassette ejection spring for above horizontal use. Ex-stock £19.10 + £2.38 VAT

- 71x Complete set of parts for Master Board, includes Bias oscillator, Relay, Controls, etc. £9.83 + £1.23 VAT.
- 72x Parts for Motor Speed and Solenoid Control for Lenco CRV Deck. £3.52 + 44p VAT.
- 73x Complete set of parts for stereo Replay Amps and VU Meter Drive. £8.12 + £1.02 VAT.
- 74x Complete set for Stereo Record Amps. £6.74 + 84p VAT.
- 75x Complete set of parts for Stabilised Power Supply including special Low Hum field Mains Transformer. This unit is a separate 3.5" x 5" PCB designed so that the motor control board fits above it to save space. £8.79 + £1.10 VAT.
- 700M. VU Meters Individual high quality meters with excellent ballistics and built-in illumination. £8.48 + £1.06 VAT PER PAIR.

## The Finest —

## KEYBOARDS

The "S.K.A." Plastic Keyboard was developed by Kimber Allen Ltd in co-operation with a Swedish company and the manufacturers state that in their opinion it is the finest moulded plastic keyboard made and is not to be confused with cheaper keyboards available.

The keys are moulded in Acrylic plastic, a material chosen for its hard wearing properties and ideal feel to the touch. They are moulded in two parts, the key face, which has to be perfect in appearance and finish, and the action, which has to be strong and carry the mechanism. The strong section of aluminium extrusion upon which they are mounted is specially designed to take all the pressures of playing. Springs, felts, and contact actuators are supplied ready-fitted.

The contact assemblies are constructed of laminated bakelite, thus giving smooth slot walls and completely free movement of the gold-clad contact wires. Types available as follows (Contact pairs normally open).


- GJ-SPCO: 24p each
- GB-2 pairs: 27p each
- GC-3 pairs: 36p each
- GE-4 pairs : 45p each
- GH-5 pairs : 57p each
- 4PS-SPCO & 3 prs: 53p ea

We also stock kits and PCBs for the P.E. Synthesiser, P.E. Joanna (electronic piano), P.E. Minisonic, and other sound synthesising and modifying projects published in Practical Electronics. Send SAE for full list (Overseas send 40p)

## PHONOSONICS

DEPT. WW74, 22 HIGH STREET  
SIDCUP, KENT DA14 6EH

## & CONTACTS

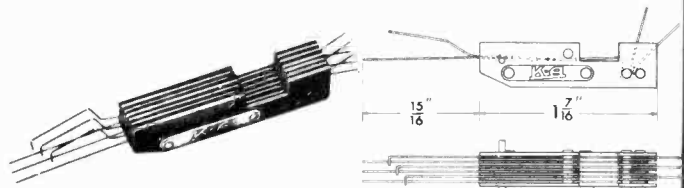


- U.K. POST & HANDLING:**
- Keyboards: £1.50 each
- Contacts:
- Orders under £15.00: 25p
- Orders over £15.00: 50p
- 37 Note C-C Keyboard : £24.85
- 49 Note C-C Keyboard : £29.50
- 61 Note C-C Keyboard : £34.50

VAT: Add 12 1/2 % to final total on all U.K. orders  
EXPORT ORDERS ARE WELCOME but please see our price list for Export Postage Rates. N.B. EIRE, CHANNEL ISLES & B.F.P.O. classify as Export.

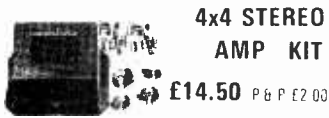MAIL ORDER AND C.V.O. ONLY — SORRY BUT NO CALLERS PLEASE  
Prices are correct at time of Press, E. & O.E. Delivery subject to availability





**4x4 STEREO AMP KIT**

£14.50 P & P £2.00

For the experienced constructor who wants to design his own stereo, kit includes all necessary components including constructors manual Plus Pair of easy to build 4 watt speakers in kit form, with teak simulate finish cabinets 12" x 9" x 5" approx.

**Sinclair I.C. 20, 20 WATTS STEREO AMPLIFIER KIT WITH PZ 20 POWER UNIT**

A build-it-yourself stereo power amplifier with latest integrated circuitry, 10W RMS per channel output, full short-circuit and overheat protection. Complete with PZ20 Power Supply

**FANTASTIC SAVING**  
OUR PRICE

**DIY SPEAKER KITS**

**EASY-TO-BUILD WITH ENCLOSURE**

Specially designed by RT-VC for cost-conscious hi-fi enthusiasts, these kits incorporate two teak-simulate enclosures, two EMI 13" x 8" (approx.) woofers, two tweeters and a pair of matching cross-overs. Easily constructed, using a few basic tools. Supplied complete with an easy-to-follow circuit diagram, and crossover components. Input 15 watts rms, 30 watts peak, each unit. Cabinet size 20" x 11" x 9 1/2" (approx.)

PER PAIR  
£25.50  
- p & p £5.50

**15-WATT KIT IN CHASSIS FORM**

When you are looking for a good speaker, why not build your own from this kit. It's the unit which we supply with the above enclosures. Size 13" x 8" (approx.) woofer (EMI), tweeter, and matching crossover. Power handling capacity 15 watts rms, 30 watts peak.

PER STEREO PAIR  
£17.00  
£3.40 P & P

**'COMPACT' FOR TOP VALUE**

How about this for incredible bookshelf value from RT-VC! A pair of high efficiency units for only £7.50 - just what you need for low-power amplifiers. These infinite baffle enclosures come to you ready mited and professionally finished. Each cabinet measures 12" x 9" x 5" (approx.) deep, and is in wood simulate Complete with two 8" (approx.) speakers for max. power handling of 7 watts.

PER PAIR  
£7.50  
- p & p £1.70


**BSR TURNTABLES**

BSR MP60 TYPE  
Single play record player (Chassis form) less cartridge  
Cartridges to suit above  
ACOS MAGNETIC STEREO  
CERAMIC STEREO  
BSR automatic record player deck (Chassis form) with cueing device and stereo ceramic head



P & P £2.00

**20 x 20 WATT STEREO AMPLIFIER**

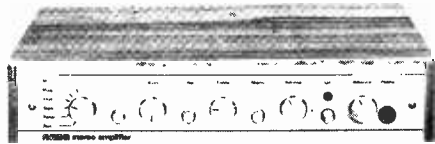

£29.90  
- p & p £2.10

Superb Viscount IV unit in teak-finished cabinet. Silver fascia with aluminum rotary controls and pushbuttons, red mains indicator and stereo jack socket. Function switch for mic, magnetic and crystal pick-ups, tape, tuner, and auxiliary. Rear panel features two mains outlets, DIN speaker and input sockets, plus fuse. 20 + 20 watts rms, 40 + 40 watts peak.

**HOW YOU CAN SAVE**

**SYSTEM 1B** For only £80, you get the 20+20 watt Viscount IV amplifier, a pair of our 12-watt-rms Duo Type 11b matched speakers; a BSR MP 60 type deck complete with magnetic cartridge, de luxe plinth and cover.

£80.00  
- p & p £8.00

Carnage surcharge to Scotland System 1B : 2.50 System 2 : 5.00

**SYSTEM 2** Comprising our 20+20 watt Viscount IV amplifier; a pair of our large Duo Type 11b matching speakers which handle 20 watts rms each, and a BSR MP 60 type deck with magnetic cartridge, de luxe plinth and cover.

£92.00  
- p & p £10.00

**SPEAKERS** Two models - Duo 11b, teak veneer, 12 watts rms, 24 watts peak, 18 1/2" x 13 1/2" x 7 1/4" approx.

£34 PER PAIR  
- p & p £6.50

Duo 111, 20 watts rms, 40 watts peak, 27" x 13" x 11 1/2" approx

£52 PER PAIR  
- p & p £7.50

**TURNTABLE** Popular BSR MP 60 type, complete with magnetic cartridge, diamond stylus, and de luxe plinth and cover.

£29.00  
- p & p £4.50



**30 x 30 WATT AMPLIFIER KIT**

Specially designed by RT-VC for the experienced constructor, this kit comes complete in every detail. Same facilities as Viscount IV amplifier. Chassis is ready punched; drilled and formed Cabinet is finished in teak veneer. Black fascia and easy-to-handle aluminium knobs. Output 30+30 watts rms, 60+60 peak.

£29.00  
+ p & p £2.10

**BSR T145 8-TRACK CARTRIDGE PLAYER MECHANISM**

Requires some attention. Complete with built in pre-amp, A.C. 240V

**SPECIAL OFFER**

£6.95  
- p & p £1.50

**TOURIST IV PUSH BUTTON CAR RADIO KIT**




**MOTOR TOP 10 AWARD**

Complete with speaker, baffle and fixing strip. The Tourist IV for the experienced constructor only. The Tourist IV has five push buttons, four medium band and one for long wave band. The tuning scale is illuminated and attractive small aluminium control knobs are used for manual tuning and volume control.

The modern style fascia has been designed to blend with most car interiors and the finished radio will slot into a standard car radio aperture. Size approx 7" x 2" x 4". Power Supply Nominal 12 volts positive or negative earth (altered internally) Power Output 4 watts into 4 ohms

£10.50  
- p & p £1.50

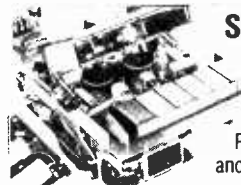

**STEREO CASSETTE DECK KIT**

Again, this kit is specially designed for the experienced constructor - for mounting into his own cabinet. Features include solenoid-assisted AUTO-STGP, 3-digit counter, record/replay PC board, mains transformer and input and output controls. AC BIAS AND ERASE.

£32.50  
+ p & p £1.50

**DELUXE ACCESSORY KIT** Comprises of a matched pair of dynamic mics. and two replacement slider level controls. This item post **POST FREE** when purchased with Cassette Deck kit

£3.95  
- p & p £1.00

**35-WATT DISCO AMP**

Here's the mono unit you need to start off with. Gives you a good solid 35 watts rms, 70 watts peak output. Big features include two disc inputs, both for ceramic cartridges, tape input and microphone input. Level mixing controls fitted with integral push-pull switches. Independent bass and treble controls and master volume.

£27.50  
- p & p £1.50



**PORTABLE DISCO CONSOLE with built-in pre-amplifiers**

Here's the big-value portable disco console from RT-VC! It features a pair of BSR MP 60 type auto-return, single-play professional series record decks. Plus all the controls and features you need to give fabulous disco performances. Simply connects into your existing slave or external amplifier.

£64.00  
+ p & p £6.50



**70 & 100 WATT DISCO AMPS**

Brilliantly styled for easy disco performance! Sloping fascia, so that you can use the controls without fuss or bother. Brushed aluminium fascia and rotary controls. Five smooth-acting, vertically mounted slide controls - master volume, tape level, mic level, deck level. PLUS INTER-DECK FADER for perfect graduated change from record deck No. 1 to No. 2, or vice versa. Pre-fade level control (PFL) lets YOU hear next disc before fading it in. VU meter monitors output level 70 watts rms, 140 watts peak output. All the big features as on the 70-watt disco amplifier, but with a massive 100 watts rms, 200 watts peak output power.

**70 WATT**  
£49.00  
- p & p £3.00

**100 WATT**  
£65.00  
- p & p £4

**ALL PRICES INC. VAT. AT 12 1/2%**  
GOODS NOT DESPATCHED OUTSIDE UK  
All items subject to availability. Price correct at 1st February 1977, and subject to change without notice.

We are unable to show all our products, so please Send stamped addressed envelope for our fully descriptive catalogue and any further information



**21E HIGH STREET, ACTON, LONDON W3 6NG**  
**323 EDGWARE ROAD, LONDON, W2**  
Personal Shoppers EDGWARE ROAD 9am - 5.30pm, Half day Thurs  
ACTON: Mail Order only No Callers

Minimum order on Access and BarclayCards £15  
**DO NOT SEND CARD**  
Just write your order giving your credit card number

# RST VALVE MAIL ORDER CO.

Climax House, 159 Fallsbrook Rd., Streatham  
London SW16 6ED  
Tel: 01-677 2424 Telex: 946 708

VALVES		INDUSTRIAL VALVES		TRANSISTORS & ICs		TUBES	
EAH81	0.35	EY86	0.50	OC71	0.25	2N1304	0.45
EAH83	0.50	EZ40	0.60	OC72	0.45	2N1305	0.45
EAH84	0.50	EZ41	0.75	OC73	0.50	2N1306	0.50
AZ31	1.00	EZ42	0.50	OC74	0.75	2N1307	0.50
CLB1	0.70	EZ43	0.50	OC75	0.75	2N1308	0.50
CLB2	1.40	EZ44	0.50	OC76	0.75	2N1309	0.50
CLB3	1.50	EZ45	0.50	OC77	0.75	2N1310	0.50
CL33	1.50	EZ46	0.50	OC78	0.75	2N1311	0.50
CY31	1.00	EZ47	0.50	OC79	0.75	2N1312	0.50
DAF31	0.40	EZ48	0.50	OC80	0.75	2N1313	0.50
DAF36	0.60	EZ49	0.50	OC81	0.75	2N1314	0.50
DCC90	1.35	EZ50	0.50	OC82	0.75	2N1315	0.50
DF91	0.40	EZ51	0.50	OC83	0.75	2N1316	0.50
DF96	0.60	EZ52	0.50	OC84	0.75	2N1317	0.50
DK91	0.50	EZ53	0.50	OC85	0.75	2N1318	0.50
DK92	1.00	EZ54	0.50	OC86	0.75	2N1319	0.50
DL92	0.50	EZ55	0.50	OC87	0.75	2N1320	0.50
DL94	0.65	EZ56	0.50	OC88	0.75	2N1321	0.50
DL96	0.55	EZ57	0.50	OC89	0.75	2N1322	0.50
DM70	0.70	EZ58	0.50	OC90	0.75	2N1323	0.50
DY96/7	0.45	EZ59	0.50	OC91	0.75	2N1324	0.50
DY902	0.47	EZ60	0.50	OC92	0.75	2N1325	0.50
EABC90	0.38	EZ61	0.50	OC93	0.75	2N1326	0.50
EAF42	0.70	EZ62	0.50	OC94	0.75	2N1327	0.50
EAF801	0.75	EZ63	0.50	OC95	0.75	2N1328	0.50
EBC33	1.00	EZ64	0.50	OC96	0.75	2N1329	0.50
EBC41	0.75	EZ65	0.50	OC97	0.75	2N1330	0.50
EBC41	0.40	EZ66	0.50	OC98	0.75	2N1331	0.50
EBC41	0.40	EZ67	0.50	OC99	0.75	2N1332	0.50
EBC41	0.40	EZ68	0.50	OC100	0.75	2N1333	0.50
EBC41	0.40	EZ183	0.50	OC215	0.75	2N1448	0.50



Zambia Gibraltar Chile Spain United Arab Emirates Singapore New Guinea Israel


Falkland Islands  
Portugal  
Guyana  
India  
Greece  
Jordan  
United States of America  
Yugoslavia  
Ascension Island  
Malaya

# POWERTRAN ELECTRONICS

INCORPORATING

# AMBIENTACOUSTICS

## HI-FI NEWS 75W/CHANNEL AMPLIFIER

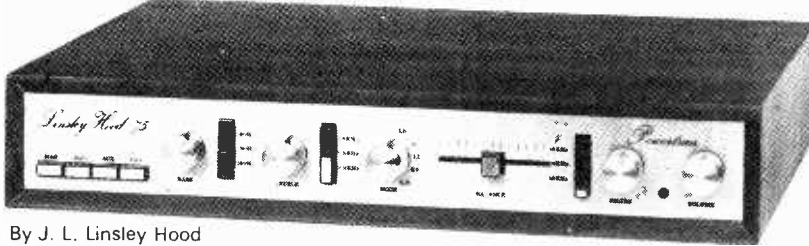

By J. L. Linsley Hood

In Hi-Fi News there was published by Mr. Linsley-Hood a series of four articles (November, 1972-February, 1973) and a subsequent follow-up article (April, 1974) on a design for an amplifier of exceptional performance which has as its principal feature an ability to supply from a direct coupled fully protected output stage, power in excess of 75 watts whilst maintaining distortion at less than 0.01% even at very low power levels. The power amplifier is complemented by a pre-amplifier based on a discrete component operational amplifier referred to as the Linciac which is employed in the two most critical points of the system, namely the equalization stage and tone control stage, positions where most conventional designs run out of gain at the extremes of the frequency spectrum. Unusual features of the design are the variable transition frequencies of the tone controls and the variable slope of the scratch filter. There is a choice of four inputs, two equalized and two linear, each having independently adjustable signal level. The attractive slimline unit pictured has been made practical by highly compact PCBs and a specially designed Toroidal transformer

- | Pack                                                                                                                 | Price  |
|----------------------------------------------------------------------------------------------------------------------|--------|
| 1. Fibreglass printed-circuit board for power amp                                                                    | £1.15  |
| 2. Set of resistors, capacitors, pre-sets for power amp                                                              | £2.15  |
| 3. Set of semiconductor for power amp                                                                                | £6.50  |
| 4. Pair of 2 drilled, finned heat sinks                                                                              | £1.10  |
| 5. Fibreglass printed-circuit board for pre-amp                                                                      | £1.75  |
| 6. Set of low noise resistors, capacitors, pre-sets for pre-amp                                                      | £3.40  |
| 7. Set of low noise, high gain semiconductors for pre-amp                                                            | £2.40  |
| 8. Set of potentiometers (including mains switch)                                                                    | £3.15  |
| 9. Set of 4 push-button switches, rotary mode switch                                                                 | £4.50  |
| 10. Toroidal transformer complete with magnetic screen/housing primary: 0-117V-234V; secondaries: 33-0-33V, 25-0-25V | £10.95 |

- | Pack                                                                                                                   | Price |
|------------------------------------------------------------------------------------------------------------------------|-------|
| 11. Fibreglass printed-circuit board for power supply                                                                  | £0.85 |
| 12. Set of resistors, capacitors, secondary fuses, semi-conductors for power supply                                    | £4.60 |
| 13. Set of miscellaneous parts including DIN skts, mains input skt, fuse holder, inter-connecting cable, control knobs | £5.35 |
| 14. Set of metalwork parts including silk screen printed fascia panel and all brackets, fixing parts, etc.             | £7.30 |
| 15. Handbook                                                                                                           | £0.30 |
| 16. Teak cabinet 18.3" x 12.7" x 3.1"                                                                                  | £9.85 |
- 2 each of packs 1-7 inclusive are required for complete stereo system. Total cost of individually purchased packs ..... £83.75

Designed in response to demand for a tuner to complement the world-wide acclaimed Linsley Hood 75W Amplifier, this kit provides the perfect match. The Wireless World (Skingley and Thompson - April, May 1974) published original circuit has been developed further for inclusion into this outstanding slimline unit and features a pre-aligned front end module, excellent a.m. rejection and temperature compensated varicap tuning, which may be controlled either continuously or by push button pre-selection. Frequencies are indicated by a frequency meter and sliding LED indicators, attached to each channel selector pre-set. The PLL stereo decoder incorporates active filters for "birdy" suppression and power is supplied via a toroidal transformer and integrated regulator. For long term stability metal oxide resistors are used throughout

- | Pack                                                                                                                                                        | Price |
|-------------------------------------------------------------------------------------------------------------------------------------------------------------|-------|
| 1. Fibreglass printed board for front end IF strip, demodulator, AFC and mute circuits                                                                      | £2.15 |
| 2. Set of metal oxide resistors, thermistor, capacitors, ceramic preset for mounting on pack 1                                                              | £4.50 |
| 3. Set of transistors, diodes, LED, integrated circuits for mounting on pack 1                                                                              | £5.25 |
| 4. Pre-aligned front end module, coil assembly, three section ceramic filter                                                                                | £8.50 |
| 5. Fibreglass printed circuit board for stereo decoder                                                                                                      | £1.10 |
| 6. Set of metal oxide resistors, capacitors, ceramic preset for decoder                                                                                     | £2.60 |
| 7. Set of transistors LED, integrated circuit for decoder                                                                                                   | £2.90 |
| 8. Set of components for channel selector switch module including fibreglass printed circuit board, push-button switches, knobs, LEDs, preset adjuster etc. | £8.80 |
| 9. Function switch, 10 turn tuning potentiometer, knobs                                                                                                     | £5.30 |
| 10. Frequency meter, meter drive components, fibreglass printed circuit board                                                                               | £9.45 |

- | Pack                                                                                                                                                                   | Price |
|------------------------------------------------------------------------------------------------------------------------------------------------------------------------|-------|
| 11. Toroidal transformer with electrostatic screen, Primary: 0-117V-234V                                                                                               | £4.45 |
| 12. Set of capacitors, rectifiers, voltage regulator for power supply                                                                                                  | £2.95 |
| 13. Set of miscellaneous parts, including sockets, fuse holder, fuses, inter-connecting wire, etc.                                                                     | £1.50 |
| 14. Set of metal work parts including silk screen printed fascia panel, acrylic silk screen printed tuning indicator panel insert, internal screen, fixing parts, etc. | £7.50 |
| 15. Construction notes (free with complete kit)                                                                                                                        | £0.25 |
| 16. Teak cabinet 18.3" x 12.7" x 3.1"                                                                                                                                  | £9.85 |
- One each of packs 1-16 inclusive are required for complete stereo FM tuner. Total cost of individually purchased packs ..... £76.85

Published in Wireless World (May, June, August 1976) by Mr. Linsley-Hood, this design, although straightforward and relatively low cost nevertheless provides a very high standard of performance. To permit circuit optimization separate record and replay amplifiers are used, the latter using a discrete component front-end designed such that the noise level is below that of the tape background. Push button switches are used to provide a choice of equalization time constants, a choice of bias levels and also an option of using an additional pre-amplifier for microphone use. The mechanism used is the Goldring-Lenco CRV, a unit distinguished in its robustness and ease of operation. Speed control and automatic cassette ejection are both implemented by electronic circuitry. This unit which is powered by a toroidal transformer and uses metal oxide resistors throughout offers an excellent match for the Wireless World Tuner and the Linsley-Hood 75 Watt Amplifier

### PRICE STABILITY


Order with confidence! Irrespective of any price changes we will honour all prices in this advertisement for two months from issue date provided that this advertisement is quoted with your order. E&OE VAT rate changes excluded. All components are brand new first grade full specification devices. All resistors (except where stated) are low noise carbon film types. All printed circuit boards are fibre-glass, drilled, roller tinned and supplied with circuit diagrams and construction layouts.

FREE CATALOGUE U.K. customers just send name and address - Overseas customers, please send 5 International Reply Coupons and you will receive your catalogue by return AIRMAIL

EXPORT ORDERS No VAT charged. Postage charged at actual cost plus 50p documentation and handling. Please make payment by Bank Draft, Postal Order, International Money Order in sterling. SECURICOR DELIVERY For this optional service (U.K. Mainland only) add £2.50 (VAT INC.) per kit. U.K. ORDERS: Subject to 12 1/2 % \* surcharge for VAT. Carriage free. MAIL ORDER ONLY (\*or at current rate if changed)


**FREE** TEAK CASE WITH FULL KITS  
KIT PRICE ONLY **£73.90**

## WIRELESS WORLD FM TUNER

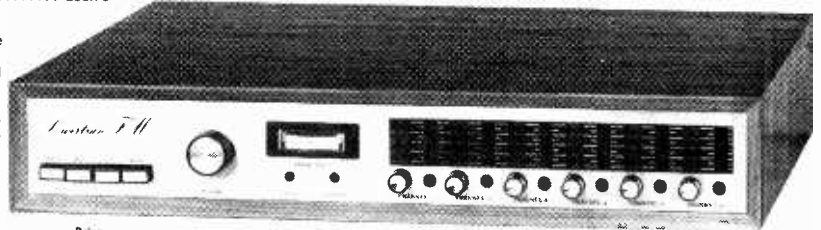

**FREE** TEAK CASE WITH FULL KITS  
KIT PRICE ONLY **£66.75**

## NEW KIT! LINSLEY-HOOD CASSETTE DECK

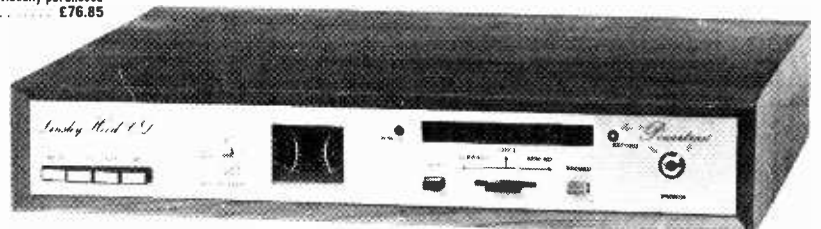

- | Pack                                                                                       | Price  |
|--------------------------------------------------------------------------------------------|--------|
| 1. Stereo PCB (accommodates 2 rep. amps, 2 rec. amps, 2 motor amps, bias/erase osc. relay) | £3.35  |
| 2. Stereo set of capacitors, M.D. resistors, potentiometers for above                      | £9.80  |
| 3. Stereo set of semiconductors for above                                                  | £8.90  |
| 4. Miniature relay with socket                                                             | £2.45  |
| 5. PCB, all components for solenoid, speed control circuits                                | £3.20  |
| 6. Goldring Lenco mechanism as specified                                                   | £21.95 |
| 7. Function switch, knobs                                                                  | £1.60  |
| 8. Dual VU meter with illuminating lamp                                                    | £7.20  |
| 9. Toroidal transformer with E.S. screen prim, 0-117V, 234V, Sec. 15V                      | £4.45  |

- | Pack                                                                                              | Price |
|---------------------------------------------------------------------------------------------------|-------|
| 10. Set of capacitors, rectifiers, i.c. voltage regulator for power supply (Powertran design)     | £2.80 |
| 11. Set of miscellaneous parts, including sockets, fuse holder, fuses, interconnecting wire, etc. | £2.50 |
| 12. Set of metalwork including silk screened fascia panel, internal screen, fixing parts, etc.    | £7.10 |
| 13. Construction notes                                                                            | £0.25 |
| 14. Teak cabinet 18.3" x 12.7" x 3.1"                                                             | £9.85 |
- One each of packs 1-14 inclusive are required for complete stereo cassette deck. Total cost of individually purchased packs ..... £85.40

**SPECIAL PRICE FOR COMPLETE KITS £81.35**

Further details of above given in our FREE CATALOGUE

PLEASE NOTE ALL PRICES VAT EXCLUSIVE - DEPT. WW4

# POWERTRAN ELECTRONICS


PORTWAY INDUSTRIAL ESTATE  
ANDOVER, HANTS SP10 3NN

Indonesia Brazil Switzerland Canada Saudi Arabia New Zealand Norway Iceland Sweden



Guernsey Cyprus Belgium Uganda Brunei Trinidad South West Africa Italy Java Grenada

# AUDIO KIT SUPPLIERS TO THE WORLD

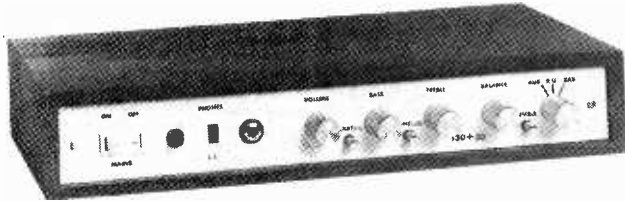

## T20+20 and our new T30+30 20W, 30W AMPLIFIERS

Designed by Texas engineers and described in Practical Wireless the Texan was an immediate success. Now developed further in our laboratories to include a Toroidal transformer and additional improvements the slimline T20 + 20 delivers 20W per channel of true Hi-Fi at exceptionally low cost. The design is based on a single F/Glass PCB and features all the normal facilities found on quality hi-fi amplifiers, including scratch and rumble filters, adaptable input selector and head phones socket. In a follow up article in Practical Wireless further modifications were suggested and these have been incorporated into the T30 + 30. These include RF interference filters and a tape monitor facility. Power output of this new model is 30W per channel.

Pack	T20	T30	Pack	T20	T30
1. Set of low noise resistors	1.40	1.50	8. Toroidal transformer - 240V prim.		
2. Set of small capacitors	2.20	2.80	9. s.s. screen	4.95	6.80
3. Set of power supply capacitors	1.90	2.30	10. Fibreglass PCB	3.20	3.60
4. Set of miscellaneous parts	3.20	3.20	11. Set of metalwork, fixing parts	4.20	4.80
5. Set of slide, main, P.B. switches	1.20	1.20	12. Set of cables, mains lead	0.40	0.40
6. Set of pots, selector switch	2.80	2.80	13. Handbook [free with complete kit]	0.25	0.25
7. Set of semiconductors, ICs, scts.	7.25	7.75	14. Teak cabinet 15.4" x 6.7" x 2.8"	4.50	4.50

## SPECIAL PRICES

FOR COMPLETE KITS!

T20+20  
KIT PRICE only **£31.10**


T30+30  
KIT PRICE only **£35.90**

## 2 NEW TUNERS!

### WW SFMT II

Following the success of our Wireless World FM Tuner kit we are now pleased to introduce our new, cost reduced model designed to complement the T20 and T30 amplifiers. The frequency meter of the more advanced model has been omitted and the mechanics simplified, however the circuitry is identical and this new kit offers most exceptional value for money. Facilities included are switchable afc, adjustable switchable muting, channel selection by slider or readily adjustable pre-set push-button controls and LED tuning indication. Individual pack prices in our free list.


KIT PRICE  
**£45.50**

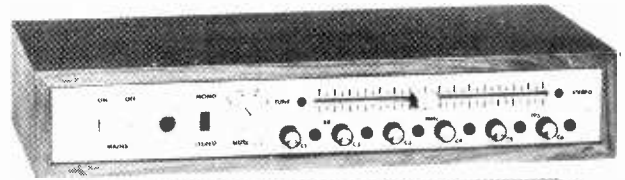

### POWERTRAN SFMT

This easy to construct tuner using our own circuit design includes a pre-aligned front end module, PLL stereo decoder, adjustable switchable muting, switchable afc and push-button channel selection. As with all our kits, all components down to the last nut and bolt are supplied together with full constructional details.

KIT PRICE  
**£32.60**

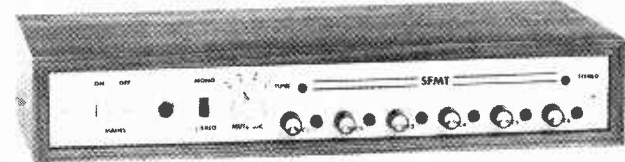

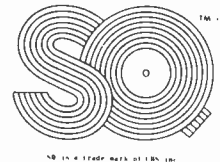
## CONVERT NOW TO QUADRAPHONICS!



SQM1 - 30 KIT PRICE **£37.15**

With 100s of titles now available no longer is there any problem over suitable software. No problems with hardware either. Our new unit the SQM1-30 simply plugs into the tape monitor socket of your existing amplifier and drives two additional speakers at 30W per channel. A full complement of controls including volume, bass, treble and balance are provided as are comprehensive switching facilities enabling the unit to be used for either front or rear channels by passing the decoder for stereo-only use and exchanging left and right channels. The SQ matrix decoder is based upon a single integrated circuit and was designed by CBS whilst the power and tone control sections are identical to those used in our T30 + 30 amplifier which the SQM1-30 matches perfectly. Kit price includes CBS licence fee.



**Special offer to T20 + 20 and Texan owners!**  
Owners of T20 + 20 and Texan amplifiers which have no tape monitor outlet, purchasing an SQM1-30 will be supplied on request, a free conversion kit to fit a tape monitoring facility to the existing amplifier. This makes simple the connection to the highly adaptable SQM1-30 quadraphonic decoder/rear channel amplifier.

**Wireless World Amplifier Designs.** Full kits are not available for these projects but component packs and PCBs are stocked for the highly regarded Bailey and 20W class AB Lindsey Hood designs, together with an efficient regulated power supply of our own design. Suitable for driving these amplifiers is the Bailey Burrows pre-amplifier and our circuit board, for the stereo version of it features 6 inputs, scratch and rumble filters and wide range tone controls which may be either rotary or slider operating. For those intending to get the best out of their speakers we also offer an active filter system described by D.C. Read which splits the output of each channel from the pre-amplifier into three channels each of which is fed to the appropriate speaker by its own power amplifier. The Read/Texas 20W, or any of our other kits are suitable for these. For tape systems a set of three PCBs have been prepared for the integrated circuit based high performance stereo Stuart design. Details of component packs are in our free list.

30W Bailey Amplifier	
BAIL Pk 1 F/Glass PCB	£1.00
BAIL Pk 2 Resistors, Capacitors, Potentiometer set	£2.35
BAIL Pk 3 Semiconductor set	£4.70
20W Lindsey Hood Class AB	
LHAB Pk 1 F/Glass PCB	£1.05
LHAB Pk 2 Resistor, Capacitor, Potentiometer set	£3.20
LHAB Pk 3 Semiconductor set	£3.35
Regulator Power Supply	
60VS Pk 1 F/Glass PCB	£0.85
60VS Pk 2 Resistor, Capacitor set	£2.20
60VS Pk 3 Semiconductor set	£3.10
60VS Pk 6A Toroidal transformer (for use with Bailey)	£8.80
60VS Pk 6B Toroidal transformer (for use with 20W LH)	£7.25
Bailey Burrows Stereo Pre-Amp	
BBPA Pk 1 F/Glass PCB	£2.80
BBPA Pk 2 Resistor, capacitor semiconductor set	£6.70
BBPA Pk 3R Rotary Potentiometer set	£2.85
BBPA Pk 3S Slider Potentiometer set with knobs	£3.10
*Active Filter	
FILT Pk 1 F/Glass PCB	£1.40
FILT Pk 2 Resistor, Capacitor set (metal oxide 2%, polystyrene 2 1/2%)	£4.20
FILT Pk 3 Semiconductor set	£2.25
2 off Pks 1, 2, 3 reqd for stereo active filter system	
Read/Texas 20W Amp	
READ Pk 1 F/Glass PCB	£1.00
READ Pk 2 Resistor, Capacitor set	£1.20
READ Pk 3 Semiconductor set	£2.30
6 off pks 1, 2, 3 required for stereo active filter system	£2.30
Stuart Tape Recorder	
TRRP Pk 1 Replay Amp F/Glass PCB	£1.30
TRRC Pk 2 Record Amp F/Glass PCB	£1.70
TROS Pk 1 Bias/Erase/Stabilizer F/Glass PCB	£1.20

Further details of above and additional packs given in our FREE LIST

## SQ QUADRAPHONIC DECODERS

Feed 2 channels (200-1000mV as obtainable from most pre-amplifiers or amplifier tape monitor outlets) into any one of our 3 decoders and take 4 channels out with no overall signal level reduction. On the logic enhanced decoders Volume, Front-Back, LF-RF balance, LB-HB balance and Dimension controls can all be implemented by simple single gang potentiometers. These state-of-the-art circuits used under licence from CBS are offered in kits of superior quality with close tolerance capacitors, metal oxide resistors and fibre-glass PCBs designed for edge connector insertion. All kit prices include CBS licence fee.

M1 Basic matrix decoder with fixed 10-40 blend	All components, PCB	£5.90
L1 Full logic controlled decoder with wave matching and front back logic for enhanced channel separation	All components PCB	£17.20
L2A More advanced full logic decoder with "variable blend" for increased front back separation	All components, PCB	£22.60
L3A Decoder similar to L2A but with discreet component front end with high precision 6-pole phase shift networks for increased frequency response	All components (carbon film resistors), PCB	£25.90
Also available with M.O. resistors, cermet pre-set - add		£4.20

## SEMICONDUCTORS as used in our range of quality audio equipment.

2N699	£0.20	40361	£0.40	BD530	£0.55	MJE521	£0.60	TIP29C	£0.55
2N1613	£0.20	40362	£0.45	BDY56	£1.60	MPSA8	£0.25	TIP30C	£0.60
2N2926G	£0.10	BC107	£0.10	BF257	£0.40	MPSA12	£0.35	TIP41A	£0.70
2N3055	£0.45	BC108	£0.10	BF259	£0.47	MPSA14	£0.30	TIP42A	£0.80
2N3442	£1.20	BC109	£0.10	BFR39	£0.30	MPSA55	£0.25	TIP41B	£0.75
2N3711	£0.09	BC109C	£0.12	BFR79	£0.30	MPSA65	£0.35	TIP42B	£0.90
2N3904	£0.17	BC125	£0.15	BFY51	£0.20	MPSA66	£0.40	1N914	£0.07
2N3906	£0.20	BC126	£0.15	BFY52	£0.20	MPSU05	£0.50	1N916	£0.07
2N4062	£0.11	BC182	£0.10	CA3046	£0.70	SBA750A	£1.90	1S920	£0.10
2N4302	£0.60	BC212	£0.12	LP1186	£6.50	SL301	£1.30		
2N5087	£0.25	BC182L	£0.10	MC1310	£2.20	SL3045	£1.20	FILTERS	
2N5210	£0.25	BC184L	£0.11	MC1351	£1.05	SN72741P	£0.40	FM4	£1.00
2N5457	£0.45	BC212L	£0.12	MC1741CG	£0.65	SN72748P	£0.40	SF110 /MA	£1.50
2N5459	£0.45	BC214L	£0.14	MFC111U	£0.95	TIL209	£0.20		
2N5461	£0.50	BCY72	£0.13	MJ381	£1.20	TIP29A	£0.40		
2N5830	£0.35	BD529	£0.55	MJ491	£1.45	TIP30A	£0.45		

## EXPORT NO PROBLEM


Our Export Department will be pleased to advise on postal costs to any country in the world. Some of the countries to which we sent kits in 1976 are shown surrounding this advertisement.

Tunisia Germany Nauru Hong Kong Australia Eire Gambia Denmark France Muscat & Oman



RETURN OF POST MAIL ORDER SERVICE


**BSR HI-FI AUTOCHANGER**  
**STEREO AND MONO £11.95** Post 75p  
 Plays 12", 10" or 7" records. Auto or Manual. A high quality unit backed by BSR reliability with 12 months guarantee. A.C. 200/250V. Size 13 1/2 x 11 1/4 x 13 speeds. Above motor board 3 3/4 in. Below motor board 2 1/2 in. with STEREO and MONO CARTRIDGE B.S.R. SINGLE PLAYER similar to above with stereo cartridge and cueing device. Large turntable £13.50 B.S.R. P128 with magnetic cartridge. Balanced arm cueing device £23.50

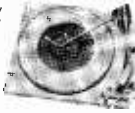

**PORTABLE PLAYER CABINET**  
 Modern design. Remixe covered. Vynair front grille. Chrome fittings. Size 17 x 15 x 8 in. approx. £4.50 Post 75p  
 \*Motor board cut for BSR or Garrard deck

**HEAVY METAL PLINTHS** £6.50 Post £1 50  
 With P.V.C. Cover. Cut out for most BSR or Garrard decks. Silver grey finish. Model "A" Size 12 1/2 x 14 3/4 x 7 1/2 in. Model "B" Size 16 x 13 3/4 x 7 in. £7.50. Extra large plinth & cover. Teak wood base. Size 20" x 17 1/2" x 9" £19.50. Callers only.

**COMPLETE STEREO SYSTEM**  
 Two full size loudspeakers 13 3/4 x 10 x 3 3/4 in. Player unit clips to loudspeakers making it extremely compact. Overall size only 13 3/4 x 10 x 8 1/2 in. 3 watts per channel. plays all records 33 r.p.m., 45 r.p.m. Separate volume and tone controls Attractive Teak finish 240V a.c. mains £22.50  
 FEW ONLY £1 carriage



**SPECIAL OFFER!**  
**SMITH'S CLOCKWORK 15 AMP TIME SWITCH** £2.95 Post 35p  
 Single pole two-way. Surface mounting with fixing screws. Will replace existing wall switch to give light for return home, garage, automatic anti-burglar lights, etc. Variable knob. Turn on or off at full or intermediate settings. Brand new and fully guaranteed. 0-6 hour version—£3.30



**TEAKWOOD LOUDSPEAKER GRILLES** will easily fit to baffle board. Size 10 1/2 x 7 1/2 in—£4.5p.

**R.C.S. "MINOR" 10 watt AMPLIFIER KIT**  
 This kit is suitable for record players, guitars, tape playback, electronic instruments or small P.A. systems. Two versions available Mono. £11.25; Stereo. £18. Post 45p. Specification 10W per channel; input 100mV, size 9 1/2 x 3 x 2 in. approx S.A.E. details. Full instructions supplied. AC mains powered

**VOLUME CONTROLS**  
 5KΩ to 2MΩ. LOG or LIN. L/S 35p. D.P. 60p. STEREO L/S 85p. D.P. £1. Edge 5K. S.P. Transistor 30p.

**80 Ohm Coax 8p yd.**  
 STANDARD TYPE VHF. FRINGE LOW LOSS 15p yd. Ideal 625 and colour PLUGS 10p. SOCKETS 10p. LINE SOCKETS 18p. OUTLET BOXES 50p.

**ELAC HI-FI SPEAKER**  
**8in. TWIN CONE**  
 Dual cone plasticised roll surround. Large ceramic magnet. 50-16,000 c/s. Bass resonance 55 c/s. 8 ohm impedance. 10 watts. music power. £3.95 Post 35p



**E.M.I. 13 1/2 x 8in. SPEAKER SALE!**  
 With tweeter and crossover. 10 watt. State 3 or 8 ohm. As illustrated. £5.95 Post 45p

Ditto 15 watts. 8 or 15 ohm. £8.50 Post 65p

With tweeter and cross-over. 20 watt. Bass res. 25 c.p.s. Flux=11,000 gauss. 8 or 15 ohm. 20 to 20,000 c.p.s. £9.50 Post 75p

**Bookshelf Cabinet** £7.50 Post £1 00  
 Teak finish. For EMI 13 x 8 speakers

**THE "INSTANT" BULK TAPSE ERASER AND HEAD DEMAGNETISER.** Suitable for cassettes, and all sizes of tape reels. A.C. mains 200/250V. Leaflet S.A.E. Will also demagnetise small tools. £4.50 Post 50p



**BLANK ALUMINIUM CHASSIS.** 6 x 4—70p; 8 x 6—90p; 10 x 7—£1.15; 12 x 8—£1.35; 14 x 9—£1.50; 16 x 6—£1.45; 16 x 10—£1.70. ANGLE ALI. 6 x 3/4 x 3/4 in—15p.

**ALUMINIUM PANELS.** 6 x 4—17p; 8 x 6—24p; 14 x 3—25p; 10 x 7—35p; 12 x 8—43p; 12 x 5—30p; 16 x 6—43p; 14 x 9—52p; 12 x 12—68p; 16 x 10—75p.

**MANY ALI BOXES IN STOCK. MANY SIZES**

**ELAC 9 x 5in HI-FI SPEAKER** £3.45 Post 35p  
 TYPE 59RM  
 This famous unit now available. 10 watts. 8 ohm

**R.C.S. LOW VOLTAGE STABILISED POWER PACK KITS** £2.95 Post 45p  
 All parts and instructions with Zener diode. printed circuit rectifiers and double wound mains transformer Input 200/240V a.c. Output voltages available, 6 or 7.5 or 9 or 12V d.c. up to 100mA or less. Size 3 x 2 1/2 x 1 1/2 in. Please state voltage required.

**R.C.S. POWER PACK KIT** £3.35 Post 30p  
 12 VOLT. 750mA. Complete with printed circuit board and assembly instructions

**R.C.S. GENERAL PURPOSE TRANSISTOR PRE-AMPLIFIER — BRITISH MADE** £1.45 Post 30p  
 Ideal for Mike. Tape. P.U. Guitar, etc. Can be used with battery 9-12V or H.T. line 200-300V d.c. operation. Size 1 3/4 x 1 1/4 x 3/4 in. Response 25 c/s to 25 kc/s. 26 dB gain. For use with valve or transistor equipment. Full instructions supplied. Details S.A.E.

**ELECTRO MAGNETIC PENDULUM MECHANISM** 95p Post 30p  
 1.5V d.c. operation over 300 hours continuous on SP2 battery. fully adjustable swing and speed. Ideal displays. teaching electro magnetism or for metronome, strobe, etc.

**MAINS TRANSFORMERS** ALL POST 50p

250-0-250V 70mA. 6.5V. 2A	£3.45
250-0-250 80mA. 6.3V 3.5A. 6.3V 1A or 5V 2A	£4.60
350-0-350 80mA. 6.3V 3.5A. 6.3V 1A or 5V 2A	£5.80
300-0-300V 120mA. 6.3V 4A C.T.; 6.3V 2A	£7.00
MIDGET 220V 45mA. 6.3V 2A	£1.75
HEATED TRANS. 6.3V 1/2 amp £1; 3 amp £1.40	
GENERAL PURPOSE LOW VOLTAGE. Tapped outputs at 2 amp 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 25 and 30V £4.60.	
1 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £4.60.	
2 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £8.70.	
5 amp. 6, 8, 10, 12, 16, 18, 20, 24, 30, 36, 40, 48, 60 £11.25.	
6.06V 500mA £1.9V 1 amp. £1.12V 300mA, £1.12V 500mA, £1.12V 750mA, £1.10V, 30V, 40V, 2 amp. £2.75, 20V, 3 amp. £2.45, 40V, 2 amp. £2.95, 30V 5A and 34V 2ACT £3.45, 16V, 2 amp. £2.20, 0, 5, 8, 10, 16V. 1/2 amp. £1.95, 20V 1/2 amp. £1.75, 20V, 1 amp. £2.20, 20V 3 amp. £2.50, 20-0-20V 1 amp. £2.95, 30V 1/2 amp. £2.75; 20V, 40V, 60V or 20-0-20V, 1 amp. £3.50.	
AUTO TRANSFORMERS. 115V to 230V or 230V to 115V 150W £5; 250W £6; 400W £7; 500W £8.	
FULL WAVE BRIDGE CHARGER RECTIFIERS. 6 or 12V outputs. 1 1/2 amp 40p; 2 amp 55p; 4 amp 85p.	
CHARGER TRANSFORMERS 1 1/2 amp £2.75; 4 amp £4.60. 12V. 1 1/2A HALF WAVE Selenium Rectifier. 25p.	

**R.C.S. BOOKSHELF SPEAKERS**  
 Size 14 1/2 in. x 9 1/4 in. x 6 in. 50 to 14,000 cps. 8 watts rms. 8 or 4 ohms



**£16 pair** Post £1.30  
**KUBA-KOPENHAGEN STEREO**

**TUNER-AMPLIFIER CHASSIS AM-FM 5+5 WATT**  
 This Continental 4-band radiogram chassis uses first class quality components throughout. Features. Large fascia panel with 7 push buttons for medium, long, short, VHF-FM, AFC, phono. mains on-off, 4-rotary controls, tuning, volume, tone, balance. Fascia size 17 x 4 1/2 inches. Chassis size 17 x 4 1/2 x 5 1/2 inches. DIN-connector sockets for tape record/playback, loudspeakers, phono pick-up, external FM-AM aerials. Automatic stereo beacon light. Built-in ferrite rod aerial for medium/longwave A.C. 240V mains. Circuit supplied Above speakers are suitable £33.50 Post £1 50

**LOW VOLTAGE ELECTROLYTICS**  
 1, 2, 4, 5, 8, 16, 25, 30, 50, 100, 200mF 15V 10p.  
 500mF 12V 15p; 25V 20p; 50V 30p.  
 1000mF 12V 17p; 25V 35p; 50V 47p; 100V 70p.  
 2000mF 6V 25p; 25V 42p; 50V 57p.  
 2500mF 50V 62p; 3000mF 25V 47p; 50V 65p.  
 3900mF 100V £1.60.  
 4700mF 63V £1.20.  
 5000mF 6V 25p; 12V 42p; 25V 75p; 35V 85p.

**SHORT WAVE** 100pF air spaced gangable tuner. 95p.  
**TRIMMERS** 10pF. 30pF. 50pF. 5p. 100pF. 150pF. 15p.  
**CERAMIC**, 1pF to 0.01mF. 5p. Silver Mica 2 to 5000pF. 5p.  
**PAPER** 350V-0 17p; 0.5 13p; 1mF 150V 15p; 2mF 150V 15p; 500V-0.001 to 0.05 5p; 0 1 10p; 0.25 13p; 0.47 25p.  
**MICRO SWITCH SINGLE POLE CHANGEVER** 20p.  
**SW-MIN MICRO SWITCH**, 25p. Single pole change over  
**TWIN GANG**, 385 + 385pF 50p; 500pF standard 75p; 365 + 365 + 25 + 25pF. Slow motion drive 65p.  
**120PF TWIN GANG**, 50p; 365pF TWIN GANG, 50p.  
**NEON PANEL INDICATORS** 250V, Amber or red 30p.  
**RESISTORS** 1/4W, 1/2W 1W 20% 2p; 2W, 10p; 10 to 10M.  
**HIGH STABILITY** 1/4W, 1/2W 2% 10 ohms to 6 meg. 12p.  
 Ditto 5% Preferred values 10 ohms to 10 meg. 5p  
**WIRE-WOUND RESISTORS** 5 watt, 10 watt, 15 watt, 10 ohms to 100K 12p each

**TAG STRIP** 28-way 12p.  
**TAPE OSCILLATOR COIL**. Valve type. 35p.  
**BRIDGE RECTIFIER** 200V PIV 1/2 amp 50p.  
**TOGGLE SWITCHES** S.P. 20p. D.P.S.T 25p. D.P.D.T 30p.  
**MANY OTHER TOGGLES IN STOCK**  
**PICK-UP CARTRIDGES** ACOS GP91 £1.50. GP93 £2.50.  
**SONOTONE** stereo £2.00.

**BAKER MAJOR 12" £14.95** Post £1 00  
 30-14 500 c/s. 12in double cone woofer and tweeter cone together with a BAKER ceramic magnet assembly having a flux density of 14,000 gauss and a total flux of 145,000 Maxwells. Bass resonance 40 c/s. Rated 25W. NOTE 4 or 8 or 16 ohms must be stated



Module kit. 30-17,000 c/s with tweeter crossover baffle £18.95 and instructions. Post £1 60p each. Please state 3 or 8 or 15 ohms

**BAKER "BIG-SOUND" SPEAKERS** Post £1 00 each

'Group 25'	'Group 35'	'Group 50/15'
12in	12in	15in
30W £11.95	40W £13.95	75W £24.95
4 or 8 or 16 ohm	4 or 8 or 16 ohm	8 or 16 ohm

**BAKER LOUDSPEAKER, 12 INCH. 60 WATT. GROUP 50/12, 8 OR 15 OHM HIGH POWER** FULL RANGE PROFESSIONAL QUALITY RESPONSE 30-16 000 CPS MASSIVE CERAMIC MAGNET WITH ALUMINIUM PRESENCE CENTRE DOME £20.95 Post £1 60

**TEAK VENEERED HI-FI SPEAKERS AND CABINETS**  
 For 12in or 10in speaker 20x13x12in. £14.50 Post £2  
 For 13x8in. or 8in speaker £7.50 Post £1  
 For 8x5in speaker 12x8x6in £5.80 Post 75p

**R.C.S. 100 watt VALVE AMPLIFIER CHASSIS**  
 Four inputs. Four way mixing, master volume, treble and bass controls. Suits all speakers. This professional quality amplifier chassis is suitable for all groups, disco, P.A., where high quality power is required. 5 speaker output. A/C mains operated. Slave output socket. Produced by demand for a quality valve amplifier. 100V line output to order. Send for leaflet. Suitable carrying cab £14. Price £85 carr £2.50



**SPEAKER COVERING MATERIALS.** Samples Large S.A.E.  
**LOUDSPEAKER CABINET WADDING** 18in. wide 20p ft. Horn Tweeters 2-16kc/s, 10W 8 ohm or 15 ohm £3.60  
 De Luxe Horn Tweeters 3-18kc/s, 30W, 8 ohm, £7.50  
**CROSSOVERS. TWO-WAY** 3000 c/s 3 or 8 or 15 ohm £1.90. 3-way 950 cps/3000 cps. £2.20.  
**LOUDSPEAKERS P.M.M. 3 OHM** 7x4in. £1.50; 6 1/2 in. £1.80; 8x5in. £1.90; 8in. £1.95.  
**SPECIAL OFFER:** 80 ohm, 2 1/4 in., 2 3/4 in., 35 ohm, 3 in., 25 ohm, 2 1/2 in., 3 in., 5x3 1/2 in., 7x4 in., 8 ohm, 2 1/2 in., 3 in., 3 1/2 in., 5 in., 15 ohm, 4 in., 3 1/2 in. dia. 6x4 in., 7x4 in., 5x3 in., 3 ohm, 2 1/2 in., 2 3/4 in., 5 in. dia. £1.25 each.  
**PHILIPS LOUDSPEAKER**, 8in., 4 ohms, 4 watts. £1.95  
**RICHARD ALLAN TWIN CONE LOUDSPEAKERS** 8in. diameter 4W £2.50, 10in. diameter 5W £2.95; 12in. diameter 6W £3.50, 3/8/15 ohms, please state  
**PIEZO ELECTRIC HORN TWEETER.** Handles up to 100 watts. No crossover required. £10.95.

Tweeter Volume Control 15 ohms 10W with one inch long threaded bush for wood panel mounting. 1/4 in. spindle 65p.

**BAKER 150 WATT PROFESSIONAL MIXER AMPLIFIER**  
 All purpose transistorised. Ideal for Groups, Disco and P.A. 4 inputs speech and music. 4 way mixing Output 4 8/15 ohms. a.c. Mains. Separate treble and bass controls. Master volume control. Guaranteed. Details S.A.E. £68 £1 50 carr



**NEW MODEL MAJOR—50 watt.** 4 input. 2 vcl. Treble and bass. Ideal stereo amplifier. £49 Carr £1

**100 WATT DISCO AMPLIFIER CHASSIS**  
 volume, treble, bass controls. 500 M V. or 1 volt input. Four loudspeaker outputs 4 to 16 ohm. All transistor £52


**BARGAIN 4 CHANNEL TRANSISTOR MONO MIXER**  
 Add musical highlights and sound effects to recordings Will mix Microphone, records, tape and tuner with separate controls into single output. 9V. £5.95

**TWO STEREO CHANNEL VERSION BARGAIN 3 WATT AMPLIFIER.** 4 Transistor Push-Pull Ready Built, with volume, Treble and bass controls. 18 volt d.c. Mains Power Pack £3.45


**ALUMINIUM HEAT SINKS.** Finned type. Sizes 6 1/2" x 4 1/2" x 2 1/4" 95p. 6 1/2" x 2 1/2" x 2 1/4" 65p.  
**BALANCED TWIN RIBBON FEEDER** 300 ohms. 5p yd.  
**JACK SOCKET Std.** open-circuit 20p, closed circuit 25p;  
**Chrome Lead-Socket** 45p. Mono or Stereo.  
**Phono Plugs** 8p. Phono Socket 8p.  
**JACK PLUGS Std.** Chrome 30p; Plastic 25p; 3.5mm 15p.  
**STEREO JACK PLUG** 30p. SOCKET 25p.  
**DIN SOCKETS Chassis** 3-pin 10p, 5-pin 10p.  
**DIN SOCKETS FREE** 3-pin 25p; 5-pin 25p. **DIN PLUGS** 3-pin 25p; 5-pin 25p. **VALVE HOLDERS**, 10p; **CANS** 10p.

**R.C.S. SOUND TO LIGHT KIT**  
 Kit of parts to build a 3 channel sound to light unit. 1,000 watts per channel. £14. Post 35p. Easy to build. Full instructions supplied Cabinet £3.

**E.M.I. TAPE MOTORS.** 240V a.c. 1,200 r.p.m. 4 pole. Spindle 0.187x0.75in. Size 3 1/4 x 2 1/2 x 2 1/4 in. D2. Post 50p  
 Collaro gram motor 120V 75p.  
 E.M.I. gram motor 240V £1.25.



# POCKET TTY

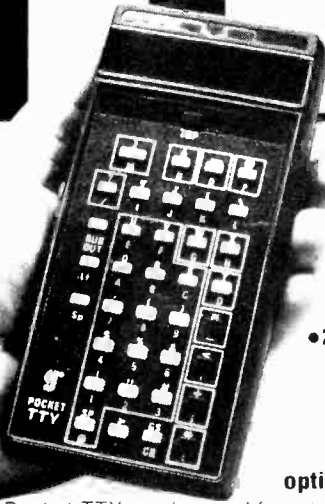

The GR Electronics Pocket TTY offers the keyboard facilities of a teletype - at a fraction of the cost.

- Outputs serial ASCII code to any Teletype-compatible device
- 20 mA loop or RS232 mode
- 36 keys giving full 64 character alphanumeric
- 9 digit LED display of characters entered
- All solid-state with optical coupling for reliability

Pocket TTY can be used for microprocessor programming, production data entry, warehousing, mobile data collection, training and education.

For further details contact:

**G.R. ELECTRONICS LTD.**




80 Church Road, Newport NPT 7EH, Gwent, England.  
Telephone: Newport (0633) 67426  
Telex: 28604 Ref: 1796

WW — 066 FOR FURTHER DETAILS

## HYBRID HIGH POWER IC AUDIO AMP. MODULES

Outline Drawing

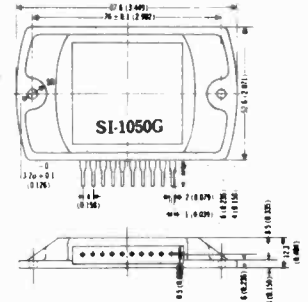

### Features

- Push-Pull Output
- Freq. Response Flat to within 1/2 dB from 20Hz to 100 KHz
- 8 Ohm Output
- Harmonic Distortion 0.5% at full output
- Input Impedance 40K-ohms

### Description

Made by the largest Hybrid Audio Amplifier Manufacturer in the world — comes in 3 popular models. These are not kits, and require a few external components, a heatsink and a power supply. Build high quality sound systems using the economical modular Sanken technique. Ideal for HI-FI systems, Stereo, tape deck, FM tuners, record players, musical instruments, public address systems, A.C. servo and wide band amplifiers. Each module has quasi-complementary class B output, employing flip-chip transistors, etc., in rugged, compact and light-weight packages. SANKEN = COMPACT POWER.

- SI1010G TEN Watts ..... £4.76 ea. (ex VAT)
- SI1020G TWENTY Watts ..... £8.34 ea. (ex VAT)
- SI1050G FIFTY Watts ..... £16.58 ea. (ex VAT)

All goods new, to full manufacturer's spec. No substandard parts sold. Callers welcome. Colleges, Govt. and account orders welcomed.  
**TERMS:** Non-Account Customers: Cash with Order. Standard P&P 50p. Please add VAT to overall total.




**RASTRA ELECTRONICS LTD.**

275-281 King Street - Hammersmith - London W6 9NF  
Tel. 01-748 3143/2960 Telex 24443

WW—105 FOR FURTHER DETAILS

## TEAC

TEAC A3340(S)  
4-CHANNEL  
RECORDER

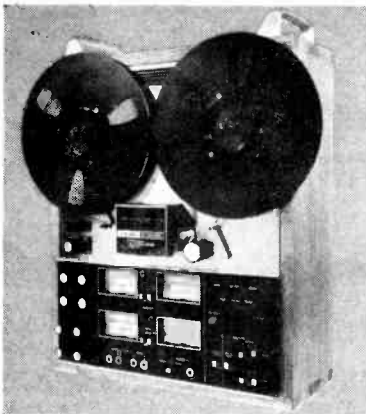

Industrial version upgraded to studio requirements, with increased signal to noise performance and improved reliability. Four totally independent channels each with sel sync, input mixing, switchable VU's and all the facilities for easy multitracking. This industrial model is in more studios than any other version.

Available only from ITA  
(Semi-pro version also available)  
IMMEDIATE DELIVERY

## REVOX

REVOX A-700 SERIES



IMMEDIATE DELIVERY

The new big Revox — ideal for all studio requirements. Highly sophisticated design features include servo tape tension, full deck logic, crystal controlled servo electronics, 3 speeds, tape footage counter.

The famous A77 has been consistently improved over the past 8 years and is now available in the latest Mk 4 version.

The wide choice of specifications includes versions for duplicating and logging applications. Backed by UK's latest fastest service.



Hire service. Check our prices  
IMMEDIATE DELIVERY

## ITA

ITA 10-4  
MODULAR MIXER



Ten balanced inputs; four output groups, 4 limiters; bass mid and treble EQ, modular construction, headphone monitoring. Extremely high quality construction only matched by mixers costing around £1,000.

- 10-4 £690
- 20-4 £1190
- EIGHT OUTPUT £1360

IMMEDIATE DELIVERY  
Also available for hire

PRICES EXCLUSIVE OF V.A.T.

## Industrial Tape Applications



1-7 Harewood Avenue, Marylebone Road, London NW1  
Telephone: 01-724 2497 Telex: 21879

WW — 100 FOR FURTHER DETAILS

**TRANSISTORISED 3cm RADAR AMPLIFIER SWITCH:** with 24v waveguide switch, .9 x .4 cm ins. with crystal CV.2355 and spark gap VX.1046. **£16.20 + £1.00 post.**

**TRANSISTORISED VIDEO INDICATOR** (used with above amplifier): 1 1/2" C.R.T. **£10.80 + £1.00 post.**

**RADAR RECEIVING ANTENNA TYPE X443 Mk. D:** Suitable for detecting signals on X, K, J and Q bands. 9gHz-60gHz. Complete with waveguide horns, associated crystals. Transistorised amplifier and geared motor, etc. **£135.00, carr. approx. £5.00.**

**DIODES:** CD.384 — **£2.00 per 100 + 20p post.**

**VACUUM & PRESSURE SEAL TEST EQUIPMENT:** Complete with 3 x 4" gauges indicating 0-20lbs p.s.i., 0-30lbs vacuum. With stand, hand pump, etc., **£32.40 + £3.00 carr.**

**ASHCROFT DEADWEIGHT GAUGE TEST SET TYPE 1300:** 0-25lbs **£64.80 + £3.00 carr.**

**E.A.L. ANALOGUE DIGITAL CONVERTER TYPE MPD. 120-0:** 7-bit or 8-bit mode. **£70.00, carr. £2.00.**

**PAIGNTON dB SWITCH:** High quality instrument stud switch. 20-way. 2-pole. Dial marked 0-60dB. As new. **£3.78 + 60p post.**

**UNISELECTORS:** Reversible action. Twin coils 120V 25-way 6-bank. **£4.90 + 75p post.**

**FAMOUS 1154 TRANSMITTER** as used in Lancasters in World War II (collector's item). **£12.50, carr. £4.00.**

**CASCAD RAIT RECEIVER 50kHz-30MHz.** ~~5-hand good condition.~~ **£365.00** (including VAT 12 1/2%).

**CT.316 SOLARTRON OSCILLOSCOPE (CD-518):** 3" tube, d.c. 5MHz calibration marker 1MHz and 100kHz. 230v a.c. single beam. Excellent condition. **£35.00, carr. £2.50.**

**EVERSHED SAFETY OHM METER:** Max 10mA. Test pressure 30v. Complete in leather case. **£27.00, post £1.00.**

**AVO TRANSISTOR ANALYSER CT.446:** **£37.80, carr. £2.20.**

**ADVANCE TCD.40 FREQUENCY DIVIDER:** 0-40MHz. **£10.80 + £1.00 post.**

**MARCONI FREQUENCY METER 1026/4:** 2000-4000MHz 'as new' condition **£32.40** or secondhand condition **£24.30.**

**1026/2:** 0-100MHz **£32.40** 'as new' or s/hand **£24.30.** Carriage for all type £2.00.

**ANTENNA MAST 36ft:** Aluminium, diameter at base 3", tapering to 2" at top, complete with red hazard lights, stays, guys, etc. Normally used with direction finding equipment. Approx. weight 3cwt. **£106.90** (including 12 1/2% VAT), carriage rates on request. WITH rotating Antenna suitable for 200-400MHz **£16.90** extra (including 12 1/2% VAT).

**BURGLAR ALARM BELL:** 6-8v, d.c. **£3.24 + £1.00 post.**

**MEGGER (Record):** 500 volts **£21.60** £1.00 post.

**R-216 RECEIVER MANUAL (Photostat copy):** **£1.50** inc. post.

**MUIRHEAD ATTENUATORS:** 75 ohms 0-8Mc/s 3V MAK 3 ranges 0-5, 0-25, 0-50dB. **£3.24 + 75p post.**

Visit our new shop in Ware High Street (old A10) opposite Church. 100s of individual bargains for callers. If you wish to collect any of the above items please telephone prior to calling to avoid disappointment.

# W. MILLS

3 & 3a BALDOCK STREET, WARE, HERTS, SG12 9DT  
WARE 66312 (STD 0920)

**POWER UNIT TYPE 234:** 200-250v. a.c. input. 250-0-250v. d.c. at 100mA and 6 3v at 4 amps output. **£8.10, carr. £2.50.**

**REDIFON TELEPRINTER RELAY UNIT NO. 12:** ZA-41196 and power supply 200-250v. a.c. Polarised relay type 3SEITR 80-0-80v. 25mA. Two stabilised valves CV-286 Centre Zero Meter 10-0-10. Size 8" x 8" x 8". New condition. **£10.80, carr. £2.50.**

**SOLARTRON PULSE GENERATOR TYPE G1101-2:** **£81.00, carr. £2.50.**

**TELEPRINTER TYPE 7B:** Pageprinter 24v. d.c. power supply, speed 50 bauds per min. S/hand cond. (excellent order), no parts broken **£21.60, carriage £3.50.**

**AUTO TRANSFORMER:** 230v. 50c/s, 1000 watts. Mounted in strong steel case 5" x 6 1/2" x 7". Bitumen impregnated. **£12.96, carr. £2.00.**

**CRYSTAL TEST SET TYPE 193:** Used for checking crystals in freq. range 3,000-10,000kHz. Mains 230v 50Hz. Measures crystal current under oscillatory conditions and the equivalent resistance. Crystal freq. can be tested in conjunction with a freq. meter. **£27.00, carr. £2.00.**

**CATHODE RAY TUBES:** 5" screen, tube CV-1536 **£4.32 + £1.00 post.** Type 95J20 square face 5" x 3" **£8.10 + £1.00 post.**

**POWER UNIT:** 110/230v. a.c. input. 28v. d.c. at 40 amps output **£32.40 + £3.50.**

**SMOOTHING UNIT (for the above Power Unit):** **£10.80 + £2.00 carr.**

**CLASS 'D' WAVEMETER NO. 1:** Crystal controlled heterodyne frequency meter covering 2-8MHz. Power supply 6v. d.c. Good s/hand cond. **£9.20 + £2.00 carr.**

**RING TOROIDAL DUST CORES:** Size 2 1/2" outside, 1 1/4" inside, 5/16" thick. Box of two **£1.10 + 30p post.**

**ROTARY INVERTERS TYPE PE-218E:** Input 24-28v. d.c. 80 amps. 4,800rpm. Output 115v. a.c. 13 amp 400 c/s. 1Ph. P.F.9 **£21.60 + £3.00 carr.**

**FREQUENCY METER BC-221:** 125-20,000kc/s complete with original calibration charts. Checked out, working order. **£22.70 + £2.00 carr.**

**RECTIFIER UNIT:** 200-250v. a.c. input. 24v. d.c. at 26 amps output continuous rling. **£37.80, carr. £5.00.**

### BARGAIN MAPS

Large stocks of unused U.S.A.F. surplus maps, weather charts, etc. including:—

- ONC-E1 — U.K. in full and part N.W. Europe. Scale 1:1,000,000.
  - JNC-9N — N. Europe, U.K., Scandinavia. Scale 1:2,000,000.
  - JN-21N — Europe (Mediterranean). Scale 1:2,000,000.
- SIZE: 58" x 42", colour. Many others. Please send S.A.E. for list.  
Price each 70p (inc. p + p)  
25 x Maps (either same type OR assorted) **£10.00 + £1.00 p + p.**  
10 x Maps (either same type OR assorted) **£6.00** (inc. p + p).

Above prices include VAT at 8% (except where stated)  
Carriage quotes given are for 50-mile radius of Herts.

## WEST HYDE Instrument cases

**MOD 3**

Offer instrument manufacturers low cost cases ex stock. Blue PVC coated steel strength and rigidity. PVC aluminium grey front and rear panels are removable. PCB and PSU mounting system available. Also available in black. 301 price of 302 Bk 302 303. Bk 304 305

All dimensions are Width x Height x Depth  
PRICES 1 off inc. P & P but not VAT

MOD 3 (including chassis)	L 4 5/8 x 10 1/2 x 6 1/2	9.44
301	7 1/2 x 5 1/2 x 6 1/2	6.32
302	7 1/2 x 5 1/2 x 6 1/2	6.78
303	7 1/2 x 5 1/2 x 6 1/2	8.65
304	11 1/2 x 5 1/2 x 7 1/2	7.78
305	11 1/2 x 5 1/2 x 7 1/2	9.18
306	11 1/2 x 5 1/2 x 7 1/2	10.98
<b>CONTIL TEXTURED</b>		
755	7 1/2 x 5 1/2 x 6 1/2	8.77
807	8 1/2 x 6 1/2 x 6 1/2	10.42
975	9 1/2 x 7 1/2 x 6 1/2	10.42
1277	12 1/2 x 7 1/2 x 7 1/2	12.01
1277	unpainted	8.92
16127	16 1/2 x 12 1/2 x 10 1/2	16.55
191010	19 1/2 x 10 1/2 x 10 1/2	22.72
<b>ELF CASES (grey fine chassis)</b>		
EH	6 1/4 x 4 1/4 x 3 1/2	3.20
Bare EH	(less fit. ch. pnt)	2.15
Giant ELF	8 1/2 x 5 1/2 x 5 1/2	4.50
Long ELF	9 1/4 x 3 1/2 x 3 1/2	3.60
Jumbo ELF	10 1/4 x 5 1/4 x 5 1/4	5.40
<b>MOD 2 CASES (including chassis)</b>		
A	4 5/8 x 3 x 6 1/2	6.65
B	4 5/8 x 7 x 6 1/2	7.72

**CONTIL**

A range of eyebrow cases in blue textured acrylic. Front panels normally white/zinc or PVC aluminium, also available unpainted up to 1277 size. Aluminium panels 20b extra up to 16127 only.

## WEST HYDE Instrument cases

**MOD 2**

Mod 2 cases over 24 sizes. Front and back panels grey PVC. Aluminium chassis included. Packed flat. Outer casing blue PVC steel or up to size L also available in wood grain and black. (Price for next price higher ie A Black is B price)

**CONTIL ELF**

These tough little cases add very little to the cost of a job. Front panel aluminium with protective coat. Elf cases are available in 4 sizes, all dough moulded in grey glass polyester. All panels, feet and chassis included.

All West Hyde cases are available with substantial discounts for quantities. Most cases have discounts at 5 off and 25 off with discounts up to 25% at 100 off. Prices include P & P and are less 10% if collected, on first three price breaks on cases only.

**BUY A CASE FROM A SMALL RANGE, YOU GET A CASE—BUY A CASE FROM A BIG RANGE, YOU GET A SOLUTION**

**Brightcase**

A prestige anodised case, black PVC steel top and bottom which can be supplied hinged at no extra cost. Free standing or rack mounting available in rack or half width assembled in special polystyrene rack for safe postage.

**Instrument cases**

<b>BRIGHTCASE MARK II</b>		<b>SAMOS</b>	
BC212 (5" Flat Rack)	21.91	S1	100x100x50mm 1.36
BC222 (3" Flat Rack)	15.84	S2	100x100x50mm 1.56
BC312 (5" Flat Rack)	24.04	S3	100x150x50mm 1.73
BC322 (5" Flat Rack)	17.72	S4	125x100x75mm 1.95
Rack Bracket available		S5	125x100x75mm 2.24
Next order Linears add £1		S6	125x150x75mm 2.62
		S7	175x200x75mm 2.91
<b>MINOS</b>		<b>HEAVY DUTY CASE</b>	
M2	65x100x50mm .70	H1	8x8x5 14.89
M3	100x130x50mm .89	H2	10x10x7 16.54
M2	Bare .46	H3	12x10x7 20.95
M3	Bare .52		

**SAMOS**

Miniature instrument cases in blue and white PVC steel. Assemble in the lower half clip on feet, 2 screws allow the cover to hinge off cases, 2 more to fix. PC feet are available to hold up to 4 PC boards horizontally in case.

**MINOS**

Smart miniature ARS cases in tough rigid high gloss black. Front panels either aluminium or PVC steel. Built in slots for PC cards, dividers etc. Chassis or PC boards can be supported on 'P' clips from internal pillars.

**THE INSTRUMENT**

OVER 400 DIFFERENT CASES IN STOCK—SIZE RANGE OVER 5000:1 IN VOLUME  
Prices as January 77. Please check with us in case of price change.

Send for catalogue

**WEST HYDE DEVELOPMENTS LIMITED**  
Ryefield Cess., Northwood Hill, Northwood, Middx., HA8 1NN  
Telephone: Northwood 24941/26732/27051  
Telex: 823231 West Hyde Wilmsd.

**HEAVY DUTY**

Available in 3 sizes. Heavily constructed in zinc steel, welded corners with heavy hinges. 2 screw fixings and foam around the drain. In the base is a gland plate with gasket and a chassis with screws provided.


**CASE SPECIALISTS**

WW—082 FOR FURTHER DETAILS

# Two books from Wireless World


These books are of very special appeal to all concerned with designing, using and understanding electronic circuits. They comprise information previously included in Wireless World's highly successful

Circards – regularly published cards giving selected and tested circuits, descriptions of circuit operation, component values and ranges, circuit limitations, modifications, performance data and graphs. Each of these magazine-size hard cover books contains ten sets of Circards plus additional circuits and explanatory introduction.

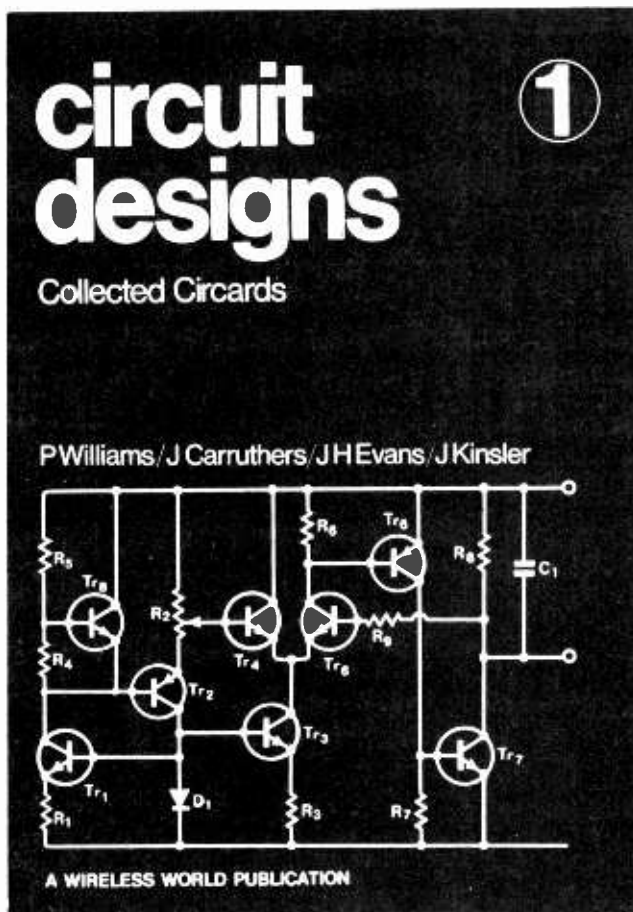

**BOOK 1**

- Basic active filters
- Switching circuits
- Waveform generators
- AC measurements
- Audio circuits
- Constant-current circuits
- Power amplifiers
- Astable circuits
- Optoelectronics
- Micropower circuits

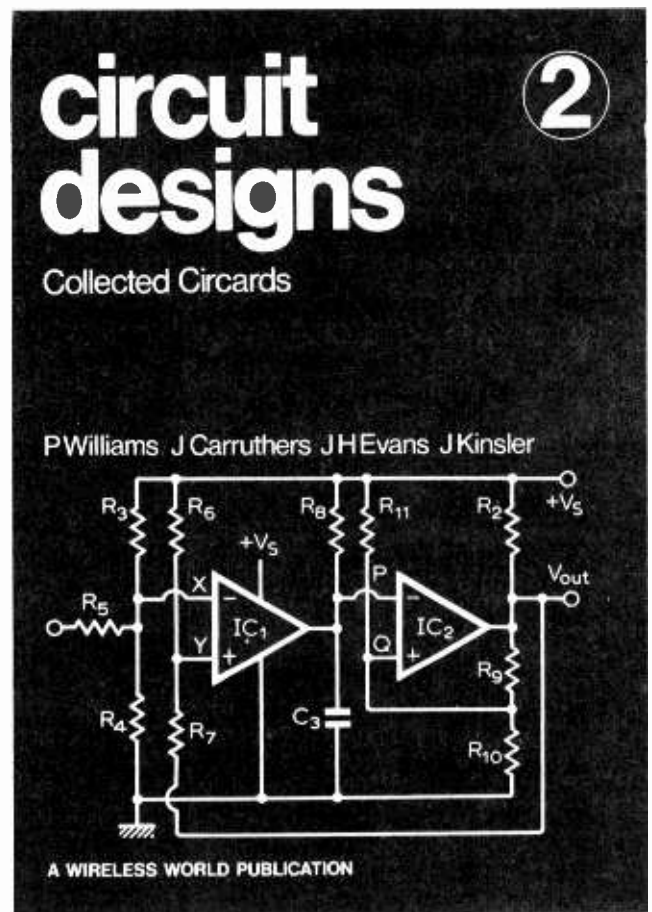

**BOOK 2**

- Basic logic gates
- Wideband amplifiers
- Alarm circuits
- Digital counters
- Pulse modulators
- C d as – signal processing
- C d.as – signal generation
- C d as – measurement and detection
- Monostable circuits
- Transistor pairs

**ORDER FORM**

To: General Sales Department,  
 IPC Business Press Limited,  
 Room 11, Dorset House,  
 Stamford Street, London SE1 9LU  
 Please send me \_\_\_\_\_ copy/copies of  
 Circuit Designs – Number 1 at £10.40   
 Circuit Designs – Number 2 at £12.50   
 each inclusive. I enclose remittance value £ .....  
 (cheques payable to IPC Business Press Ltd.)

Name (please print)

Address

Company registered in England and a subsidiary of Reed International Limited Registered No. 677128 Regd. office Dorset House, Stamford Street, London SE1 9LU.



# The SECOND-USER Computer Specialists

# Systems, Peripheral Equipment & Components for Data Processing



## Mini-Computer Exchange

**PDP8M-ML 8K Processor.**  
**PDP11/34-MN 32K Processor** with RX11 Twin Floppy Disk LA36 DECWriter, PC11 High Speed Reader/Punch  
**PDP8I 20K Processor** with Extended Arithmetic, Teletype Control, Clock, 2xTU55 DECtape drives, PC08 Reader/Punch, 9-track Incremental Deck, RFO8 256K Disk.  
**Nova 3/12 48K Processor** with Teletype Control, Clock, Memory Management  
**Nova High Speed Paper Tape Reader.**  
**Nova 1200 4K Processor** with Teletype Control Clock.  
**RTO2 DEC Data Entry Terminal** with single line 32-character display complete with control for PDP8E.  
**TU60 DEC Dual Cassette Drive** with control for PDP11 series.  
**Calcomp Digital Incremental Plotters.**  
 Model 563: 31" drum, 300 steps per second  
 Model 565: 12" drum, 300 steps per second.  
 Model 663: 31" drum, 300 steps per second.  
**DF32 DEC 32K Disk Drive & Control** (slave drives type DS32 also available).  
**KK8E set of PDP8E series processor modules.**

**OUR STOCKS ARE CONSTANTLY CHANGING** — please phone for latest availabilities.

# ELECTRONIC BROKERS

**JUST RECEIVED — SPECIAL PURCHASE OF DATA DYNAMICS MODEL 390 TELETYPE TERMINALS IN BRAND NEW CONDITION.**  
**TERMINALS — LARGE STOCKS AVAILABLE.** ASR33 Teletype from £500.00. KSR33 Teletype from £325.00. ASR35 Teletype from £750.00. IBM731/0 Golfball Typewriter from £275.00.

**SPECIAL OFFER**  
 Cossor DIDS 401 2A Visual Display Units. 13 lines x 80 characters (8½x4½" screen) 64 character repertoire with detachable ASCII keyboard (Control device required) **Bargain Price: £145.00**  
 Also available Cossor DIDS 402 2A, as above but incorporating control logic. **Price £295.00.**


**FOR IBM 360 USERS.** Sanders 720 Data Display System consisting of six VDUs, control unit and communications buffer. Complete with connecting cables and technical documentation. **Price £2,750.00.**

**MINIATURE MATRIX PROGRAMME BOARDS:** Brand new X.Y Matrix boards, with 3mm grating. 3x10 positions (1¼" x 1¼") £4.00 P&P 40p.

**MAGNETIC TAPES.** Manufacturers surplus stocks, brand new in original sealed packing. ½" x 2400' £4.00 per reel. P&P extra.

## Keyboards

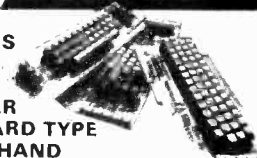**FRESH STOCKS OF THE POPULAR CLARE-PENDAR ASCII KEYBOARD TYPE KB6 NOW TO HAND**



ASCII-Coded TTL-compatible 4-bank alphanumeric keyboards with ROM encoder chip strobed output, two-key rollover and debounce. Standard 7-bit ASCII code (no parity). Supplied complete with circuit diagrams and code chart.

**SPECIFICATIONS**  
 Power Supply +5VDC ± 5% 150mA —12VDC ± 10% 10mA Output Logic Levels Data Bits 1 through 7 0v 0 45v 2.6v 1 5.25v 0v 0 45v Fan Out 10 standard TTL loads Strobe signal delay 10 microseconds nominal to allow data to stabilise.  
**KB6:** 56-station standard Teletype layout. AS RECOMMENDED FOR PRACTICAL WIRELESS VIDEO WRITER PROJECT **Price £39.50 + £1 P&P + 8% VAT** (send £43.74)

**ALSO AVAILABLE — SPECIAL LOW-COST KEYBOARD**  
**KB5:** 3-bank alphanumeric. Baudot-coded. 36-station TTL-compatible strobed output. **Price £20.00**, plus £1 P&P + 8% VAT (send £22.68)

**NEW ARRIVALS**  
**FABULOUS NEW 96-STATION CRT DISPLAY KEYBOARDS.** 8-bit ASCII code, upper and lower case output PLUS separate numeric pad TTL Logic. Delayed strobe signal and two-key rollover feature. Mounted in attractive box, overall dimensions 20½" x 7¾" x 3¼". **Price £65.00 + £3 carriage + 8% VAT** (send £73.44)

**BCD-CODED 54-STATION KEYBOARD,** brand new, upper and lower case outputs. Mounted on double PCB and in attractive panel incorporating 5 indicator lamps and on/off switch. Dimensions 15½" x 5½" x 2½". **Price £39.50 + £2 P&P + 8% VAT** (send £44.82). Also available. A few only of the above model WITHOUT ENCODING OR PANEL. **Price £25.00 + £1.50 P&P + 8% VAT** (send £28.62)

**18-KEY CALCULATOR KEYBOARDS** (0-9 CK + - X = ÷) Make/break switches mounted on PCB. Overall dimensions 150 x 110 x 40mm. **Price £4 plus 50p P&P + VAT** (Send £4.86p)

Add 8% VAT to all prices shown. Carriage extra details on request.



**ELECTRONIC BROKERS LIMITED (Computer Sales & Services Division)**  
 49-53 Pancras Road, London NW1 2QB. Tel: 01-837 7781

Callers welcome Monday to Friday 9 a.m. to 5 p.m.

WW-112 FOR FURTHER DETAILS

**LYNX ELECTRONICS (London) LTD.**  
 92 Broad Street, Chesham, Bucks. Tel (02405) 75154  
 VAT 8% except \* which are 12 ½ % Return Post Service  
 P&P 30p. Overseas 90p. Matching 20p per pair New Price List 20p  
 Prices correct at 28th Feb. '77. ACCESS WELCOME

REGULATORS		OPTO ELECTRONICS		CLOCK CHIPS		IC SOCKETS	
723	0.45	DISPLAYS		2 Red	0.13	8 Pin	0.16
7812	1.50	704	0.99	2 Green	0.20	14 Pin	0.16
7815	1.50	707	0.99	MM5314	4.25	16 Pin	0.18
7818	1.50	727	1.95	MM5316	5.95	24 Pin	0.45
LM340.5	1.35	728	1.95	AA5-1224A.3.25		40 Pin	0.80
LM340.12	1.35	747	1.80	AA5-5-4007D	9.95		
LM340.15	1.35	750	1.80				
LM340.18	1.35						

TRANSISTORS											
AC126	0.15	BC161	0.38	BD131	0.36	BFV60	0.36	OC72	0.22	2N3705	0.10*
AC127	0.16	BC168	0.09	BD132	0.40	BFX29	0.26	OC84	0.40	2N3706	0.10*
AC128	0.16	BC169	0.12	BD133	0.36*	BFX30	0.30	OC139	0.30	2N3707	0.10*
AC128K	0.25	BC169C	0.14*	BD136	0.39*	BFX84	0.23	OC140	1.30	2N3708	0.09*
AC141	0.22	BC170B	0.12*	BD137	0.40*	BFX85	0.25	OC170	0.23	2N3709	0.09*
AC141K	0.34	BC171	0.12*	BD138	0.48*	BFX86	0.25	1P29A	0.44*	2N3710	0.10*
AC142	0.18	BC172B	0.12*	BD139	0.58*	BFX87	0.20	1P30A	0.52*	2N3711	0.10*
AC142K	0.32	BC182	0.11*	BD144	2.20	BFX88	0.20	1P31A	0.54	2N3715	1.80
AC176	0.16	BC182L	0.12*	BD157	0.60	BFX89	0.90	1P32A	0.64	2N3716	1.80
AC176K	0.32	BC183	0.10*	BD181	0.86	BFY11	1.10	1P41A	0.68	2N4123	1.14*
AC187	0.18	BC183L	0.10*	BD182	0.92	BFY18	0.50	1P42A	0.72	2N3772	1.90
AC187K	0.36	BC184	0.11*	BD183	0.97	BFY40	0.50	2N404	0.40	2N3773	2.10
AC188	0.18	BC184L	0.12*	BD184	1.20	BFY41	0.60	2N696	0.20	2N3819	0.28*
AC188K	0.32	BC187	0.24*	BD232	0.60	BFY50	0.20	2N697	0.20	2N3904	0.16*
AD149	0.09	BC207	0.12*	BD233	0.48	BFY51	0.18	2N706	0.15	2N4347	1.10
AD161	0.35	BC207B	0.12*	BD237	0.55	BFY52	0.19	2N718	0.18	2N4306	0.11*
AO162	0.35	BC212	0.11*	BD238	0.60	BFY53	0.25	2N929	0.22	2N4124	0.14*
AF114	0.20	BC212L	0.12*	BD410	0.60	BFY64	0.35	2N1131	0.15	2N4290	0.14*
AF115	0.20	BC213	0.12*	BDX32	2.30	BFY90	0.90	2N1132	0.16	2N4291	0.14*
AF116	0.20	BC213L	0.14*	BDY11	2.00	BSX19	0.16	2N1302	0.40	2N4292	0.14*
AF117	0.20	BC214	0.14*	BDY11	2.00	BSX19	0.16	2N1303	0.40	2N4347	1.10
AF118	0.50	BC214L	0.15*	BDY20	0.80	BSX20	0.18	2N1304	0.45	2N4348	1.20
AF124	0.25	BC237	0.16*	BDY38	0.60	BSX21	0.20	2N1305	0.45	2N4870	0.35*
AF125	0.25	BC238	0.16*	BDY60	1.70	BSX76	0.30	2N1306	0.50	2N4871	0.35*
AF126	0.25	BC300	0.34*	BDY61	1.65	BSX77	0.30	2N1307	0.50	2N4918	0.60*
AF139	0.35	BC301	0.32	BDY62	1.15	BSX78	0.35	2N1308	0.60	2N4919	0.70*
AF239	0.37	BC302	0.40	BDY95	2.15	BSY52	0.28	2N1309	0.60	2N4920	0.60*
AL102	1.45	BC303	0.46	BDY96	2.46	BSY53	0.39	2N1711	0.24	2N4922	0.58*
AL103	1.30	BC307	0.15*	BDY97	4.95	BSY54	0.33	2N2102	0.44	2N4923	0.46*
AL107	3.30*	BC308	0.16*	BF127	0.50	BSY55	0.74	2N2217	0.10		
AL110	1.75*	BC309	0.18*	BF157	0.50	BSY65	0.30	2N2369	0.30		
AL113	1.60*	BC310	0.17*	BF177	0.25	BSY76	1.75	2N2483	0.60		
BC107	0.09	BC317	0.12*	BF178	0.28	BSY78	0.20	2N2369A	0.14		
BC107B	0.09	BC319	0.13*	BF179	0.28	BSY95A	0.16	2N2484	0.16		
BC108	0.09	BC320	0.18*	BF180	0.30	BU105	1.80*	2N2646	0.50		
BC108B	0.09	BC321	0.18*	BF181	0.30	BU105.02	1.90*	2N2711	0.20		
BC109	0.09	BC323	1.60*	BF182	0.30	BU108	3.00*	2N2712	0.15		
BC109B	0.09	BC327	0.83*	BF183	0.30	BU109	2.50*	2N2904A	0.20		
BC109C	0.12	BC328	0.18*	BF184	0.20	BU126	1.60*	2N2905	0.18		
BC117	0.19*	BC337	0.17*	BF185	0.20	BU133	1.60*	2N2905A	0.22		
BC119	0.25	BC338	0.17*	BF194	0.10*	BU204	1.60*	2N2906	0.18		
BC125	0.18*	BC407	0.22*	BF196	0.12*	BU205	1.90*	2N2925	0.14*		
BC126	0.20*	BC408	0.22*	BF197	0.12*	BU206	2.40*	2N2926	0.09*		
BC140	0.32	BCY30	0.55	BF200	0.40	BU208	2.60*	2N2926B	0.10*		
BC141	0.28	BCY31	0.55	BF218	0.30	MJ480	0.80*	2N2926C	0.09*		
BC142	0.23	BCY32	0.60	BF219	0.30	MJ481	1.05	2N2926G	0.10*		
BC143	0.23	BCY33	0.55	BF220	0.28	MJ490	0.90	2N3053	0.20		
BC144	0.30	BCY34	0.55	BF224J	0.18*	MJ491	1.15	2N3055	0.50		
BC147	0.08*	BCY38	0.18*	BF244	0.17*	MJ520	0.40*	2N3133	0.30		
BC148	0.09*	BCY39	1.15	BF257	0.35	MJ521	0.45	2N3134	0.30		
BC149	0.09*	BCY40	0.75	BF258	0.35	MJ521	0.55	2N3137	1.10		
BC152	0.25*	BCY42	0.30	BF259	0.48	OC43	0.95	2N3440	0.56		
BC153	0.18*	BCY44	1.60	BF336	0.35*	OC44	0.32	2N3442	1.20		
BC157	0.09*	BCY70	0.12	BF337	0.32*	OC45	0.32	2N3570	3.60		
BC158	0.09*	BCY71	0.12	BF338	0.45*	OC46	0.20	2N3702	0.10*		
BC159	0.09*	BCY72	0.12	BFW30	1.75	OC70	0.30	2N3703	0.10*		
BC160	0.32	BD115	0.15	BFW59	0.50	OC71	0.35	2N3704	0.10*		

TTL 7400 SERIES			
7400	0.16	7480	0.55
7401	0.16	7482	0.75
7402	0.16	7486	0.32
7403	0.16	7489	2.92
7404	0.18	7490AN	0.49
7405	0.18	7491AN	0.65
7408	0.18	7492	0.57
7409	0.18	7493	0.45
7410	0.16	7494	0.85
7412	0.25	7495	0.67
7413	0.25	7496	0.82
7414	0.72	74100	1.07
7417	0.43	74107	0.35
7420	0.16	74121	0.34
7425	0.30	74122	0.47
7427	0.48	74123	0.47
7430	0.16	74141	0.78
7432	0.37	74145	0.68
7437	0.35	74154	1.62
7441AN	0.76	74164	0.93
7442	0.65	74165	0.93
7445	1.50	74174	1.00
7447AN	0.81	74175	0.94
7448	0.81	74180	1.06
7470	0.32	74181	3.20
7472	0.26	74191	1.32
7473	0.30	74192	1.35
7474	0.32	74193	1.35
7475	0.47	74194	1.20
7476	0.36	74196	1.6*

THYRISTORS											
PV	1A	3A	4A	4A	5A	8A	10A	15A	10A	15A	10A
	[05]	[Stud]	[C106]	[T0220]	[T0220]	[T0220]	[T0220]	[T0220]	[T0220]	[T0220]	[T048]
200	0.35	0.50	0.45	0.40	0.58	0.60	0.68	1.14			
400	0.64	0.60	0.50	0.45	0.88	0.88	0.98	1.40			
600	0.65	0.85	0.70	-	1.09	1.19	1.26	1.80			
BT106	BT107	BT108	BT109	BT116	BT116	BT3525					
£1.00	£1.60	£1.60	£1.00	£1.00	£1.00	£0.50					

**TRIACS — Plastic TO-220 Package Isolated Tab**

	4A	6.5A	8.5A	10A	15A
100V	0.60	0.60	0.70	0.78	0.83
200V	0.64	0.64	0.75	0.87	0.97
400V	0.77	0.78	0.80	0.83	0.97
600V	0.96	0.99	1.		



# low cost ~ top quality COMPONENTS

Distributors for Plessey · Siemens ·  
A.E.G. Telefunken and Toshiba Components



### Diodes

Type	Price (p)	Type	Price (p)
BA115	10	OA90	7
BA145	18	OA95	6
BA148	18	OA202	11
BA154	12	IN60/OA91	7
BA155	15	IN914	6
BAX13	6	IN4001	6½
BAX16	10	IN4002	7
BY126	10½	IN4003	8
BY127	12	IN4004	8
BY133	17½	IN4005	9
BY199	25	IN4006	9½
BY206	17	IN4007	10
BYX10	16	IN4148	4½
QA47	8		

### Semi Conductors

Type	Price (p)	Type	Price (p)
AC107	25	AF115	27
AC126	20	AF116	27
AC127	20	AF117	27
AC128	15	AF118	65
AC128K	30	AF124	40
AC141	24	AF125	32
AC141K	34	AF126	38
AC142	20	AF127	42
AC142K	36	AF139	45
AC151	28	AF178	69
AC154	18	AF180	69
AC155	18	AF181	69
AC156	28	AF239	45
AC176	22	AF240	20
AC176K	34	AL102	£1.40
AC187	20	AL103	£1.30
AC187K	36	AU107	£1.50
AC188	25	AU110	£1.30
AC188K	38	AU113	£1.30
AC193K	36	BC107	14
AC194K	35	BC107B	16
AD140	69	BC108	14
AD142	75	BC109	14
AD143	65	BC109C	14
AD149	70	BC113	15
AD161	50	BC114	15
AD161/2	£1.00	BC115	17½
AD162	50	BC116	17½
AF114	27	BC116A	30

### Semi Conductors

Type	Price (p)	Type	Price (p)
BC117	14	BC237	12
BC118	15	BC238	12
BC119	27	BC301	30
BC125	17½	BC303	30
BC125B	18	BC327	13
BC126	16	BC328	13
BC132	15	BC337	12
BC135	20	BC338	12
BC136	16	BC546	13
BC137	25	BC547	12
BC138	33	BC548	12
BC139	28	BC549	13
BC140	32	BC550	14
BC141	28	BC557	13
BC142	25	BC558	12
BC143	28	BCY72	16
BC147	10	BD115	39
BC147A	11	BD116	65
BC147B	11	BD124	75
BC148	10	BD131/	
BC149	10	BD233	43
BC153	20	BD132	45
BC154	20	BD133	45
BC157	11	BD135	29
BC158	10	BD136	30
BC159	11	BD137	30
BC160	30	BD138	33
BC161	33	BD139	37
BC171	10	BD140	39
BC172	10	BD144	£1.99
BC173	15	BD160	£1.65
BC178	18	BD181	90
BC178B	20	BD182	90
BC179	24	BD183	80
BC182	11	BD184	£1.10
BC182L	12	BD222	50
BC183L	12	BD225	47
BC184	13	BD232	50
BC186	25	BD233	43
BC187	25	BD234	49
BC204	14	BD235	49
BC212	11	BD236	53
BC212L	12	BD237	49
BC213	12	BD238	55
BC213L	11	BDX32	£2.75
BC214	13	BDY20	80
BC214L	15		

### Semi Conductors

Type	Price (p)	Type	Price (p)
BF115	38	BFX88	25
BF123/		BFY50	20
T092	25	BFY51	30
BF152	20	BFY52	20
BF158	20	BFY90	£1.10
BF160	35	BR100	32
BF167	28	BR101	38
BF173	32	BRC4443	80
BF178	33	BRY39	38
BF179	38	BSY52	30
BF180	36	BT106	£1.20
BF181	36	BT108	£1.50
BF182	30	BT116	£1.25
BF183	30	BU105/02	£1.90
BF184	30	BU108	£2.10
BF185	30	BU126	£1.49
BF186	32	BU204	£1.80
BF194	10	BU205	£1.67
BF195	10	BU206	£2.10
BF196	10	BU208/02	£2.75
BF197	11	BUY69B	£2.50
BF197A/		BUY69A	£2.65
BF597A	17½	E1222	38
BF198	30	MJE340/	
BF199	25	BF459	48
BF200	30	MJE520	44
BF218	56	2N696	30
BF224	20	2N706	15
BF240	18	2N3053	20
BF241	18	2N3054	65
BF257	28	2N3055	60
BF258	30	2N3702	12
BF259	30	2N3703	12
BF336	37	2N3704	10
BF337	35	2N3705	10
BF338	34	2N3706	10
BF355	50	2N3819	38
BF457	37	2N5293	52
BF458	37	2N5294	52
BF459	48	2N5295	52
BFT42	36	2N5296	46½
BFT43	35	2N5297	52
BFX29	29	2N5298/	
BFX84	29	TIP31A	52
BFX85	30	2N5496	53
BFX86	28	OC71	29

### Semi Conductors

Type	Price (p)	Type	Price (p)
OC72	38	TIP32A	62
R2008B	£2.10	TIP41A	70
R2010B	£2.10	TIP42A	75
RCA16334	80	TIS91	27
RCA16335	80	2SC1172A	£2.73
S.2802	2.99	2SC643A	£1.48
S.6080A	£4.90	4.43MHZ	
TIP31A/		Crystal	£1.10
2N5298	52		

### Integrated Circuits

MC1349	£1.02	SN76660N	66
ML231B	£4.20	SN76666N	£1.10
ML232B	£4.20	TAA550	39
SL414A	£1.68	TAA570	£1.30
SL415A	£2.20	TAA661B	81
SL1310	£1.54	TAA700	£2.56
SL1327	97	TBA120AS	69
SL3046	73	TBA120SQ	£1.14
SL76544	£1.50	TBA440	£3.00
SN76003N	£2.45	TBA480Q	£1.40
SN76013N	£1.65	TBA520Q	£2.06
SN76013ND	£1.40	TBA530Q	£1.30
SN76023N	£1.65	TBA540Q	£2.00
SN76023ND	£1.40	TBA550Q	£2.56
SN76033N	£2.45	TBA560Q	£2.56
SN76110N	£1.75	TBA750Q	£1.43
SN76228N	£2.20	TBA800	£1.10
SN76227N	£1.65	TBA920Q	£2.64
SN76532N	£1.60	TBA990Q	£2.56
SN76533N	£1.60	TCA270Q	£2.64
SN76544N	£1.80	TCA800	£4.60
SN76650N	£1.50	TDA440	£3.00

### Toshiba

Type	Equivalent	Price
TA7050P	CA3044 RCA	£1.13
TA7051P	CA3042 RCA	£1.45
TA7072P	MC1351 Motorola	£1.53
TA7074P	MC1352 Motorola	£1.34
TA7141AP	MC1327 Motorola	£1.40
TA7171P	SAS560S Siemens	£1.65
TA7172P	SAS570S Siemens	£1.65
TA7173P	TCA270 Philips	£2.20
TA7176P	CA3065 RCA	£1.30



## COMBINED PRECISION COMPONENTS LTD.

Good people to deal with

C.P.C. Dept ERT 194 · 200 North Road, Preston, Lancashire, PR1 1YP, England.  
Phone Preston (STD 0772) 55034. Telex 677122. Cables 'Comprecom' Preston

WORLD WIDE EXPORT SERVICE ask for ROBIN PRATT

NEW PRICE LIST 1.3.77

# SEMICONDUCTORS - COMPONENTS

## TRIACS

2 Amp			TO5 Case			10 Amp			TO48 Case		
Volts	No.	Price	Volts	No.	Price	Volts	No.	Price	Volts	No.	Price
100	TR12A 100	£0.31	100	TR110A 100	£0.77	200	TR12A 200	£0.51	200	TR110A 200	£0.92
200	TR12A 200	£0.51	400	TR110A 400	£1.12	400	TR12A 400	£0.71			

6 Amp			TO66 Case			10 Amp			TO220 Case		
Volts	No.	Price	Volts	No.	Price	Volts	No.	Price	Volts	No.	Price
100	TR16A 100	£0.51	200	TR16A 200	£0.61	400	TR16A 400	£0.77			

## DIACS

BR100 £0.23 D32 £0.23

## SUPER UNTESTED PAKS

PAK No.	Description	Order No.	Price
U50	100 Germ. Gold bonded OA47 diode	16130	£0.60
U51	150 Germ. OA70 B1 diode	16131	£0.60
U52	100 Silicon Diodes 200mA OA200	16132	£0.60
U53	150 diodes 75mA 1N4148	16133	£0.60
U54	50 Sil Rect. Top Hat 750mA	16134	£0.60
U55	20 Sil Rect. Stud type 3 Amp	16135	£0.60
U56	50 400mW Zeners D07 Case	16136	£0.60
U57	30 NPN Trans BC107 B Plastic	16137	£0.60
U58	30 PNP Trans BC177 178 Plastic	16138	£0.60
U59	25 NPN TO39 2N697 2N1711 sil	16139	£0.60
U60	25 PNP TO59 2N2905 silicon	16140	£0.60
U61	30 NPN TO18 2N706 silicon	16141	£0.60
U62	25 NPN BY50 51	16142	£0.60
U63	30 NPN Plastic 2N3906 silicon	16143	£0.60
U64	30 PNP Plastic 2N3905 silicon	16144	£0.60
U65	30 Germ. 0071 PNP	16145	£0.60
U66	15 Plastic Power 2N3055 NPN	16146	£1.20
U67	10 TO3 Metal 2N3055 NPN	16147	£1.20
U68	20 Unijunction trans IS43	16148	£0.60
U69	10 1 amp SCR TO39	16149	£1.20
U70	8 3 amp SCR TO66 case	16150	£1.20

Code No's mentioned above are given as a guide to the type of device in the pak. The devices themselves are normally unmarked.

## COMPONENT PAKS

Pack No.	Qty.	Description	Order No.	Price
C1	200	Resistor mixed value approx (Count by weight)	16164	£0.60
C2	150	Capacitors mixed value approx (Count by weight)	16165	£0.60
C3	50	Precision resistors Mixed values	16166	£0.60
C4	80	1/8 W Resistors mixed preferred values	16167	£0.60
C5	5	Pieces assorted ferrite rods	16168	£0.60
C6	2	Tuning ganged MW 1W VHF	16169	£0.60
C7	1	Pack wire 50 metres assorted colours single strand	16170	£0.60
C8	10	Reed switches	16171	£0.60
C9	3	Micro switches	16172	£0.60
C10	15	Assorted pots	16173	£0.60
C11	5	Metal jack sockets 3 x 3.5mm 2 x standard switch types	16174	£0.60
C12	30	Paper condensers preferred types mixed values	16175	£0.60
C13	20	Electrolytics trans types	16176	£0.60
C14	1	Pack assorted hardware - Nuts bolts grommets etc	16177	£0.60
C15	5	Mainis slide switches ass	16178	£0.60
C16	20	Assorted tag strips and panels	16179	£0.60
C17	15	Assorted control knobs	16180	£0.60
C18	4	Rotary wave change switches	16181	£0.60
C19	2	Relays 6 - 24V operating	16182	£0.60
C20	1	Pak copper laminate approx 200 sq ins	16183	£0.60
C21	15	Assorted fuses 100mA-5 amp	16184	£0.60
C22	50	Metres PVC sleeving assorted size and colour	16185	£0.60
C23	60	1/2 watt resistors mixed preferred values	16186	£0.60
C24	25	Presets assorted type and value	16187	£0.60
C25	30	Metres stranded wire assorted colours	16188	£0.60

## SLIDER PAKS

Pack No.	Qty.	Description	Order No.	Price
S1	6	Slider potentiometers mixed values - 470pf 560pf 680pf 820pf	16190	£0.60
S2	6	Slider potentiometers all 470 ohms	16191	£0.60
S3	6	Slider potentiometers all 10k lin	16192	£0.60
S4	6	Slider potentiometers all 22k lin	16193	£0.60
S5	6	Slider potentiometers all 47k lin	16194	£0.60
S6	6	Slider potentiometers all 47k log	16195	£0.60

## CERAMIC PAKS

Containing a range of first quality miniature ceramic capacitors Unrepeatable value

Order No.	Price		
MC1	24 miniature ceramic capacitors 3 of each value - 22pf 27pf 33pf 39pf 47pf 68pf 82pf	16160	£0.60
MC2	24 miniature ceramic capacitors 3 of each value - 100pf 120pf 150pf 180pf 220pf 330pf & 390pf 270pf	16161	£0.60
MC3	24 miniature ceramic capacitors 3 of each value - 470pf 560pf 680pf 820pf 1000pf 1500pf 2200pf & 3300pf	16162	£0.60
MC4	24 miniature ceramic capacitors 3 of each value - 470pf 560pf 680pf 820pf 1000pf 1500pf 2200pf & 3300pf	16163	£0.60

## ORDERING

Please word your orders exactly as printed not forgetting to include our part number.

## V.A.T.

Add 12 1/2% to prices marked \*. Add 8 1/2% to others excepting those marked † these are Zero

## CARBON POTENTIOMETERS

SINGLE GANG with wire end terminations 6mm x 50mm plastic shaft 10mm bushes supplied with shake proof washer and nut. Tolerance ±20% of resistance.

### LINEAR TRACK

Value	No.	Price
1K	1831	£0.22
2K2	1832	£0.22
4K7	1833	£0.22
10K	1834	£0.22
22K	1835	£0.22
47K	1836	£0.22
100K	1837	£0.22
220K	1838	£0.22
470K	1839	£0.22
1M	1840	£0.22
2M2	1841	£0.22

### LOG TRACK

Value	No.	Price
4K7	1842	£0.22
10K	1843	£0.22
22K	1844	£0.22
47K	1845	£0.22
100K	1846	£0.22
220K	1847	£0.22
470K	1848	£0.22
1M	1849	£0.22
2M2	1850	£0.22

DUAL GANG These high quality pots are fitted with wire end terminations 6mm x 50mm plastic shaft 10mm bushes supplied with shakeproof washer and nut. Track tolerance ±20% but matched to within ±0.8 of each other.

### LINEAR TRACK

Value	No.	Price
4K7	1851	£0.68
10K	1852	£0.68
22K	1853	£0.68
47K	1854	£0.68
100K	1855	£0.68
220K	1856	£0.68
470K	1857	£0.68
1M	1858	£0.68
2M2	1859	£0.68

### LOG TRACK

Value	No.	Price
4K7	1860	£0.68
10K	1861	£0.68
22K	1862	£0.68
47K	1863	£0.68
100K	1864	£0.68
220K	1865	£0.68
470K	1866	£0.68
1M	1867	£0.68
2M2	1868	£0.68

SINGLE GANG SWITCHED. Fitted with double pole on/off switches. The switch action is incorporated within the rotary action of the pot. Switch rating 1.5 amps at 250V AC.

### LINEAR TRACK

Value	No.	Price
4K7	1870	£0.48
10K	1871	£0.48
22K	1872	£0.48
47K	1873	£0.48
100K	1874	£0.48
220K	1875	£0.48
470K	1876	£0.48
1M	1877	£0.48
2M2	1878	£0.48

### LOG TRACK

Value	No.	Price
4K7	1879	£0.48
10K	1880	£0.48
22K	1881	£0.48
47K	1882	£0.48
100K	1883	£0.48
220K	1884	£0.48
470K	1885	£0.48
1M	1886	£0.48
2M2	1887	£0.48

## VEROBOARDS

### DRILLED COPPER P.C.B.

.1 Pitch			.15 Pitch			
Size	No.	Price	Size	No.	Price	
2.5 x 5	2201	£0.46	2.5 x 17	2209	£1.13	
2.5 x 3.75	2202	£0.39	2.5 x 5	2210	£0.42	
2.5 x 17	2203	£1.42	2.5 x 3.75	2211	£0.31	
3.75 x 5	2204	£0.52	3.75 x 17	2212	£1.51	
3.75 x 3.75	2205	£0.45	3.75 x 5	2213	£0.57	
3.75 x 17	2206	£1.82	3.75 x 3.75	2214	£0.42	
4.75 x 17.9	2207	£2.34	2.5 x 1	(pack of five)	2216	£0.52
2.5 x 1	(pack of five)	2208	£0.57			

### DRILLED PLAIN P.C.B.

.1 Pitch			.15 Pitch		
Size	No.	Price	Size	No.	Price
3.75 x 17	2217	£1.18	2.5 x 17	2221	£0.78
3.75 x 2.5	2218	£0.26	3.75 x 17	2222	£1.00
5 x 3.75	2219	£0.42	2.5 x 5	2223	£0.26
			2.5 x 3.75	2224	£0.21
			5 x 3.75	2225	£0.36

### VERO SPOT-FACE CUTTER

Order No. 2231 Price £0.68

## PLUGS AND SOCKETS

### PLUGS

P1	Description	No.	Price
P1	DIN 3 pin 2 pin speaker	1689	£0.08
P2	DIN 3 pin	1690	£0.12
P3	DIN 4 pin	1691	£0.16
P4	DIN 5 pin 180	1692	£0.14
P5	DIN 5 pin 240	1693	£0.15
P6	DIN 6 pin	1694	£0.20
P7	DIN 7 pin	1695	£0.20
P8	Jack 2 5mm screened	1696	£0.12
P9	Jack Plug 4.5mm plastic	1697	£0.10
P10	Jack Plug 3.5mm screened	1698	£0.15
P11	Jack Plug mono plastic	1699	£0.14
P12	Jack Plug mono screened	16100	£0.28
P13	Jack Plug stereo screened	16101	£0.32
P14	Phono	16102	£0.10
P15	Car aerial	16103	£0.16
P16	Coax free TV	16104	£0.16
P17	Right angle jack	16105	£0.12
P18	Jack 2 5mm plastic	16106	£0.12
P19	Jack stereo plastic	16107	£0.20
P20	Phono free screened	16108	£0.14
P21	D.C. 2 pin plug	16109	£0.12
P22	D.C. 2 5mm plug	16110	£0.12
P23	2 pin AC plug U.S. type	16111	£0.18
P24	AM aerial	16112	£0.13
P25	Cassette mains plug	16113	£0.15
P26	FM 300 ohms plug	16114	£0.13

### CHASSIS SOCKETS

CS1	Description	No.	Price
CS1	DIN 3 pin loudspeaker	1652	£0.08
CS2	DIN 3 pin	1653	£0.10
CS3	DIN 4 pin	1654	£0.10
CS4	DIN 5 pin 180	1655	£0.12
CS5	Jack 6mm	1656	£0.06
CS6	Jack 4.5mm	1657	£0.06
CS7	Jack Mono-switched	1658	£0.15
CS8	Jack Stereo-switched	1659	£0.18
CS9	Phono single	1660	£0.08
CS10	Phono couple	1661	£0.10
CS11	Coax surface	1662	£0.21
CS12	Coax plug	1663	£0.25
CS13	Jack switched Mono	1664	£0.20
CS14	Jack socket DPDT switch	1665	£0.32
CS15	Car aerial	1666	£0.10
CS16	AC mains US type	1667	£0.16
CS17	Phono 4 way	1668	£0.16
CS18	D.C. power	1669	£0.18
CS19	AC switched	1670	£0.32
CS20	Phono 8 way	1671	£0.32

Just a selection from our huge stocks!

## SEE OUR 1977 CATALOGUE

126 pages packed with valuable information

ORDER NOW ONLY 50p

plus 15p p&p

## LINEAR PAKS

Manufacturers' Fall Outs which include Functional and part Functional Units. These are classed as out-of-spec from the makers very rigid specifications but are ideal for learning about I.C.s and experimental work.

### U721 30 ASSORTED LINEAR TYPES

709 741 747 748 710 588 Etc  
ORDER No 16227 Price £1.50

### U765D FM STEREO DECODER

5 I.C.s 75110 Ekv to MC1310P-MA767 Data supplied with pak  
ORDER No 16229 Price £4.50

### U76A AUDIO POWER OUTPUT AMPLIFIERS

8 Assorted types SL403 76013 76003 Etc Data supplied with pak  
ORDER No 16228 Price £1.00

## 74 SERIES PAKS

Manufacturers' Fall Outs which include Functional and part Functional Units. These are classed as out-of-spec from the maker's very rigid specifications but are ideal for learning about I.C.s and experimental work.

74G 100 Gates assorted 7400-01-04-10-50-60  
74F 50 Flip Flops assorted  
7470 72 73 74 76-104-109 Etc  
ORDER No 16225

74M 30 MSI Assorted Types 7441-47-90-154 Etc  
ORDER No 16226

## VEROBOARD PAKS

V81 Approx 30 sq ins various sizes all 1 matrix  
Order No 16199 £0.60  
V82 Approx 30 sq ins various sizes 15 matrix  
Order No 16200 £0.60

## ELECTROLYT

# BI-PAK

High quality modules for stereo, mono and other audio equipment.

**NEW**



**PUSH-BUTTON STEREO FM TUNER**


**OUR PRICE ONLY £20.45**

Fitted with Phase Lock-loop Decoder

- ★ FET Input Stage
- ★ VARI-CAP diode tuning
- ★ Switched AFC
- ★ Multi turn pre-sets
- ★ LED Stereo Indicator

The 450 Tuner provides instant program selection at the touch of a button ensuring accurate tuning of 4 pre-selected stations, any of which may be altered as often as you choose, by simply changing the settings of the pre-set controls. Used with your existing audio equipment or with the BI-KITS STEREO 30 or the MK60 Kit etc. Alternatively the PS12 can be used if no suitable supply is available, together with the Transformer T538. The S450 is supplied fully built, tested and aligned. The unit is easily installed using the simple instructions supplied.

**Typical Specification:**  
Sensitivity 3µ volts  
Stereo separation 30db  
Supply required 20-30v at 90 Ma max.

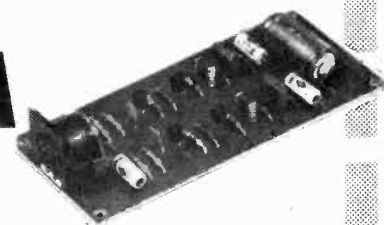

**MPA 30**

Enjoy the quality of a magnetic cartridge with your existing ceramic equipment using the new M.P.A. 30, a high quality pre-amplifier enabling magnetic cartridges to be used where facilities exist for the use of ceramic cartridges only. It is provided with a standard DIN input socket for ease of connection. Full instructions supplied.

**£2.85**

**STEREO PRE-AMPLIFIER**



**PA 100**

**OUR PRICE £13.75**

Frequency Response + 1dB 20Hz 20KHz. Sensitivity of inputs  
1 Tape Input 100mV into 100K ohms  
2 Radio Tuner 100mV into 100K ohms  
3 Magnetic P.U. 3mV into 50K ohms  
P.U. Input equalises to R1AA curve with 1dB from 20Hz to 20KHz  
Supply — 20-35V at 20mA

Dimensions 299mm x 89mm x 35mm.

**AL-20-30 AUDIO AMPLIFIER MODULES**

The AL20 and AL30 units are similar in their appearance and in their general specification. However, careful selection of the plastic power devices has resulted in a range of output powers from 5 to 10 watts R.M.S. The versatility of their design makes them ideal for use in record players, tape recorders, stereo amplifiers and cassette and cartridge tape players in the home.

**SPÉCIFICATION:**

- Harmonic Distortion  $P_o = 3$  watts  $f = 1$ KHz 02.5%
- Load Impedance 8-16ohm
- Size: 75mm x 63mm x 25mm
- Frequency response  $\pm 3$ dB  $P_o = 2$  watts 50Hz 25Hz
- Sensitivity for Rated O/P —  $V_s = 25$ v. RL = 8ohm  $f = 1$ KHz 75mV.RMS

**AL20 5w R.M.S. £2.95 AL30 10w R.M.S. £3.25**

**VAT ADD 12 1/2%**

**POSTAGE & PACKING**  
Postage & Packing add 25p unless otherwise shown. Add extra for airmail. Min. £1.00

**STEREO 30 COMPLETE AUDIO**



**7 + 7 WATTS R.M.S.**

**£16.25**

The Stereo 30 comprises a complete stereo pre-amplifier, power amplifiers and power supply. This, with only the addition of a transformer or overwind will produce a high quality audio unit suitable for use with a wide range of inputs i.e. high quality ceramic pick-up, stereo tuner, stereo tape deck etc. Simple to install, capable of producing really first class results, this unit is supplied with full instructions, black front panel knobs, main switch, fuse and fuse holder and universal mounting brackets enabling it to be installed in a record plinth, cabinets of your own construction or the cabinet available ideal for the beginner or the advanced constructor who requires Hi-Fi performance with a minimum of installation difficulty (can be installed in 30 mins).

**TRANSFORMER £2.45 plus 62p p & p**  
**TEAK CASE £5.25 plus 62p p & p**

**AL 60 25 Watts (RMS)**



- ★ Max Heat Sink temp 90C.
- ★ Frequency response 20Hz to 100KHz
- ★ Distortion better than 0.1 at 1KHz
- ★ Supply voltage 15-50v
- ★ Thermal Feedback
- ★ Latest Design Improvements
- ★ Load — 3,4,8, or 16 ohms
- ★ Signal to noise ratio 80db
- ★ Overall size 63mm. 105mm. 13mm.

Especially designed to a strict specification. Only the finest components have been used and the latest, solid-state circuitry incorporated in this powerful little amplifier which should satisfy the most critical A.F. enthusiast

**£4.35**

**NEW PA12**

NEW PA12 Stereo Pre-Amplifier completely redesigned for use with AL 20/30 Amplifier Modules. Features include on/off volume, Balance, Bass and Treble controls. Complete with tape output.

Frequency Response 20Hz-20KHz (-3dB). Bass and Treble range 12dB. Input Impedance 1 meg ohm. Input Sensitivity 300mV. Supply requirements 24V. 5mA. Size 152mm x 84mm x 33mm.

**£6.70**

**Stabilised Power Supply Type SPM80**

SPM80 is especially designed to power 2 of the AL60 Amplifiers, up to 15 watts (R.M.S.) per channel simultaneously. With the addition of the Mains Transformer BMT80, the unit will provide outputs of up to 1.5A at 35V. Size: 63mm. 105mm. 30mm. Incorporating short circuit protection.

**Transformer BMT80 £2.60 + 62p postage**

**£3.75**

**PS12** Power supply for AL20/30, PA12, SA450 etc.

Input voltage 15-20v A.C. Output voltage 22-30v D.C. Output current 800 mA Max. Size 60mm x 43mm x 26mm.

**OUR PRICE £1.30**

Transformer T538 £2.30

**BI-PAK**

P.O. BOX 6, WARE, HERTS.

SHOP AT 18 BALDOCK ST., WARE, HERTS  
OPEN 9 to 5.30 Mon. / Sat. Tel. 61593

**MARCONI NOISE GENERATOR  
TF987/1.**

4 Ranges 0-5, 0-10, 0-15, 0-30  
Due to large purchases now priced at **£15 ea.**

**COMPRESSOR/VACUUM  
PUMP**

Twin Cylinder opposed with Integral 1/2 H.P.  
50HZ Single Phase Motor Tested & Checked.  
110 Volts models only **£15 ea.**  
1/2 H.P. Motor 110V **£10 ea.**

**MARCONI TF675F WIDE  
RANGE PULSE GENERATOR**

+/- variable outputs up to 50V. Optional  
delay. Small compact unit **£18 ea.**

**SPOOLS OF 1/2" MAG  
TAPE  
APPROX. 2000ft  
50p ea. P&P £1 ea****AVO VALVE TESTER CT160  
"THE SUITCASE"**

Size approx. 15" wide x 10" high x 11" deep.  
Limited quantity **£25 each.**

**WE ARE BREAKING COMPUTERS**

UNIVAC/HONEYWELL/ICL 1900 etc.  
Boards, Power Supplies, Core Stores are available  
**CALL AND SEE**

**TEKTRONIX OSCILLOSCOPE Type 561A**

Complete with 3BI Time Base &  
3AI Dual Trace Amplifier  
**£375 each**

**THE HONEYWELL KEYSPE UNIT**

is a multi-channel Keyboard to Magnetic Tape System recording Keyboard entered data on 1/2" tape in 80 or 120 character records in a form easily usable as a computer input/output and verifier. 240 Volt operation.

From the simple to understand electro mechanical / vacuum system to the +15 -15 +5 Power Supply and hinged wire wrapped card frame. The flexibility and reliability are outstanding. This coupled with the ease of interfacing to a VDU, Mini/Micro computer, etc. make all the Honeywell Keytapes on offer very fine value.

Honeywell Keypate Unit, checked, tested with Manual **£215 ea.**

As above but less data boards. Tested forward / backward tape movement and control, etc. Data entry / exit via read / write boards. **£105 ea.**

Exactly as above but less keyboard and table **£80 ea.**

All units carriage paid.

KEYBOARDS also available at **£20 each**. Carr. **£2.50**

**TEKTRONIX OSCILLOSCOPE Type 506**

Complete with 3BI Time Base &  
9AI Dual Trace Amplifier **£450 each.**

**TEKTRONIX OSCILLOSCOPE** Type 585A with type 82 plug-in **£500.**  
**RHODE & SCHWARZ GENERATOR** BN41022 300-1000MHZ **£185.**  
**R&S DIAGRAPH & GENERATOR** 3-300MHZ. Very nice condition **£475.**  
**RHODE & SCHWARZ ADMITTANCE METER** BN3511. As new **£65.**  
**POLARAD RECEIVER** Model FIM B2. Complete 1-10GHZ **£425.**  
**TELONIC SWEEPER** 2000.1 with LA-1M 20HZ-20KHZ **£120.** Other freq. available.  
**MARCONI OSCILLATOR** TF1101 20HZ-20KHZ. Nice condition. Special price **£50.**  
**MARCONI Wide Range Oscillator** TF1370. Freq. range 10HZ to 10MHZ. Sine Wave. 10HZ to 100KHZ. Square Wave. High outputs up to 31.6V. Fantastic value at **£90 ea.**  
**MARCONI Generator** TF867 15KHZ to 30MHZ **£60 ea.**  
**MARCONI ADAPTOR** TM6113 for TF2700, TF1313, TF868B **£20 ea.**  
**AIRMEC** 4 trace scope Type 279. Large screen **£120.**  
**MARCONI TF142F DISTORTION FACTOR METER** giving percentage distortion on a directly calibrated dial and includes all spurious components up to 30KHZ **£32.50 ea.**  
**AVO TRANSISTOR ANALYSER** CT446 **£30 ea.**  
**MARCONI PORTABLE FREQUENCY METER** TF1026/11. 100 to 160MHZ. Very fine condition. **£27.50 ea.**  
**DECCA NAVIGATOR DISPLAY UNIT.** Very impressive **£12.50 ea.**  
**COURTENAY MAJOR Mk. 2.** 250 joules. 5 outputs. Can be combined — 1250 joules. No heads. **£40 ea.**  
**MARCONI SIGNAL GENERATORS.** TF801B from **£140**; TF801D from **£190.** Usually available ex stock.  
**MARCONI DEVIATION METER.** TF791D **£75 ea.**  
**RHODE & SCHWARZ POWER METER.** BNRD-BN2412/50 **£50.**  
**MARCONI RF POWER METER.** TF1020A/1 50 ohms **£65.**  
**HEWLETT PACKARD** 11 Channel Numerical Printer **£30.**  
**MARCONI 20MHZ SWEEP GENERATOR.** TF1099 **£45.**  
**MARCONI DOUBLE PULSE GENERATOR.** TF1400S with TM6600/S **£20.**  
**MARCONI TRAVELLING WAVE TUBE AMPLIFIER.** TF1278 **£15.**  
**I.C. TESTER** by SCHLUMBERGER. Model TCL232 — tests 741, 709 etc. Dual in lines. Flat packs or TO's **£65 each.**  
**AIRMEC Generator** type 304A 50KHZ to 100MHZ **£120.**  
**AIRMEC MODULATION METER** 210 **£130.**

**TELEQUIPMENT OSCILLOSCOPE.** Type S32. Very good condition. Small, compact size 7 x 9 x 1.4in approx. Ideal for colour TV servicing. Superbly reliable. FANTASTIC VALUE at **£85 ea.**

**HILGER & WATTS SPECTROMETER** H1170 **£350.**  
**RHODE & SCHWARZ 10 KWatt Power Meter** **£120.**  
**RHODE & SCHWARZ** Tunable Indicating Amplifier UBM **£75.**  
**TEKTRONIX** 180A Time Marker Generator **£60.**

OUR PRICES TOO HIGH? — THEN MAKE US AN OFFER WE CAN CONSIDER

S.E. Labs Oscilloscope type 102 **£220.**

**MARCONI UHF-SHF** Signal Generator Type TF1058 **£80.**

**TEKTRONIX 181** Time Marker Generator **£40.**

**TELONIC** Sweeper 0-200MHZ **£80.**

**HEWLETT PACKARD** Oscilloscope type 175 DC-50MHZ Double Beam **£180** with delay amplifier **£220.**

**GENERAL RADIO PULSE SWEEP & Time Delay Generator** type 1391B **£120.**

**ROYAL INVERTORS** manufactured USA. 28V DC Input. Output 115V AC 400HZ up to 2KVA. Brand new. Crated **£12.50 ea.**

**SPECTRUM ANALYSER** by NELSON ROSS. Plug-in for TEKTRONIX 561/506 Oscilloscopes **£225.**

**SOLARTRON** CD1212 SB 40 meg **£85.** DB24meg. twice. **£120.** Many other types available.

**EX-MINISTRY OSCILLOSCOPE.** CT436 Double beam DC-6MHZ **£95 each.**

**\*TELEPHONES.** Post Office style 746. Black or two-tone grey **£6.50 ea.** Modern style 706. Black or two-tone grey **£4.50 ea.** P&P 75p ea. Old black style **£1.50 ea.** P&P 75p.

**TELEPHONE EXCHANGES.** eg 15-way automatic (exchange only) from **£95.**

**MODERN FANS.** 4 1/4 x 4 3/4 x 1 1/2". 240 Volts. Superbly quiet. 6 Blades **£4.50 ea.** P&P 75p.

**PAPST** model 240V available at **£7.50 ea.** P&P 75p.

**PHOTOMULTIPLIER** Type 931A **£4 ea.** P&P 75p. Other types available.

**\*POTENTIOMETERS** — All **5p ea.** P&P extra. Metal bodied AB Linear. PCB Mount. Brand New. 10K, 100K ganged. 250K ganged. 100K ganged, concentric shafts.

**\*BEEHIVE TRIMMERS** 3/30pt. Brand New. 10 off **40p** P&P 15p. 100 off **£3.50** P&P 75p. 500 off **£15** P&P £1.25. 1,000 off **£25** P&P £1.50.

**LARGE RANGE ELECTROSTATIC VOLTMETERS.** From 0-300V 2" **£3.** to 20KV Max. General guide 5KV 3 1/2" **£5.** Thereafter **£1 per KV.** P&P 75p.

**VARIACS** 240V input 0-240V output 8A **£18 ea.** 20A **£30 ea.** Carr. **£2.50**

**E.H.T. TRANSFORMERS** 20KV 2KVA **£70 ea.** Many other EHT transformers and EHT Capacitors available.

**DON'T FORGET YOUR MANUALS.** S.A.E. with requirements.

**TUBE** type DB7/36 — Replacement for Telequipment S31 **£11 ea.** P&P **£1.50.**

**FOR THE VDU BUILDER.** New stock of Large Rectangular Screen 30 x 20cm tube Type M38 at the ridiculous price of **£4 ea.** And also still available the CME1220. 24 x 15cm at **£9 ea.** Base connections for both tubes supplies.

**SEMICONDUCTORS** — All at **5p ea.** P&P extra. Guaranteed all full spec. devices. Manufacturer's markings.  
BC147. BC158. 2N3707. BC107. BF197. BC327. 2N4403. BC172B. BC261B. BC251B. BC348B. 8C171A/B. 2N3055RCA **50p ea.** P&P Bp.  
2N5879 with 2N5881 Motorola 150 Watt. Comp. pair **£2 pr.** P&P 15p.  
\*Linear Amp 709 **25p ea.** P&P Bp.

**CREED 5-LEVEL COMBINED PRINTER AND PERFORATOR CRATED £35 each**

**CREED 5-LEVEL  
PAPER TAPE READER £25 each**

**CREED 7B  
TELEPRINTER CRATED £40 each**

**SPECIAL OFFER**  
**CREED 7B TELEPRINTER LATE MODEL WITH PERFORATOR, £60 ea.**  
**FREE WITH ALL PURCHASES PLESSEY READER**

Minimum Mail Order £2. Excess postage refunded. Unless stated — please add **£2.50** carriage to all units  
**VALUE ADDED TAX** not included in prices — Goods marked with \* 12 1/2 % VAT, otherwise 8 %  
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order  
Open 9 a.m. to 5.30 p.m., Mon. to Sat.



**CHILTMHEAD LTD**



7/9 ARTHUR ROAD, READING, BERKS. (rear Tech. College, King's Road). Tel. Reading 582605



# Strobes, Tachos, Meters, Generators and Telecommunications Test Equipment

E. B. import and distribute high-grade products from World-renowned British & Overseas Manufacturers.

## NEW FUNCTION GENERATORS!



G430 provides Sine-wave (0-10Vrms) and Square-wave (0-20V p-p) from 600Ω, continuously variable, via 4-position 0-60dB, push-button operated step attenuator. Frequency range 1Hz to 1MHz.

**£95**

Send for details of our complete range



## NEW PULSE GENERATOR Model 70 (illustrated above)


Compact, low-cost pulse and square-wave generator, featuring

- P. R. F. 4Hz to 400kHz, gated or free-running
- O/P 10V peak from 50Ω, also synch. O/P.
- Pulse width 1 μSec to 100mSec.
- Delay 1 μSec to 100mSec.
- Pulse mark / space inversion.
- TTL/CMOS HI LO gating facility

**£89**
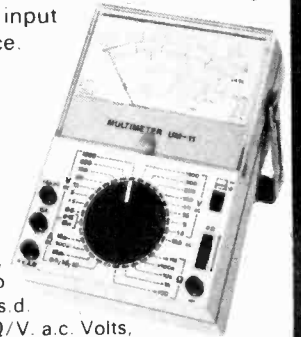
## NEW WIDE-RANGE MULTIMETER UM-11


Features 38-colour-coded ranges with high input impedance.



d.c. Volts, 150mV to 1500V f.s.d. at 100kΩ/V. a.c. Volts, 1.5V to 1500V f.s.d. at 31.6kΩ/v. d.c. Current, 10μA to 15A. a.c. Current 15A. Other star features include mirror-scale, rugged taut band suspension, dB scale, diode and fuse protection.

Supplied complete with test-leads and leather carrying case.

**£39.50**

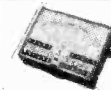

See inside back cover for details of ICE Super range of multimeters!


Add 8% VAT to all prices shown. Carriage extra details on request



**ELECTRONIC BROKERS LIMITED (New Products Division)**  
49-53 Pancras Road, London NW1 2QB. Tel: 01-837 7781

Callers welcome—Monday to Friday 9 a.m. to 5 p.m.

WW—103 FOR FURTHER DETAILS

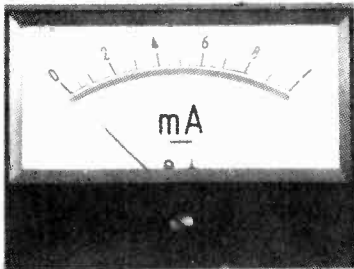

MODEL SU

## What more could you ask for?

We are confident you can't do better

than to incorporate ALPS Panel Meters in your next project whether it be Original Equipment Manufacture, Educational or the Replacement of an Existing Instrument.

- ★ SUPERB QUALITY AND SCALE PRODUCTION
- ★ ATTRACTIVE MODERN STYLING
- ★ EX STOCK DELIVERY FOR STANDARD RANGES
- ★ RAPID PROTOTYPE SERVICE
- ★ PRODUCTION FOR SPECIAL REQUIREMENTS
- ★ REASONABLE DELIVERY OF PRODUCTION QUANTITIES

available as:— True VU METERS  
DC MICROAMMETERS AC & DC VOLTMETERS  
AC & DC MILLIAMMETERS AC & DC AMMETERS

**SERVO AUTOTESTERS:**—A range of four types of instrument to measure auto/mobile currents and voltages dwell angle engine speed, etc.

Details from:—

**SERVO AND ELECTRONIC SALES LTD.**

Tel. LYDD 20252

24 HIGH STREET, LYDD, KENT TN29 9AJ TLX 965265



WW — 090 FOR FURTHER DETAILS

# New! from sanwa

## THE MULTIMETER TO MAKE YOUR TESTER OBSOLETE!

The fabulous LCD900 incorporates a liquid crystal display only of the range to which the meter is switched.

- 7 DC voltage ranges ±1-1000V at 50K Ω/V
- 5 AC voltage ranges 10-1000V at 10K Ω/V
- 4 DC current ranges ±0.3-300mA
- 1 AC current range 3A
- 4 resistance ranges 1K-1000K
- Basic movement 17.5μA



**PRICE**  
**£58.25**  
**(+ £1 P&P)**  
**exc. VAT**

Also shortly available the **VS-100 ultra-safe industrial tester.**

For full details on these and 24 other standard instruments in the **sanwa** range contact.

**QUALITY ELECTRONICS LTD.**

24 High Street, Lydd, Kent TN29 9AJ

Tel. Lydd (0679) 20252, TLX 965265

WW — 091 FOR FURTHER DETAILS





SINTEL for PCBs — KITS — CASES — MPUs — BOOKS — MEMORIES Components from leading manufacturers only

HIGH QUALITY KITS

CRYSTAL CONTROLLED 6 DIGIT CAR CLOCK WITH INDEPENDENT JOURNEY-TIMER. Shows time or elapsed time in hrs mins secs... Order as CCK £38.00

CMOS AND OTHER COMPONENTS

Table listing various CMOS components like CD4000, CD4001, CD4002, etc. with prices.

A FREE CATALOGUE requested by post or phone will be sent by return with details of our range of CASES • BOOKS • DISPLAYS • MPUs • MPU KITS • MEMORIES and other components not listed here, with same day despatch for goods in stock.

MEMORIES

TTL COMPATIBLE STATIC RAMS

Table listing TTL compatible static RAMs like 4K STATIC RAM, 1024 x 4 bit, etc. with prices.

USEFUL PRINTED CIRCUIT BOARDS

Table listing useful printed circuit boards like DISPLAY HOLDING PCBs, DISPLAY PCBs WIRED FOR MULTIPLEXING, etc. with prices.

Our offices are at Link Property, 209 Cowley Road, Oxford, but please do not use this as a postal address.

FAST SERVICE We guarantee that Telephone Orders for goods in stock, received by 4.15 p.m. (Mon-Fri) will be despatched the same day by 1st Class Post...

ORDERS Add VAT at 8% + 25p p&p. Phone orders see FAST SERVICE. Export orders welcome. No VAT but add 10% (Europe), 15% (Overseas) for Air Mail p&p. For export postage rates on heavy items — contact us first.

SEND YOUR ORDER TO SINTEL P.O. BOX 75C, OXFORD Tel. 0865 49791

Get a great deal from Marshall's

A. Marshall (London) Ltd Dept: WW 40-42 Cricklewood Broadway, London NW2 3ET Tel: 01-452 0161/2 Telex: 21492 & 85 West Regent St Glasgow G2 2QD Tel: 041-332 4133 & 1 Straits Parade Fishponds Bristol BS16 2LX Tel: 0272 654201/2 Call in and see us 9-5.30 Mon-Fri 9-5.00 Sat Trade and export enquiries welcome. Please enquire for types not listed NEW 168 PAGE CATALOGUE WITH 500 NEW LINES 55p post paid (40p to callers)

Our range covers over 7,000 items. The largest selection in Britain. Top 200 ICs, TTL, CMOS & Linears

Large table listing various ICs and components with prices, including CA3020A, LM382N, NE555, etc.

POPULAR SEMICONDUCTORS (A very small selection from our vast stocks, please enquire about devices not listed.)

Table listing popular semiconductors like 2N696, 2N3053, 2N4058, etc. with prices.

SEND FOR OUR NEW 168 PAGE CATALOGUE WITH 500 NEW LINES 55p post paid or 40p to callers

Prices correct at 8th February 1977, but please add V.A.T. Post & Packing 30p SEE US AT THE ALL ELECTRONIC SHOW — GROSVENOR HOUSE 19-21 APRIL

### SIGNAL SOURCES

**ADVANCE**  
VHF Square wave Generator SG21 10 KHz-100MHz Max o.p. 2V £35  
H1 Audio Signal Generator 15Hz-50KHz Sine and Square £35.00  
E2 R.F. Signal Generator 10KHz-100MHz £76.00

**H1E Audio Signal Generator. Sine & Square Wave 15Hz-50KHz, 200 V<sub>o</sub> 20V (Sine) Distortion 1% 1.4mV 140V (square). Brand new condition £70.00**

**AIRMEC**  
Signal Generator Type 701 30 KHz 30 MHz (2 only) £75.00

**GENERAL RADIO**  
Unit Oscillator 1209C. Freq. 250-920MHz Accuracy 1% Drift 0.2% O pin 50ohms = 150mW supplied with Power Supply Type 1201-CQ £145

**HEWLETT PACKARD**  
10515A Frequency Doubler Extends the useable frequency range of signal generators. Operating on input frequencies 0.5MHz to 500MHz it provides a doubled output in the range of 1MHz to 1GHz. The frequency response of this 50 ohm device is very flat ( $\pm 2dB$  typically) over the entire frequency range and undesired harmonics are well suppressed. Brand 211A Square Wave Generator 1Hz-1MHz £75.00  
F.M. A.M. Signal Generator 202H F.M. A.M. CW & pulse coverage 54 to 216 MHz R.F. o.p. 0.1-1.0 V<sub>o</sub> 2V 50ohms Impedance £450  
Audio Signal Generator 206A 20Hz-20KHz accuracy Distortion  $\pm 1\%$  £90  
612A U.H.F. Signal Generator 450-1230MHz 0.1-1.0 V<sub>o</sub> 50 (50 ohms) A.M. internal & external Pulse mod facilities. SUPERB CONDITION £1250.00

**MARCONI INSTRUMENTS**  
TF1050 U.H.F. Signal Generator 450-1250MHz. Sine wave and pulse a.m. £350.00  
TF867 Signal Generator 15KHz-30MHz 0 p. volts 0.4-1V.4V £185.00  
TF2005R Two Tone Source. The instrument comprises two identical low distortion a.f. oscillators and a monitored attenuator unit to form a compact test set for the measurement of inter-modulation distortion using the methods recommended by S.M.P.T.E. and C.C.T.F. Frequency range 20Hz to 20KHz in six bands (each oscillator can be adjusted and used independently). Harmonic distortion Less than 0.05% between 63Hz and 6KHz when using unbalanced output. Generally less than 0.1% under other conditions. Intermodulation Below -80dB with respect to the wanted signal. Amplitude Reference Level Up to +10dBm from each oscillator. Output attenuator 11dB in 0.1dB steps. Output impedance 600 $\Omega$  unbalanced or 600 $\Omega$  (150 $\Omega$ ) or 75 $\Omega$  balanced and centre-tapped. £485.00

S.H.F. Signal Generator 618C 2.8-7.6GHz 1-1.50 ohms £500  
F.M. A.M. Signal Generator TF 995A/3S Ministry type No. CT402 1.5MHz-220MHz R.F. o.p. 2-1V.200mV Internal & External Mod. Facilities. V. good condition £395  
F.M. A.M. Signal Generator TF995A 5 1.5-220MHz in 5 bands 0.1-1V.200mV F.M. up to -120KHz from 50Hz-15KHz A.M. up to 50% from 100Hz-10KHz o.p. (1) 2-1V.200mV (2) with terminating unit 1-1V.100mV Int. mod. fregs. 400Hz 1KHz & 1.5KHz Distortion (1) on internal F.M. -25Hz (2) on internal A.M. 6% at 30% mod. £300 to £450  
A.M. Signal Generator TF801D 1 Freq. range 10-470MHz R.F. output 0.1-1V. Piston attenuator. 50ohms Impedance. Modulation Int. A.M. 1KHz Ext. A.M. 30Hz-20KHz. Low spurious F.M. & drift V.S.W.R. 1.2 or less £400-£800  
A.M. Signal Generator TF801D 1S Military version. 10-485MHz £450-£800  
R.C. Oscillator TF1370A 10Hz-10MHz Square Wave up to 100KHz High Outputs up to 31.6V £285  
Phase A.M. Signal Generator TF 2100 0.4-12MHz £150  
A.M. Signal Generator TF 801B 3S 12-485MHz 0.1-1V.1V £195  
R.C. Oscillator TF1101 Frequency range, 20Hz-200KHz Output Direct into 600 $\Omega$  20V variable Attenuator 0.6dB in 10dB steps Impedance 600 $\Omega$  Distortion Via 1KHz Filter less than 0.1% Direct or via Attenuator Less than 0.5% 50Hz-20KHz Less than 1% 20Hz-200KHz £120-£150  
F.M. A.M. Signal Generator TF937 1 CT320 15KHz-18.3MHz As seen condition £80  
Signal Generator TF144H 4 Late models in superb condition £500 to £650  
TF995B 2 F.M. A.M. Signal Generator. Freq. range 200KHz-220MHz Output 200mV to 0.1-1V F.M. normal deviation Continuously variable in 2 ranges -25KHz & 75KHz up to 50% Ext. A.M. & F.M. available £585.00

**MARCONI-SANDERS**  
Microwave Sweep Generator type 6600A c.w. 6619 plug in 1.7GHz-4.2GHz £2900.00  
**MURHEAD L.F.** Decade Oscillator DB80A 2 phase 0.01Hz-11.2KHz £295  
Decade Oscillator DB90D 1Hz-11.2KHz £260  
**NEUWIRTH (WEST GERMANY)**  
VHF Signal Generator MS4 U.F. Freq. Range 9.6MHz to 230MHz Turret Osc. for each band Accuracy 1.2% o.p. 30mV-1.1V Freq. Dev. 1KHz-100KHz Amp. Mod. 0-100% £175.00

**PHILIPS**  
PM 5167 Function Generator. Sine triangle square positive pulse negative pulse and ramp. 9.1 to 9.0001 Hz to 10MHz (sawtooth and pulse up to max. 1MHz) Output 40V(P.P.I) Impedance 50 ohms Variable DC Offset External sweep Single shot set phase Hold function Overrange warning light Superb condition £615.00  
PM5501 Colour bar generator. Extremely light and compact instrument for mobile maintenance 5 different test patterns for colour and black white TV

Electronic Brokers Ltd. are one of the leading electronic instrumentation companies in the UK, providing a full range of services to Universities, Industry, Colleges and Governments both at home and overseas.

We have the largest stocks of secondhand test equipment in Europe as well as a selected range of new products. These are on display at our London showrooms where customers can examine the equipment of their choice and see it working.

Electronic Brokers Ltd. have fully equipped workshops on the premises to test and report on the majority of equipment we sell.



## WRITE NOW...

for a FREE copy of our latest Test Equipment Catalogue. Please apply on headed paper.

installation and service. R.F. output signal switchable VHF Band III and UHF Band IV. 1KHz tone for sound performance checks (sine wave) £165.00  
50MHz Pulse Generator PM5712 £435.00  
Pulse Generator PM5775 £800.00  
Pulse Generator PM5776 £900.00

**PHILIPS PM5324 HF Signal Generator. Freq. range 100KH-110MHz. Crystal calibration. Special band spread ranges. High freq. stability. Electronically stabilised output max. 50mV(RMS) in 75 ohms. 100mW open circuit. Calibrated output attenuator. Facilities for internal and external A.M. & F.M. Wobblulating with sweep width control. Simultaneous A.M. & F.M. Superb condition £295**


**SANBERS**  
CT478 Microwave Signal Generator 1.5GHz-4.5GHz £285.00  
**RADIOMETER**  
Stereo signal generator SMG1C Full spec. on request. Superb condition £350  
**RHODE & SCHWARTZ**  
S.H.F. generator SMCB-BN 41042 1700-5000MHz P.O.A.  
**WAYNE KERR**  
Video Oscillator O 222 7KHz-8KHz in 6 ranges £75  
**WANDEL & GOLTERMAN**  
U.H.F. Power Oscillator LMS 68 c.w. plug-in Oscillators:  
Type LO.4 4-41MHz  
Type LO.40 40-108MHz  
Type LO 170 170-330MHz  
Type LO 610 610-960MHz

### MULTIMETERS

**AVO**  
Test Leads £4.00  
Multimeter Mk 4 c.w. carrying case & leads £13.50

### OSCILLOSCOPES

**COSSOR**  
35MHz Plug-in Scope Type 3100 5mV cm sensitivity Calibrated sweep delay Gated Trigger 8 x 10cm display BRAND NEW CONDITION £355

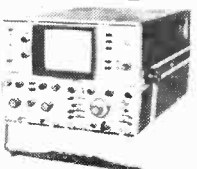

**Cossor 3100**

**DYNAMCO**  
Type 7200 15MHz Dual Channel Portable c.w. Plug Ins 7201 & 7212 Solid State 10mV/div to 5V/div X10 on channel 1 permits 1mV/div to 12.5V/div Calibrated Sweep Delay c.w. batt pack £310.00

**GREENPAR**  
Probe Kits GE81600/1 - New £25.00

**HEWLETT PACKARD**  
75MHz Model 1707A £675.00  
175A 50MHz Oscilloscope c.w. Plug-ins 1750B Dual Trace Vert. Amp. 50mV cm 1780A Auxiliary Plug-in £295.00  
185B 1000 MHz Oscilloscope Sampling c.w. Plug-in 186A or Plug-in 187C £395.00

1707B Transistorised 75MHz Superb condition £1350.00

**PHILIPS**  
10MHz Portable double scope PM3226 £380.00

**SOLARTRON**  
Portable Scope DC-6MHz Double Beam CT436 £95  
Portable Scope CD 140DC-15MHz Plug ins available CX1441 1443 1445 1571 £180  
DC-40MHz Scope CT484 Dual Trace Displays. Sensitivity 50mV cm Collection from our premises only 90-day Warranty £150.00

**TEKTRONIX**  
Sampling Scope 661 c.w. plug ins £450  
Scope Camera C-12 Superb cond. & complete £190.00

50MHz Model 546 c/w 1A1 plug-in £635.00  
Spectrum Analyser plug-in 1L5 50Hz-1MHz £675.00  
50MHz Model 547 c/w 1A1 plug-in £695.00

TV Waveform Monitor 525 Freq. response Flat within 1% between 60Hz & 5MHz Low Pass - Passes start steps eliminates H.F. High Pass - Passes H.F. eliminates start steps IRE - meets IRE standards for level measurements Sensitivity - Deflection factor of the vertical amplifier is 0.015V cm Vert. Atten - 1 x 2 x 5 x Keyed Clamp type DC Restorer Gain stability within 1% Differential Unit 10A1 Used on 647 Series £125

585 c.w. Type 82 Plug-in Dual Trace 80MHz B width Sweep Delay £675. Other plug-ins available 80 and 86

Transistor Curve Tracer 575 Displays curves of NPN & PNP transistors and dynamic characteristics of a wide range of semiconductor devices. P.O.A.

Dual Beam Scope 551 2 vertical deflection systems. Accepts Amp. Spec. analyser. Sampling and special purpose Plug-ins DC-27MHz. Price dependent on plug-ins required. P.O.A.

531A DC-15MHz Oscilloscope c.w. K Plug-in Single Trace 50mV cm £195.00

531A 15MHz Oscilloscope c.w. CA Plug-in Dual Trace 50mV cm £210.00

544 DC-50MHz Oscilloscope c.w. 1A1 Plug-in (1 trace) £600.00

544 DC-50MHz Oscilloscope c.w. CA Plug-in Dual Trace 24MHz 50mV cm £375.00

549 Storage Oscilloscope (Mainframe) £610.00

**TELEQUIPMENT**  
D75 50MHz Solid State Portable 5mV 20V/div £515

**WANDEL & GOLTERMAN**  
BLS 21B Storage Oscilloscope c.w. Power Supply £325.00

**PROBES (New)**  
X1 Part No. 90 £6.50  
X10 Part No. 91 £8.50  
X1 & X10 (switchable) Part No. 95 £10.50

**MISCELLANEOUS**

**ADVANCE**  
Frequency Counter TC16 £110.00  
Recorder Calibrator HC20 £15  
X-Y Plotter LR100 - Further details on request

Digital Panel Meter DPM302 (new) £325.00  
Digital Panel Meter DPM301 (new) £45.00  
£50.00

**AIRMEC**  
Time Interval Meter 369 Mains operated transistorised unit. Time Intervals 100nsecs to 30msecs. Superb condition £95.00

**BECKMAN**  
Transfer Oscillator 7580H DC 15GHz with counter 7.5MHz-15GHz without counter. Sensitivity 100mV (R.M.S.) SPECIAL OFFER £250

**B & K**  
Impedance Bridge 1504 P.O.A.

**BIRD**  
Coaxial Resistor 8053 10W 10V coaxial load resistor £20.00

Wattmeter Termaline 6835 3 ranges 0-120 0-600 0-1200W 30-500MHz £425.00

Wattmeter Termaline 67 3 ranges 0-25 0-100 0-500W 30-50MHz £265.00

**B.P.L.**  
Component Comparator CZ457 5 P.O.A.

**BRUEL & KJAER**  
Automatic Vibration Exciter Control 1018 £395.00

**DECCA**  
Power Supply for Noise Source MW 61 P.O.A.

**ELDORADO**  
10mS Time meter 784 £475.00

**FLUKE**  
Industrial Counter Totaliser 1941A Freq. Measurement 5Hz-40MHz 40mV sensitivity. Totalise measurements to 999999 units. Presettable display. RPM measurement £150.00

**HEWLETT PACKARD**  
Digital Recorder 560A £110  
Digital Recorder 561B £140  
Directional detector 787D 1.9-4.1GHz £90  
Directional detector 788C 3.7-8.3GHz £95  
UHF Attenuator 355C £90

**ELECTRONIC**

**the test**

# ELECTRONIC

49-53 Pancras Road  
London NW1 2QB  
Tel: 01-837 7781

ADD 8% VAT TO ALL PRICES



**BROKERS LTD**  
**equipment people**

On these pages you will find just the briefest selection from the vast range which we hold in stock at any one time.

If you are seeking a specific item and it is not listed, it will pay you to ring us first — we believe we offer the best prices and the best service.


**WORLD WIDE EXPORT**

Enquiries and tenders welcome from any part of the world.

**HOW TO REACH US . . .**

We are easy to reach, no matter where you live. Minutes away from Kings Cross or St. Pancras main-line stations, and a bus ride from Euston; only just over half an hour from Heathrow Airport.

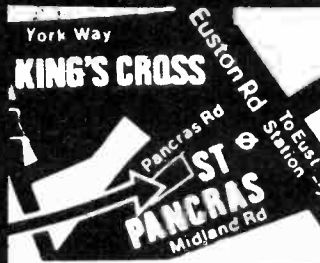49-53  
 Pancras Rd  
 London  
 NW1 2QB  
 Telephone:  
 01-837 7781



- Electronic Voltmeter TF2604 £225.00
- Voltmeter No. 3 CT 208 TF 958 AC 100mV-150V multiplier extends AC range to 1.5KV DC 50mV-100V Freq Range 20Hz-100MHz £55
- Valve Voltmeter TF2600 £175
- PHILIPS**
- MF Millivoltmeter GM 6014 Measuring Ranges 1mV-200mV in 6 ranges Accuracy at 20KHz at 3% of FSD = Amplitude Char 1KHz 30KHz fat within ±5% £55
- DC Microvoltmeter GM6020 10µV-1KV current 10pA-10µA Accuracy 5% (FSD) 0.100µV 3% (FSD) AU other ranges Recorder o/p facility £65

**TELEPHONE TEST EQUIPMENT**

- SIEMENS**
- Level Meter 3D 332 0.3-1200KHz £250
- Level Meter 3D 335 10KHz-17MHz £300
- Level Oscillator 3W29 0.3-1200KHz £250
- Level Oscillator 3W518 £300

**BRIDGES**

- MARCONI INST.**
- TF936 Impedance Bridge £125.00
- Universal Bridge TF1313A £525
- LCR Bridge TF 8688 £115.00
- TF1245 CCT Magn Meter c/w Oscillator £685.00
- WAYNE KERR**
- Radio Freq Bridge B601 £95
- R F Admittance Bridge B701 £85
- COMPONENT BRIDGE B521 (CT 375)**
- Self-contained portable mains operated equipment designed to provide accurate measurements over an extremely wide range of resistance, capacitance, inductance and impedance values. Resistance 10 ranges from 1m ohm to 1000 M ohm Capacitance 10 ranges from 50kµF to 500pF Inductance 10 ranges from 1µH to 500 KH Capable of measuring components in situ £105.00

**TRANSMISSION TEST EQUIPMENT**

- AIRMEC/RACAL**
- Wave Analyser 248A 5-300MHz £250 to £300
- Wave Analyser 24B Freq range 5MHz-300MHz £145.00
- Modulation Meter 409 P.O.A.
- Type 210 Modulation Meter (earlier version of 210A) £85-£100
- Type 210A Modulation Meter 2.5-300 MHz A.M. Range 0-100% F.M. Range 0 to ± 100 KHz in 4 ranges £185-£245
- HEWLETT PACKARD**
- Sweeping Local Oscillator 3595A Plug-in for use with 3590A Wave Analyser Freq range 20Hz to 620KHz £650.00
- MARCONI INSTS.**
- Distortion Factor Meter TF 142F Fundamental Freq Range 100Hz-8KHz Dist measuring ranges 0.5% to 0.50% Measures all spurious components up to 30KHz £85
- Attenuator 70dB in 10dB & 1dB steps O/p Z = 75 150 & 600 ohms balanced or unbalanced Distortion

- 0.1% Level Meter Measurements +25 to 70dBm Full Spec on Request £400.00
- A.F. TRANSMISSION MEASURING SET, Model TF2332** Frequency Range 20Hz to 20KHz Accuracy ±1% ±0.2Hz Max output at least +15 dBm £400.00
- RADIOMETER**
- Wave Analyser FRA 2 T3 Special version of FRA 2 with facilities for intermodulation measurements and selective measurements of frequency responses Freq range 30Hz to 16KHz Incremental freq. 0Hz to ±60Hz Selectivity 3 curves with following 1dB points = 1.25Hz ± 12.5Hz ± 63Hz and 60dB points ± 40Hz = 130 Hz = 350 Hz = 150 Hz = 450 Hz
- Voltage range 100µV - 1KV Auxiliary Oscillator Range 0Hz to 1.6 KHz and 1.5 to 1.6KHz o/p - 10V (EMF) continuously variable Impedance 1 Kohms 16µF £375.00
- WANDEL & GOLTERMAN**
- Level Transmitter TFFS 42 10 KHz 14MHz Generator 0 p level 0.8mV-2.5V FSO Lowest adjustable 50µV Synchronous tuning of generator and level meter possible Output impedance 150, 75, 70, 60, 50 and ohms ±25KHz Fine Tuning range £250.00
- Level Meter TFFM - 43 10KHz-14MHz 3dB Bandwidth (600Hz and 4KHz) Selective measuring range 8V to 40µV (lowest readable 2µV) Switchable bandwidth ± 15KHz fine tuning High sensitivity Full specification for the above on request £250.00
- Distortion Meter VZM 83 52/304/556 kHz This unit comprises a generator and receive portion and operates according to the intermodulation method This distortion measuring set is mainly used to measure transmission distortions occurring on FM radio link systems £190.00
- VZM2 Distortion measuring set for phase and amplitude mod For multichannel FM Radio Systems up to 12MHz base bands £350

**DIGITAL VOLTMETERS AND MULTIMETERS**

- DYNAMCO**
- DVM DM 2022S 10µV-2KV Max reading 39999 Accuracy 0.02% Resolution 1 in 40,000 Input impedance 25Kohms £265.00
- Digital Voltmeter DM 2023 C/w DC Ranging unit C1 Scale 99999 0.001% F.S.O DC Accuracy 10µV-1Kv DC £450.00
- D.V.M DM 2004 P.O.A.
- J. FLUKE**
- Digital Multimeter 8120A Measures AC and DC volts to 1200 volts AC and DC current to 12A Resistance to 12Mohm, 4 digit plus 20% overage Compact and lightweight £235.00
- HEWLETT PACKARD**
- DVM type 3430A 3 digit, 5 ranges 100mV to 100V F.S. Input resistance 10Mohms Overload protection £145.00

Digital Multimeter 34702A with Display 34740A 4 digit display, 4 ranges both AC & DC plus 6 ranges of ohms AC function covers 45Hz to 100KHz Ohms ranges are 100ohms to 10Mohms F.S. LED display, New condition. A much sought after device still in current production £400

- PHILIPS**
- D.M.M. TYPE PM2423 3 1/2 digit, DC Volts 2V-1 KV AC VOLTS 2V-350V R=200 M-ohms Accuracy 0.1% of reading Automatic range switching for all functions. Automatic polarity indicator £140.00
- D.M.M. TYPE PM2522, 3 1/2 digit DC Volts 0.2-1KV, AC Volts 0.2-600 V AC/OC Current 0.2mA-2A R = 200 ohms - 20 M ohms Accuracy 0.1% ± 0.1% of range DC Volts Full circuit protection. LED display £150.00
- SIGN/ROGERS**
- A.F. Voltmeter AM324 £50.00
- SOLARTRON**
- A.C. Converter LM1219 30mV-300V mean reading Freq range 10Hz-10KHz P.O.A.
- D.C. Digital Voltmeter LM1420 2.25µV-1KV in 6 ranges 0.05% DC accuracy £235.00
- D.V.M. Type LM1420 2BA DC true R.M.S. and mean AC sensing Accurate measurement irrespective of harmonic distortion accuracy ±0.25% Freq. 40Hz-20KHz £325
- DVM Type LM 1440 2 10µV-2KV DC in 5 ranges Over controlled zeroize Accuracy ±0.033% FSD ±0.005% reading P.O.A.
- D.V.M LM1480 3 Autorangeing version of LM 1440 3 Max reading 39999 5µV-2KV DC Full spec on request P.O.A.
- D.V.M LM 1604 DC only 1µV sensitivity 0.01% accuracy Max reading 19999 1µV-1KV Remote and Autorangeing 110dB series mode reject on No common Mode error P.O.A.
- D.M.M 7050 (autorangeing) £245.00
- VIDAR**
- Integrating D.V.M 520 6 ranges 10mV-1KV Guarded can be floated to ±500V High measurement speed with ultimate C.M.R. No filters Up to X6 faster than most integrating D.V.M's Built-in calibrator Manual, automatic and remote operation Wideband Freq and period measurements are standard 10mV F.S. range built-in eliminates ext pre-amp, no loss of C.M.R. Freq range 10Hz-2MHz £525.00

**REMEMBER . . . We also buy**  
 We are interested in providing quotations for the purchase of good quality used and unused Test Equipment.



**POWER SUPPLIES**

- APT ELECTRONICS**  
 (Ex ICL Computers) 240V I/P
- Type 10459/11 - ±10V 7.5A £18.00
- Type 10459/8 - ±20V 5A £12.00
- Type 10459/13 - ±24V 5A £12.00
- Type 10459/12 - ±10V 3A £15.00
- I.B.M.**
- Ex Computer Load regulation of 1% or better Low ripple, fast response time 220/240V I/P
- 3V - 4V £12.00
- 3V - 8A £15.00
- 3V - 16A £20.00
- 6V - 6A £15.00
- 112/115V I/P
- 6V - 12A £15.00
- 20V - 15A £20.00
- Also stabilised but unregulated 48V - 2.7A, 7.25V 4 BA £8.50
- ICL Power Supplies (ex computer)
- 6V-25A (variable from 4.5V to 8V)
- 28V-20A (variable from 25-30V)

**VOLTMETERS**

- ADVANCE**
- VM77D AC Millivoltmeter £50.00
- GENERAL RADIO**
- Electronic Voltmeter 1806A AC, DC & OHMS ±2% Accuracy Wide freq. Range up to 1500 MHz £200.00
- HEWLETT PACKARD**
- DC Vacuum Tube Voltmeter 412A 1mV-1000V 1% Accuracy. Can also be used as Ohmmeter and Ammeter. £75
- ICL Power Supplies (ex computer)
- VTVM 400D 1mV to 300V FSO 12 ranges 10Hz to 4MHz 2% accuracy Input Impedance 10Mohms £85
- VTVM 400L Logarithmic version of 400D Reads RMS value of sine wave Log voltage scale 0.3 to 1 & 0.8 to 3 Linear dB scale Input Impedance 10Mohms £90
- Vacuum Tube Voltmeter 400H Freq Range 10Hz-4MHz Volts 10mV-300V F.S. (12 ranges) Accuracy ±1% (50Hz-500KHz) ±2% (20Hz-1MHz) P.O.A.
- AC Voltmeter 400F & 400E £155
- MARCONI**
- Sensitive Valve Voltmeter TF 1100 100µV-300V AC Freq coverage 10Hz-10MHz Meter has dB scale facility £85
- Valve Voltmeter TF 1041B General Spec 0-300V AC 0-1KV DC Resistance up to 500Mohms £60/£95

- HOUSTON**
- XY Omnicographic Recorder type 6520 P.O.A.
- XY & XYY Omnicographic Recorder type 6452 P.O.A.
- MARCONI INSTS.**
- Attenuator TF 1073A/2S £85
- Quantization Distortion Tester TF2343 P.O.A.
- Probe Kit TM8120/1x1 for use with valve voltmeter TF2600 Brand new £20
- A.F. Power Meter TF893A 20Hz-20KHz 1mW to 10 Watts F.S. Z = 2.5 ohms to 20Kohms in 48 Steps £150.00
- Q Meter TF 329G £200
- Out of Limits Indicator TF 24D4/2M1 Checks readings from electronic counters and other digital insts. Local and remote visual and electrical indication suitable for use by unskilled personnel and with A.T.E. P.O.A.
- Blank & Sync Mixer TF 2908 £90
- PYE**
- Thermocouple test set 7556 £95
- RHODE & SCHWARTZ**
- Polyscop Swob II £1000
- Selektomat USVV £836.00
- Frequency Indicator FKN-BN 47051 £476
- TEKTRONIX**
- Programmer 262 P.O.A.
- Sq Wave Gen 105 Risetim - 13m secs Freq range - 25Hz-1MHz continuously variable Freq Meter - Direct reading O/P Amplitude 0-100V max £90
- TELEONIC**
- Band Pass Filter: TBA 140 60.5CCI 5 Section TNC to INC connectors 1/2" tubular 60MHz bandwidth 140MHz centre freq. Brand new £20
- Sweep Generator Sm2000 c/w plug-ins 8-3M and S.6 and S4MM P.O.A.
- WAYNE KERR**
- Current Ratio Transformer T102C P.O.A.

**BROKERS LTD**

Carriage and packing charge extra on all items unless otherwise stated

Please note: All instruments offered are secondhand and tested and guaranteed 12 months unless otherwise stated



# TRAMPUS ELECTRONICS LTD

58-60 GROVE RD.  
WINDSOR, BERKS.  
SL4 1HS.  
TEL. 54525

ADD 8% VAT TO PRICES MARKED \*  
ADD 12% TO ALL OTHER PRICES.  
OR AS CURRENT VAT LEGISLATION  
SEND C.W.O. (EXCEPT GOVT DEPT)  
POST & PACKING 20P FOR THE U.K.  
BARCLAYCARD & ACCESS BY POST  
OR 45 MIN ON TELEPHONE ORDERS.  
NEW CATALOGUE 1.1ST FREE S.A.E.  
MONEY BACK IF NOT SATISFIED.

## FAST SERVICE



NORMALLY 24 HOURS  
ON EX STOCK ITEMS



SEVEN SEGMENT LED DISPLAYS  
BRIGHT DL707 (COM ANODE) &  
DL701 COM CATH. 0.3" x 1"  
DL717 0.6" x 0.6" x 1.25"

DIGITAL CLOCK IC 51224 £4\*  
ZENON STROBE TUBES £4 & 7\*

## RED LEADS 10P.

RED LEADS 209 STYL 0.125"  
OR 0.2" DIA. NO CLIP 10P\*

TIL209 RED LED & CLIP 12p\*  
BIG 0.2" RED LED " 14p\*  
GREEN OR ORANGE LEADS 29p\*  
ORP12 54p\* 2X5777/OC771 34p\*

TRAMPUS  
THE GREAT  
BRITISH  
DISTRIBUTOR



INDUSTRIAL, EDUCATIONAL, TRADE &  
EXPORT SUPPLIED. SEND FOR  
OUR FREE CATALOGUE LIST SAE  
MANUFACTURERS EXCESS STOCKS  
PURCHASED. DISCOUNTS 10% OFF  
100 sp. 15% OFF 1000 sp. ....

## TOP DISCOUNTS.

### INTEGRATED CIRCUITS

555 TIMER	34p*	LM3800 (C) 44	£1
556 2 x 555	90p*	LM381 Preamp	£2
703 RF/IF AMP	29p	LM3900 4xOPA	53p*
709 T099 or DIL26p		NC1303 2xPre	£2
710 DILL1	35p*	NC1310 stereo	£2
723 Regulator	14p*	NC1312P SQ	£1.70p
711 DIL Rpin	21p*	NC1330	75p
711 DIL Lipin	31p*	NC1339 Preamps	2
714 T099	33p*	MFC4000B 1W	72p
717 DUAL 711	69p*	MFC6030	£1
718 DIL 8 pin	32p*	NE536 FETOPA	£2*
7805 5V1A+reg	£1.35*	NE540 or 550	£2*
7812 & 7815ea	£1.40*	NE555 TIMER	34p*
76013 6W AF	£1.50	NE556 2x555	90p*
AY51224 CLOCK	£4*	NE560 1/2/2.5/6/7/13	
CA3016	54p*	SN72711 AF	74p
ICL8038 Sigen	£4*	SN76611 IF	£1
LM300H	£1*	TBA800 5W AF	81p
LM301A DIL 8	33p*	TBA810 7W AF	94p
LM309K 5V reg	£2*	ZN411 Radio	£1.10
LM309H T05 can	£1*	NEW 1466/69	£1
LM318 70VusOPA	£3*		

## CMOS TTL

4000 14p*	7400 12p*	7490 39p*
4001 15p*	7401 13p*	7491 75p*
4002 16p*	7402 15p*	7492/93 45p*
4007 16p*	7404 10p*	7495/96 72p*
4009 30p*	7408/10 18p*	74100 £1.25*
4011 16p*	7413 29p*	74107 32p*
4012 17p*	7416 16p*	74121 29p*
4049 50p*	7411 71p*	74123 69p*
1069 20p*	7412 72p*	74111 71p*
4501 26p*	7447 79p*	74145 85p*
4511 £1.65*	7470/72 27p*	74147 £2.50*
1528 £1*	7173/74 31p*	74151 75p*
1543 £2*	7475/36 35p*	74151 £1.40*
4553 £5*	7186 33p*	74196 £1.50*

DIL SOCKETS PROFESSIONAL QUALITY  
8pin, 14pin & 16pin ALL 12p ea \*  
SOLDERCONS 100 49p\* 1000 £3.95\*

## NEW LOW PRICES.

### TRANSISTORS AND DIODES

1YS BUSH SET 1p ea*	TIP31/32 50p*
MATCHING 20p Pr*	TIP31c32c68p*
AC127/8 176 15p*	TIP41/42ea 66p*
AD161/162 ea36p*	TIP41c2c11 £1.50*
BC107 8p*	TIP2955 69p*
BC107B 13p*	TIP3055 65p*
BC108 8p*	TIS43 UJT 26p*
BC108B or C 13p*	1N914/1118 4p*
BC109 9p*	1N4001/2 4p*
BC109B or C 12p*	1N4004 5p*
BC147/8/9 8p*	1N4007 7p*
BC157/8/9 11p*	2N706/8 14p*
BC167/8/9 12p*	2N2616 UJT 40p*
BC177/8/9 16p*	2N2904/5pnnp29p*
BC182/3/4/7/10p	2N2926 ory 7p*
BC212/3/4/7/12p	2N3053 17p*
HCY70/1/2 15p*	2N3055 90p 33p*
BC213/132ea 36p*	2N3055 115w45p*
BFY50/51 13p*	2N3614 T03 £1*
BFY52/53 16p*	2N3702/3/1 10p*
BSX 19/20/21/19p*	2N3705/6/7 9p*
BZY88 ZENER 10p	2N3708/9 9p*
C106D SCR 54p*	2N3710/11 15p*
MJ2955 T03 99p*	2N3819 £23e17p
MJE2955 99p*	2N3820 PEF410p
MJE3055 65p*	2N3904/5/6 15p
OA81/91 3p	2N5457 FIT 32p
TIP29 & 30 40p*	BRIDG1A50 20p*

## BARGAIN PAKS FULL SPEC 11ea.

PAK A: 11 RED LEADS full spec £1*
PAK B: 5 711C 8 PIN OP AMP £1*
PAK C: 1 2N3055 £1 + D 12 BC109 £1*
PAK E: 1 BC182 £1 F 11 2N3701 £1
PAK G: 7 BFY51 £1 H 8 2N3819 £1
PAK J: 6 2N3053 £1 K 10X1N911 £1
PAK M: 2 T099 3055 £1 N 25 OA91 £1
PAK P: 20 PLASTIC BC109 TYPnpn £1

10-365PF TUNER SINGLE GANG FOR  
MED/SHORT WAVE. XTAL SET etc £1\*  
SETTS/IF CANS 455/470KHZ TOKO £1\*

## Full spec devices

# DALO pen 75p

PCB ETCH KIT 3 ITEMS £2\*  
ETCH RESIST PEN 2TIPS 75p\*  
ETCH PAK TIB 600mg £1\*  
6x1 SRBP 45p\* NYLON F/GU1  
SCR AND TRIACS BR100 25p\*  
TAG 1A400V 50p\* 1A600V 69p\*  
1A50V 37p\* C106D 1A400 60p\*  
TRIACS SC146D 10A400V £1\*  
DISCO TRIAC 15A400V £2\*  
AUDIBLE WARNING BLEEPER  
12V35mA 1.1.20.10 off £1\*  
CAPACITORS 22pf - .01 5p  
ELECTROLYTIC 1N 10 & 35V  
1/2/10/50/100 7p 50V 10p  
200/500 10p, 1000/25 20p  
POTENTIOMETERS AB etc 20p  
PRESENTS 6p CHRISTMAS 2p  
HEATSHINK T05 or 16 7p  
T03 10p, T03 15p, Finned 50p  
DIN PLUGS all 15p, Sock 10p  
SWITCHES SPST 20p Dpdt 29p

## vero

VERO 0.1" PITCH COPPERCLAD  
24 X31 10p\* 31 X50 14p\*  
24 X31 30p\* 31 X50 30p\*  
31 X17 1/2" FACE CUTTER 65p\*  
DIL BREADBOARD 2x4 £1 or  
6x4 £2. VERO PINS 36 30p\*

BLACK PLASTIC CASES 42mm  
80x60 50p\* 100x75 60p\* 90x  
120 70p. DESOLDER BRAID 50p

# AMATEUR COMPONENTS

ORCHARD WORKS, CHURCH LANE, WALLINGTON, SURREY SM6 7NF

MAIL ORDER DIVISION OF SEMICONDUCTOR SUPPLIES (CROYDON) LTD.

For Semiconductors Capacitors Resistors I/C Sockets L.E.D.'s and


## Hi-Fi Accessories

AC125 20	BC108B 12	BC173 15	BC121L 15	BC307A 16	BCY58 22	BF257 30	BU133 1.95	TIP31A 57
AC126 20	BC108C 13	BC173A 16	BC212LA 15	BC307B 16	BCY70 17	BF258 40	BU205 2.00	TIP31B 64
AC127 20	BC109 13	BC173B 16	BC212LB 15	BC307C 16	BCY71 18	BF259 42	BU206 2.30	TIP31C 79
AC127K 30	BC109B 13	BC173C 16	BC213 12	BC308 16	BCY72 14	BF274 34	BU208 2.45	TIP32 60
AC128 28	BC109C 14	BC174 16	BC213A 12	BC308A 14	BCY73 14	BF274 34	BU209 2.45	TIP32A 67
AC128K 26	BC113 12	BC177 17	BC213B 12	BC308B 14	BCY74 14	BF274 34	BU210 2.45	TIP32B 76
AC132 35	BC114 15	BC177A 17	BC213C 12	BC308C 15	BCY75 14	BF274 34	BU211 2.45	TIP32C 94
AC141 20	BC115 15	BC177B 17	BC213D 12	BC308D 15	BCY76 14	BF274 34	BU212 2.45	TIP33 84
AC141K 30	BC116 15	BC178 17	BC213E 12	BC308E 15	BCY77 14	BF274 34	BU213 2.45	TIP33A 94
AC142 20	BC116A 15	BC178A 17	BC213F 12	BC308F 15	BCY78 14	BF274 34	BU214 2.45	TIP33B 105
AC142K 25	BC117 15	BC178B 17	BC213G 12	BC308G 15	BCY79 14	BF274 34	BU215 2.45	TIP33C 111
AC151 24	BC118 15	BC178C 17	BC213H 12	BC308H 15	BCY80 14	BF274 34	BU216 2.45	TIP34 100
AC151K 34	BC119 28	BC179 18	BC213I 12	BC308I 15	BCY81 14	BF274 34	BU217 2.45	TIP34A 116
AC153 27	BC125 16	BC179B 18	BC213J 12	BC308J 15	BCY82 14	BF274 34	BU218 2.45	TIP34B 123
AC153K 37	BC126 20	BC179C 19	BC213K 12	BC308K 15	BCY83 14	BF274 34	BU219 2.45	TIP34C 129
AC176 22	BC128 25	BC179D 19	BC213L 12	BC308L 15	BCY84 14	BF274 34	BU220 2.45	TIP35 127
AC176K 28	BC132 14	BC179E 19	BC213M 12	BC308M 15	BCY85 14	BF274 34	BU221 2.45	TIP35A 127
AC187 22	BC134 14	BC180 18	BC213N 12	BC308N 15	BCY86 14	BF274 34	BU222 2.45	TIP35B 127
AC187K 27	BC135 14	BC182 18	BC213O 12	BC308O 15	BCY87 14	BF274 34	BU223 2.45	TIP35C 120
AC188 20	BC136 16	BC182A 18	BC213P 12	BC308P 15	BCY88 14	BF274 34	BU224 2.45	TIP36 80
AC188K 27	BC137 16	BC182B 18	BC213Q 12	BC308Q 15	BCY89 14	BF274 34	BU225 2.45	TIP36A 302
AD149 20	BC138 28	BC182C 18	BC213R 12	BC308R 15	BCY90 14	BF274 34	BU226 2.45	TIP36B 363
AD161 92	BC139 35	BC182D 18	BC213S 12	BC308S 15	BCY91 14	BF274 34	BU227 2.45	TIP36C 410
AD162 62	BC140 30	BC182E 18	BC213T 12	BC308T 15	BCY92 14	BF274 34	BU228 2.45	TIP37 60
AF114 24	BC141 22	BC182F 18	BC213U 12	BC308U 15	BCY93 14	BF274 34	BU229 2.45	TIP37A 60
AF115 24	BC142 22	BC182G 18	BC213V 12	BC308V 15	BCY94 14	BF274 34	BU230 2.45	TIP37B 60
AF116 24	BC143 28	BC182H 18	BC213W 12	BC308W 15	BCY95 14	BF274 34	BU231 2.45	TIP37C 60
AF117 24	BC147 20	BC182I 18	BC213X 12	BC308X 15	BCY96 14	BF274 34	BU232 2.45	TIP37D 60
AF118 70	BC147A 11	BC182J 18	BC213Y 12	BC308Y 15	BCY97 14	BF274 34	BU233 2.45	TIP37E 60
AF124 30	BC147B 11	BC182K 18	BC213Z 12	BC308Z 15	BCY98 14	BF274 34	BU234 2.45	TIP37F 60
AF125 30	BC148 08	BC182L 18	BC213AA 12	BC308AA 15	BCY99 14	BF274 34	BU235 2.45	TIP37G 60
AF126 28	BC148A 09	BC182M 18	BC213AB 12	BC308AB 15	BCY100 14	BF274 34	BU236 2.45	TIP37H 60
AF127 28	BC148B 09	BC182N 18	BC213AC 12	BC308AC 15	BCY101 14	BF274 34	BU237 2.45	TIP37I 60
AF139 34	BC148C 09	BC182O 18	BC213AD 12	BC308AD 15	BCY102 14	BF274 34	BU238 2.45	TIP37J 60
AF178 20	BC149 10	BC182P 18	BC213AE 12	BC308AE 15	BCY103 14	BF274 34	BU239 2.45	TIP37K 60
AF179 120	BC149B 12	BC182Q 18	BC213AF 12	BC308AF 15	BCY104 14	BF274 34	BU240 2.45	TIP37L 60
AF180 120	BC149C 12	BC182R 18	BC213AG 12	BC308AG 15	BCY105 14	BF274 34	BU241 2.45	TIP37M 60
AF181 20	BC153 18	BC200 18	BC213AH 12	BC308AH 15	BCY106 14	BF274 34	BU242 2.45	TIP37N 60
AF186 120	BC154 18	BC204A 18	BC213AI 12	BC308AI 15	BCY107 14	BF274 34	BU243 2.45	TIP37O 60
AF239 37	BC157 11	BC204B 18	BC213AJ 12	BC308AJ 15	BCY108 14	BF274 34	BU244 2.45	TIP37P 60
ASV26 40	BC157A 12	BC205 14	BC213AK 12	BC308AK 15	BCY109 14	BF274 34	BU245 2.45	TIP37Q 60
ASV27 45	BC158 12	BC205A 15	BC213AL 12	BC308AL 15	BCY110 14	BF274 34	BU246 2.45	TIP37R 60
ASV28 45	BC158B 12	BC205B 15	BC213AM 12	BC308AM 15	BCY111 14	BF274 34	BU247 2.45	TIP37S 60
ASV29 45	BC158A 11	BC205C 15	BC213AN 12	BC308AN 15	BCY112 14	BF274 34	BU248 2.45	TIP37T 60
ASV67 140	BC158B 11	BC206 15	BC213AO 12	BC308AO 15	BCY113 14	BF274 34	BU249 2.45	TIP37U 60
ASZ21 200	BC159 12	BC206B 15	BC213AP 12	BC308AP 15	BCY114 14	BF274 34	BU250 2.45	TIP37V 60
BA145 15	BC159B 13	BC207 11	BC213AQ 12	BC308AQ 15	BCY115 14	BF274 34	BU251 2.45	TIP37W 60
BA148 15	BC159C 13	BC207B 11	BC213AR 12	BC308AR 15	BCY116 14	BF274 34	BU252 2.45	TIP37X 60
BA154 10	BC167 15	BC208 11	BC213AS 12	BC308AS 15	BCY117 14	BF274 34	BU253 2.45	TIP37Y 60
BA155 12	BC168 13	BC208B 11	BC213AT 12	BC308AT 15	BCY118 14	BF274 34	BU254 2.45	TIP37Z 60
BA156 13	BC169 14	BC208A 11	BC213AU 12	BC308AU 15	BCY119 14	BF274 34	BU255 2.45	TIP38 60
BAX12 11	BC170 11	BC208B 11	BC213AV 12	BC308AV 15	BCY120 14	BF274 34	BU256 2.45	TIP38A 60
BAX13 07	BC171 14	BC209 12	BC213AW 12	BC308AW 15	BCY121 14	BF274 34	BU257 2.45	TIP38B 60
BAX16 07	BC171A 14	BC209B 12	BC213AX 12	BC308AX 15	BCY122 14	BF274 34	BU258 2.45	TIP38C 60
BC107 12	BC171B 15	BC209C 13	BC213AY 12	BC308AY 15	BCY123 14	BF274 34	BU259 2.45	TIP38D 60
BC107A 12	BC172 15	BC212A 13	BC213AZ 12	BC308AZ 15	BCY124 14	BF274 34	BU26	



# ELECTRONIC DIGITAL CLOCK

**From this . . .** **KIT** **— to this**

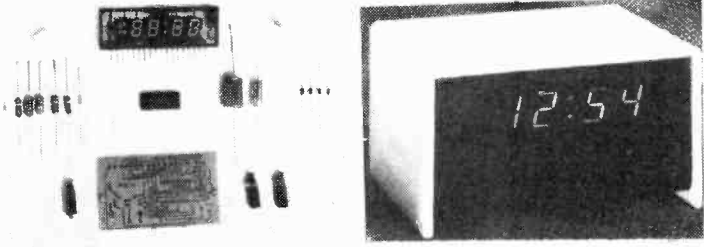

Size 10.5 x 5.7 x 8 cms

**SAME DAY DISPATCH**  
ORDERS RECEIVED BEFORE 2 p.m. are posted on the same day.

A professional product for the home constructor. It has been designed by engineers using the most modern techniques and components. It will appeal both to the confirmed hobbyist and to the man who simply wants to 'have a go'. The kit contains everything except a mains lead. The only tools required are a small soldering iron, solder, screwdriver and wire cutters.

- ★ LARGE BRIGHT GREEN DISPLAY
- ★ ATTRACTIVE ACRYLIC CASE
- ★ 12/24-HOUR READOUT

**£9.60** + 76 Pence VAT

**METAC — Electronics & Time Centre**

67 HIGH ST., DAVENTRY, NORTHANTS  
TEL. DAVENTRY (032 72) 76545  
OR 3 THE NEW ARCADE, UXBRIDGE, MIDDX.  
TEL. UXBRIDGE (0895) 56961


Cash, Cheques or Postal Orders, Barclay & Access  
welcome. Just send Credit Card number.

**WW—104 FOR FURTHER DETAILS**

## THE REAL THING

**PPM2 DRIVE CIRCUIT UNDER LICENCE FROM THE BBC WITH HIGH QUALITY Ernest Turner SPECIAL BALLISTICS PEAK PROGRAMME METER MOVEMENT**

PPM2 is based on the ME 12 9 but with an electronic floating input which withstands mains or static voltages on the signal lines. It meets BS4297, the proposed revision of BS4297, the proposed IEC Type 2 meter specifications and fulfills the requirements of the IBA, EBU and BPO. Reviewed Studio Sound September 1976. Meter movements 642, 643 and 1WIN from stock. The 1WIN is a flush mounting type and flush mounting add-ons which allow illumination are available for the 642 and 643. NEW illumination kits for 642 and 643 mouldings to support a 38mm festoon bulb.



### PEAK DEVIATION METER

For monitoring mono or stereo FM stations either off air or at the transmitter. This is a rack mounting unit calibrated in KHz, percent and decibels including a 7.5KHz deviation standard with 400Hz and 53KHz modulating frequencies, and a high impedance probe head for use with a monitor receiver. During programme monitoring the true peak multiplex deviation with a very fast attack time meter gives much more insight into modulation levels and limiter overshoots than spectrum analyser displays or standard programme meters showing the decoded stereo signals. Chart recorder addition available in June.

**SURREY ELECTRONICS**  
The Forge, Lucka Green, Cranleigh, Surrey GU6 7BG (STD 04866) 5997

# Wilkinsons RELAYS

**B.P.O. TYPE 3000 AND 600**



Built to your own specifications and requirements. The best known of all relays with a large variety of contact arrangements. Known throughout the world. Complete banks of contacts made to order and component parts supplied. Highest quality at competitive prices with a quick delivery service. Quotations by return home and overseas. Twin relays. Latching Relays and Relays with high voltage contacts made to order. We are suppliers of mountings to house B.P.O. Type 3000 Relays and associated components B.P.O. Uniselectors, Relay sets and Relay Selector units B.P.O. 2000 and 4000 type.

**APPARATUS RACKS**, POST OFFICE STANDARD 7FT HIGH WITH U-CANNEL SIDES DRILLED FOR 19 INCH PANELS. HEAVY ANGLE BASE. P.O. STANDARD LIGHT STRAW COLOUR. **£25 EACH.**

**HIGH SPEED COUNTER** 10 counts per second with four digits size 3 1/2" x 1" available in the following DC voltages 6, 12, 24, 50 or 100 volts **£1.75 each**, also available with five digits **£2.75 each.**

**BLOWER UNIT** with glass fibre air filter and directional duct. 200, 250 volts or 100/125 volts **£15 each.**

**ELLIOTT Test Set** reading absolute DC volts with mirror scale **£20 each.**

**AVOMETER** Power Factor and wattage unit **£10 each.**

**BRIDGE MEGGER** 1 000 volts with resistance box **£95 each.**

**L. WILKINSON (CROYDON) LTD., LONGLEY HOUSE, LONGLEY ROAD, CROYDON, CRO 3LH**  
Phone: 01-684 0236. Grams: WILCO CROYDON

**WW—109 FOR FURTHER DETAILS**

**NEW! AMERICAN STYLE CRADLE TELEPHONE AMPLIFIER**



**ONLY £13.95**  
+ VAT £1.12

Latest transistorised Telephone Amplifier is completely automatic with detachable plug-in speaker. Placing the receiver on to the cradle activates a switch for immediate two-way conversation without holding the hand-set. Many people can listen at a time. Increase efficiency in office, shop, workshop. Perfect for 'conference' calls, leaves the user's hands free to make notes, consult files. No long waiting. On/Off switch volume control. Model with tape-recording facility. £16.95 + VAT £1.36 P & P 75p C.W.O. 10-day price refund guarantee.

**WEST LONDON DIRECT SUPPLIES (W/W)**  
169 Kensington High Street, London W.8

**NEW IMPROVED MAINS INTERCOM**




**ONLY £29.99**  
per pair  
+ VAT £3.75

Made to British Safety and Telecommunications Standards. The modern way of instant 2-way communications. Supplied with 3-core wire. Just plug into power socket. Ready for use. Crystal clear communications from office to office. Operates over 1/2-mile range on the same mains phase. On/off switch. Volume control. Useful as office intercom, surgery and homes, between office and warehouse. No GPO licence required. Full price refund if returned in 10 days. **Six months' service guarantee.** P & P 90p.

## buy, lease or rent:

- Teletype 33 and DD390 (10cps) printer terminals
- DECWRITER LA36 and DD303 (30cps) printer terminals
- OKIDATA 110 (66 lpm) and Teletype 40 (300 lpm) high-speed printers
- Lear Siegler ADM 1,2 and 3A video keyboard display
- Teletype 40 (7200 baud) asynchronous and synchronous displays
- DD Paper tape punch range (up to 110 cps)



for prompt delivery  
telephone London (01) 848 9781  
Edinburgh (031) 226 6201  
Manchester (061) 224 3306  
telex 935429

**WW — 052 FOR FURTHER DETAILS**

# BI-PRE-PAK

## COMPONENT BARGAIN SALE

**PRICES INCLUDE V.A.T., POSTAGE IN U.K. NO EXTRAS POSTAGE DEDUCTED FOR PERSONAL SHOPPERS**

<p><b>100 TRANSISTORS</b> mixed types. PNP germanium, PNP and NPN silicon. AF and RF types. Unmarked and untested. Good yield. <b>£1.35</b></p> <p><b>100 I.C.s</b> mixed types, marked. Ideal for experimenters etc. Limited supplies. <b>£1.35</b></p> <p><b>40 WIRE WOUND RESISTORS</b> mixed values and wattages. <b>85p</b></p> <p><b>40 POTENTIOMETERS</b> various values and types some switched, pre-set, etc. <b>£1.35</b></p> <p><b>100 DIODES</b> silicon, equal to 1N914, 1N4148, etc. unsorted, untested. <b>75p</b></p> <p><b>100 DIODES</b>, germanium, glass and metal types, untested. <b>75p</b></p> <p><b>10 EHT RECTIFIER STICKS</b> for colour TV triplers. 12 KV working. Type CSD11 8XP. <b>65p</b></p> <p><b>100 ZENER DIODES</b> 400 types. Mixed voltages. Unsorted. <b>75p</b></p> <p><b>PCB</b> Printed circuit board plain copper laminate. approx. 250 sq. ins. in about 7 pieces. <b>£1.35</b></p>	<p><b>2 LIGHT ACTIVATED S.C.R.s</b> 50v, 1.6A. Type LF9. With full data and 14 project details. <b>£1.35</b></p> <p><b>PUSH BUTTON TUNER ASSEMBLIES</b> for FM, TV, and Radio varicap tuners. Brand new by famous maker. 4-button assemblies <b>£1.95</b> 7-button assemblies <b>£2.80</b></p> <p><b>EX-G.P.O. INSTRUMENT CASES</b> Heavy gauge stove enamelled (grey) aluminium. Internal racking and panels usable as heatsinks, etc. Ideal for P.A. power supplies, oscilloscopes, instruments, etc. <b>BRAND NEW, BOXED</b> SIZE 'A' — 14" x 15" x 6" deep SIZE 'B' — 17" x 16" x 12" deep</p> <p><b>50 ONLY SIGNAL GENERATORS</b> Med Wave &amp; I.F. 1" pocket size. <b>£5.25</b></p> <p><b>POCKET SIGNAL INJECTOR</b> to trace fault in A.F., R.F., T.V. etc. <b>£2.75</b></p> <p><b>WHEN ORDERING</b> Make enquiries, identify orders, payment by B.P.O. or cheque. PRE-PAK IS NOT IN U.K. Any other valid form of payment will be considered, but is not credited to you accordingly. Above offers open for as long as stocks last.</p>
-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

**BI-PRE-PAK LTD.** 220-224 WEST ROAD WESTCLIFF-ON-SEA, ESSEX SSO 9DF  
Telephone Southend (0702) 46344  
*Personal shoppers welcome*

# BENTLEY ACOUSTIC CORPORATION LTD.

7A GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX, TEL. 6743  
ALL PRICES SHOWN INCLUDE V.A.T. AT 12 1/2 %

0A2	0.85	688G	0.35	6L6GC	0.70	2AT7	0.34	30PL12	0.40	B719	0.39	EBL21	2.00	ELR3	0.70	PR1	0.80	PY88	0.40	U18/20	1.80	Z145	0.87	AF102	1.04	CG12E	0.23	OC42	0.73		
0B2	0.40	68A6	0.40	6B8C	0.80	6L12	0.30	12AU6	0.50	30PL13	1.00	B729	0.79	EC52	1.00	EM85	1.20	PCC89	0.49	Q85/10	1.00	U19	1.00	Z152	0.29	AF106	0.58	CG64H	0.23	OC43	1.37
0Z4	0.55	68C8	0.80	6L12	0.30	12AU7	0.34	30PL14	1.20	BL63	2.00	EL63	2.00	EC53	1.00	EM86	0.60	PC86	0.42	PY301	1.20	U22	0.85	Z239	0.70	AF114	0.30	FSY11A	0.26	OC44	1.12
1A3	0.60	68E6	0.40	6L18	0.80	12AV6	0.60	30PL15	1.00	CL33	1.75	EC54	1.00	EM8003	3.20	PCC85	0.75	PY500A	1.20	U25	0.71	Z719	0.29	AF115	0.30	FSY41A	0.26	OC45	0.13		
1A5GT	0.55	68G6G	1.00	6L19	2.00	12AX7	0.34	35A3	0.75	CV6	0.60	EC86	0.84	EY1	0.50	PCC80	0.40	U26	0.60	Z729	0.45	AF117	0.23	GD4	0.38	OC46	0.18	OC65	0.13		
1A7GT	0.80	68H6	0.70	6LD12	0.40	12AY7	1.00	35C5	0.80	CV63	1.00	EC88	0.84	EY81	0.45	PCF80	0.40	U31	0.50	Z749	0.65	AF121	0.35	GD5	0.32	OC65	1.31	OC70	0.14		
1B3GT	0.55	68J6	0.85	6LD20	0.80	12BA6	0.50	35D5	0.90	CV988	0.25	EC92	0.55	EY83	0.60	PCF82	0.45	U33	1.75	Z759	5.85	AF124	0.36	GD6	0.32	OC70	0.14	OC71	0.13		
1C2	1.00	68K7A	0.65	6N7GT	0.70	12BE6	0.55	35L6GT	0.80	CY1C	1.00	EC32	1.00	EY84	1.20	PCF84	0.70	U35	0.50	Z839	1.15	AF125	0.50	GD8	0.23	OC72	0.13	OC78D	0.18		
1D5	0.75	68Q5	0.54	6PL12	0.40	12B8A	0.55	35W4	0.55	CY31	0.70	EC33	2.00	EY86/7	0.37	PCF87	0.77	U36	0.50	Z844	0.21	AF128	0.38	GET113	0.23	OC79	0.13	OC81D	0.13		
1G6	1.00	68Q7A	0.60	6P15	0.34	12BY7	0.70	35Z3	0.80	D1	0.50	EC35	2.00	EY91	0.50	PCF200	1.20	U37	2.00	QV03/10	U37	2.00	Transistors	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1H5GT	0.80	68R7	1.00	6Q7G	0.50	12E1	3.50	724GT	0.70	D63	0.30	EC40	0.90	EY95	0.50	PCF201	1.00	U38	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1L4	0.25	68R8	1.25	6Q7GT	0.50	12J5GT	0.50	725GT	0.80	DAC32	0.80	EC41	0.34	EZ31	0.50	PCF800	0.77	U39	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1LD5	0.70	68S7	1.70	6Q7M	0.70	12K7G	0.70	72	1.50	DAF91	0.35	EC82	0.34	EZ40	0.52	PCF800	0.77	U40	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1LN5	0.70	68W6	1.70	6R7G	0.70	12K7G	0.70	72	1.50	DAF96	0.60	EC83	0.34	EZ41	0.52	PCF800	0.77	U41	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1N5GT	0.70	68W7	0.65	6R7(M)	1.00	12K7GT	0.50	50C5	0.70	DC90	0.70	EC84	0.35	EZ40	0.32	PCF802	0.54	U42	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1R4	0.50	68X6	0.29	6SA7	0.55	12K8	0.75	50CDBG	1.20	DA	0.80	EC85	0.30	EZ31	0.40	PCF806	0.53	U43	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1S5	0.40	68Y7	0.38	6SC7GT	0.75	12Q7GT	0.50	50EH5	0.85	DF33	0.75	EC88	1.25	EZ90	0.45	PCH200	1.00	U44	1.00	U45	1.20	U46	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1S5	0.35	68Z6	0.60	6S7G	0.50	12SA4GT	0.75	50L6GT	1.00	DF91	0.30	EC88	0.51	FC4	1.00	PCL82	0.40	U45	1.20	U46	1.20	U47	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1T4	0.30	6C4	0.40	65H7	0.55	12S4GT	0.75	66K6U	0.52	DF96	0.60	EC91	0.35	FW4/500	1.00	PCL83	0.40	U46	1.20	U47	1.20	U48	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1U4	0.70	6C5G	0.60	6S7G	0.60	12S7G	0.55	72	0.70	DH63	0.50	EC189	0.80	FW4/500	1.00	PCL84	0.46	U47	1.20	U48	1.20	U49	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
1U5	0.35	6C6	0.45	6SK7GT	0.55	12SH7	0.50	77	0.45	DH76	0.50	EC80A	0.79	G230	0.40	PCF806	0.53	U48	1.20	U49	1.20	U50	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
2D21	0.55	6C9	2.80	6SQT	0.60	12SK8	0.75	85A2	0.75	DH81	0.80	ECF80	0.50	EZ32	0.40	PCL805/85	0.80	U49	1.20	U50	1.20	U51	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
2K5	0.70	6C10	0.71	6U4GT	0.80	12SK7	0.60	85A3	0.75	DH81	0.80	ECF80	0.50	EZ32	0.40	PCL805/85	0.80	U50	1.20	U51	1.20	U52	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
2X2	0.70	6C8A	0.50	6L7E	0.55	12SN7GT	0.75	90CV2	2.80	DK40	0.70	ECF86	0.80	G234	0.75	PEN4DD	0.60	U51	1.20	U52	1.20	U53	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3A4	0.55	6C12	0.4	6D8	0.50	12SQ7	0.80	108C1	0.40	DK40	0.70	ECF86	0.80	G234	0.75	PEN4DD	0.60	U52	1.20	U53	1.20	U54	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3B7	0.55	6CD8G	1.10	6V8G	0.30	12T07GT	0.80	108B2	1.00	DK91	0.50	EC81	2.00	G232	1.00	PEN4DD	0.60	U53	1.20	U54	1.20	U55	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3D6	0.40	6CG8A	0.50	6V8GT	0.80	12SR7	0.75	150C2	0.85	DK92	1.00	EC85	1.00	HABC80	0.80	PEN25	1.00	U54	1.20	U55	1.20	U56	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3Q4	0.70	6C6	0.75	6K4	0.40	12SR7	0.75	215G2	0.60	DK96	0.70	EC84	0.71	HL13C	0.60	PEN4DD	0.60	U55	1.20	U56	1.20	U57	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3Q5GT	0.80	6CL8A	0.55	6K5GT	0.45	14S7	1.00	302	1.20	DL63	0.70	EC81	0.40	HL23	0.70	PEN4DD	0.60	U56	1.20	U57	1.20	U58	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3V4	0.45	6CM7	1.00	6Y6G	0.95	18	1.25	303	1.20	DL82	0.80	EC83	0.50	HL23D	0.68	PEN4DD	0.60	U57	1.20	U58	1.20	U59	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
3V4	0.80	6C56	0.45	6Y7G	1.25	19A05	0.85	305	1.20	DL92	0.45	EC84	0.50	HL41	1.00	PEN4DD	0.60	U58	1.20	U59	1.20	U60	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
4CB6	0.75	6C55	0.90	7A7	1.00	19B6G6	1.00	807	1.10	DL94	0.80	EC80	0.45	HL41DD	1.00	PEN4DD	0.60	U59	1.20	U60	1.20	U61	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5C6G	0.75	6D3	0.75	7B6	0.80	19G6	6.50	956	0.50	DL96	0.60	EC82	0.50	HL42DD	1.00	PEN4DD	0.60	U60	1.20	U61	1.20	U62	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5R4GY	1.00	6E27	0.80	7B7	0.80	19H1	1.00	1625	2.50	DM70	0.80	ECL82	0.74	HN309	1.70	PEN4DD	0.60	U61	1.20	U62	1.20	U63	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5T4	1.00	6D15A	0.85	7D6	2.00	19Y3	0.40	1821	1.00	DM71	1.00	ECL84	0.65	HL23	0.70	PEN4DD	0.60	U62	1.20	U63	1.20	U64	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5A4G	0.60	6EW6	0.85	7F8	2.00	20D1	0.70	5702	1.20	DW4/350	1.15	ECL85	0.70	HYR2A	1.00	PFL200	0.70	U63	1.20	U64	1.20	U65	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5V4G	0.60	6E5	1.00	7H7	0.80	20D4	2.50	5763	1.65	DY87	0.65	EC86	0.64	KT2	0.90	PL33	1.00	U64	1.20	U65	1.20	U66	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5Y3GT	0.55	6F1	0.80	7R7	2.00	20F2	0.85	6057	1.00	DY802	0.45	EF22	1.00	KT8	3.00	PL36	0.60	U65	1.20	U66	1.20	U67	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5Z3	1.00	6F6G	0.60	7V7	2.00	20L1	1.20	6060	1.00	E80CC	2.50	EF40	0.78	KT41	1.00	PL81	0.49	U66	1.20	U67	1.20	U68	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5Z4G	0.48	6F12	0.50	7Y4	0.50	20P1	1.00	6067	1.00	E80CF	5.00	EF41	0.75	KT44	1.00	PL81A	0.53	U67	1.20	U68	1.20	U69	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
5Z4GT	0.55	6F13	0.80	7Z4	0.80	20P3	1.00	6068	3.50	E80F	2.20	EF42	0.90	KT63	0.80	PL82	0.50	U68	1.20	U69	1.20	U70	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
6/30L2	0.70	6F14	0.80	8D2	0.50	20P7	0.84	6068	2.90	E83F	1.60	EF73	1.75	KT66	3.00	PL83	0.45	U69	1.20	U70	1.20	U71	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
6A8L2	1.40	6F15	0.85	8D8	0.45	20P5	1.50	7025	1.50	E88CC	1.20	EF80	0.20	KT71	1.00	PL84	0.50	U70	1.20	U71	1.20	U72	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
6AC7	0.55	6F16	0.75	9B76	0.90	25A6G	0.70	7193	0.80	E92CC	0.70	EF83	1.25	KT81	2.00	PL302	0.90	U71	1.20	U72	1.20	U73	1.20	AF139	GD9	0.23	OC79	0.13	OC81D	0.13	
6AG5	0.35	6F18	0.60	9D7	0.70	25L6G	0.70	7475	1.20	E18																					

# SPECIAL LOW PRICE ARRANGEMENTS FOR VISITING OVERSEAS TRADE FAIRS



IPC Electrical-Electronic Press Ltd., the world's largest publishers of computer, electrical and electronic journals, have made special arrangements for readers wishing to visit important overseas trade fairs. The cost, in most cases, is little more than the normal air fare but includes – travel by scheduled airline from Heathrow and Manchester \* first-class hotel accommodation \* arrival and departure transfers \* admission to the trade fair \* services of an experienced tour manager. The current programme comprises the following tours.


To obtain a brochure and booking form, tick the box against the tours in which you are interested, complete the coupon and post to the exclusively appointed travel agent, Commercial Trade Travel Ltd., Carlisle House, 8 Southampton Row, London WC1. Telephone 01-405-8666 or 01-405-5469.

International Exhibition of Electronics Components <input type="checkbox"/>	Paris	March 31- April 6 1977	Computer, Systems & Peripheral Exhibition & Conference – COMPEC EUROPE <input type="checkbox"/>	Brussels	May 10-12 1977
Hanover Fair <input type="checkbox"/>	Hanover	April 20-28 1977	International Radio & TV Exhibition <input type="checkbox"/>	Berlin	August 26- September 4 1977
International Electric Vehicle Exhibition and Conference <input type="checkbox"/>	Chicago	April 26-29 1977	International Exhibition of Computers and Peripheral equipment – SYSTEMS <input type="checkbox"/>	Munich	October 17-21 1977
			International Exhibition for Electronic Production – PRODUCTRONICA <input type="checkbox"/>	Munich	November 22-26 1977

Please send details of the tours indicated above.

NAME..... COMPANY.....

ADDRESS..... Telephone.....

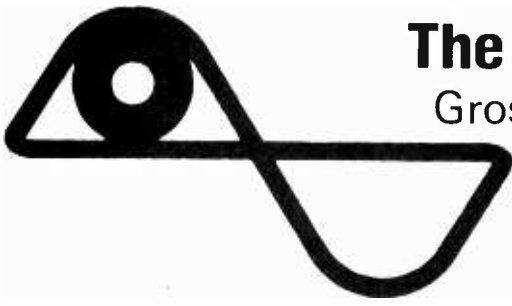

## The All-Electronics Show 1977

Grosvenor House, Park Lane, London

April 19-21, 1977

# ELECTRON

---

# wireless world


Visit our combined stand at the All-Electronics Show, and prove your skill as a driver—

\*Enter and play the all-new racing game 'Le Mans', a challenge of speed and skill, with prizes for the winners, donated by Light Soldering Developments, C.B.M. Ltd., Siliconix Ltd. and National Semiconductor Ltd. companies exhibiting at the show.

**ELECTRON/WIRELESS WORLD**  
published by IPC Electrical & Electronic Press Ltd.

\* Proceeds will be forwarded to EEIBA
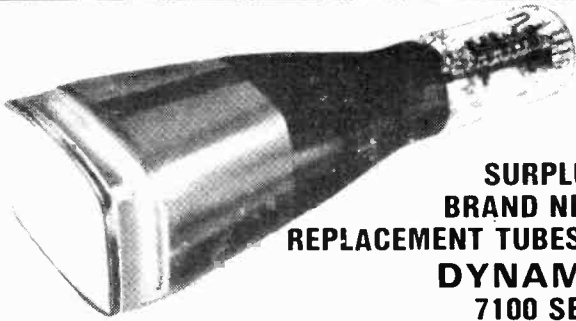
## OUR PURCHASE FROM THE DYNAMCO FACTORY CLEARANCE SALE



**SURPLUS —  
BRAND NEW —  
REPLACEMENT TUBES FOR  
DYNAMCO  
7100 SERIES  
OSCILLOSCOPES TYPE  
BRIMAR D13-5IGH**

Mesh P.D.A. Transistor Scan. Wide Bandwidth 60MHZ+. 6 x 10 cm-1KV EHT. X Sensitivity 15V/CM. Y Sensitivity 6V/CM. Standard heaters.

THIS IS A MUST AS A SPARE FOR THE DYNAMCO 7100 SCOPE OR IDEAL FOR THE HIGH QUALITY TRANSISTOR SCOPE BUILDER.

At **£65 each**. Carriage £2.50  
Numetal Shields available at £2.50

### DATA LOGGER by DYNAMCO



These are BRAND NEW — not finished — DATA LOGGERS BY DYNAMCO

They are completed but for the plug-in boards. The case with hinged lid is quite superb and extremely adaptable. It contains as well as the mother board an equally superb Power Supply with the following voltages +28V; +15V; +5V (2.5A) — this supply is crowbar protected; -5V; -14V; -20V; -24V; -48V and other supplies including auto 110V. This unit supplied in its original cardboard box complete with original manual must be of serious interest to the professional constructor and any one considering the construction of a micro processor system. Unit size 7½" high x 19" wide x 23" deep.

Price **£45 each**. Carriage £2.50

ALSO AVAILABLE **TUBE TYPE BRIMAR D10-210GH/32**  
BRAND NEW at **£70 ea.** Carriage £2.50

**SUPERB PROFESSIONAL VDU CASES**, size 23" x 16" x 27" on stands. Hammer grey. BRAND NEW SCHLUMBERGER Surplus **£40 each**. Carriage £2.50

**C.D.C. DISK DRIVES** complete with electronics, power supply, etc. Fine condition with Disk Pack. **£100 each**. Carriage £15

**LINE PRINTERS — VARIOUS MODELS**  
**£100 each**. Carriage £15

MINIATURE — OXLEY PATCH PANELS — BRAND NEW  
**EX DYNAMCO**  
10 x 10 complete with pins. **£10 each**. P&P 50p

**EDWARDS HIGH VACUUM PUMPS**  
Type 1SC30 @ **£55 each**. Type ES35 @ **£45 each**  
Carriage £2.50

**Quantity of CABINETS** — Approximately 5ft. 6in. and smaller. Computer types — very smart. Prices from **£4 to £20** dependent on size. Carr. £2.50

**VARIOUS MODELS OF PUNCHES/READERS** available for your inspection  
PRICES FROM **£15**. Carriage £2.50

**APOLLO SCRIBEMASTER**  
PRINTED CIRCUIT BOARD MAKER  
**£475**

**FRY'S ELECTROVERT WAVESOLDERING MACHINE**  
Type WASL 12 — Complete with Ultrasonic cleaner, Fluxwave applicator, jet blower, etc.  
**£1,250**

LARGE QUANTITY **DYNAMCO** TEST UNITS, OSCILLOSCOPE TUBES, RESISTORS, CAPACITORS, TRANSISTORS, PUNCHES, READERS, PATCH PANELS, PATCH PANEL PLUGS, ASSEMBLIES, FERRITE CORES, KNOBS, FREQUENCY COUNTERS, DVM's, SCHLUMBERGER BATTERY PACKS, 74 HUNDRED IC BOARDS, COMPUTER PANELS, FIBREGLASS BOARD, TRANSFORMER C CORES, CITENCO REDUCTION GEARED MOTORS, AB POTENTIOMETERS VARIOUS VALUES, KEYBOARDS, TUNING CAPACITORS, TRIMMERS, SMOOTHING CAPACITORS and VARIOUS TEST EQUIPMENT including SOME UNFINISHED OSCILLOSCOPES and other ITEMS. Available for your inspection NOW.  
CALL — SEE AND BE TEMPTED

VALUE ADDED TAX not included in prices — VAT at 8%  
Official Orders Welcomed. Gov./Educational Depts., Authorities, etc., otherwise Cash with Order  
Open 9 a.m. to 5.30 p.m., Mon. to Sat.



# CHILTMHEAD LTD



7/9 ARTHUR ROAD, READING, BERKS (rear Tech. College, King's Road). Tel. Reading 582605



# Why settle for yesterday's news?

News ● Reviews ● Technical Developments  
 Production Methods ● New Products ● Design  
 Finance ● Share Index ● Management  
 Marketing ● Appointments ● Vacancies  
 Exhibitions

## Electronics Weekly

THE TECHNICAL AND BUSINESS NEWSPAPER  
 OF ELECTRONICS AND COMMUNICATIONS

**Order your copy by using this form**

Electronics Weekly, c/o Room 218, Dorset House  
 Stamford Street, London SE1 9LU

I wish to take out a one year subscription to Electronics Weekly  
 Remittance enclosed for £6.00 (U.S.A./Canada \$ 15.60)

NAME .....  
 (Please print)

ADDRESS .....

.....

.....

Registered in England No. 677128  
 Regd Officer, Dorset House, Stamford Street, London SE1 9LU

<p><b>TTLs by TEXAS</b></p> <p>7400 16p, 74109 89p, 74400 28p, 74110 55p, 74S00 63p, 74111 90p, 74LS00 33p, 74112 96p, 7401 18p, 74116 200p, 7402 18p, 74118 84p, 7403 18p, 74120 120p, 7404 23p, 74121 32p, 74H04 36p, 74122 54p, 7405 25p, 74123 76p, 7406 43p, 74125 73p, 7407 43p, 74126 70p, 7408 25p, 74128 75p, 7409 27p, 74132 70p, 7410 18p, 74136 75p, 74H10 28p, 74141 75p, 7411 24p, 74142 320p, 7412 25p, 74145 90p, 7413 36p, 74147 190p, 7414 75p, 74148 160p, 7416 33p, 74150 140p, 7417 36p, 74151 72p, 7420 18p, 74153 85p, 7421 40p, 74154 150p, 7422 22p, 74155 90p, 7423 37p, 74156 90p, 7425 30p, 74157 90p, 7427 37p, 74158 140p, 7428 36p, 74159 190p, 7430 18p, 74160 120p, 7432 36p, 74161 120p, 7437 36p, 74162 120p, 7438 36p, 74163 120p, 7440 19p, 74164 120p, 7441 75p, 74165 220p, 7442 70p, 74166 160p, 7443 140p, 74167 340p, 7444 140p, 74170 250p, 7445 120p, 74173 160p, 7446 100p, 74174 120p, 7447 85p, 74175 85p, 7448 80p, 74176 120p, 7450 18p, 74177 100p, 7451 20p, 74179 160p, 7453 20p, 74180 110p, 7454 18p, 74181 298p, 7460 18p, 74182 82p, 7470 36p, 74185 150p, 7472 30p, 74186 920p, 7473 34p, 74190 160p, 7474 34p, 74191 160p, 7475 45p, 74192 120p, 7476 36p, 74193 160p, 7480 50p, 74194 120p, 7481 95p, 74195 95p, 7482 90p, 74196 120p, 7483 90p, 74197 120p, 7484 110p, 74198 250p, 7485 120p, 74199 250p, 7486 34p, 74221 160p, 7489 320p, 74251 140p, 7490 40p, 74265 90p, 7491 85p, 74278 290p, 7492 55p, 74279 140p, 7493 40p, 74283 190p, 7494 90p, 74290 150p, 7495 70p, 74293 150p, 7496 84p, 74298 200p, 7497 340p, 74365 150p, 74100 120p, 74366 150p, 74104 65p, 74390 200p, 74105 65p, 74393 225p, 74107 36p</p> <p><b>C-MOS I.C.s</b></p> <p>CD4000AE 20p, CD4001AE 20p, CD4002AE 20p, CD4006AE 95p, CD4007AE 20p, CD4009AE 61p, CD4011AE 20p, CD4012AE 20p, CD4013AE 55p, CD4015AE 90p, CD4016AE 50p, CD4017AE 100p, CD4018AE 110p, CD4019AE 52p, CD4020AE 120p, CD4022AE 100p, CD4023AE 22p, CD4024AE 80p, CD4025AE 22p, CD4026AE 170p, CD4027AE 65p, CD4028AE 98p, CD4029AE 120p, CD4030AE 55p, CD4040AE 120p, CD4042AE 90p, CD4043AE 100p, CD4046AE 140p, CD4047AE 100p, CD4049AE 63p, CD4050AE 57p, CD4054AE 120p, CD4055AE 140p, CD4056AE 135p, CD4060AE 130p, CD4069AE 27p, CD4071AE 27p, CD4072AE 27p, CD4073AE 30p, CD4078AE 21p, CD4082AE 27p, CD4093AE 95p, CD4510AE 130p, CD4511AE 160p, CD4516AE 112p, CD4518AE 130p, CD452AE 120p, MC14553 525p</p> <p><b>TEXAS 75 SERIES</b></p> <p>75107 160p, 75450 120p, 75451 72p, 75452 72p, 75453 72p, 75454 72p</p> <p><b>TEXAS DTLs</b></p> <p>930 36p, 936 40p, 946 40p, 955 60p, 962 36p, 963 40p</p> <p><b>MEMORIES</b></p> <p>2102 RAM 250p, 2107 RAM 1000p, 2112 RAM 450p, 2513 ROM 850p, 2602 RAM 250p, X887 ROM 1600p</p>	<p><b>OP. AMPS</b></p> <p>1458 Dual Op Amp Int Comp 8 pin DIL 70p, 301A Ext Comp 8 pin DIL 36p, 3130 COSMOS/Bi-Polar MosFet 8 pin DIL 100p, 3900 Quad Op Amp 14 pin DIL 70p, 5361 FET Op Amp TO 99 275p, 709 Ext Comp 8/14 pin DIL 30p, 741 Int Comp 8/14 pin DIL 22p, 747 Dual 741 14 pin DIL 70p, 748 Ext Comp 8/14 pin DIL 36p, 776 Programmable Op Amp TO 5 140p</p> <p><b>LINEAR I.C.s</b></p> <p>*AY 1 0212 Tone Generator 16 pin DIL 600p, *CA3028A Diff Cascade Amp 105 95p, ICA3046 Quad Low Noise Amp 16 pin DIL 80p, *CA3048 Diff Cascade Amp 105 70p, *CA3053 Diff Cascade Amp 105 70p, CA3080E Op. Transcond Amp. 8 pin DIL 90p, *CA3089E FM IF System 16 pin DIL 225p, *CA3090 FM stereo Multi. Dec 16 pin DIL 400p, ICI8038CC VCO Fun. Gen 14 pin DIL 340p, *LM380 2W Audio Amp 14 pin DIL 95p, *LM381 Stereo Preamp 14 pin DIL 175p, *LM389N Aud. Amp + 3 Tris Array 18 pin DIL 160p, *M252 Rhythm Generator 16 pin DIL 800p, *MC1310P FM Stereo Dec 14 pin DIL 190p, *MC1351P Lrm/Dei. Aud Preamp 14 pin DIL 97p, *MC1495 Multipler 14 pin DIL 300p, *MC1496L Bal. Mod. Demod. 14 pin DIL 100p, *MC1596 Bal. Mod./Demod. TO DIL 300p, *MC3340P Electronic Attenuator 8 pin DIL 160p, *MFC4000B 1/4W Audio Amp PCB 90p, *NE540L Audio Pwr driver TO99 140p, NE555 Timer 8 pin DIL 40p, NE556 Dual 555 14 pin DIL 100p, NE561 PLL with AM Demod. 16 pin DIL 425p, NE562 PLL with VCO 16 pin DIL 425p, NE565 PLL 14 pin DIL 200p, NE566 PLL Fun. Gen 8 pin DIL 200p, NE567 PLL Tone Dec 8 pin DIL 200p, 2567 Dual 567 16 pin DIL 370p, SN72710 Diff. Comparator 14 pin DIL 50p, *SN72733 Video Amp 14 pin DIL 125p, *SN7603N Pwr Aud Amp with int HS 16 pin DIL 240p, *SN7603H 10W Amp in 4 chms 5 pin Plastic 250p, *SN7603M Pwr Aud Amp with int HS 16 pin DIL 140p, *SN7603N 10W Amp in 8 chms 5 pin Plastic 250p, *SN7603N Pwr Aud Amp with int HS 16 pin DIL 140p, *SN76033N Pwr Aud Amp with int HS 16 pin DIL 230p, *TAA621A Aud Amp for TV QIL 225p, *TAA661B FM IF Amp-Limiter /Oet QIL 120p, *TBA611B Audio Amp QIL 140p, *TBA651 Tuner &amp; IF Amp 16 pin QIL 200p, *TBA800 5W Audio Amp QIL 90p, *TBA810 7W Audio Amp QIL 100p, *TBA820 2W Audio Amp QIL 80p, *TDA2020 20W Audio Amp QIL/Oil 325p, XR2240 Prog. Timer/Counter 16 pin DIL 370p, *ZN414 TRF Radio Receiver TO-18 110p</p> <p>Basic data sheets on above at 20p each + S A E</p> <p><b>OPTO-ELECTRONICS</b></p> <p>Phototransistors L.D. Ro 70p, OCP70 75p, OCP71 120p, ORP60 75p, ZN5777 45p, ORP61 75p</p> <p><b>LEDS</b></p> <p>0 2" Red 18p, 0 2" Green 36p, 0 2" Yellow 36p, Tri-state Red/Green 160p, Off 160p</p> <p><b>SEVEN SEGMENT DISPLAYS</b></p> <p>3015F 0.3" 160p, DL704 0.3" Red 140p, DL707 0.3" Red 140p, DL747 0.3" Red 225p, Xciton: 0 3" Green 160p, 0 3" Green 160p, 0 6" Green 225p, Drivers: 75491 84p, 75492 96p</p> <p><b>SCR-THYRISTORS</b></p> <p>1A 50V TO5 40p, 1A100V TO5 42p, 1A400V TO5 45p, 1A600V TO5 70p, 3A100V Stud 65p, 3A400V Stud 75p, 7A100V TO5+HS 84p, 7A400V TO5+HS 80p, 8A 50V Plastic 130p, 12A400V Plastic 160p, 16A100V Plastic 160p, 16A400V Plastic 180p, 6A600V Plastic 220p, BT106 1A, 700V Stud 110p, C106D 4A, 400V Plastic 63p, *MCR101 50V 0.5A/15V TO-92 25p, 2N3525 50V 0.5A/40V TO-66 120p, 2N4444 15V 2N4444 8A 600V Plastic 185p, *2N5060 0.8A 30V TO-92 34p, *2N5062 0.8A/100V TO-92 37p, *2N5064 0.8A/200V TO-92 40p</p>	<p><b>TRANSISTORS</b></p> <p>AC126 25p, AC125 20p, AC127 20p, AC128 18p, AC141 20p, AC142 20p, AC176 20p, AC187 20p, AC187K 25p, AC188 20p, AC188K 25p, AD149 49p, AO161 36p, AD162 36p, AF114 20p, AF115 20p, AF116 20p, AF117 20p, AF127 25p, AF139 43p, AF239 48p, BC107/B 9p, BC108/B 9p, BC109/B 10p, BC109C 12p, *BC117 22p, *BC147 9p, *BC148 9p, *BC149C 10p, *BC157 11p, *BC158 10p, *BC159 11p, *BC169C 12p, *BC172 11p, BC178 17p, BC179 18p, *BC182 12p, *BC183 12p, *BC184 13p, *BC185 11p, *BC212 11p, *BC213 10p, *BC214 14p, BC278 11p, *BCY70 18p, BCY71 22p, BD124 130p, BD131 36p, BD132 40p, *BD135 40p, *BD136 50p, *BD139 52p, *BD140 58p, BDY20 125p, BDY56 200p, BF115 22p, BF167 23p, BF170 23p, BF173 25p, BF177 26p, BF178 28p, BF180 33p, BF181 33p, BF184 22p, *BF194 10p, *BF195 9p, *BF196 14p, *BF197 15p, BF200 32p, BF257 32p, BF258 36p, *BF139 30p, *BF140 30p, *BF141 30p, *BF179 30p, *BF180 30p, *BF188 30p, *BF189 30p, *BF190 30p, *BF892 30p, *BF8</p>
----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------

## RELAYS—UNISELECTORS—SWITCHES

**MINIATURE PLUG-IN RELAYS** (Siemens/Varley)  
with perspex dust cover and base.  
6-12-24.48v D.C. In Stock  
2 c/o 50p: 6 make 60p  
4 c/o 75p: P & P 10p

**S.T.C. MINIATURE (P.C. Mounting)**  
with dust cover  
2 c/o (18/24v) 45p P.P. 10p  
4 c/o (24/36v) 50p P.P. 10p  
6 c/o (36/48v) 75p P.P. 10p

**CLARE-ELLIOTT MINIATURE RELAYS**  
(Hermetically sealed) 2 c/o 675 ohm  
24v D.C. Coils (22 x 22 x 10 mm) 75p

**I.T.T. 240v A.C. Plug-In RELAYS**  
(with perspex cover) 10 amp contacts  
2 c/o 65p 3 c/o 75p P.P. 10p

**REED RELAY 3 MAKE (50 x 20 x 20 mm)**  
3500 ohm coil 24v D.C. 50p

**REED SWITCHES (1 MAKE)**  
Type 1 (18 x 3 mm) 12 for £1  
Type 2 (48 x 5 mm) 8 for £1

**G.E.C. RATCHET RELAYS**  
310 ohm Red or Blue Cam. £1 P.P. 20p

**UNISELECTORS 25 WAY**  
5 Bank Full Wipe 75 ohm £5.50 P.P. 50p  
6 Bank Full Wipe 75 ohm £6.25 P.P. 50p  
8 Bank Full Wipe 75 ohm £7.50 P.P. 50p  
12 Bank Half Wipe 68 ohm £8.50 P.P. 60p  
**SMALL 12V UNISELECTORS** 4 Bank 11 way £2.50 P.P. 50p

**D.C. SOLENOIDS 24v** (Cont Rated)  
10lb Pull, 20 mm Stroke Size 50 x 48 x 42 mm  
75p P.P. 15p

**FOOT SWITCH "SQUARE-D" H.D.**  
20 A Make/10A Break at 240v A.C.  
600v A.C./D.C. Max. £4 P.P. 75p

**BURGESS MICRO SWITCHES (VCSP)**  
Single Pole c/o 8 for £1 P.P. 10p

**H.D. HONEYWELL MICRO-SWITCH** (contacts 2 N O/2  
N.C. 20 amp) ¼ turn action complete with roller actuator  
£2 P.P. 35p

**DECADE (THUMBWHEEL) SWITCHES**  
6mm Digits. 50p each. Bank of 8 with mounting brackets £3  
P.P. 20p

**DECADE INDICATOR SWITCHES** with plus & minus  
Push Buttons 6 mm digits 75p each P.P. 10p  
Also in B.C.D.

**KEY SWITCHES '1000' TYPE**  
4 c/o each way locking 60p P.P. 10p  
6 make each way locking 60p P.P. 10p  
Bank of 4, 4 c/o each way, 1 biased £1.25 P.P. 15p

## MULTICORE CABLES

**8 CORE RIBBON (RAINBOW) CABLE**  
8 x 14/76 Forming ½ in wide strip  
10m—£1.50: 50m—£6.50: 100m—£12.00 P.P. 1p per  
metre

**5 CORE H.D. CABLE** 5 x 70/76 P.V.C.  
Black Outer P.V.C. O.D. ½ in  
10m—£2.50: 50m—£12: 100m—£22.50 P.P. 2p per  
metre

**6 CORE ARMoured** 6 x 40/76 P.V.C. INS  
Outer Sheath-Flexible Galvanised Tubing. O.D. ⅝ in  
10m—£3: 50m—£14: 100m—£25. P.P. 2p per metre

**6 CORE SCREENED** 6 x 7/76 O.D. 6 mm  
10m—£1.50: 50m—£6.50: 100m—£12.00 P.P. 2p per  
metre

**36 CORE SCREENED** 36 x 7/76 (36 colours) O.D.  
11 mm  
10m—£3: 50m—£14: 100m—£25 P.P. 2p per metre

## VARIOUS

**E.H.T. MODULES.** Input 190-260v 50 HZ Output 13 Kv.  
PK @ 0.50 m/a. (150 x 95 x 70mm) £12. P.P. £1.

**AIR PRESSURE SWITCH** 0-10 lb Variable  
Switch Contacts 15 amp. Change-Over £1.50 P.P. 25p

**MYRIA MEGOHMMETER TYPE 35A.** 20-200K  
MEG/OHMS 500v test. Excellent condition. £45, carr  
£2 50.

**EQUIPMENT COLLING FANS** (System Papst) Precision  
made. Silent running. 110v 50 Hz. 120mm x 120mm. £5.  
P.P. 50p.

**"BLEEPTONE" AUDIO ALARMS**  
12v D.C. 50p P.P. 10p

**GEARED MOTORS 230v A.C.** (Int. Rating)  
110 r.p.m. £2.25 P.P. 75p

**MAGNETIC COUNTERS**  
6 digit 48v D.C. (Non-Reset) 92 x 32 x 22 mm  
New/Boxed £1 ea P.P. 15p

**3 DIGIT RESET COUNTERS** (240v A.C.) Veeder-root  
£1.75 P.P. 25p

**D.C. POWER SUPPLIES** Input 240v A.C.  
TYPE 1 20v D.C. at 1 amp. Fully regulated 155 x 155 x 75  
mm totally enclosed £5 P.P. 75p  
TYPE 2 20v D.C. at 500 m/a stabilised on open chassis 170  
x 100 mm £2.50 P.P. 75p

**PHILIPS MOBILE RADIO P.S.U.**  
Input 240v A.C. Output 32v at 1.5 Amp D.C. £5.25 P.P.  
75p

**TELEPHONE HANDSET** with "Press to Speak" switch  
£1.50 P.P. 25p

**2000 W. AUTO TRANSFORMERS.** Tapped  
100/125/200/225/250v New in wooden boxes £15  
P.P. £1.50

PLEASE ADD 8% V.A.T.

**J. B. PATTRICK**  
191/193 LONDON ROAD  
ROMFORD, ESSEX RM7 9DJ  
ROMFORD 44473

# Wilmslow Audio



## THE firm for speakers!

Baker Group 25. 3. 8 or 15 ohm . . .	£13.00	Goodmans 12P 8 or 15 ohm . . . . .	£16.50
Baker Group 35. 3. 8 or 15 ohm . . .	£14.50	Goodmans 12P-D 8 or 15 ohm . . .	£18.75
Baker Deluxe 8 or 15 ohm . . . . .	£17.50	Goodmans 12P-G 8 or 15 ohm . . .	£17.75
Baker Major. 3. 8 or 15 ohm . . . . .	£15.00	Goodmans Audiom 200 8 ohm . . .	£14.95
Baker Regent. 8 or 15 ohm . . . . .	£12.50	Goodmans Axent 100 8 ohm . . . . .	£8.50
Baker Superb. 8 or 15 ohm . . . . .	£22.50	Goodmans Axiom 402 8 or 15 ohm	£22.00
Celestion HF1300 8 or 15 ohm . . . . .	£7.50	Goodmans Twinaxiom 8" 8 or 15 ohm	£10.60
Celestion MH 1000 horn. 8 or 15 ohm	£13.50	Kef T27 . . . . .	£8.50
Coles 400 1 G super tweeter . . . . .	£5.90	Kef T15 . . . . .	£10.75
Coles 400 1 K super tweeter . . . . .	£5.90	Kef B110 . . . . .	£10.95
Decca London and X over . . . . .	£38.45	Kef B200 . . . . .	£11.95
Decca DK30 and X over . . . . .	£25.25	Kef B139 . . . . .	£24.95
EMI 5" Mid range . . . . .	£3.50	Kef DN8 . . . . .	£2.75
EMI 6½" d/cone roll surr. 8 ohm . . .	£3.95	Kef DN12 . . . . .	£7.25
EMI 8 x 5. 10 watt. d/c. roll/s 8 ohm	£3.95	Kef DN13 . . . . .	£4.95
EMI 14" x 9" Bass 8 ohm . . . . .	£12.50	Richard Allan HP8B 8" 45 watt . .	£12.50
Elac 59RM 109 15 ohm. 59RM 1148 ohm	£3.50	Richard Allan CG8T 8" d/c roll/s .	£7.95
Elac 6½" d/c roll/s 8 ohm . . . . .	£3.95	Baker Major Module, each . . . . .	£18.00
Fane Pop 15 watt 12" . . . . .	£5.75	Goodmans Mezzo Twinkit, pair . .	£51.95
Fane Pop 33T 33 watt 12" . . . . .	£9.95	Goodmans DIN 20. 4 ohm, each . .	£15.75
Fane Pop 50 watt, 12" . . . . .	£12.50	Helme XLK35, pair . . . . .	£26.75
Fane Pop 55. 12" 60 watt . . . . .	£16.95	Helme XLK40, pair . . . . .	£38.50
Fane Pop 60 watt, 15" . . . . .	£19.95	Helme XLK30, pair . . . . .	£21.95
Fane Pop 70 watt 15" . . . . .	£21.75	Kefkit 1, pair . . . . .	£59.50
Fane Pop 100 watt, 18" . . . . .	£33.95	Kefkit III, each . . . . .	£56.00
Fane Crescendo 12A or B. 8 or 15 ohm	£42.95	Richard Allan Twinkit, each . . . . .	£13.95
Fane Crescendo 15. 8 or 15 ohm . . .	£54.95	Richard Allan Triple 8, each . . . .	£20.75
Fane Crescendo 18. 8 or 15 ohm . . .	£75.95	Richard Allan Triple 12, each . . .	£25.95
Fane 807T 8" d/c. rolls/s. 8 or 15 ohm	£5.40	Richard Allan Super Triple, each .	£29.50
Fane 801T 8" d/c roll/s 8 ohm . . . .	£9.50	Richard Allan RA8 kit, pair . . . . .	£37.80
Goodmans 8P 8 or 15 ohm . . . . .	£6.50	Richard Allan RA82 kit, pair . . . .	£59.40
Goodmans 10P 8 or 15 ohm . . . . .	£6.95	Wharfedale Denton 2XP, pair . . .	£23.25
		Wharfedale Linton 3XP, pair . . . .	£34.25
		Wharfedale Glendale 3XP kit, pair	£49.50

All Radford, Gauss, Castle, Jordan Watts, Eagle, Lowther, Peerless Tannoy units in stock

Prices correct at 12/1/77

**ALL PRICES INCLUDE VAT**  
Cabinets wadding, Vynair, Crossovers etc.  
Send stamp for free 38-page booklet  
"Choosing a Speaker"

**FREE with all orders over £10 —**  
**Hi-Fi Loudspeaker Enclosures Book**  
**All units are guaranteed new and perfect**  
Prompt despatch

Carriage: Speakers up to 12" 60p; 12" £1; 15" £1.75; 18" £2.50  
Kits £1 each (£2 per pair). Tweeters & Crossovers 33p each.

## WILMSLOW AUDIO

Dept. WW

Loudspeakers & Export Dept: Swan Works, Bank Square,  
Wilmslow, Cheshire SK9 1HF. Discount Hi-Fi, PA, etc.: 10 Swan  
Street, Wilmslow, Radio, Hi-Fi, TV; Swife of Wilmslow, 5 Swan  
Street, Wilmslow. Tel. (Loudspeakers), Wilmslow 29599 (Hi-Fi,  
etc.), Wilmslow 26213.

Access and Barclaycard orders accepted by phone

WW—013 FOR FURTHER DETAILS


# Appointments

Advertisements accepted up to 12 noon Monday, April 4, for the May issue, subject to space being available.

**DISPLAYED APPOINTMENTS VACANT:** £7.50 per single col. centimetre (min. 3cm).  
**LINE advertisements (run on):** £1.10 per line, minimum three lines.  
**BOX NUMBERS:** 50p extra. (Replies should be addressed to the Box Number in the advertisement, c/o Wireless World, Dorset House, Stamford Street, London SE1 9LU.)  
**PHONE:** Eddie Farrell on 01-261 8508  
*Classified Advertisement Rates are currently zero rated for the purpose of V.A.T.*

# mi

## Careers in Professional Electronics

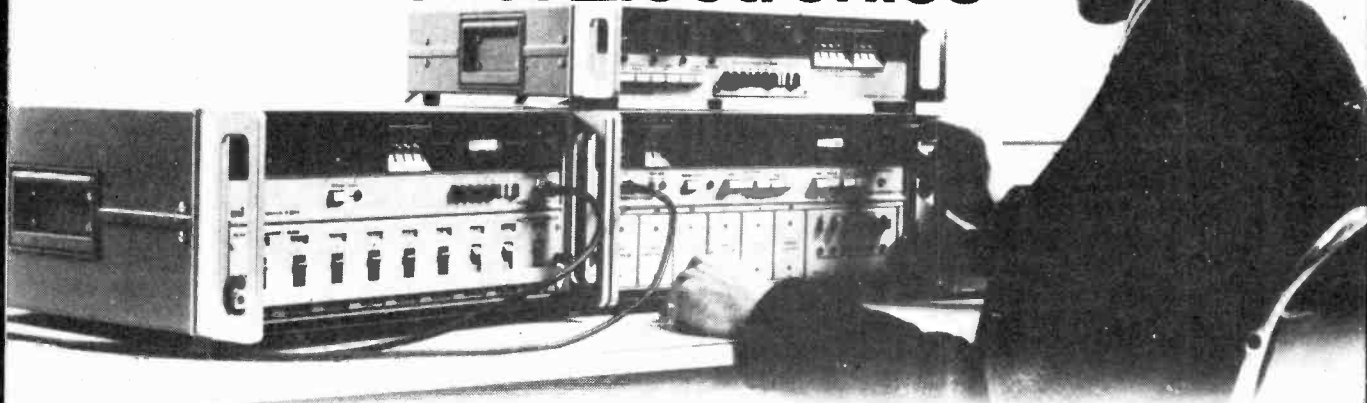

Your experience could open the door to a range of interesting and rewarding opportunities in the Design, Production or Service departments of a Company whose products complement the most advanced modern electronic techniques.

For more information apply in confidence to:— John Prodger,  
**MARCONI INSTRUMENTS LIMITED**  
Longacres, St. Albans, Herts. Tel: St. Albans 59292

A GEC-Marconi Electronics Company

(7085)

### UNIVERSITY OF SOUTHAMPTON Department of Chemistry **INSTRUMENT TECHNICIAN**

required to join a section carrying out the maintenance and repair of scientific, electronic and optical instruments  
Applicants should have a technical qualification of HNC or ONC or equivalent with several years' relevant experience in electronics and/or scientific instruments  
The appointment will be made at grade 5 on salary scale £2889-£3367 (which includes two supplements under Government pay policy)  
Applications giving details of age, qualifications and experience and the names and addresses of two referees, should be sent to Mr D A S Copland, The University, Southampton SO9 5NH, quoting reference 217/T./WW

(7060)

## Oxfordshire AREA HEALTH AUTHORITY (TEACHING)

Churchill Hospital

### Medical Physics Technician

**Grade III (Electronics)**  
**£2961.00-£3834.00 + £312.00**

To work in the Department of Radiotherapy and Oncology on the design and building of new circuits and the maintenance and updating of existing radiotherapy equipment. HNC or equivalent in electronics necessary.

Enquiries to Mr R. J. Thorne, Chief Technician, Department of Radiotherapy & Oncology, Churchill Hospital, Oxford OX3 7LJ. Closing date 25th February, 1977

### UNIVERSITY OF ABERDEEN **ELECTRONICS TECHNICIAN**

required for Department of Medical Physics for duties concerned mainly with the development of digital and analogue circuitry for prototype equipment used in clinical/research projects and the maintenance/repair of medical electronic equipment

Applicants should hold ONC or equivalent qualification and have had previous experience in electronics.

For suitably qualified candidate, salary on scale £2455-£2788 (inclusive of supplements under Stages 1 & 2 of incomes policy).

Applications giving details of age, qualifications and experience should reach the Secretary, University Office, Regent Walk, Aberdeen AB9 1FX by 31st March and quote Ref No. 36/77.

(7095)

## CALIBRATION ENGINEERS

### MEASURE YOUR SUCCESS BY OURS

EMI's commitment to excellence in its electronic products is achieving best ever sales and creating many new opportunities for expansion and development.

We depend upon very high standards of quality assurance, so we are looking for professionals who work to these standards and who have the ability to extend them still further.

The work is varied and involves the calibration and maintenance of electronic and electro-mechanical test equipment, covering a wide range of test and measuring techniques such as optical, thermal, digital and computer.

Qualified to City & Guilds (full certificate), ONC or equivalent in electronics, candidates should have experience of fault diagnosis and current measuring techniques. Knowledge of micro-wave techniques, and/or the utilisation of automatic test equipment would be an advantage.

To appreciate the satisfaction of working to EMI standards, come and see for yourself. You can also be sure that the salaries and benefits we offer — including the security of working for a highly successful organisation — reflect our awareness of the importance of your skills.

For further details and an application form, please telephone or write to: Barry Page, Personnel Department, EMI Limited, 135 Blyth Road, Hayes, Middlesex. Tel: 01-573 3888 ext. 639 or Record-a-Call anytime on 01-573 5524.



The international music, electronics and leisure Group. (7081)

## WANTED

**RADIO-TELEPHONE  
BENCH ENGINEERS  
AND FIELD SERVICE  
ENGINEERS**

TOP SALARIES FOR TOP ABILITY

We need people who have experience in V.H.F. Mobile Radio-Telephone

We are a young, friendly, independent company, who are currently the busiest and fastest expanding radio-telephone firm in London — we reward hard work with high incentives.

Ring now, with details of past experience, ask for Mike Rawlings or Bill Clarke.

30 Boundary Road, London NW8  
Telephone: 01-328 5344

**London  
Communications  
(Equipment) Ltd**

## APPOINTMENTS IN ELECTRONICS

Take your pick of the permanent posts in:

MISSILES — MEDICAL  
COMPUTERS — COMMS  
MICROWAVE — MARINE  
HARDWARE — SOFTWARE

For expert advice and immediate action on career improvement, phone, or write to, Mike Gernat BSc.

**Technomark**  
*Engineering and Technical Recruitment*

11 Westbourne Grove  
London W2. 01-229 9239.

7098

## LONDON COLLEGE OF PRINTING

Faculty of  
Visual Communications  
Department of Photography  
Film and Television

## TELEVISION TECHNICIAN/ ENGINEER

Applications are invited for the above post in the expanding Television Department of Photography, Film and Television.

Candidates should be conversant with ½", ¾" and 1" black and white and colour equipment and be capable of electronic maintenance. Experience in professional broadcasting would be an advantage, as well as an interest in experimental video work. The successful applicant will be expected to assist in running studio productions, and video tape editing. Salary scale £3190-£4702 inclusive (ST1/2).

Application forms, returnable within 14 days, obtainable from the Senior Administrative Officer at the college.

(7050)

## ITN

## SENIOR ENGINEER — INSTALLATION PROJECTS £5,712 p.a.

An engineer is required to work as part of a newly formed team responsible for installation projects. The work will be varied and will involve a wide range of broadcast equipment. The successful applicant will have a good knowledge of broadcast and sound equipment and techniques. Current projects include the replacement of major studio sound desks, telecine sound followers, multi track recording and communication systems.

A broad base of experience, gained either with a broadcaster or a manufacturer is essential.

In addition to practical experience, academic achievements will be taken into account.

Candidates should telephone the Personnel Department of Independent Television News Ltd. on 01-637 3144 quoting reference 3217.

(7088)

Re-advertisement

## UNIVERSITY COLLEGE OF NORTH WALES BANGOR

School of Physical and  
Molecular Sciences

## ELECTRONICS TECHNICIAN GRADE 5

Applications are invited for the post of Electronics Technician Grade 5 in the above mentioned School.

The successful applicant would be concerned with the development, construction and maintenance of specialised electronic equipment for a wide range of research work and teaching in the School.

Applicants should have had several years' relevant practical experience coupled with theoretical knowledge, preferably to H.N.C. standard or equivalent.

Salary at an appropriate point on scale: £2,889-£3,367 per annum.

Pension Scheme.

Applications (two copies), giving details of age, education and experience, together with the names and addresses of two referees should be submitted to the Assistant Registrar (Personnel), University College of North Wales, Bangor, Gwynedd LL57 2DG.

(7053)



## **ELECTRONIC DESIGN/ DEVELOPMENT ENGINEERS FERRANTI OFFERS YOU FREEDOM**

..... freedom to create. Over the years leading design and development engineers have been attracted to Ferranti by our reputation for truly innovative engineering and together they have formed specialised teams involved on a variety of sophisticated projects related to the Tornado, Sea Harrier, Jaguar, Nimrod 2 and other front line aircraft.

We now require additional engineers to join these teams engaged on the creative work of designing and developing airborne radar, laser and inertial navigation systems and their associated test equipment.

**Engineers are required in the following technical fields:-**

**Digital and analogue electronic circuitry design.**

**Design and application of small digital computers.**

**Microwave and laser techniques.**

**Advanced instrument design including gyroscopes of inertial quality.**

**Design of small mechanical structures and analysis of stress.**

In addition to the above we have vacancies for production engineers with either electrical or mechanical backgrounds in these fields.

Applicants should have some design/development experience to offer in avionics and a desire to expand their experience to project leader level.

Edinburgh, with its outstanding facilities for education, housing, sport and entertainment, is one of the ideal cities in Europe in which to live, work and bring up a family. And to make moving here easier, we pay realistic relocation expenses. Salaries are negotiable and the Company operates a contributory pension and life assurance scheme.

Apply in writing, with full details of experience and qualifications to

**Staff Appointments Officer,  
Ferranti Limited,  
Ferry Road,  
EDINBURGH, EH5 2XS.**

Please quote Ref. WW/1.

# **FERRANTI**

## Electronic Test Technicians- put your skills to the test!


Here at Havant where we currently manufacture large systems we're looking for Technicians, male or female, with experience of sophisticated electronics, and the ability to diagnose and rectify malfunctions on a complex computer system.

You're probably an experienced Technician with ONC/HNC in electronics or relevant Service experience in digital equipment.

Starting salaries are very competitive, together with first-class working conditions. You may be expected to work on a double shift basis for which an attractive premium will be paid.

As well as a wide range of fringe benefits we also offer generous relocation expenses to this attractive part of the south coast which provides outstanding social and recreational facilities.

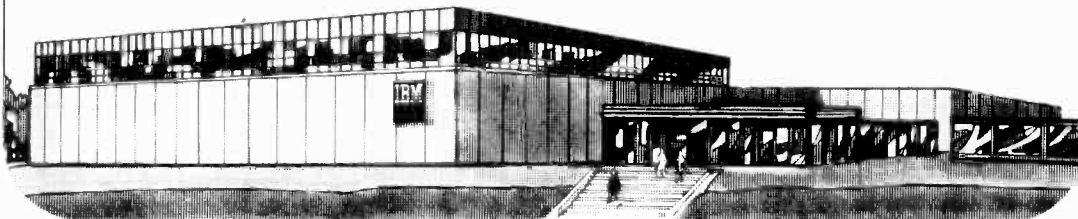If you feel this opportunity is suited to your ability and experience phone or write for an application form to: Marjorie Menereau, Personnel Officer, IBM United Kingdom Limited, Langstone Road, Havant, Hants. Tel: Havant 6363. Quoting ref: WW / 92838



### Thames Polytechnic

School of Materials Science and Physics

#### Electronics Technician (Grade 4)

Applications are invited for a technician for the electronics workshop who will be required to construct, maintain and repair a variety of electronic equipment for teaching and research. A good understanding and a flair for electronics is needed. Candidates should have an ONC or OND or equivalent qualification and at least seven years relevant experience.

Salary scale: £2835-£3216 including London weighting plus personal allowance (i.e. 5% of gross pay; min. £2.50 max. £4.00).

Further particulars and form of application may be obtained from the Staffing Officer, Thames Polytechnic, Wellington Street, London, SE18 6PF, to whom completed applications should be returned by 22 March, 1977.

## Join the leaders in Telecine Development

Rank Cintel — a division of Rank Precision Industries — has developed the world's most sophisticated telecine machine, and is currently engaged in a vast export programme. These achievements result from concentration on technical superiority and excellence of quality, and demand the highest standards of engineering at all levels. In order to maintain and develop our technical advantages, we now have a number of progressive positions for the following specialists:

### R & D Electronic Engineers

To apply their expertise to circuit design, using analogue and digital techniques in audio, video and servos. Candidates, men or women, should have good practical experience and be qualified to at least HNC level.

### Test Engineers (Broadcast Equipment)

To test and fault-find sub-units and PCB's using test specifications and a traditional range of test equipment. Candidates, men or women, should be qualified to T4 level, and preferably will have some work experience in electronics testing.

### Mechanical Design Draughtsman

To design and develop film and tape transports and associated instruments. Candidates, men or women, should be qualified to at least HNC Mech Eng., and have a number of years' experience in designing precise and dynamic devices.

All positions carry good starting salaries — with excellent prospects for career development. Working conditions and benefits are first-rate.

To apply please contact  
Ian Waterhouse  
Personnel Manager  
Rank Cintel  
Watton Road  
Ware, Herts.  
Tel. 0920 3939



## RANK CINTEL

## Development Engineers

### Consumer Electronics Hastings


Accepting that good Development Engineers are in universal demand, we nevertheless believe that our vacancies here at Hastings, open to both men and women, offer attractions second to none. Such as . . .

- \* Technically challenging, professionally rewarding, personally satisfying work on: Advanced colour television and audio-product design, incorporating the latest concepts in digital and integrated circuitry, microprocessors, and L.S.I. Then there's the development of Teletext, Viewdata — the list is almost endless.
- \* Opportunity to become involved with a successful company, which intends to accelerate its growth and build on its already high reputation for quality and innovation.
- \* The probability of overseas travel. The certainty of a good salary, generous holidays, "big company" fringe benefits, Pension and Life Assurance schemes, subsidised sporting and social facilities.
- \* Assistance, where appropriate, in moving to this pleasant, socially attractive, healthy coastal area, where housing is available and more reasonably priced, yet the amenities of the "big city" are within easy reach.

Sounds good? Then, if you have a degree or HNC, plus experience in a relevant speciality, write giving brief personal and career details (or phone for Application Form) to: —George Greaves, Personnel Officer, ITT Consumer Products (UK) Ltd., Theaklen Drive, Hastings, E. Sussex. Tel: Hastings (0424) 437061.

7080

TV • Radio • Stereo **ITT**

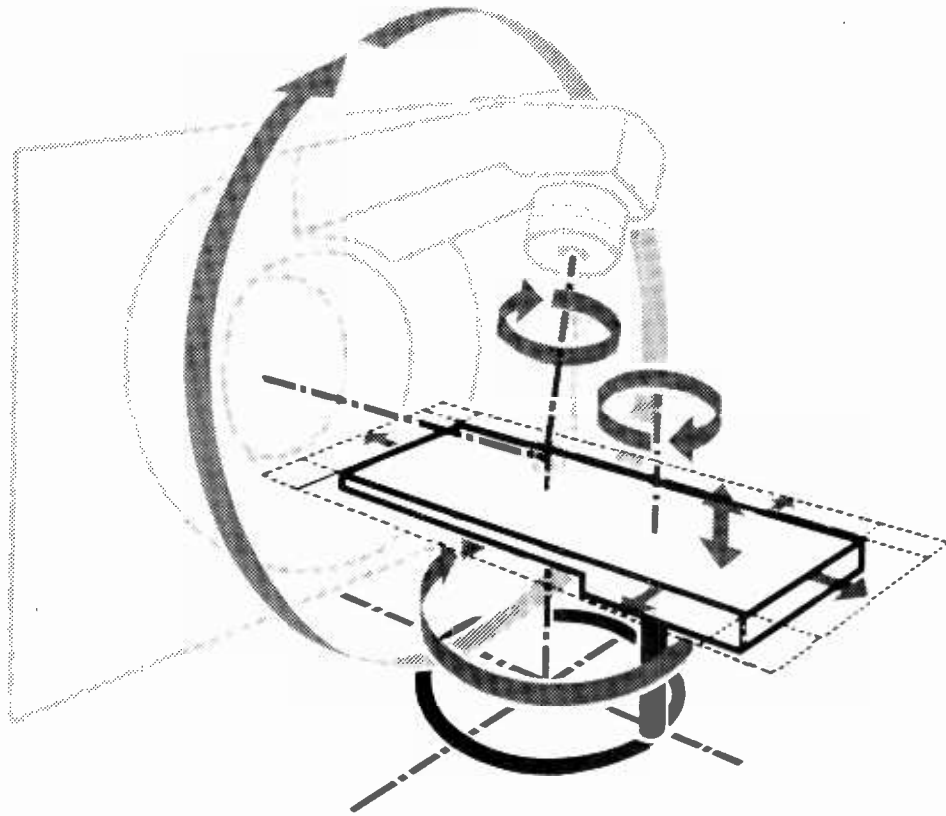

## INDEPENDENCE & WORLD TRAVEL IN A CHALLENGING FIELD FOR EXPERIENCED **Service & Installation Engineers**

The MEL Equipment Company Limited, the professional electronic division of the International Philips Group produce the advanced linear accelerators used in many of the major hospitals throughout the world for the treatment of cancer.

The equipment is highly sophisticated and offers those involved with installation and field support the opportunity to develop skills in this innovative area.



At present we are looking for self reliant, adaptable engineers who would appreciate the challenge and rewards of working on advanced medical equipment. Spending periods of up to 4 months duration overseas they would work in important medical centres installing and servicing the equipment.

Applicants will need professional qualifications of at least HNC level and a good knowledge of semi-conductor circuitry and ideally have experience of equipment such as high power radar systems. They will also need personal qualities which will enable them to deal with various senior members of organisations and act as "ambassadors" for our company.


We offer excellent progressive salaries with full expenses and allowances, an annual bonus, Pension and Life Assurance schemes and at least 4 weeks and 3 days annual holiday entitlement. Where candidates do not live in the Crawley area relocation will be necessary. Assistance will be given, including nomination for rented

accommodation from Crawley New Town Commission. Crawley is an established New Town situated on the Surrey/Sussex borders offering excellent educational and recreational facilities, including a local sports centre and swimming pool.



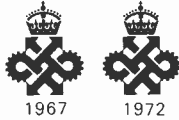If you would like to take this opportunity to work on vital, highly sophisticated equipment please write or telephone for an application form to Barbara Newman, Personnel Officer, M.E.L. Equipment Company Limited, Manor Royal, Crawley, Sussex. Tel: 0293 28787.





## OXFORD INSTRUMENTS DEVELOPMENT ENGINEER

Applicants should be practical, innovatory electronics engineers with experience in r.f., and precision analogue circuit design. A knowledge of digital techniques, would be useful, but is not a prime requirement.

The successful applicant will be a key member of a small new group with multidisciplinary interests. He or she will primarily supply the electronics expertise required for the development of sophisticated new instruments, but will also be expected to become involved in other aspects of innovation. The ability to work with minimal supervision and to be self-motivated is essential.

Salary negotiable according to age and experience.

Contact Dr. Peter Hanley, telephone Oxford 41456 or write to The Oxford Instrument Co., Osney Mead, Oxford OX2 0DX, to arrange an interview.

(7064)

**CABLESYSTEMS  
CANADIAN LIMITED**

## SYSTEMS ENGINEER

**CANADA**

We have an opening in our London, Ontario, Engineering Office, for a shirt sleeves professional engineer who has a strong background in Video Engineering. A working knowledge of R.F. Transmission, preferred in C.A.T.V. would be an asset. You would be a highly results orientated individual who will enjoy the challenge of making your place in a small team of engineers. Canadian Cablesystems is a company with ten C.A.T.V. Systems in Ontario with over 400,000 Subscribers. Salary will be in the range of \$20,000 per annum. If you wish to pursue this position within our organisation please send your résumé in confidence to

**G. F. Stone**

9 Great Lawn, Ongar, Essex

Interviews will be held in London, England.

(7113)

## Electronic Research & Design

W. London To £4,600

Our client is the Development Division of a major and highly successful international company. To ensure continued leadership in the field of Special Application Control Systems, 5 additional engineers are needed to strengthen small teams developing new and advanced products.

Applicants (male or female), aged 21+, should have a Degree or HNC and experience of Analogue/Digital Circuit Design. A knowledge of Micro-processors, Hydraulic Systems or Scientific Programming would be an advantage.

The posts carry a good basic salary and other "big company" benefits. In addition, there are excellent opportunities for promotion on merit within an expanding organisation.

For further information, please contact Mike Gernat.



**Technomark**  
Engineering and Technical Recruitment

5-11 Westbourne Grove, London W2.  
Telephone 01-229 9239

7070

## ELECTRONIC DESIGN ENGINEERS

**DO YOU** want to earn a better than average salary?

**DO YOU** want to join a go-ahead company?

**DO YOU** have experience in the design of audio to UHF circuitry or Assembly level programming of mini or micro processors?

**DO YOU** like working with the minimum of supervision?

**YOU DO?** Then apply to:



**The Technical Director  
Burndept Electronics (ER) Ltd  
St. Fidelis Road  
Erith, Kent  
Erith 39121**

(7062)



**LONDON BOROUGH  
OF  
LEWISHAM**

**TOWN CLERK & CHIEF EXECUTIVES  
DEPARTMENT**

## Administrative Officer (Telecommunications)


**£4836-£5142**

To provide and maintain an effective integrated telecommunications service for all Council establishments and to ensure that the service fully meets the Council's current and anticipated requirements.

Applicants must have a wide knowledge of Post Office and commercial communication installations.

**Application form, returnable by 1st April, and detailed job description from Chief Personnel Officer, Town Hall, Catford, London SE6 4RU, or telephone 01-690 7666 (24-hour Ansafone service) quoting reference CE 78 and job title.**

(7052)

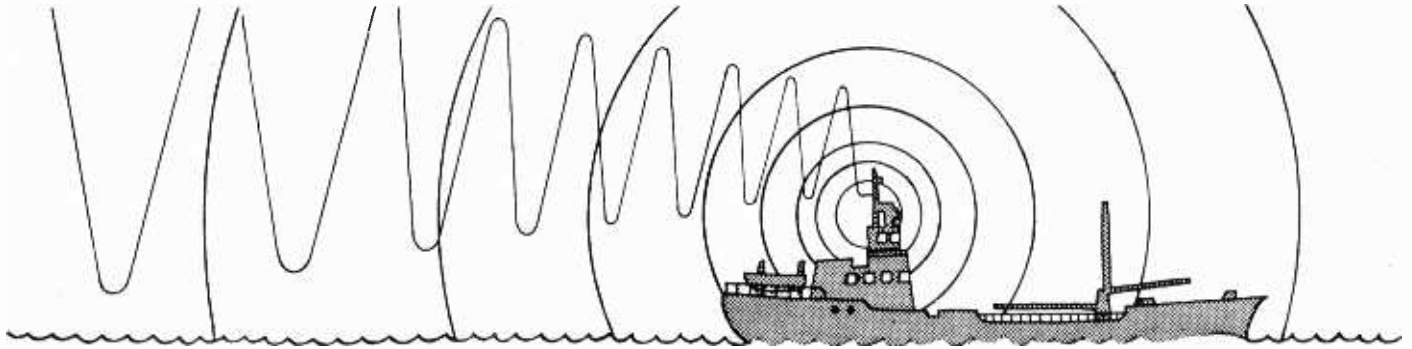

## Radio Officers—now you can enjoy the comforts of home.

Working for the Post Office Maritime Services really makes sense. You still do the work that interests you, but with all the advantages of a shore-based job: more time to enjoy home life, job security and good money. To qualify, you need a United Kingdom Maritime Radiocommunication Operator's General Certificate or First Class Certificate of competence in Radiotelegraphy, or an equivalent certificate issued by a Commonwealth Administration or the Irish Republic.

Starting salaries, at 25 or over, are £2905 rising to £3704 after three years service. Between 19 and 24, the starting salary varies from £2234 to £2627 according to age. In addition, a supplement of £312

p.a. is payable. You'll also receive an allowance for shift duties which at the maximum of the scale averages £900 a year and there are opportunities to earn overtime. There's a good pension scheme, sick pay benefits and prospects of promotion to senior management.

Right now we have a few vacancies at some of our coastal radio stations, so if you're 19 or over, preferably with sea-going experience, write to: ETE Maritime Radio Services Division (L690), ET 17.1.1.2., Room 643, Union House, St. Martins-le-Grand, London EC1A 1AR.

Post Office Telecommunications

### SOUTH COAST

Several of our clients require the following personnel urgently, offering excellent salaries and relocation expenses where necessary.

**PROJECT ENGINEERS  
ELECTRONIC ENGINEERS  
TEST ENGINEERS AND  
TECHNICIANS  
QUALITY ASSURANCE ENGINEERS  
TECHNICAL AUTHORS  
SYSTEMS PROGRAMMERS  
DRAUGHTSMEN/WOMEN. Electro-Mechanical and BUYERS**

Please write or ring - **CBS APPOINTMENTS**  
224 Old Christchurch Rd., Bournemouth, Bournemouth  
292155 or Wimborne 4891 after 7 p.m. (7084)

### PIPCO (S & W SERVICES)

For Electronic Engineers, Technicians & TV Service Engineers.

26a High Street  
Hounslow, Middx.  
Tel: 01-572 7363  
Telex PIPCO Hounslow 935413  
(6552)

### CA CAPITAL APPOINTMENTS LTD.

**FREE JOBS LIST**  
for  
**FIELD SERVICE ENGINEERS**  
BASIC SALARIES TO  
£5,000 + CAR (7083)

34 Percy Street, London, W.1  
01-636 9659 (day) or  
550 0836 (evening)

**ELECTRONICS ENGINEER** wanted. With experience in modern amplification and electronic keyboards. Hiring Department, Maurice Patquet. Tel. 01-749 3232. (7107)

## Applications and Production Engineers

Dolby Laboratories manufacture and market professional audio noise reduction equipment which is widely used by major recording companies, recording studios and broadcasting authorities throughout the world. Established in London, the Company has enjoyed successful growth since incorporation in 1968.

### Applications Engineer c.£5,000

Reporting to and working closely with the International Marketing Manager the person appointed will be involved in all aspects of sales, eg providing technical information to distributors and customers, giving demonstrations and training courses, and visiting recording studios and broadcasting organisations in the UK and abroad.

The successful applicant will be an electronics engineer who enjoys dealing with people and problems. Aged between 25 and 35 he, or she, will probably have a degree and may well have experience of recording studio or broadcasting practice. European languages would be a distinct advantage.

### Production Engineer c.£4,000

The person appointed will join a small team which provides the technical support to the production department. Working under the Production Technical Manager this section is responsible for establishing assembly and testing procedures, quality control and interfacing with sales and design engineers on product improvements and new product introductions.

The successful applicant will be an electro-mechanical engineer who enjoys using his specialist knowledge to resolve day-to-day problems as much as the more theoretical aspect of the job. He, or she, will probably have a degree and experience in electronic equipment manufacturing.

Write or telephone:

Gary Holt, General Manager  
Dolby Laboratories Inc  
346 Clapham Road, London SW9  
Telephone 01-720 1111 (7094)

  
Dolby Laboratories

### THE OPEN UNIVERSITY Faculty of Technology ELECTRONIC TECHNICIAN



An Electronic Technician (Calibration) is required to join the general electronic facilities of the Open University.

Main duties of the post are to provide a 95% in-house calibration and maintenance service for all measuring equipment using mainly electronic techniques

To assist all O U staff (academic, research, technicians and maintenance) with electronic problems and the use of their equipment

To set up and maintain the necessary record system to operate such a service.

**Experience:** Ten years in electronics, five years of which should be relevant to the above duties

**Qualifications:** HNC or C and G in an appropriate subject

**Salary:** Technician Grade 5 £2889-£3367 per annum

**Holidays:** 20 working days, plus 6 university closed days plus 7 national days. The post is within the New City of Milton Keynes

There is a university office to assist with housing. The applicant may be eligible for development housing and part removal expenses from the Open University

Application forms and further particulars are available, by postcard request please, from the Personnel Manager (ET2) The Open University, P O Box 75, Walton Hall, Milton Keynes, MK7 6AL Telephone Milton Keynes 63868

Closing date for applications 31st March 1977

(7065)

### TRAINEE ELECTRONICS EXPORT SALESMAN

Good basic knowledge and German Language required by active Company. Interesting position with variety

**EMPEXION LTD.**

233/243 Wimbledon Park Road

S.W.18

Tel: Abott 01-874 4362

7111



## Transmitter Engineering

# SENIOR DEVELOPMENT ENGINEER

# DEVELOPMENT ENGINEER

Pye TVT Limited are among the world's leaders in the field of professional broadcast equipment. Expanding activities in our transmitter engineering department now create the need for more personnel to join a team working on the design and development of TV and broadcast transmitters. The more senior position involves greater responsibility and some supervision activities. The successful candidates are likely to have a degree or equivalent, but more importantly should have had several years of development experience on transmitting equipment – broadcast or radar. Relocation expenses to this pleasant part of East Anglia will be given in approved cases. Other benefits



include a pleasant working environment, a good salary (with recently implemented supplement), restaurant and cafeteria service, staff shop and an active sports and social club. Please telephone or write to: Mr. D. Barnicoat, Personnel Officer, Pye TVT Limited, P.O. Box 41, Coldhams Lane, Cambridge CB1 3JU. Tel: Cambridge 45115. 7074



**Pye TVT Limited**  
The Broadcast Company of Philips

A member of the Pye of Cambridge Group

### SALOP AREA HEALTH AUTHORITY

Electronic and Bio-medical Engineering Department

## TECHNICIAN IV

required for the Area Works Department based initially at Copthorne Hospital South

Qualifications: O N C / H N C Electronics

Responsible to: Area Engineer

Salary scale: £2 346-£3 267 p.a. + £312 p.a. supplement

A technician is required for the above department to be responsible for the maintenance of medical (mechanical) and electronic apparatus used in the Area

The Technician will join a team who carry out a continuous servicing and overhauling programme to ensure that the equipment in their charge will run at the peak of its available efficiency at all times

Application form and job description to be obtained from the Area Engineer, Shrewsbury Hospital, Copthorne South, Mytton Oak Road, Shrewsbury, Salop. Tel Shrewsbury 52244 Ext 3273. Completed application forms to be returned by 14 days after insertion date.

711

# X-Ray Service Engineer

(\*4190 Saudi Riyals per month)

for the  
**King Faisal Specialist Hospital and Research Centre,  
Riyadh, Saudi Arabia.**

If you are an experienced Service Engineer, fully conversant with the most modern therapeutic and diagnostic radiology equipment, here is a unique opportunity to make a break for two years and practise your skills in one of the most modern hospital and research complexes in the world.

We urgently need an experienced Service Engineer, who will be responsible to the Chief Bio-Medical Engineer, to service and maintain a range of predominantly Philips' radiology equipment.

Newly-built, air-conditioned accommodation is provided, together with wide facilities for sport and recreation.

Two year contracts will be offered to suitably qualified applicants. Passages and accommodation will be provided for up to three dependants and there are generous leave periods.

At this time no income tax is payable in Saudi Arabia.

\*Sterling exchange rate at the time of going to press 5:97 riyals to the £.

Please apply in writing or telephone:

**Peter Coles,**  
Director of Human Resource Management (UK)  
**HOSPITAL CORPORATION  
INTERNATIONAL LTD.,**  
33 Cavendish Square,  
London W1M 0AA.  
Tel: (01)-491 3211

7079



**CAPITAL APPTS.**

**FREE LISTS**  
101 Design/Development and Test Jobs  
Permanent and Contract  
**To £6,000** (7093)

36, Percy St. London, W.1.  
637 5557 day, 550 0836 eve.

**ELECTRONICS TECHNICIAN** (Grade 6) required by Physiology Dept. for the design and construction of biophysical instrumentation to be used in muscle research. Experience in analog, digital and computer interfacing circuitry desirable. This is a three-year grant supported post. Salary in range £3,802-£4,435 inc. of London Weighting. Application form from Personnel Officer (Technical Staff FF5) University College London Gower Street London WC1E 6BT (7106)

### COURSES

**RADIO and Radar M.P.T. and C.G.L.I. Courses.** Write: Principal, Nautical College, Fleetwood, FY7 5JZ. (25)

### BOOKS

**"VINTAGE CRYSTAL SETS, 1922-1927"**. Just published by Wireless World, contains 128 pages. Chapters on the first days of broadcasting. The Crystal Set Vintage Wireless Trademarks. Also catalogue sections listing and describing crystal sets together with their original prices in £:s:d. A book for the collector or those interested in nostalgia. Available from main bookshops or direct from us. Please send £2.50 inclusive to IPC Business Press Ltd., Room 11 Dorset House, Stamford Street, London, SE1 9LU. (6125)

**LINK****BROADCAST TELEVISION**

We have several vacancies for top electronic engineers to be involved in various aspects of our organisation, which covers the design and manufacture of a full range of studio television equipment, including colour cameras and complete studio/O. B. systems. We are a young successful company supplying sophisticated equipment world wide to major broadcasting organisations.

All positions require engineers with at least two or three years' experience in an industrial/broadcasting environment and offer the chance to make your individual ability felt within an expanding company.

**Systems Engineer**

To be involved in all stages of project management on the design and the building of studio and mobile TV systems. Occasional world wide travel. The appointment requires someone with a knowledge of the operational side of television engineering and the ability to take charge of people and deal with problems in the field.

**Development Engineer**

For this position we need someone with a thorough knowledge of the latest circuit techniques plus the ability to put theory into practice in the design of sophisticated professional electronic equipment. You should be of HND/Degree level although relevant experience could outweigh formal qualifications.

**Test Engineers**

This position again requires somebody with a good knowledge of current analogue and digital circuit techniques plus recent experience with broadcast television or similar equipment sufficient to enable you to integrate quickly into the team engaged in the testing of colour and monochrome cameras.

Experience solely of domestic television is insufficient and we regret that at the moment we are unable to consider further applications from newly qualified engineers.

We can offer satisfying work in a congenial environment. Our modern factory is in a pleasant part of rural Hampshire with easy access to London and major towns. There is a good choice of housing and special arrangements exist for those moving from the G. L. C. area.

Salary offered depends on age and experience but will be above average for the right people. Fringe benefits include a pension scheme, free life and health insurance, generous holidays, staff restaurant and assistance with relocation.

Please phone for an application form or write with sufficient detail of your qualifications and experience to make this unnecessary.

Contact: **Mic Comber — Personnel Manager — Andover (0264) 61345**

**LINK**  
ELECTRONICS

Walworth Industrial Estate,  
Andover, Hampshire, England Telephone: Andover (0264) 61345

(7078)

**There's only  
one person  
who can get  
you a good  
job...  
...and that's  
you.**

**But we've already made the right contacts.**

**They're yours — and we don't need to interview or to see you first.**

**All you have to do is to complete our special — highly confidential — application form.**

**Then we'll simply pass on your particulars to those — and only those — companies really keen to meet a man or woman with your credentials and, aged between 20 and 45 years.**

**And they'll approach you direct.**

**We guarantee to safeguard all your correspondence and never to get in touch with any company you specify — from among our list of clients.**

**Like all good ideas — ours is very simple. It's simply the best way to find a new job.**

**Try it and see ...**

**Phone us today for an application form or, clip the coupon for our comprehensive and confidential information pack.**

**Lansdowne Appointments Register,  
Design House, The Mall, London W5 5LS.  
Tel: 01-579 6585  
(24 hour answering service)**

Tear out this  
confidential coupon

Name \_\_\_\_\_

Address \_\_\_\_\_

WW15/3

**Lansdowne***influence in high places*

(7099)

## Interested in computers?

### Lecture on Computer Servicing

## International Computers

think computers—think ICL

(7001)



We are looking for Lecturers to teach the practicalities of computer servicing

You will be based at our Engineering Training Centre in Letchworth, Herts – the largest of its kind in Europe. Here you will be given a comprehensive grounding in computer technology in general and ICL equipment in particular.

You will be thoroughly prepared to train engineers to the point where they will be capable of maintaining computers at the optimum operational specification.

Ideally, you will have an HNC or Forces' training in a technical subject. Any experience of digital electronics, computers or instructing on these subjects, while not essential, will be useful. Fluency in written and spoken French or German would be a distinct advantage but is not essential.

We'll start you as an Assistant Lecturer on a salary of not less than £3800 a year. You'll be encouraged and expected to progress to the position of Senior Lecturer which carries a salary in excess of £5000.

Relocation expenses will be considered where appropriate

For an application form, phone David Reeves on 01-788 7272 extension 4150, or write to him at ICL, 85/91 Upper Richmond Road, Putney, London SW15 2TE. Please quote reference WW 1134

#### UNIVERSITY OF SURREY

#### DEPARTMENT OF ELECTRONIC AND ELECTRICAL ENGINEERING AN ELECTRONICS ENGINEER/TECHNICIAN

is required to join the Industrial Electronics Group working on a wide range of advanced electronic design and construction projects. The post entails working with the minimum of supervision on the construction and testing of high quality prototypes and presents an opportunity for career development in instrumentation, computers and communications.

A second post exists in the Department's Electronics Workshop where an ELECTRONICS ENGINEER is required to join a team designing, building and servicing a wide range of specialised electronic equipment. The successful candidate will be expected to work with a minimum of supervision and be capable of taking projects from outline design to final product

The successful candidates will be appointed in one of the Technician Grades 2 to 5, depending on qualifications and experience. For the higher grades a minimum of 3 years' relevant experience and qualifications equivalent to ONC are expected. Opportunities are provided for further study leading to higher professional qualifications. There are promotion prospects to higher grades.

Salaries Technician Grade

2A	£2152 — £2452	4	£2689 — £3087
3	£2455 — £2788	5	£2889 — £3367
		6	£3314 — £3950

Application forms may be obtained from the Staff Officer, University of Surrey, Guildford, Surrey GU2 5XH, or Tel. Guildford 71281, Ext. 452, and should be returned as soon as possible.

(7056)

## SERVICE ENGINEER

L.K.B. Instruments require an additional engineer to service their range of clinical and nuclear products installed in customers' premises throughout the West Country and South Wales. The applicant should live or be prepared to move to this area.

Experience with nuclear counting equipment would be an advantage but a good general knowledge of digital electronics and a mechanical aptitude is considered essential.

The company offers a salary commensurate with experience, bonus scheme, company car, and assisted B.U.P.A. membership.

Please contact for application form —

**The Service Manager**  
**L.K.B. Instruments Limited**  
**232 Addington Road**  
**South Croydon, Surrey**  
**Tel: 01-657 8822**

(7059)

#### UNIVERSITY OF MANCHESTER

Hester Adrian Research Centre  
Anson House Pre-School Project for  
Mentally Handicapped Children

#### A vacancy exists immediately for a TECHNICIAN

(Grade 3)

in the above project. The successful applicant will work in the pre-school facility which is one mile from the University but will have access to electronic and mechanical workshops in the University itself. A major requirement will be that the technician will be responsible for the operation of an extensive CCTV system and will undertake the editing of tapes. Experience with CCTV is therefore important. Subsidiary functions will involve some electronic and mechanical work. ONC is essential and HNC (Electronics or Physics) (or equivalent qualification) is desirable. Salary Scale £2325-£2655 p.a. plus earnings supplement of £130 p.a. Applications with full details of age, qualifications and previous experience should be addressed to Dr J. Hogg, Hester Adrian Research Centre, The University, Manchester M13 9PL (7015)

## VIDEO & ELECTRONICS ENGINEER

required with experience of servicing and installation of Video and HiFi equipment for a responsible position in a new organisation in the centre of Bath. This is a challenging job for the right man, with excellent salary and promotion prospects.

**Apply in writing to: Video South, 101 Eden Vale Road, Westbury, Wilts, or telephone Westbury (Wilts) 823140.**

(7038)

## Aural and Visual Aids Technician

£3963-£4299 per annum

An experienced technician is required by the Croydon Education Service to maintain and repair a range of Audio and Video equipment including T.V. Receivers in schools.

Commencing salary in the scale will be according to qualification and experience.

In an appropriate case consideration will be given towards assistance with removal and lodging expenses.

## CROYDON

Apply in writing giving details of age, qualifications, present post and relevant work experience to **The Superintendent, Education Service Centre, Princess Road, Croydon CR0 2QZ** or telephone the **Superintendent, Mr. A. Bevan (tel: 01-684 9093)** for further details.

(7037)

**APPOINTMENTS**



**HF RADIO SYSTEMS ENGINEER**

£5,000 to £6,000 per annum

The Cable and Wireless Group, a leader in global telecommunications, has an interesting career opening at its Central London Head Office for a design engineer (male/female) of radio systems operating below 30 MHz.

Duties will include responsibility for provision of HF prediction services, propagation studies, advice on technical characteristics of antennae and modulation methods.

Applicants should preferably have an acquaintance with working systems, knowledge of the ionosphere and some computer programming experience. A suitable degree in electrical engineering, professional engineering qualification or HNC would be an advantage.

Excellent conditions of service are offered with commencing salary of between initially £5,000 and £6,000 per annum, depending on experience and qualifications, on progressive career scales rising to over £7,000 per annum. Generous leave and pension arrangements, Sports and Social Club, and other benefits.

Application forms may be obtained from:—  
**Recruitment Manager,**  
**Cable and Wireless Limited, Dept. A.443a/643**  
**Theobalds Road, London WC1X 8RX.**  
**(01-242 4433 ext. 211)**

(7066)

**Cable & Wireless**

**ARTICLES FOR SALE**

**EXCLUSIVE OFFER**

**WORLD-WIDE RANGE NEVER BEFORE OFFERED**

**PHILCO HC-150 POINT-TO-POINT STRIP RADIO HF RECEIVERS** 2.30 m.c.s. Ten fully tuneable channels (to 0.5 Mcs with synthesizers) Single and diversity reception on ISB, DSB, SSB with 4 sub-bands to each channel. Full details and prices on application.

**HIGHEST QUALITY 19" RACK MOUNTING CABINETS & RACKS**

**ENQUIRIES INVITED FOR NEW STOCKS NOW AVAILABLE**

**AUDIO AND INSTRUMENTATION-TAPE RECORDER-REPRODUCERS**

- \* Plessey 1D33 Digital Units, 7 track 1/2"
- \* Plessey M5500 Digital Unit, 7 tracks 1/2"
- \* Ampex FR-1100, 6 speeds, stereo 1/4"
- \* Ampex FR900, 4 speeds, 7 tracks 1/2"
- \* D.R.I. RMI, 4 speeds, 4 tracks 1/4"
- \* EMI TR90 2 speeds, 1 track 1/2"
- \* EMI BTR1, 1 speed, 1 track 1/4"
- \* EMI R301G, 2 speeds, 2 tracks 1/4"
- \* EMI RE321 1/4", 7 1/2" 1 track
- \* Licord IA, 1/4", 1/4", 7 1/2" 1 track
- \* Minicom CMP 100, 6 speeds, 7 tracks 1/4", 1/2"
- \* Leavers Rich DA 2P, 2 speeds, 2 tracks 1/4"
- \* Leavers Rich Console 2 track 1/4", 2 speeds

Prices of above £70 to £500

Also Transport Decks only available

We have a large quantity of "bits and pieces" we cannot list — please send us your requirements, we can probably help — all enquiries answered.

All our aerial equipment is professional MOD quality

- \* Oscilloscopes Gen. purpose 3" £35.00
- \* Solartron CD 711/52 D/U Oscilloscopes £110.00
- \* Airmec 702 Sig Gen 30/300KCS £85.00
- \* 10T Lightweight Mast sections, 6 sides £14.00
- \* Oscilloscope Trolleys from £12.00
- \* I.B.M. Video Display Units 4 col. £48.00
- \* Vener 5336 Counters £40.00
- \* Autopion VHF Receivers 20/120mcs £140.00
- \* Solartron CD 524 Oscilloscopes £90.00
- \* 100 amp Beiling Lee Interference Filters £75.00
- \* Marcom TF231 Distortion Meters £160.00
- \* AVO VI Voltmeters CT-471A £75.00
- \* Solartron Digital Voltmeters LM 1420/2 £120.00
- \* Racal MA197 Pre-Selectors £85.00
- \* Marcom TF-888 Receiver Testers £60.00
- \* Collins 500 watt 2/18 mcs. Transmitters £1000.00
- \* Collins KW16 SSB 500w Transceivers £1250.00
- \* Collins KW16 200 m. w AM Transceivers £750.00
- \* STC RX5 2/25 mcs Receivers Diversity £140.00
- \* Rack Mounting Operator Tables £18.00
- \* Gaumo Kalec 584 Jitter Meters £75.00
- \* Hewlett Packard 618B Sig. Gen. 3.8-7.2 GHz £120.00
- \* Rohn 95ft masts lattice 12 sides P.U.R.
- \* 30ft Lattice Masts, 14 sides £55.00
- \* 15ft Lattice Mast sections, 12 sides £35.00
- \* 12ft Lattice Masts, 15 sides P.U.R.
- \* 75/90ft Sky Towers, self-supporting £70.00
- \* Heavy Aerial Rotators P.U.R.
- \* Racal SA 504 Voltage converters £25.00
- \* Elliot Recording M.A. Meters £75.00
- \* 75ft Aluminium Lattice Masts, 20ft sides £400.00
- \* Plessey peak distortion meters £35.00
- \* Polarad Microwave power meters £55.00
- \* Rhode & Schwarz SSB sig gen. 1.6/2.4 gmc £70.00
- \* S.E. 4000 System Units P.U.R.
- \* Large Aerial Turning Units P.U.R.
- \* 45 feet Uniradio 4 Co-ax 50 ohms £2.00
- \* Baluns Professional Exterior 600/75 ohms £6.00
- \* 25ft Telescopic Aerial Masts £24.00
- \* Addo 5/8 Track Tape Punches £48.00
- \* Digital Cassette Recorders 1/2 1000 bps £250.00
- \* Quality Weather Vanes 8 contacts (unused) £25.00
- \* Racal RA17 Front Panels (new) £15.00
- \* Racal MA-175 I.S.B. Modulators (new) £45.00
- \* Inslide Cabinet Shelf Sliders £3.00
- \* DG-7/32 or DG7 5/4 R.F. £3.00
- \* Tally 5/8 Track Tape Readers 60 cps £48.00
- \* Tally 5/8 Track Tape Readers 1 track Spooling £65.00
- \* Cawickl FU 4 Band Pass Filter Testers £60.00
- \* Avo Geiger Counters (new) £14.00

We have a quantity of Power Transformers 250 watts to 15KVA at voltages up to 40KV. Best quality at low prices. Lists available.

- \* Racal RA-63 SSB Adaptors, new £70.00
- \* Racal RA-237 L-W Converters, new £70.00
- \* Portable Mains Battery Hospital Lights £24.00
- \* 400 Channel Pulse Height Spectrum Analysers £600.00

We have a varied assortment of industrial and professional Cathode Ray Tubes available. List on request.

**Electronics Engineers**

**Cheltenham**

The Scanner Division of Linotype-Paul is world renowned for the design and production of sophisticated systems used in the colour printing industry.

The Division now requires top-class electronics engineers to carry out complex testing operations during sub-assembly and final test stages.

Applicants, male or female, must have wide experience of analogue and digital circuitry, preferably gained in a test environment, and should be educated to ONC. An understanding of precision mechanical engineering and associated materials, as well as the principal processes in colour photography, would be advantageous.

We can offer top salaries and excellent conditions of employment. Assistance with relocation will be provided in appropriate cases.

Please write with career details to:



Barrie Witt, Personnel Officer  
 Linotype-Paul Limited  
 Block 22, Lansdown Industrial Estate  
 Cheltenham, Glos.

(7103)

**ARTICLES FOR SALE**

**HIGH POWER TRANSISTOR**  
 160 Volt. 30 Amp

2N 3773 £1.30 each in 100's  
 £1.20 each in 1000's VAT extra.

**J.A.T.A. Electronics Ltd.**  
 9 Heaton Road, Bradford  
 West Yorkshire BD9 5EU  
 Phone (0274) 45712

(7052)

**60KHz MSF Rugby Receiver, BCD TIME OF DAY OUTPUT.** High performance, phase locked loop radio receiver. 5V operation with 1 second LED indication. Kit complete with tuned ferrite rod aerial £14.08 (including postage and VAT). Assembled circuit and cased-up version also available. Send for details Toolex, Sherborne (4359). Dorset. (21)

**MAGNETIC MICROPHONE SPEAKERS**

4T Inserts, ideal for all sound speaking and listening applications. Very rugged DC res. .20 ohms  
 Size: 1 1/4" dia. 3/8" deep  
 40p ea. + 10p P&P  
 0 for £2.20 + 20p P&P  
 12 for £4.50. P&P free  
 S.A.E. for list. Many other items. Trade enquiries welcome.

**B.B. SUPPLIES, 141 Shelmford Street**  
 Nr. CANTERBURY, Kent CT4 7QZ

(6792)

**PLEASE ADD CARRIAGE AND V.A.T.**

**P. HARRIS**  
**ORGANFORD-DORSET**

**BOURNMOUTH (0202) 765051**

## APPOINTMENTS

We are a major force in the business of nuclear instrumentation and wish to appoint a

# CHIEF OF TEST

to head a team of Test Engineers working on fault finding and testing of both analogue and digital circuits and systems for a wide variety of electronic equipment.

Applicants must have a proven administrative record to MOD standard and possess an inquisitive and logical attitude to problem solving. A minimum qualification of HNC is desirable but academic qualifications are less important than sound test experience and a background of Industrial Relations.

An attractive salary is offered together with excellent career prospects. Please write or telephone for further details to:




Mr. D. Moy, Q.A. Manager  
Nuclear controls Division  
**GEC-ELLIOTT PROCESS INSTRUMENTS LIMITED**  
Century Works, Conington Road  
Lewisham, London SE13 7LN  
Tel: 01-692 1271 ext 393

## ARTICLES FOR SALE

# The Soundcraftsmen 20-12A Graphic Equalizer

Exclusive to **REW**

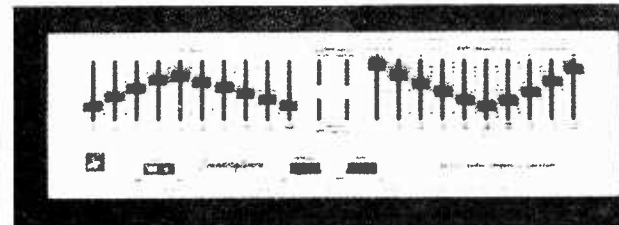

REW are proud to present the Soundcraftsmen Graphic Equalizer—undoubtedly the finest unit of its kind for both Hi-Fi and professional use. Each of the stereo channels is divided into 10 frequency bands, from 20 Hz to 20,480 Hz. Boost and cut of 12 dB is provided on each band and a gain control adjusts the output to match any amplifier. The unit has a champagne gold anodised front panel, enclosed in an attractive wood-grained cabinet. The Soundcraftsmen can be used as a sophisticated tone control enabling you to highlight individual instruments. Alternatively it can be used to produce a near-perfect flat frequency response in any domestic conditions by compensating for either poor room acoustics or various deficiencies in Loudspeakers. Also perfect for equalizing tape recordings. Send for full literature

Full range of Equalizers by other leading manufacturers also in stock including Altec, JVC, BSR, MXR, Technics.

- REW Centrepoint 20-21 St Giles High Street London WC2  
Tel 01-240 3066/7
- 146 Charing Cross Road, London WC2 Tel 01-240 3064/5
- Mail orders to REW House (dept WW), 10-12 High Street  
Colliers Wood, London SW19 Tel 01 540 9684/5/6

70591

## ARTICLES FOR SALE

### SOFTWARE DESIGN FOR MICROPROCESSORS

by J. G. Webster

Price £12.70

**INTRODUCTION TO DIGITAL FILTERING** by R. E. Bogner Price £8.50

**ACTIVE-FILTER COOKBOOK** by D. Lancaster Price £10.00

**THE CATHODE-RAY OSCILLOSCOPE & ITS USE** by G. N. Patchett Price £3.85

**PRINCIPLES OF TRANSISTOR CIRCUITS** by S. W. Amos. Price: £4.65

**110 ELECTRONIC ALARM PROJECTS FOR THE HOME CONSTRUCTOR** by R. M. Marston Price £3.25

**IC OP-AMP COOKBOOK** by W. G. Jung. Price: £9.00

**HI FI YEAR BOOK 1977.** Price £3.60

**VIDEOTAPE RECORDING** by J. F. Robinson Price £7.00

**FREQUENCY SYNTHESIZERS THEORY & DESIGN** by V. Mannasewitsch Price £20.00

**TTL DATA BOOK** by National Price £3.10

\* PRICES INCLUDE POSTAGE \*

**THE MODERN BOOK CO.**  
SPECIALISTS IN SCIENTIFIC & TECHNICAL BOOKS  
19-21 PRAED STREET  
LONDON W2 1NP  
Phone 723 4185  
Closed Sat. 1 p.m.

**C.R.T. REGUNNING PLANT.** New and secondhand reconditioned training demonstration colour or B/W. Barretts, Mayo Road, Croydon, Surrey. CRO 2QP. 01-684 9917.

**16mm BELL HOWELL 631 750/100 W lamp, separate speaker and transformer.** £150 + VAT. Hilton's 9 West Hill, Dartford, Kent. Tel: 20009. (WW15)

**VALVES RADIO** — T.V.-Industrial-Transmitting. We dispatch valves to all parts of the world by return of post, air or sea mail. 2,700 types in stock, 1930 to 1976. Obsolete types a speciality. List 20p. Quotation S.A.E. Open to callers Monday to Saturday 9.30 to 5.00. Closed Wednesday 1.00. We wish to purchase all types of new and boxed valves. Cox Radio (Sussex) Ltd., Dept WW, The Parade, East Wittering, Sussex PO20 5BN. West Wittering 2023 (STD Code 024366). (5392)

**VACUUM** is our speciality, new and secondhand rotary pumps, diffusion outfits, accessories, coaters, etc. Silicone rubber or varnish out-gassing equipment from £40. V. N. Barrett (Sales) Ltd., 1 Mayo Road, Croydon. 01-684 9917. (24)

**RECHARGEABLE NICAD BATTERIES.** 'AA' (HP7) £1.26. 'Sub C' £1.29. 'C' (HP11) £2.38. 'D' (HP2) £2.92. PP3 £4.98. Matching chargers respectively £4.48, £4.48, £5.24, £5.24, £3.98. all prices include VAT. Add 10% post & package. SAE for full list, plus if wanted 50p for 'Nickel Cadmium Power' booklet. Sandwell Plant Power Ltd., 1 Denholm Road, Sutton Coldfield, West Midlands B73 6PP. Tel No 021-354 9754. (6554)

**SPOTWELDERS** new from £85. Sameside from £220. — Ring 01-540 7337/8. Rentweld's, 14 Clarendon Road, London S.W.19. (6518)

**ELECTRONIC INSTRUMENTATION.** If you are interested in the buying or selling of good quality used Electronic Test Instruments, ring Reading 51074. Martin Associates and converse with our Sheila Hatch who will deal promptly with your enquiry. (6758)

**OSCILLOSCOPE** 100Mhz Cossor 4100 Almost brand new, with manual. Nearest offer to £495. — Teleradio, 325 Fore St, London N9. 01-807 3719. (7063)

**SCHLUMBERGER SIGNAL GENERATOR** D.O. 1001 a/25mhz AM-FM. offers over £750. Drake R7 digital receiver same as DSR2 Am CW-SSB. 0/30mhz. £400 or near offer. Pye on freq repeater. 450 470 mhz. £220. Pye T470/R470 U.H.F. link, unused. offers. (7077)

**SILICON SOLAR CELLS:** MS 11A 10M.W £5.96 MST 12 250mw £9.55. Price includes data postage and VAT. — Dept W, Edencumbe Ltd, P.O. Box 276, 67 Gloucester Street, London SW1V 4DZ. (7056)

**TELEPHONE ANSWERING** Machines for Sale. New £120. Answers and Records. Plus 2-way Conversations and Dictation Free Accessories and guaranteed 1 year. Callsaver. — C.R.V Electronics Ltd. 01-249 0416. 01-580 1800 30 Goudge Street, London W1.

### SOWTER TRANSFORMERS

**FOR SOUND RECORDING AND REPRODUCING EQUIPMENT**  
We are suppliers for many well known companies studios and broadcasting authorities and were established in 1941 Early deliveries Competitive prices. Large or small quantities Let us quote  
**SOWTER TYPE 2678**  
A recent release  
**MULTITAP MICROPHONE TRANSFORMER**  
Primary windings for 600 ohm, 200 ohm and 60 ohm with Secondary loadings from 2k ohm to 10 k ohm. Frequency response plus/minus 10dB 20 Hz to 25 KHz. Contained in well finished Mumetal box. 33mm diameter by 22mm high with colour coded and leads. low distortion. DELIVERY (small quantities) EX STOCK. HIGHLY COMPETITIVE PRICE. FULL DETAILS ON REQUEST.  
**E. A. SOWTER LTD.**  
Transformer Manufacturers and Designers  
7 Dedham Place, Fore Street  
Ipswich IP4 1JP. Tel. 0473 52794 6042

### ARMATURE & COIL WINDING ENAMELLED COPPER WIRE

Only top quality materials supplied. All orders dispatched within 24 hours

SWG	1lb reel	1/2lb reel
10 to 19	£2.95	£1.60
20 to 29	£3.15	£1.80
30 to 34	£3.45	£1.90
35 to 40	£3.65	£2.10

All prices inclusive of P&P in U.K.  
**COPPER SUPPLIES**  
102 Parrswood Road  
Wingington Manchester 20  
Tel 061-445 8753

### ATTENTION MANUFACTURERS

**LARGE STOCKS OF ROTARY POTS**

10K LOG PC type	} Offers around 10p each dependent on quantity.
5K LIN PC type	
500K LOG PC type	
500K LIN STD type	
25K LIN STD type	
5K LIN STD type	} ALSO LARGE STOCKS OF SLIDER POTS
1m LOG STD type	
10K LOG } Offers around 15p dependent on quantity	
50K LOG }	
100K LOG }	

Widdows Road, Hamworthy, Poole, Dorset  
Telephone: Poole (02013) 78989 (7058)



### ARTICLES FOR SALE

Buy, Access and Barclaycard Welcomes  
Official Orders accepted from Educational and Government Departments.  
SHOP HOURS 9-12.30, 1.30-6.00  
5 days. CLOSED WEDNESDAY.

**B.H. COMPONENT FACTORS LTD.**

1977 ISSUE 66 PAGES — 3000 ITEMS

- FULLY ILLUSTRATED
- 20p CREDIT VOUCHERS
- ALL NEW STOCK
- SATISFACTION GUARANTEED
- DISCOUNTS
- NEW PRICE LIST—SAE

**ELECTRONIC COMPONENTS Catalogue 5**

TRANSFORMERS  
SEMICONDUCTORS  
MIDWIVES - AUDIO  
MATCHING - S.W.C.  
AUDIO ACCESSORIES  
TOOLS - TEST METERS  
CALCULATORS - AUDIO  
LEADS - BATTERIES - KITS  
RESISTORS - CAPACITORS  
BARNS - COILS - BURNERS  
CONNECTORS - VERBOBOARD  
PC MATERIALS - HARDWARE  
BOXES - SCREWS - KNDS  
POTS - STORAGE UNITS ETC. ETC.

This month's special offer: 4 x 741P for £1.00 Full spec

58 North Street, Leighton Buzzard LU7 2EG  
Tel. Leighton Buzzard 2316 (Std. Code 06293) (7061)

**CMOS WITH DISCOUNTS! Any mix. 10% for 25+, 25% for 100+, 33% for 1000+**

4000 0.20	4028 1.00	4053 1.04	4086 0.80	14163 1.18	14526 2.16	14566 1.67
4001 0.20	4029 1.27	4054 1.29	4089 1.74	14174 1.08	14527 1.76	14568 3.16
4002 0.20	4030 0.60	4055 1.46	4093 0.89	14175 1.04	14528 1.22	14569 3.72
4006 1.31	4031 2.46	4056 1.46	4094 2.08	14194 1.17	14529 1.72	14572 0.27
4007 0.20	4032 1.19	4057 28.81	4095 1.16	14419 2.67	14530 0.95	14580 0.35
4008 1.07	4033 1.56	4058 2.60	4096 1.16	14490 6.61	14531 1.74	14581 4.30
4009 0.60	4034 2.11	4080 1.24	4097 4.13	14501 2.20	14532 1.39	14582 1.64
4010 0.60	4035 1.31	4081 2.80	4098 1.22	14502 1.38	14534 8.16	14583 0.84
4011 0.20	4036 3.09	4082 10.10	4099 2.03	14503 0.76	14536 4.00	14585 1.10
4012 0.20	4037 1.06	4083 1.22	4010 1.76	14506 0.57	14537 13.17	14600 0.25
4013 0.60	4038 1.20	4066 0.69	4012 2.16	14506 0.75	14539 1.24	14602 0.25
4014 1.12	4039 3.09	4067 4.13	4013 2.16	14507 0.80	14541 1.82	14604 0.25
4015 1.12	4040 1.19	4068 0.24	4014 2.28	14508 3.08	14543 1.82	14608 0.25
4016 0.60	4041 0.93	4069 0.24	4017 0.86	14510 1.51	14549 4.10	14610 0.25
4017 1.12	4042 1.93	4070 0.65	40108 0.18	14511 1.74	14552 10.50	14620 0.25
4018 1.12	4043 1.12	4071 0.24	40109 2.21	14512 1.03	14553 4.66	14620 0.25
4019 0.60	4044 1.04	4072 0.24	40181 4.30	14514 3.47	14554 1.67	14632 0.25
4020 1.24	4045 1.66	4073 0.24	40182 1.73	14515 3.47	14555 1.01	14642 1.84
4021 1.12	4046 1.48	4075 0.24	40194 2.26	14516 1.51	14556 1.01	14648 2.26
4022 1.07	4047 1.01	4076 1.71	40257 2.26	14517 4.02	14557 4.66	14673 0.67
4023 0.20	4048 0.60	4077 0.65	4700 1.75	14518 1.39	14558 1.26	14674 0.60
4024 0.67	4049 0.60	4078 0.24	7083 4.25	14519 0.57	14559 4.10	14690 0.66
4025 0.20	4050 0.80	4081 0.24	14160 1.18	14520 1.39	14560 2.17	14693 0.66
4026 1.62	4051 1.04	4082 0.24	14161 1.18	14521 2.77	14561 0.70	14695 1.26
4027 0.60	4052 1.04	4085 0.80	14162 1.18	14522 2.15	14562 5.59	14696 7.89

TERMS: Add VAT to all prices at 8%. Postage etc. UK 25p (+ 2p = 27p) per order export £2.00 (no VAT). Orders processed same day. \*7068

**GREENBANK ELECTRONICS (Dept W4W)**  
34 New Chester Road, New Ferry, Wirral, Merseyside L62 5AG, England. Tel: 051-645 3391

**PRECISION POLYCARBONATE CAPACITORS**  
AN High Stability — extremely Low Leakage

440V A.C. RANGE			63V D.C. RANGE		
Value	Dims	Price	Value [μF]	Tol.	
[μF]	Series	each	[μF]	-1%	±2% ±5%
0.1	27	12.7	68p	0.1	£1.28 75p 50p
0.15	27	12.7	80p	0.22	£1.32 77p 51p
0.22	33	16	86p	0.33	£1.32 77p 51p
0.25	33	16	92p	0.47	£1.32 77p 51p
0.33	33	16	99p	0.68	£1.44 84p 56p
0.47	33	16	1.10	1.0	£1.56 91p 60p
0.5	33	19	1.16	1.5	£1.74 1.16 67p
0.68	50.8	19	1.25	2.2	£1.98 1.32 75p
1.0	50.8	19	1.37	3.3	£2.40 1.60 99p
1.5	50.8	25.4	1.64	4.7	£2.82 1.88 1.23
2.0	50.8	25.4	1.95	6.8	£3.48 2.32 1.47
				10	£4.98 3.32 1.81
				15	£7.14 4.76 2.88
				22	£9.66 26.44 33.90

ANTIALUM BEAD CAPACITORS—Value available: 0.1, 0.22, 0.33, 0.47, 0.68, 1.0, 2.2, 3.3, 4.7, 6.8 μF at 15V/25V or 35V; 10.0 μF at 16V/20V or 25V; 22.0 μF at 6V/10V or 16V; 33.0 μF at 6V or 10V; 47.0 μF at 3V or 6V; 100.0 μF at 3V. All at 12p\* each. 10 for £1.10\*, 50 for £3\*, 100 for £9\*.

TRANSISTORS I.C.'s:

- BC107/8/9 9p \*BC121/212L 12p \*2N3055 50p
- \*BC114 12p \*BC213/213L 11p BC17/2 12p
- \*BC147/9 10p \*BC214/214L 11p \*NE555 Timer 61p
- \*BC153 16p \*BF194/5 32p \*741 Opn. DM 32p
- BC154/7/8/9 12p BF150/1/2 20p 2N414 1.15
- \*BC182/182L 11p AF178 40p SHT6013MD 1.15
- \*BC183/183L 12p AF229 36p SHT6023MD 1.15\*
- \*BC184/184L 12p \*2N3702/4 11p \*TB410AS 1.42\*

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 6p, 8 for 45p, 14 for 50p; 1S44 6p, 11 for 50p, 24 for £1.00; 1N4140 5p, 6 for 27p, 12 for 40p; 1N4001 9p; 002 6p; 003 6p; 004 7p; 005 7p; 006 6p; 007 8p.

LOW PRICE ZENER DIODES—400mW Tol. - 5% at 5mA. 3V: 3V6; 4V: 5V1; 5V6; 6V2; 6V8; 7V5; 8V2; 9V1; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each; 5 for 30p, 10 for 65p, 50 for £3.12. SPECIAL OFFER: 100 Zeners (just to meet) for £6.00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C. C 1/4W at 70°C. £12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p\* each. 50p\* for 10 of any one value, 70p\* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2Ω (1730 resistors) £5.

SILICON PLASTIC RECTIFIERS—1.5 amp, wire-coded 0027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp; 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only. All at 5p\* each; 50: 100; 220; 470; 680 ohm; 1K; 2K; 4K7; 6K8; 10K; 15K; 22K; 47K; 47K; 100K; 220K; 680K; 1M; 2M5; 5M.


PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with \* which are 12%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

**MARCO TRADING (Dept P5)**  
The Old School, Edgmonton, Wam, Strapford  
Tel: Wmstad 464/465 (STD 084 672)  
(Proprietary Trading Ltd.)

**COLOUR, UHF AND TV SPARES.**  
NEW colour bar generator kit Mk 3 aerial input type, R.Y. B.Y. etc. (adds on to Minor Supplies cross hatch units) £25\* pp 85p. Also Mk 4 combined colour bar generator and cross hatch kit £35\*, pp 85p. "Wireless World" TV Tuner and FM Tuner Projects by D. C. Read. Kits of parts available. Cross Hatch kit, Aerial Input type. No other connections. Battery operated, portable. Incl. Sync & UHF Modulator units £11\*. Add-on Grey Scale kit, £2.90\* p/p 45p. CRT Reactivator kit for colour and mono, £17.48\* p/p 80p. Signal Strength Meter kit £18\*, p/p 70p. 625 TV IF Unit, for Hi-Fi amps or tape recording £6.80 p/p 85p. Decca Colour TV Thyristor Power Supply Unit, incl. H.T., L.T., etc. Incl. circuits £3.80 p/p 95p. Bush CTV 25 Power Supply Unit, incl. H.T., L.T., etc. £3.20 p/p £1.20. Bush CTV 25 Convergence panel plus yoke, blue lateral £3.60 p/p 80p. Philips single stand convergence units complete, incl 16 controls, £3.75 p/p 75p. Colour Scan Coils, Mullard or Plessey £6 p/p 80p. Mullard AT1023/05 or Plessey Converg. Yoke £2.50 p/p 55p. Mullard or Plessey Blue Laterals 75p p/p 30p. BRC 3000 type scan coils £2 p/p 80p. Bush CTV 25 Scan Coils £2.50 p/p 80p. Delay Lines: DL20 £3.50 DL40 £1.50 DL18 DL1 85p p/p 40p. Lum. Delay Lines 50p p/p 30p. Bush/Murphy CTV 25 37174 EHT quadrupler £8.50 p/p 75p. Special offer colour triplers, ITT TH25 1TH £2 GEC 2040 £1.75 p/p 50p. Philips G8 Panels, part complete, surplus/salvaged; Decoder £2.50, IF incl. 5 modules £2.25, T. Base £1 p/p 70p. CRT Base 75p p/p 30p. GEC 2040 Decoder panel for spares £3.50 p/p 70p. VARICAP TUNERS, UHF: ELC 1043 £4.00, ELC 1043/05 £4.50, VHF: ELC 1042 £4.40, Philips VHF £3.30. Salvaged UHF & VHF Vari-caps £1.50 p/p 35p. SPECIAL OFFER: RBM 6 psn. Varicap control unit £1 p/p 35p. UHF Tuners transd. incl. slow motion drive £3.80. 4 Psn. and 6 Psn. push button transd. £4.20 p/p 70p. Philips. Bush, Decca integrated UHF/VHF transd. tuners £4.50 p/p 80p. Thorn 850 dual stand, time base panels 50p. Philips 625 IF panel incl. ect. 50p. p/p 65p. VHF Turret tuners AT 7650 for KB Featherlight, Philips 19TG170, GEC 2010, etc. £2.50. Pve miniature incremental tuners £1. Fireball tuners, Ferguson, HMV, Marconi 80p p/p all tuners 70p. Mullard Mono scan coils for Philips, Stella, Pye, Ekco, Ferranti, Invicta £2 p/p 70p. Large selection LOPTS. FOPTS available for most popular makes MANOR SUPPLIES, 172 West End Lane, London, N.W.8. Shop premises. Callers welcome. (Nos. 28, 159 buses or West Hampstead/Bakerloo Line and British Rail). Mail Order: 64 Golders Manor Drive, London, N.W.11. Tel: 01-794 8751. V.A.T. Please Add 12% TO ALL PRICES (EXCEPT WHERE MARKED \* VAT 8%). (60)

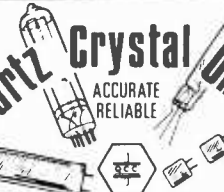**Quartz Crystal Units**  
ACCURATE RELIABLE



Private enquiries, send 13p in stamps for brochure

**THE QUARTZ CRYSTAL CO. LTD.**  
Q.C.C. WORKS, WELLINGTON CRESCENT  
NEW MALDEN SURREY Tel: 044 0314 x 2988

**QUARTZ CRYSTAL UNITS from**

- 1-999.9 MHZ
- FAST DELIVERY
- HIGH STABILITY
- TO DEF 5271-A

WRITE FOR LEAFLET AT 1

**McKNIGHT CRYSTAL Co. Ltd.**  
HARDLEY INDUSTRIAL ESTATE, HYTHE SOUTHAMPTON SO4 6ZV (6044)

TEL HYTHE 848961 STD CODE 0703

**WE INVITE ENQUIRIES from anywhere in the world.** We have in stock several million carbon resistors (½, ¼, and 1 watt, ¼ million wire wound resistors 5 and 10 watt — 1 million capacitors — 1 million electrolytic condensers — ¼ million transistors and diodes, thousands of potentiometers, and hosts of other components. Write phone or call at our warehouse. — Broadfields and Mayco Disposals Ltd., 21 Lodge Lane, North Finchley, London, N.12. 01-445 0749, 445 2713. (5907)

**PROFESSIONAL TV TUBE RE-BUILDING PLANT** designed and manufactured with 20 years' experience of tube rebuilding. Also all associated supplies including Electron guns, Regular training courses, Western-Whybrow Engineering, WECO Works, Penzance, TR20 9QT (073676) 2265. (6542)

**KERABOARD PCB** 18 x 12 covered with Ultraviolet negative photo resist. Packs of five. Single sided £11, double sided £13. per pack. Including postage. Harpum, 82 Shrubcote, Tenterden, Kent. (60)

Venner TSA 3336 Timer Counters 1MHz £40 or with 15MHz converters £50

Solartron CA512 Voltage standing wave ratio indicator £40

Marconi TF1041A Vacuum Tube Voltmeter £35

Philips GM6014 Valve Voltmeter £35

Siemens 3D332K Level Meter £125

Siemens 3W29K Level Oscillator £125

Marconi TF455E Wave Analyser £60

Robton 2028 Signal Generator £100

Boisnet — Desjardins type 4118 Sweep Signal Analyser £200

**HAWK SECURITY LTD.**  
190 SPON STREET, COVENTRY  
WEST MIDLANDS, CV1 3BB  
(0203) 20609 (7090)

**\*MANUFACTURERS\*  
\*WHOLESALERS\***

**WE STOCK A COMPREHENSIVE RANGE OF ELECTRICAL AND ELECTRONIC COMPONENTS, INCLUDING CABLES AND FLEXES, AT VERY COMPETITIVE PRICES**

Phone or write for quotations

**ELECTRONIC EQUIPMENT CO.**  
Springfield House  
Tyssen Street  
London E8 2ND  
01-249 5217 (7101)

**SURPLUS STOCKS.** High Stab Welwyn, Electrosl Resistor. Also, Quantities Potentiometers, Wire-Wound and Carbon, Pre-sets, Plus E.H.V. Water Cooled Capacitors. — R.S.P. Electronics, 53 Barton Street Gloucester, GU 1PY. Tel. 0452 23607. (7082)

**OSCILLOSCOPE** storage type (Remscope) with full manual including circuit Diagrams. Ice condition. £80 ono. — Ring 445 7041 (North London). (7087)

**LINSLEY-HOOD** 75 watt amplifiers constructed and repaired. Brand new guaranteed spares by return. BDY56 £1.85, BD529 55p, BD530 55p, 2N5457 35p BFR39 25p BFR79 25p, MPSA12 45p. Interference suppression kit (also reduces preamp noise) with instructions £1.35. Inclusive prices. P&P 15p. SAE for list. — I. G. Bowman (Dept WW), 59 Fowey Avenue, Torquay, S. Devon. (7102)

TRANSISTORS I.C.'s (Continued)

- BC107/8/9 9p \*BC121/212L 12p \*2N3055 50p
- \*BC114 12p \*BC213/213L 11p BC17/2 12p
- \*BC147/9 10p \*BC214/214L 11p \*NE555 Timer 61p
- \*BC153 16p \*BF194/5 32p \*741 Opn. DM 32p
- BC154/7/8/9 12p BF150/1/2 20p 2N414 1.15
- \*BC182/182L 11p AF178 40p SHT6013MD 1.15
- \*BC183/183L 12p AF229 36p SHT6023MD 1.15\*
- \*BC184/184L 12p \*2N3702/4 11p \*TB410AS 1.42\*

POPULAR DIODES—1N914 6p, 8 for 45p, 18 for 90p; 1N916 6p, 8 for 45p, 14 for 50p; 1S44 6p, 11 for 50p, 24 for £1.00; 1N4140 5p, 6 for 27p, 12 for 40p; 1N4001 9p; 002 6p; 003 6p; 004 7p; 005 7p; 006 6p; 007 8p.

LOW PRICE ZENER DIODES—400mW Tol. - 5% at 5mA. 3V: 3V6; 4V: 5V1; 5V6; 6V2; 6V8; 7V5; 8V2; 9V1; 10V; 11V; 12V; 13V; 13.5V; 15V; 16V; 18V; 20V; 22V; 24V; 27V; 30V; 33V. All at 7p each; 5 for 30p, 10 for 65p, 50 for £3.12. SPECIAL OFFER: 100 Zeners (just to meet) for £6.00.

RESISTORS—High stability, low noise carbon film 5% 1/4W at 40°C. C 1/4W at 70°C. £12 series only—from 2.2Ω to 2.2MΩ. ALL at 1p\* each. 50p\* for 10 of any one value, 70p\* for 100 of any one value. SPECIAL PACK: 10 of each value 2.2Ω to 2.2Ω (1730 resistors) £5.

SILICON PLASTIC RECTIFIERS—1.5 amp, wire-coded 0027: 100 P.I.V. 7p (4 for 26p); 400 P.I.V. 8p (4 for 30p).

BRIDGE RECTIFIERS—2 1/2 amp; 200V 40p; 350V 45p; 600V 55p.

SUBMINIATURE VERTICAL PRESETS—0.1W only. All at 5p\* each; 50: 100; 220; 470; 680 ohm; 1K; 2K; 4K7; 6K8; 10K; 15K; 22K; 47K; 47K; 100K; 220K; 680K; 1M; 2M5; 5M.

PLEASE ADD 20p POST AND PACKING ON ALL ORDERS. EXPORT—ADD COST OF SEA/AIRMAIL. Add 8% VAT to all items except those marked with \* which are 12%.

Send S.A.E. for additional stock lists. Wholesale price lists available to bona fide companies.

**MARCO TRADING (Dept P5)**  
The Old School, Edgmonton, Wam, Strapford  
Tel: Wmstad 464/465 (STD 084 672)  
(Proprietary Trading Ltd.)

**SOLARTRON D.V.M.** LM 1420-2 rack mounting, perfect working order with manual. £100, needs meter lead only.

### RECEIVERS AND AMPLIFIERS

**HRO** Rx5s, etc., AR88, CR100, BRT400, G209, S640, etc., etc., in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley'4986. (65)

**SIGNAL** Generators, Oscilloscopes, Output Meters, Wave Voltmeters, Frequency Meters, Multi-range Meters, etc., etc. in stock. R. T. & I. Electronics, Ltd., Ashville Old Hall, Ashville Rd., London, E11. Ley 4986. (64)

### TAPE RECORDING ETC.

**YOUR TAPES TO DISC.** Mono or Stereo Cutting. Vinylite Pressings, Sleeves/Labels. Top professional quality. S.A.E. for photo leaflet. DEROY Records, "Eastwood," Cove Dunbartonshire, Scotland. (82)

## CAPACITY AVAILABLE

### ENAMELLED COPPER WIRE

swg	1 lb.	4oz.	2oz.
14-19	2.40	.69	.50
20-29	2.45	.82	.59
30-34	2.60	.89	.64
35-40	2.85	1.04	.75

inclusive of p&p and VAT

SAE brings Catalogue of copper and resistance wires in all coverings

**THE SCIENTIFIC WIRE COMPANY**  
PO Box 30, London E4 9BW (6243)

**AIRTRONICS LTD.**, for Coil Winding — large or small production runs. Also PC Boards Assemblies. Suppliers to P.O., M.O.D., etc. Export enquiries welcomed. 3a Walerand Road, London SE13 7PE. Tel: 01-852 1706. (61)

**BATCH** Production Wiring and Assembly to sample or drawings. McDeane Electricals, 19B Station Parade, Ealing Common, London. W.5. Tel: 01-992 8976.

**SMALL BATCH PRODUCTION** wiring, assembly to sample or drawings. Specialists in printed circuit assembly. Rock Electronics, 41 Silver Street, Stansted, Essex. Tel. Stansted (0279) 33018/814006. (19)

**PRINTED** Circuits. Ultra fast turnaround. Very competitive prices. Also prototypes, artwork, photography, and drilling service. Kibmore Circuits, 120 Garlands Road, Redhill, Surrey. Phone 68850. (6739)

**P.C.B. ARTWORK DESIGN** — East Anglia. Fast precise work at competitive prices. Also instrument panel designs, etc. Contact tangent Electronics, 136 Whitehall Road, Norwich, Norfolk. Tel (0603) 28015.

**DESIGN, ARTWORK,** development, test and production of electrical equipment. Powerline Electronics, High Street Bognor Regis, Sussex PO21 1EZ. Telephone B.R. 25889. (7062)

## SERVICES

### SPEECH-PLUS RECORDINGS LTD

Specialists in Recording for Education, Commerce, Industry, A/V Programmes/Pulsing for Training and Sales, Cassette and Open-reel Duplicating

32 PAGES WALK, LONDON SE1

Telephone 01-231 0961/2 (6250)

### EURO CIRCUITS

Printed Circuit Boards — Master layouts — Photography — Legend printing — Roller tinning — Gold plating — Flexible films — Conventional fibre glass — No order too large or too small — Fast turnaround on prototypes. All or part service available NOW

**EURO CIRCUITS TD.**

Highfield House  
West Kingsdown  
Nr. Sevenoaks, Kent. WK2344

**LABELS, NAMEPLATES, FASCIAS** on aluminium or plastic. Speedy delivery G.S.M. Graphic Art Ltd., 1-5 Rectory Lane, Guisborough (02873-4443), Yorks. U.K (13)

### PRINTED CIRCUIT BOARDS —

Quick deliveries, competitive prices, quotations on request, roller tinnings, drilling, etc., speciality small batches, larger quantities available Jamiesons Automatics Ltd, 1-5 Westgate, Bridlington, N. Humber-side, for the attention of Mr. J. Harrison. Tel: (0262) 4738/77877. (18)

**DESIGN AND DEVELOPMENT.** Our Electronics Laboratory work in most fields for customers throughout the world. Including Telecommunications, RF, TV Links, TX and RXs from 1 MHz to 1 GHz all types of logic, digital and analogue systems, counters microprocessors R.P.Vs, control, telemetry and D.F. Production facilities also available. Write or phone Mr. Falkner, R.C.S. Electronics, 6 Wolsey Road, Ashford, Middlesex. Ashford 53661. (7021)

**PRECISION TURNED PARTS** — spacers, pillars, shafts, etc. Large/small batches. Quotations by return. Send for plant/service capacity specials, no problem. Drury Bros., Unit 6, Hedley Road, St Albans, Herts. Phone: 65094. (6548)

**PCB ARTWORK DESIGN SERVICE.** Component screens, solder resist and assembly masters. Pads Electrical Ltd., 01-850-6516, 45 Southwood Road, New Eltham SE9. (7055)

**CABLEFORMS** PCB's Gun Wire Wrappings, Panel and Chassis Wiring from drawings/maps supplied, parts supplied — faster turnaround — B.M.A. Electronic Assembly, Unit 6, Fen Road, Chesterton. Tel: Cambridge 861305. (7054)

**"PROTOTYPE AND PRODUCTION ASSEMBLY** from your drawings or sample. Peter Everard Ltd., Stroud (Glos) 77309. (7076)

## EQUIPMENT WANTED

### BROADFIELDS AND MAYCO DISPOSALS

21 Lodge Lane, N. Finchley  
London, N12 8JG  
Telephone:  
01-445 2713

01-445 0749 01-958 7624

WE ARE INTERESTED IN PURCHASING ALL KINDS OF RADIO, T.V. AND ELECTRONIC COMPONENTS AND EQUIPMENT IN BULK QUANTITIES. WE PAY PROMPT CASH AND CLEAR MATERIAL BY RETURN. (46)

## BUSINESS FOR SALE

**SMALL EAST LONDON BUSINESS FOR SALE** as a going concern. Specialising in Public Address and similar Sound Installations direct to user. Certain amount of manufacturing. Old established and highly regarded. Staff, few in number, but loyal and efficient. Excellent potential. Sale through ill health of owner. Principals only. Box W/W 7089.

**EXPORTER** requires high quality turntables, pick-up arms, cart ridges and amplifiers for own trademark home and export distribution. Box No. W/W 6774.

## ARTICLES WANTED

### WANTED: TEST AND COMMUNICATION EQUIPMENT



single items or quantities, also RF plugs, sockets and connectors.

Call or phone.

170 Goldhawj Road, London. W.12  
01-743 0899 (7006)

### ★ MINICOMPUTERS ★ PERIPHERALS ★ INSTRUMENTATION

For fastest best CASH offer phone

**COMPUTER APPRECIATION**  
Godstone (088 384) 3221

### TOP CASH AVAILABLE for NEW SURPLUS COMPONENTS

All details to:  
**SKYWAVE ELECTRONICS**  
01-560 3046

### ★ MINICOMPUTERS ★ PERIPHERALS ★ INSTRUMENTATION

For fastest, best CASH offer, phone.

**CHILTMead LTD.**  
Reading (0734) 586419

**WANTED,** all types of communication receivers and test equipment. Details to R. T. & I. Electronics Ltd., Ashville Old Hall, Ashville Rd., London, E.11. Ley 4986. (63)

**SURPLUS COMPONENTS,** Equipment and Computer panels wanted for cash. Ring Southampton 772501. (16)

**WE BUY** new valves, transistors and clean new components, large or small quantities, all details, quotations by return. — Walton's, 55 Worcester St., Wolverhampton. (62)

**WANTED: AUGUST, SEPTEMBER, OCTOBER BACK ISSUES OF WW 1976.** — Write Neville Cresdee, 30 Stoke Road, Gosport, Hants with price offer. (7069)

### WE PURCHASE ALL FORMS OF ELECTRONIC EQUIPMENT AND COMPONENTS, ETC.

SPOT CASH  
**CHILTMead LTD.**  
7, 9, 11 Arthur Road  
Reading, Berks.  
Tel. (0734) 582 605

**ALL SURPLUS** or used equipment wanted. Radio telephones — complete systems purchased. Ships equipment and small boat radio's — components, partly assembled chassis etc, etc. Established 20 years. For prompt attention contact Mr Grout at Worthing 34897. GWM Radio Limited 40/42 Portland Road, Worthing, Sussex. (6594)

**ELECTRONIC INSTRUMENTATION.** If you are interested in the buying or selling of good quality used electronic test instruments, ring Reading 51074, Martin Associates and converse with our Sheila Hatch who will deal promptly with your enquiry. (6757)

**WILL BUY ANYTHING,** any quantity if price is right ring Stan Willetts, West Bromwich, 021 553 0186. (6815)

**B-D ELECTRONICS** offer prompt settlement for your surplus components. Our main field of interest is consumer electronics. Please telephone our Miss Hughes, Peterborough (0733) 265219. (22)


**WESTREX 10A** pickup cartridge, Goodmans Axion 80 speakers, PX-4, PX-25, STC 4300B valves. Wanted urgently. — Box WW7049.

**R. F. INDUCTION HEATER** about 1.5KW. — Barrett, 1 Mayo Road, Croydon, CRO 2QP. (6038)

# FOR CLASSIFIED ADVERTISING

# RING EDDIE FARRELL ON

# 01-261 8508

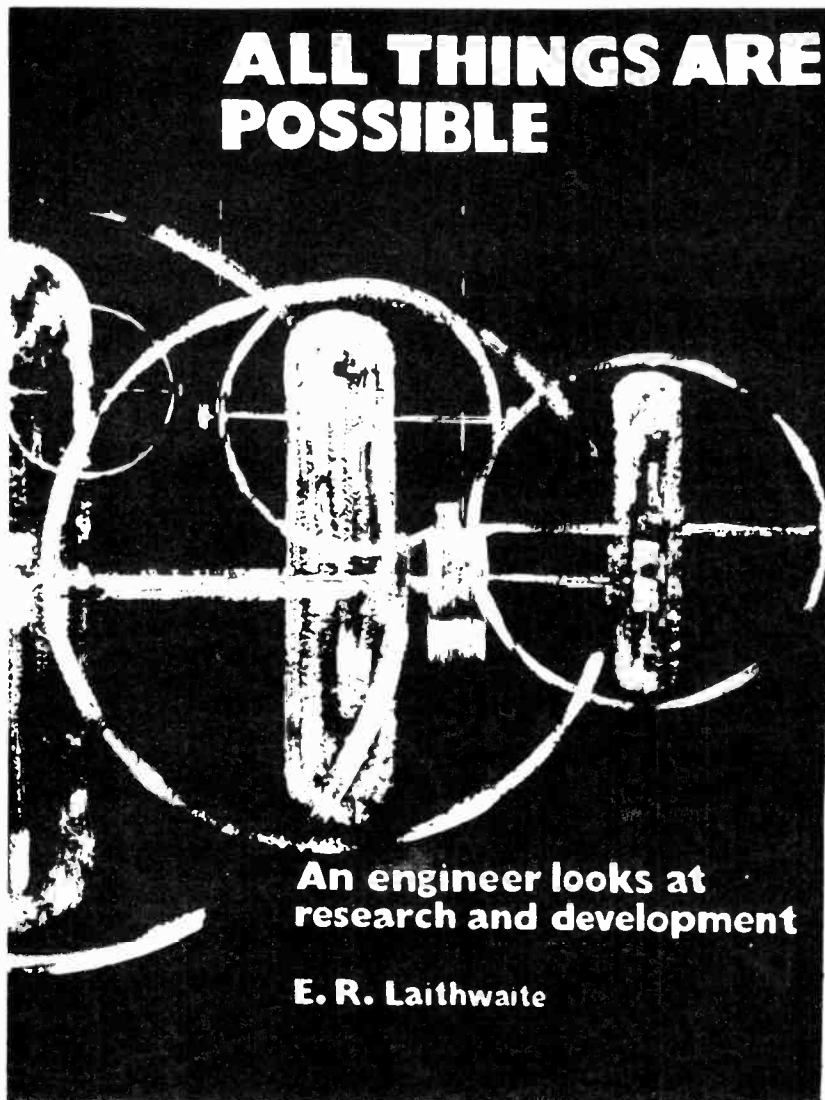

## All Things are Possible

In this, Professor Laithwaite's seventh book, he again offers us a rich mixture of controversial and always thought provoking articles. In the manner that we have learned to expect, he conveys through his writings and experiments the excitement of engineering and invention, and the ways in which man in his laboured progress has so often merely mimicked nature's own engineering achievements.

The author, famous in the academic world and for numerous television appearances, presents us with two series of articles, 44 in all, which will appeal to the engineer, scientist and all interested readers equally. The price of the book is £2.85.



Available from Selected Stockists. Write or phone for list.

# INCREDIBLE VALUE IN PRECISION TEST METERS

## MICROTEST 80 — I.C.E.

**20,000 OHMS/VOLT 40 RANGES**  
 20 000 ohms/Volt 4 000 ohms Volt (AC) 2% accuracy  
 V DC 100mV to 1KV (6 Ranges) I DC 50 A to 5A (6 Ranges)  
 V AC 1.5V to 1KV (5 Ranges) I AC 250 A to 2.5A (5 Ranges)  
 Ohms Low ohms ohms x 1 ohms x 10 ohms x 100  
 Power Output Measurements 1.5V to 1000V (5 Ranges)  
 + 6dB to 62dB (5 Ranges)  
 Capacitance 25 pF to 25 000 pF (4 Ranges)  
 1000 times overload protection (on OHM ranges)  
 Meter movement diode protection  
 Size (without case) 90 x 70 x 18 mm  
 Electronic zero non-parallax mirror scale Unbreakable carrying case and probes supplied  
 Full After Sales Service available  
 Price **£14.95** Post & Packing 60p VAT @ 8% £1 24 SEND TOTAL £16 79

## SUPERTESTER 680R — I.C.E.

**20,000 OHMS/VOLT 80 RANGES**  
 20 000 ohms Volt 1 D.C. 2 A C V DC 100mV to 2KV (13 Ranges) V AC 2 to 2KV (11 Ranges) I DC 50 A to 10A (12 Ranges) I AC 250 A to 5A (10 Ranges) R x1 x100 x1000 x10 000 and Low ohms Detector Reactance 0.10 M ohms Freq. Measurement 0.5000 Hz (2 Ranges) Power Output 10 2000V (9 Ranges) Decibels 24 to 70 dB (10 Ranges) Capacitance 0.500 000 pF (2 Ranges using mains supply) 0.20 000 pF (4 Ranges using internal 3 Volt battery) 1000 times overload protection on ohms ranges and meter movement diode protection 10 Fields of Measurement and 80 ranges  
 Size 128 x 95 x 32 mm Non parallax mirror scale Unbreakable carrying case supplied which contains probes mains lead crocodile clips and shorting link  
 Price **£25.25** Post & Packing 85p VAT 8% £2 09 SEND TOTAL £28 19

The I.C.E. Measurement Systems includes a comprehensive range of accessories: shunts, transformers, specialised probes, transistor tester, etc. Send for full details.  
 "Amperclamp" enables a multimeter to measure a.c. currents, in 6 ranges, from 2.5A to 500A! Ideal for use where breaking the circuit to insert an ammeter is impracticable, or where high initial currents are encountered. Versions available for use with other 50µA/100mV multimeters.  
 Price **£13.50**, P&P 60p, VAT £1 13. Total **£15.23**.



Sole Importers and Distributors **ELECTRONIC BROKERS LTD.** 49-53 Pancras Road, London NW1 2QB Tel: 01-837 7781


WW — 102 FOR FURTHER DETAILS

## INDEX TO ADVERTISERS

Appointments Vacant Advertisements appear on pages 133-146

	PAGE		PAGE		PAGE
AEI Transformers Ltd.	86	Genrad Ltd.	22	Q. Max Electronics Ltd.	15
AEL Ltd.	14	Gould Advance	64	Quality Electronics	119
AEL Crystals Ltd.	25	Greenwood Electronics Ltd.	9		
Alex Lawrie Factors Ltd.	63	G.R. Electronics	111		
All Electric Show	29			Radio Component Specialists	110
Amateur Components	124	Hampton Video Systems Ltd.	30	Rastra Electronics Ltd.	111
Ambit International	19	Harmsworth Townley & Co. Ltd.	98	R.C.S. Electronics	24
Antex	97	Harris Electronics (London) Ltd.	12, 17	Rola Celestion Ltd.	101
Arrow-Hart (Europe) Ltd.	5	Hart Electronics	104	R.S.T. Valves Ltd.	106
Aspen Electronics Ltd.	19	Hepworth Electronics	16	RTVC	105
Audio Fair	21	Herbert Controls Ltd.	25		
Audix Ltd.	13	Heyco Mfg. Co. Ltd.	20		
				Scopex Instruments Ltd.	100
Barrie Electronics Ltd.	107	Icon Designs	6	Scott, James (Elec. Eng.) Ltd.	100
Bayliss, A. D. & Sons Ltd.	10	ILP Electronics Ltd.	23	Service Trading Co.	99
Belling & Lee	107	Industrial Tape Applications	111	Servo & Electronics Sales Ltd.	119
Bentley Acoustic Corp. Ltd.	126	Integrex Ltd.	102, 103	Shure Electronics Ltd.	34
Beyer Dynamics (G.B.) Ltd.	8	Interface Quartz Devices Ltd.	31	Sintel	121
Bi-Pak Semiconductors Ltd.	116, 117	ITF-Lecs	7	Soundex Ltd.	29
Bi-Pre-Pak	125	ITT Electronic Services	72	Special Products Ltd.	16
Boss Industrial Mouldings Ltd.	14	International Rectifier	85	Storno Ltd.	30
Bradley, G. & E. Ltd.	Cover iii			Stringer Clark Antennas	18
Bywood Electronics	30	JPS Associates	26	Strumech Engineering Ltd.	12
				Sugden, J. E. & Co. Ltd.	11
Cambridge Learning	9	Leevers-Rich Equipment Ltd.	12	Surrey Electronics Ltd.	125
Catronics	29	Levell Electronics Ltd.	1	Swanley Electronics Ltd.	28
CEC Corporation	17	Lynx (Electronics) London Ltd.	114	Swift of Wilmslow	24
Chiltmead Ltd.	118, 129				
Circuit Designs	113	MacInnes Laboratories Ltd.	6	Tamba Electronics	28
Click Shelving Ltd.	28	McLennan Servo Supplies Ltd.	18	Technomatic Ltd.	131
Cliffpalm Ltd.	13	Maplin Electronic Supplies	52	Tektronix Ltd.	49
Coles Electroacoustics Ltd.	17	Marconi Instruments Ltd.	Cover ii	Teleprinter Equipment Ltd.	24
Colomor (Electronics) Ltd.	120	Marshall, A. & Sons (London) Ltd.	121	Teletop Ltd.	32
Combined Precision Components Ltd.	115	Medelec	16	Teleradio Hi Fi	31
Commercial Trade Travel	127	Metac Electronics & Time Centre	125	Television	31
Compcor Electronics Ltd.	18	Microprocessor	27	Tempus	28
Computer Appreciation	106	Mills, W.	112	The All Electric Show	29
Crimson Elektrik	19	Monolith Electronics Co. Ltd.	25	Thomson CSF	89
Crofton Electronics Ltd.	29	Mullard Ltd.	50, 51	Time Electronics	26
		Multicore Solders Ltd.	Cover iv	Trampus Electronics	124
Data Dynamics	125				
Dema Electronics International	98	Nombrex (1969) Ltd.	14	Vero Electronics Ltd.	18
Drake Transformers Ltd.	10				
		Otari Corp.	2	West Hyde Developments Ltd.	112
Eddystone Radio Ltd.	4			West London Supplies	125
Edicron Ltd.	15	Patrick, J. B.	132	Widney Dorlec	20
Electronic Brokers Ltd.	114, 119, 122, 123, 148	PB Electronics (Scotland) Ltd.	25	Wilkinson, L. (Croydon) Ltd.	125
Electro-Tech Components Ltd.	120	PBRA Ltd.	31	Without Breeden Electronics Ltd.	3
Electron/W. World	128	Phonosonics	104	Wilmslow Audio	132
Electronic Services & Products Ltd.	11	Pinnacle Electronic Comps. Ltd.	90		
Enelectroval Ltd.	131	Powertran Electronics	108, 109	Z. & I. Aero Services Ltd.	8, 19, 126
Ene Electronics Ltd.	15, 20, 30	Precision Petite Ltd.	26	Zettler (UK) Division	26
ES Electronics	29	Purnell	Loose insert		
Farnell Instruments Ltd.	71				
Flight Link Controls Ltd.	31				
Future Film Developments	26				

Printed in Great Britain by QB Ltd, Sheepen Road, Colchester and Published by the Proprietors IPC ELECTRICAL ELECTRONIC PRESS LTD, Dorset House, Stamford St, London, SE1 9LU, telephone 01-261 8000. Wireless World can be obtained abroad from the following: AUSTRALIA and NEW ZEALAND: Gordon & Gotch Ltd; INDIA: A. H. Wheeler & Co. CANADA: The Wm. Dawson Subscription Service Ltd, Gordon & Gotch Ltd; SOUTH AFRICA: Central News Agency Ltd; William Dawson & Sons (S.A.) Ltd; UNITED STATES: Eastern News Distributors Inc., 14th Floor, 111 Eighth Avenue, New York, N.Y. 10011

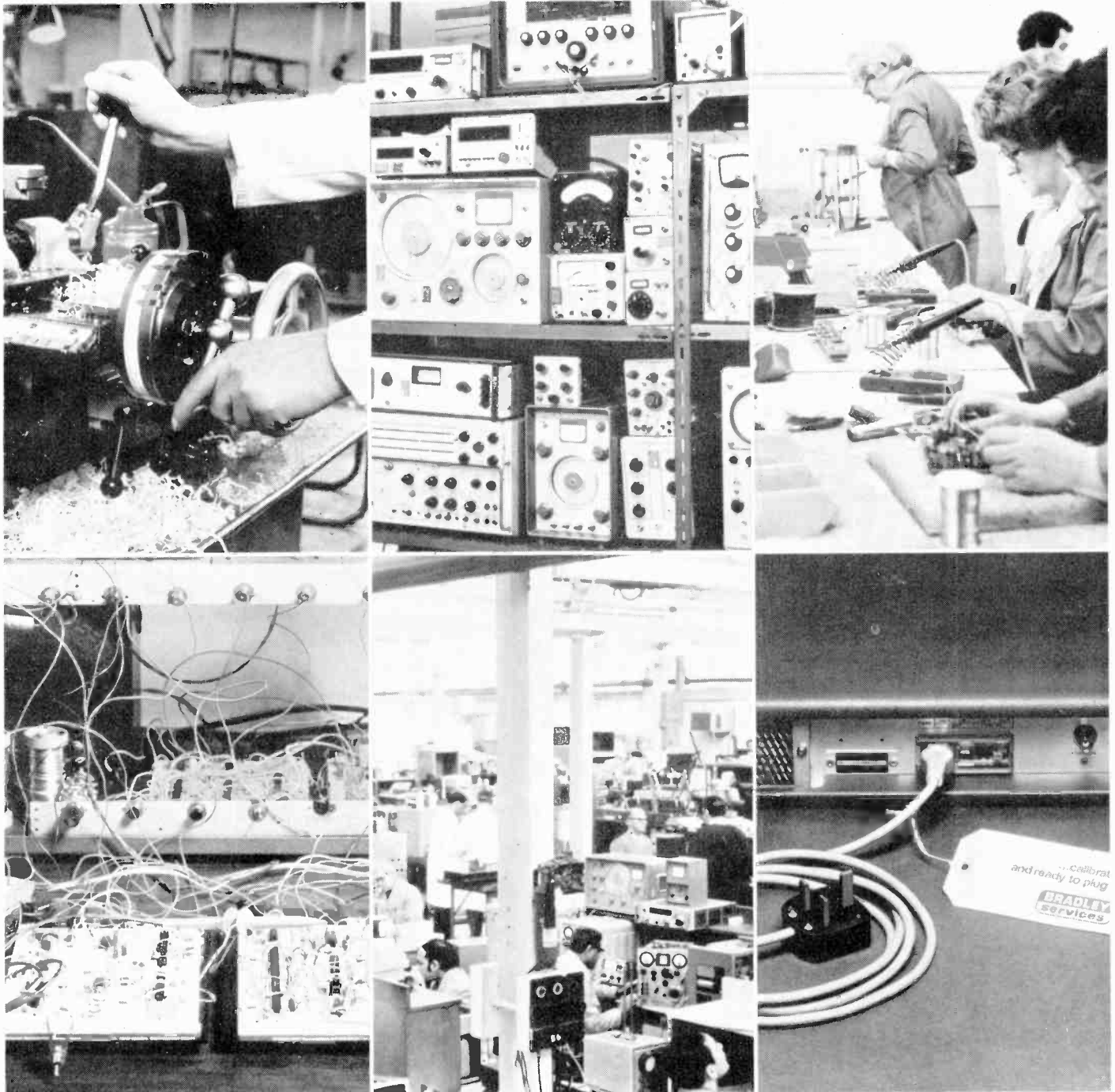

## Even if we didn't make it, we'll make it work.

Bradley Services have the expertise and manufacturing capability necessary to make the most sophisticated electronic systems and electro-mechanical devices. However, equally important are the facilities we have for repair and calibration. We can handle virtually any type of instrument within the frequency range DC to 36 GHz – irrespective of manufacturer.

We also have a Post Design Services Group which provides every type of

after-sales engineering support, from the provision of technical literature to the upgrading of complete systems.

These facilities all approved to MOD Def. Stan. 05-21, have been developed over more than 20 years and during that time we've handled practically every type of instrument in use. So, if you've got a problem with some equipment, the chances are that, even if we didn't make it, we can still make it work.

## Bradley Electronics

G & E Bradley Limited  
Electral House, Neasden Lane  
London NW10 1RR  
Telephone : 01-450 7811  
Telex : 25583



# Ersin Multicore- the international solder

## Ersin Multicore 5-Core Solder


The proved superiority of ERSIN Multicore Solder for over thirty years is due to many factors. We have specialised throughout this period in the manufacture of cored solders. Consequently our research and manufacturing staff have been able to devote all their energies to the development of Multicore Solders. All alloys are of highest purity, carefully formulated and checked.

Our unsurpassed ERSIN flux is rigorously tested before and after it is incorporated in the solder wire. Our five separate cores of flux ensure flux continuity, leave only an ultra-thin layer of solder separating flux from work for instant wetting and provide a more accurate ratio of flux to solder. It is therefore possible to

use less solder and obtain greater reliability.

Our Quality Control at all stages of manufacture is guaranteed and recorded by the batch number on every reel.


## Needle fine gauges

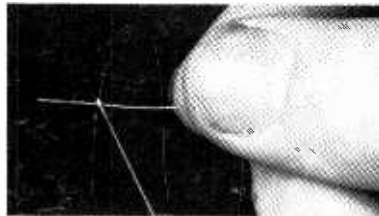

In addition to our standard range of wire diameters (10-22 swg: 3.2-0.7 mm) supplied on 2½ kg and ½ kg reels we also mass-produce needle-fine gauges (24-34 swg: 0.56-0.23 mm) on 250 g reels for microminiature soldering applications—still with 5 Cores of flux.
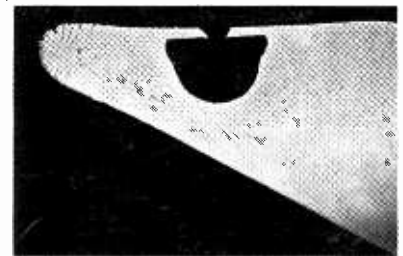
## Savbit Solder

One of our most popular special ERSIN Multicore Solder alloys is SAVBIT alloy. Compared with ordinary tin/lead solders it dramatically reduces the erosion of soldering iron bits, copper wires and printed circuit conductors. It also saves costs and increases reliability. SAVBIT alloy containing 5-Cores ERSIN 362 flux has received special Ministry approval—under DTD. 900/4535 for Military applications.



Sectioned iron-plated bit, after 40,000 simulated operations using 60/40 Solder.




Sectioned iron-plated bit, after 40,000 simulated operations using SAVBIT Solder.

### ALLOY

Composition (nominal major elements)	Grade	Melting Temperature		Specification
		Solidus °C	Liquidus °C	
50/33/17 Sn/Pb/Cd	TLC	145	145	DIN 1707
62/36/2 Sn/Pb/Ag	LMP	179	179	DIN 1707
62/35.7/2/0.3 Sn/Pb/Ag/Sb	Sn62	179	179	QQ-S-57 1E
63/36.7/0.3 Sn/Pb/Sb	Sn63	183	183	QQ-S-57 1E
60/40 Sn/Pb	K	183	188	B.S. 219
60/39.7/0.3 Sn/Pb/Sb	Sn60	183	188	QQ-S-57 1E
50/50 Sn/Pb	F	183	212	B.S. 219
50/49.7/0.3 Sn/Pb/Sb	Sn50	183	212	QQ-S-57 1E
50/48.5/1.5 Sn/Pb/Cu	Savbit 1	183	215	DTD 900/4535 DIN 1707
45/55 Sn/Pb	R	183	224	B.S. 219
40/60 Sn/Pb	G	183	234	B.S. 219
40/59.7/0.3 Sn/Pb/Sb	Sn40	183	234	QQ-S-57 1E
30/70 Sn/Pb	J	183	255	B.S. 219
20/80 Sn/Pb	V	183	275	B.S. 219
15/85 Sn/Pb	—	225	290	—
Pure Tin	P.T.	232	232	B.S. 3252
95/5 Sn/Sb	95A	236	243	B.S. 219
5/93.5/1.5 Sn/Pb/Ag	H.M.P.	296	301	B.S. 219



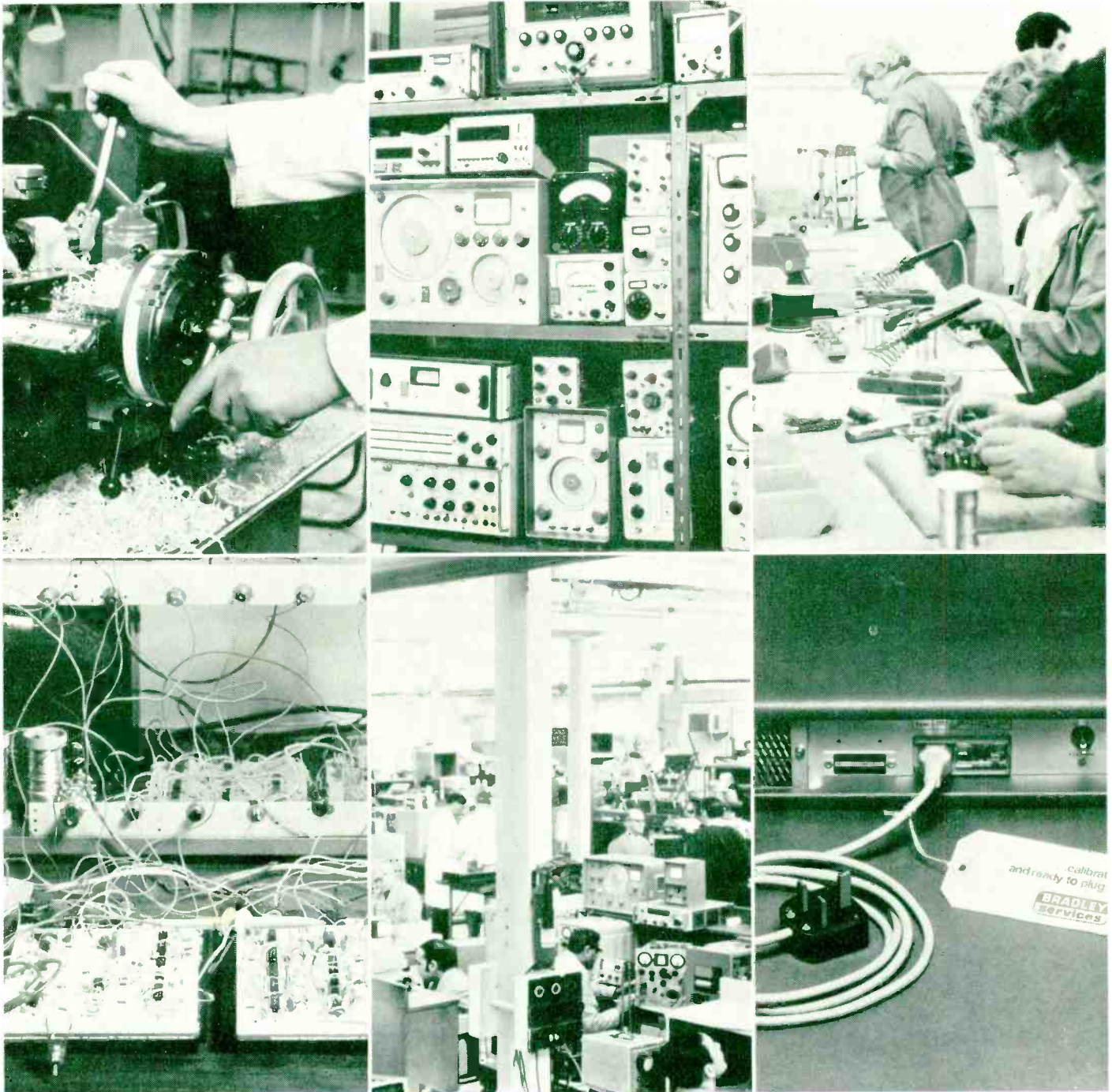For full information on these and a Selector Guide to other MULTICORE products please write on your Company's letterhead direct to:  
**Multicore Solders Limited**, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP.  
 Tel: Hemel Hempstead 3636 Telex: 82363



## Even if we didn't make it, we'll make it work.

Bradley Services have the expertise and manufacturing capability necessary to make the most sophisticated electronic systems and electro-mechanical devices. However, equally important are the facilities we have for repair and calibration. We can handle virtually any type of instrument within the frequency range DC to 36 GHz – irrespective of manufacturer.

We also have a Post Design Services Group which provides every type of

after-sales engineering support, from the provision of technical literature to the upgrading of complete systems.

These facilities all approved to MOD Def. Stan. 05-21, have been developed over more than 20 years and during that time we've handled practically every type of instrument in use. So, if you've got a problem with some equipment, the chances are that, even if we didn't make it, we can still make it work.

### Bradley Electronics

G & E Bradley Limited  
Electral House, Neasden Lane  
London NW10 1RR  
Telephone : 01-450 7811  
Telex : 25583





# Ersin Multicore- the international solder

## Ersin Multicore 5-Core Solder


The proved superiority of ERSIN Multicore Solder for over thirty years is due to many factors. We have specialised throughout this period in the manufacture of cored solders. Consequently our research and manufacturing staff have been able to devote all their energies to the development of Multicore Solders. All alloys are of highest purity, carefully formulated and checked.

Our unsurpassed ERSIN flux is rigorously tested before and after it is incorporated in the solder wire. Our five separate cores of flux ensure flux continuity, leave only an ultra-thin layer of solder separating flux from work for instant wetting and provide a more accurate ratio of flux to solder. It is therefore possible to

use less solder and obtain greater reliability.

Our Quality Control at all stages of manufacture is guaranteed and recorded by the batch number on every reel.


## Needle fine gauges

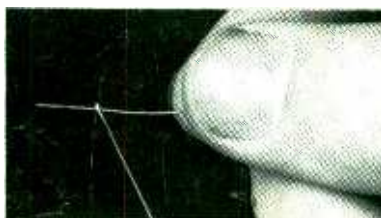

In addition to our standard range of wire diameters (10-22 swg: 3.2-0.7 mm) supplied on 2½ kg and ½ kg reels we also mass-produce needle-fine gauges (24-34 swg: 0.56-0.23 mm) on 250 g reels for microminiature soldering applications—still with 5 Cores of flux.
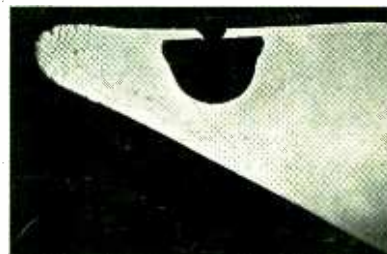
## Savbit Solder

One of our most popular special ERSIN Multicore Solder alloys is SAVBIT alloy. Compared with ordinary tin/lead solders it dramatically reduces the erosion of soldering iron bits, copper wires and printed circuit conductors. It also saves costs and increases reliability. SAVBIT alloy containing 5-Cores ERSIN 362 flux has received special Ministry approval—under DTD. 900/4535 for Military applications.



Sectioned iron-plated bit, after 40,000 simulated operations using 60/40 Solder.



Sectioned iron-plated bit, after 40,000 simulated operations using SAVBIT Solder.

Composition (nominal major elements)	Grade	Melting Temperature		Specification
		Solidus °C	Liquidus °C	
50/33/17 Sn/Pb/Cd	TLC	145	145	DIN 1707
62/36/2 Sn/Pb/Ag	LMP	179	179	DIN 1707
62/35.7/2/0.3 Sn/Pb/Ag/Sb	Sn62	179	179	QQ-S-57 1E
63/38.7/0.3 Sn/Pb/Sb	Sn63	183	183	QQ-S-57 1E
60/40 Sn/Pb	K	183	188	B.S. 219
60/39.7/0.3 Sn/Pb/Sb	Sn60	183	188	QQ-S-57 1E
50/50 Sn/Pb	F	183	212	B.S.219
50/49.7/0.3 Sn/Pb/Sb	Sn50	183	212	QQ-S-57 1E
50/48.5/1.5 Sn/Pb/Cu	Savbit 1	183	215	DTD 900/4535 DIN 1707
45/55 Sn/Pb	R	183	224	B.S.219
40/60 Sn/Pb	G	183	234	B.S.219
40/59.7/0.3 Sn/Pb/Sb	Sn40	183	234	QQ-S-57 1E
30/70 Sn/Pb	J	183	255	B.S.219
20/80 Sn/Pb	V	183	275	B.S.219
15/85 Sn/Pb	—	225	290	—
Pure Tin	P.T.	232	232	B.S.3252
95/5 Sn/Sb	95A	236	243	B.S.219
5/93.5/1.5 Sn/Pb/Ag	H.M.P.	296	301	B.S.219



For full information on these and a Selector Guide to other MULTICORE products please write on your Company's letterhead direct to:

**Multicore Solders Limited**, Maylands Avenue, Hemel Hempstead, Hertfordshire HP2 7EP.  
Tel: Hemel Hempstead 3636 Telex: 82363